#### Warm up

Try to prove  $p \rightarrow q \equiv \neg q \rightarrow \neg p$  if you didn't get all the way through it last time.

# Digital Logic CSE 311 Autumn 2020 Lecture 4

### Contrapositive

$$p \rightarrow q \equiv \neg p \lor q$$

$$\equiv q \lor \neg p$$

$$\equiv \neg \neg q \lor \neg p$$

$$\equiv \neg q \lor \neg p$$

$$\equiv \neg q \lor \neg p$$

$$\equiv \neg q \rightarrow \neg p$$
Law of Implication

All of our rules deal with ORs and ANDs, let's switch the implication to just use AND/NOT/OR.

And do the same with our target

It's ok to work from both ends. In fact it's a very common strategy!

Now how do we get the top to look like the bottom?

Just a few more rules and we're done!

### Announcements

Everyone should have access to gradescope (you should have gotten a sign-up email if you don't already have an account).

If you can't access the course on gradescope, let us know as soon as possible.

Turning in an assignment to gradescope often takes about 15 minutes. You have to tell gradescope which page each problem is on.



It's notation day! Two new different ways to represent propositions.

Also vocabulary catch-up.



# **Digital Circuits**

**Computing With Logic** 

- **T** corresponds to **1** or "high" voltage
- **F** corresponds to 0 or "low" voltage

#### Gates

Take inputs and produce outputs (functions)

Several kinds of gates

**Correspond to propositional connectives (most of them)** 

# And Gate


AND Connective vs.


**AND Gate** 


AND

-OUT

р

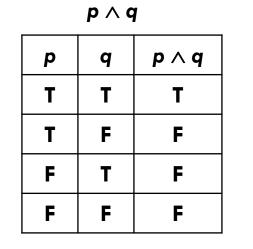


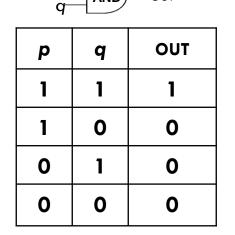


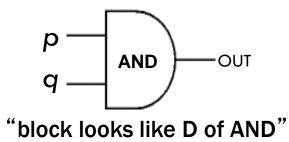


# Or Gate

#### OR Connective vs.

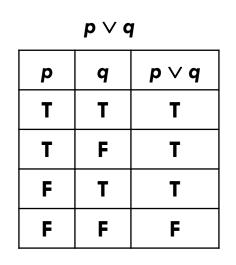

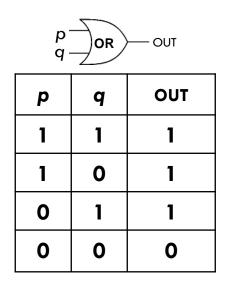



**OR Gate** 

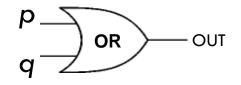

"arrowhead block looks like  $\ensuremath{\mathsf{V}}\xspace$ "


#### Not Gates

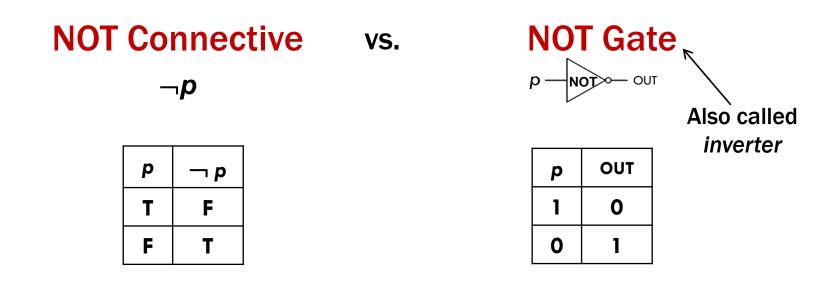


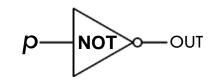

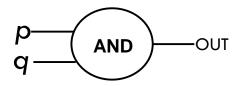
# Blobs are Okay!

You may write gates using blobs instead of shapes!




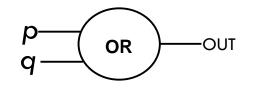



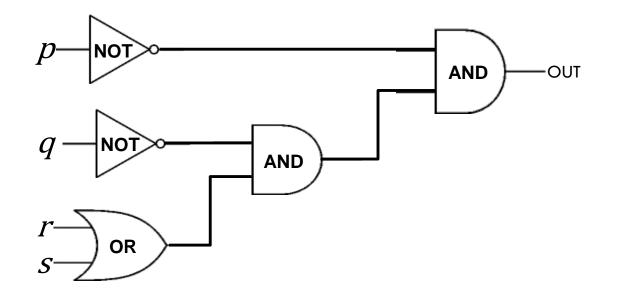

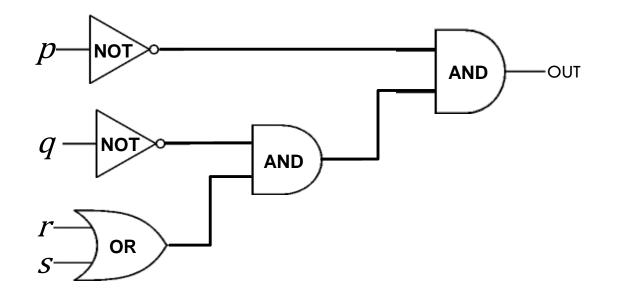
#### Values get sent along wires connecting gates




Values get sent along wires connecting gates

 $\neg p \land (\neg q \land (r \lor s))$ 

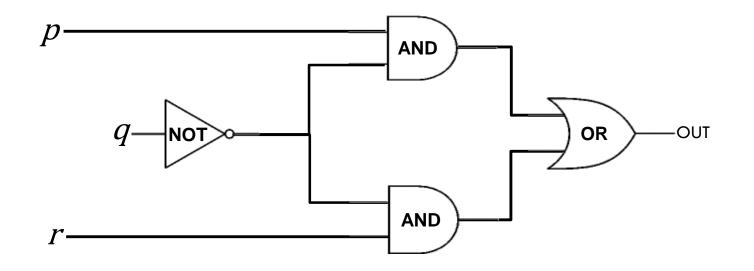

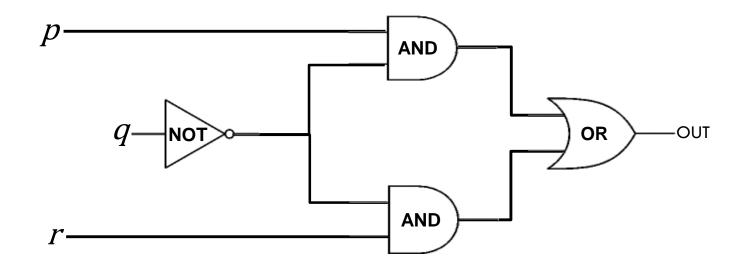Wires can send one value to multiple gates!



Wires can send one value to multiple gates!

$$(p \land \neg q) \lor (\neg q \land r)$$



# Vocabulary!

#### A proposition is a....

*Tautology* if it is always true. *Contradiction* if it is always false. *Contingency* if it can be both true and false.

 $p \lor \neg p$ 

Tautology

If p is true,  $p \lor \neg p$  is true; if p is false,  $p \lor \neg p$  is true.

 $p \oplus p$ 

Contradiction

If p is true,  $p \oplus p$  is false; if p is false,  $p \oplus p$  is false.

 $(p \rightarrow q) \land p$  **Contingency** If p is true and q is true,  $(p \rightarrow q) \land p$  is true; If p is true and q is false,  $(p \rightarrow q) \land p$  is false.

# More Vocabulary

#### $p \rightarrow q$

*p* is called the "hypothesis" or "antecedent" (or other names...)*q* is called the "conclusion" or "consequent" (or other names...)



# On notation...

Logic is fundamental. Computer scientists use it in programs, mathematicians use it in proofs, engineers use it in hardware, philosophers use it in arguments,....

...so everyone uses different notation to represent the same ideas.

Since we don't know exactly what you're doing next, we're going to show you a bunch of them; but don't think one is "better" than the others!

# Meet Boolean Algebra

Preferred by some mathematicians and circuit designers. "or" is +

```
"and" is · (i.e. "multiply")
```

"not" is ' (an apostrophe after a variable)

#### Why?

Mathematicians like to study "operations that work kinda like 'plus' and 'times' on integers."

Circuit designers have a lot of variables, and this notation is more compact.

# Meet Boolean Algebra

Name	Variables	"True/False"	"And"	"Or"	"Not"	Implication
Java Code	boolean b	true,false	& &		!	No special symbol
Propositional Logic	"p,q,r"	Т, F	Λ	V	Г	$\rightarrow$
Circuits	Wires	1,0	And	OR	Noto	No special symbol
Boolean Algebra	a, b, c	1,0	("multiplication")	+ ("addition")	, (apostrophe after variable)	No special symbol

Propositional logicBoolean Algebra $(p \land q \land r) \lor s \lor \neg t$ pqr + s + t'

# Comparison


Propositional logicBoolean Algebra $(p \land q \land r) \lor s \lor \neg t$ pqr + s + t'

Remember this is just an alternate notation for the same underlying ideas.

So that big list of identities? Just change the notation and you get another big list of identities!

### Boolean Algebra

### Axioms

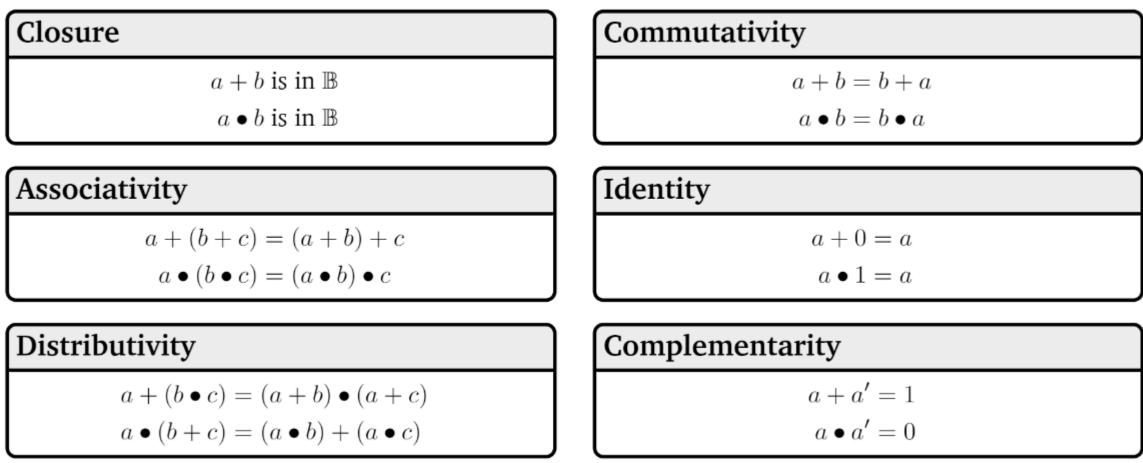

### Boolean Algebra

### Theorems

Null

X + 1 = 1 $X \bullet 0 = 0$ 

Idempotency

X + X = X

$$X \bullet X = X$$

Involution

(X')' = X

Uniting

$$X \bullet Y + X \bullet Y' = X$$
$$(X + Y) \bullet (X + Y') = X$$

# Boolean Algebra

Absorbtion

$$X + X \bullet Y = X$$
$$(X + Y') \bullet Y = X \bullet Y$$
$$X \bullet (X + Y) = X$$
$$(X \bullet Y') + Y = X + Y$$

DeMorgan $(X + Y + \cdots)' = X' \bullet Y' \bullet \cdots$  $(X \bullet Y \bullet \cdots)' = X' + Y' + \cdots$ 

Consensus

$$(X \bullet Y) + (Y \bullet Z) + (X' \bullet Z) = X \bullet Y + X' \bullet Z$$
$$(X + Y) \bullet (Y + Z) \bullet (X' + Z) = (X + Y) \bullet (X' + Z)$$

Factoring

$$(X+Y) \bullet (X'+Z) = X \bullet Z + X' \bullet Y$$
$$X \bullet Y + X' \bullet Z = (X+Z) \bullet (X'+Y)$$

# An Exercise in Notation

The rest of today we're solving a problem.

See the concepts we learned the last few days "in action" And practice Boolean algebra and propositional logic.

## Today's Goal

Go from a problem statement to code to logical/circuit representation to an "optimized" version.

#### Why?

Practice translating between different representations.

Practice applying simplification laws

Historical context! This process is reminiscent of "hardware acceleration" – designing custom hardware to do a single task very fast.

Most design is done automatically these days, but it's still nice to see once.

# Our Goal

Given what day of the week it is and what kind of question you have, what's the quickest way to get it answered?

(this is an example, not actual advice)

**Input:** day of the week, Boolean talkToSomeone

**Output:** The way to get your question answered, according to the following rules:

On M,Tu,W,F if you want to talk, go to office hours

On Th if you want to talk, go to section

Monday through Friday, if you don't want to talk ask on Ed

On Saturday or Sunday, text a friend (whether you want to talk or not)

# Step One

Input: day of the week, Boolean talkToSomeone

**Output:** The way to get your question answered, according to the following rules:

- On M,Tu,W,F if you want to talk, go to office hours
- On Th if you want to talk, go to section
- Monday through Friday, if you don't want to talk ask on Ed
- On Saturday or Sunday, text a friend (whether you want to talk or not)

Take 2 minutes **plan** what your code might look like.

# Step One


```
if ( (day==Monday || day==Tuesday || day==Wednesday || day==Friday) ) {
   Ð
 2
             if (talkToSomeone)
 3
                 return "office hours";
 4
             else
 5
                 return "Ed";
 6
 7
        else if(day==Thursday) {
   Ξ
 8
             if(talkToSomeone)
 9
                 return "section";
10
             else
11
                 return "Ed";
12
13
        else //day is Saturday or Sunday
14
             return "text a friend";
15
```

One possibility (there are many)
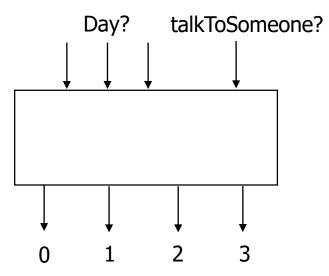
# Step Two


Go from a problem statement to code to logical/circuit representation to an "optimized" version.

We want a logical/circuit representation.


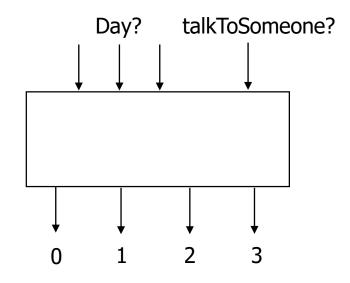
# Step Two

Input? Day in binary and talkToSomeone Monday – 000 0 for false, 1 for true. Tuesday – 001 Wednesday – 010 Thursday – 011 Friday – 100 Saturday – 101 Sunday – 110 (invalid) – 111



# Step Two


Output? We'll turn on only the wire for what to do called a "one-hot" encoding, because one wire is on ('hot')

Office Hour – 0

Section – 1

Ed – 2

Text a Friend – 3

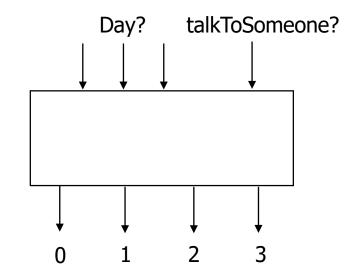

Day	<i>d</i> <sub>2</sub>	<i>d</i> <sub>1</sub>	$d_0$	talkToSomeone	out <sub>0</sub> (OH)	$out_1$ (Se)	$out_2$ (Ed)	$out_3$ (TF)
Monday	0	0	0	0			1	
Monday	0	0	0	1	1			
Tuesday	0	0	1	0			1	
Tuesday	0	0	1	1	1			
Wednesday	0	1	0	0			1	
Wednesday	0	1	0	1	1			
Thursday	0	1	1	0			1	
Thursday	0	1	1	1		1		
Friday	1	0	0	0			1	
Friday	1	0	0	1	1			
Saturday	1	0	1	0				1
Saturday	1	0	1	1				1
Sunday	1	1	0	0				1
Sunday	1	1	0	1				1
	1	1	1	0				
	1	1	1	1				

Day	<b>d</b> <sub>2</sub>	<i>d</i> <sub>1</sub>	$d_0$	talkToSomeone	$out_0$ (OH)	$out_1$ (Se)	$out_2$ (Ed)	$out_3$ (TF)	
Monday	0	0	0	0			1		_
Monday	0	0	0	1	1				$\neg d_2 \land \neg d_1 \land \neg d_0 \land s$
Tuesday	0	0	1	0			1		
Tuesday	0	0	1	1	1				$\neg d_2 \land \neg d_1 \land d_0 \land s$
Wednesday	0	1	0	0			1		
Wednesday	0	1	0	1	1				$\neg d_2 \wedge d_1 \wedge \neg d_0 \wedge s$
Thursday	0	1	1	0			1		
Thursday	0	1	1	1		1			
Friday	1	0	0	0			1		_
Friday	1	0	0	1	1				$d_2 \wedge \neg d_1 \wedge \neg d_0 \wedge s$
Saturday	1	0	1	0				1	
Saturday	1	0	1	1		•	-		
Sunday	1	1	0	0	out -			) $\vee$ ( $d$ )	
Sunday	1	1	0	1					$\neg d_1 \wedge d_0 \wedge s ) \vee _1 \wedge \neg d_0 \wedge s )$
	1	1	1	0					
	1	1	1	1					

Day	<b>d</b> <sub>2</sub>	<i>d</i> <sub>1</sub>	$d_0$	talkToSomeone	<i>out</i> <sub>0</sub> (OH)	$out_1$ (Se)	$out_2$ (Ed)	$out_3$ (TF)	
Monday	0	0	0	0			1		
Monday	0	0	0	1	1				$d_2'd_1'd_2$
Tuesday	0	0	1	0			1		
Tuesday	0	0	1	1	1				$d_2'd_1'd_2$
Wednesday	0	1	0	0			1		
Wednesday	0	1	0	1	1				$d_2'd_1d_1$
Thursday	0	1	1	0			1		
Thursday	0	1	1	1		1			
Friday	1	0	0	0			1		
Friday	1	0	0	1	1				$d_2 d_1 c$
Saturday	1	0	1	0				1	
Saturday	1	0	1	1		-			
Sunday	1	1	0	0					
Sunday	1	1	0	1	out	$d_0 = d_2' d_1' d_0'$	$s + d_2' d_1' d_1$	$_{0}s+d_{2}'d_{1}d_{0}$	$s+d_2d_1d_0s$
	1	1	1	0					
	1	1	1	1					

Day	<b>d</b> <sub>2</sub>	<i>d</i> <sub>1</sub>	$d_0$	talkToSomeone	out <sub>0</sub> (OH)	$out_1$ (Se)	$out_2$ (Ed)	$out_3$ (TF)	
Monday	0	0	0	0			1		
Monday	0	0	0	1	1				$d_2'd_1'd_0'$
Tuesday	0	0	1	0			1		
Tuesday	0	0	1	1	1				$d_2' d_1' d_0 s$
Wednesday	0	1	0	0			1		
Wednesday	0	1	0	1	1				$d_2' d_1 d_0' s$
Thursday	0	1	1	0			1		
Thursday	0	1	1	1		1			
Friday	1	0	0	0			1		
Friday	1	0	0	1	1				$d_2 d_1' d_0'$
Saturday	1	0	1	0				1	
Saturday	1	0	1	1					
Sunday	1	1	0	0					
Sunday	1	1	0	1	out	$\overline{f_0} = (d_2'd_1'd_1'd_1'd_1'd_1'd_1'd_1'd_1'd_1'd_1$	$d_0' + d_2' d_1' d_1' d_1' d_1' d_1' d_1' d_1' d_1$	$d_0 + d_2' d_1 d_0$	$'+d_2d_1'd_0')s$
	1	1	1	0					
	1	1	1	1					

Day	<b>d</b> <sub>2</sub>	<i>d</i> <sub>1</sub>	$d_0$	talkToSomeone	<i>out</i> <sub>0</sub> (OH)	$out_1$ (Se)	$out_2$ (Ed)	$out_3$ (TF)
Monday	0	0	0	0			1	
Monday	0	0	0	1	1			
Tuesday	0	0	1	0			1	
Tuesday	0	0	1	1	1			
Wednesday	0	1	0	0			1	
Wednesday	0	1	0	1	1			
Thursday	0	1	1	0			1	
Thursday	0	1	1	1		1		
Friday	1	0	0	0			1	
Friday	1	0	0	1	1			
Saturday	1	0	1	0				1
Saturday	1	0	1	1				1
Sunday	1	1	0	0				1
Sunday	1	1	0	1				1 F
	1	1	1	0				(
	1	1	1	1				

Find the formula for  $out_1$  in both Boolean algebra and propositional logic.

If you have extra time, draw the circuit representation.


Fill out the poll everywhere for Activity Credit! Go to pollev.com/cse311 and login with your UW identity Or text cse311 to 22333


Day	<i>d</i> <sub>2</sub>	<i>d</i> <sub>1</sub>	$d_0$	talkToSomeone	out <sub>0</sub> (OH)	$out_1$ (Se)	$out_2$ (Ed)	$out_3$ (TF)
Monday	0	0	0	0			1	
Monday	0	0	0	1	1			
Tuesday	0	0	1	0			1	
Tuesday	0	0	1	1	1			
Wednesday	0	1	0	0			1	
Wednesday	0	1	0	1	1			
Thursday	0	1	1	0			1	
Thursday	0	1	1	1		1		
Friday	1	0	0	0			1	
Friday	1	0	0	1	1			
Saturday	1	0	1	0				1
Saturday	1	0	1	1				
Sunday	1	1	0	0			$out_1 = d_1$	${}_{2}^{\prime}d_{1}^{}d_{0}^{}s$
Sunday	1	1	0	1		011		d
	1	1	1	0		00	$dt_1 = \neg d_2 \land$	$u_1 \wedge u_0 \wedge s$
	1	1	1	1				

Day	<b>d</b> <sub>2</sub>	<b>d</b> <sub>1</sub>	$d_0$	talkToSomeone	<i>out</i> <sub>0</sub> (OH)	$out_1$ (Se)	$out_2$ (Ed)	$out_3$ (TF)
Monday	0	0	0	0			1	
Monday	0	0	0	1	1			
Tuesday	0	0	1	0			1	
Tuesday	0	0	1	1	1			
Wednesday	0	1	0	0			1	
Wednesday	0	1	0	1	1			
Thursday	0	1	1	0			1	
Thursday	0	1	1	1		1		
Friday	1	0	0	0			1	
Friday	1	0	0	1	1			
Saturday	1	0	1	0				1
Saturday	1	0	1	1				1
Sunday	1	1	0	0				
Sunday	1	1	0	1	out	$\overline{t_2} = d_2' d_1' d_0'$	$b_{0}s'+d_{2}'d_{1}'d$	$_0s' + d_2'd_1d$
	1	1	1	0		out - d'	d' d' + d'	$d_0 + d_1 d_0$
	1	1	1	1		$uu_2 - u_2s$	$-(u_1u_0 + u_1)$	$\left[u_0 + u_1 u_0\right)$

.


Day	<i>d</i> <sub>2</sub>	<i>d</i> <sub>1</sub>	$d_0$	talkToSomeone	out <sub>0</sub> (OH)	$out_1$ (Se)	$out_2$ (Ed)	$out_3$ (TF)
Monday	0	0	0	0			1	
Monday	0	0	0	1				
Tuesday	0	0	1	0				
Tuesday	0	0	1	1		(	$out_3 = d_2(d)$	$d_1'd_0 + d_1d_0'$
Wednesday	0	1	0	0				
Wednesday	0	1	0	1	,			
Thursday	0	1	1	0			1	
Thursday	0	1	1	1		1		
Friday	1	0	0	0			1	
Friday	1	0	0	1	1			
Saturday	1	0	1	0				1
Saturday	1	0	1	1				1
Sunday	1	1	0	0				1
Sunday	1	1	0	1				1
	1	1	1	0				
	1	1	1	1				

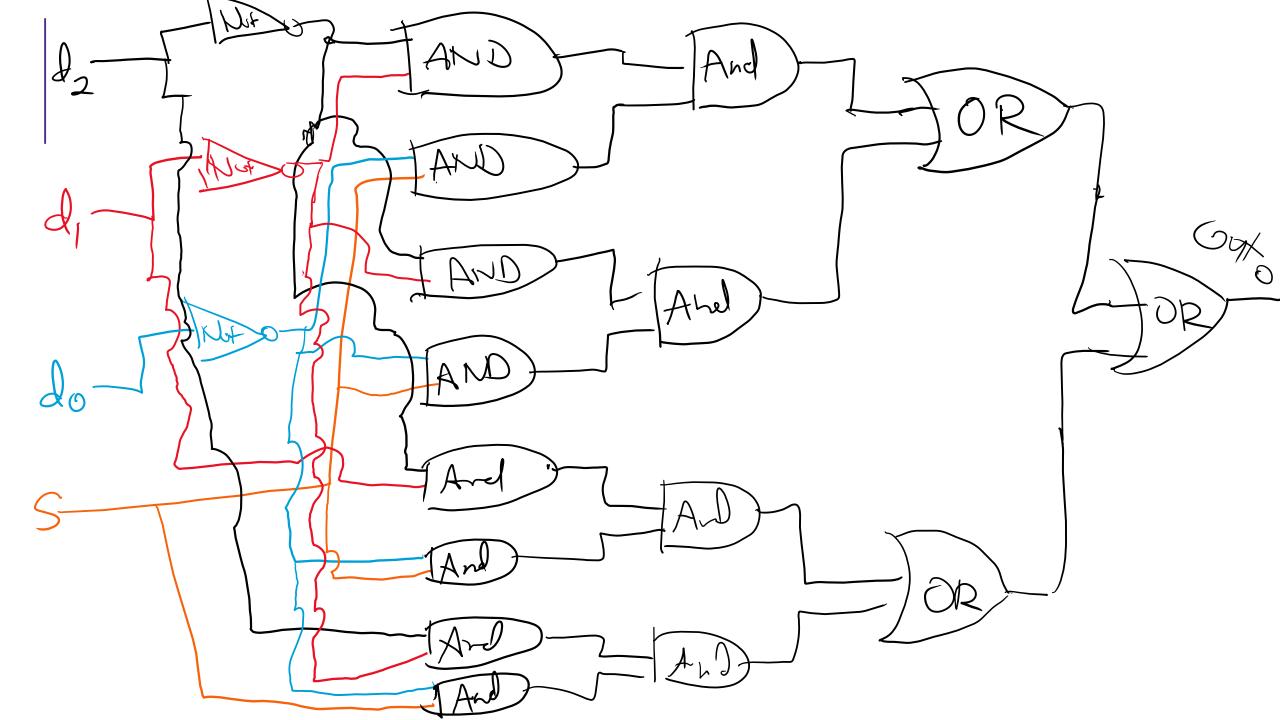

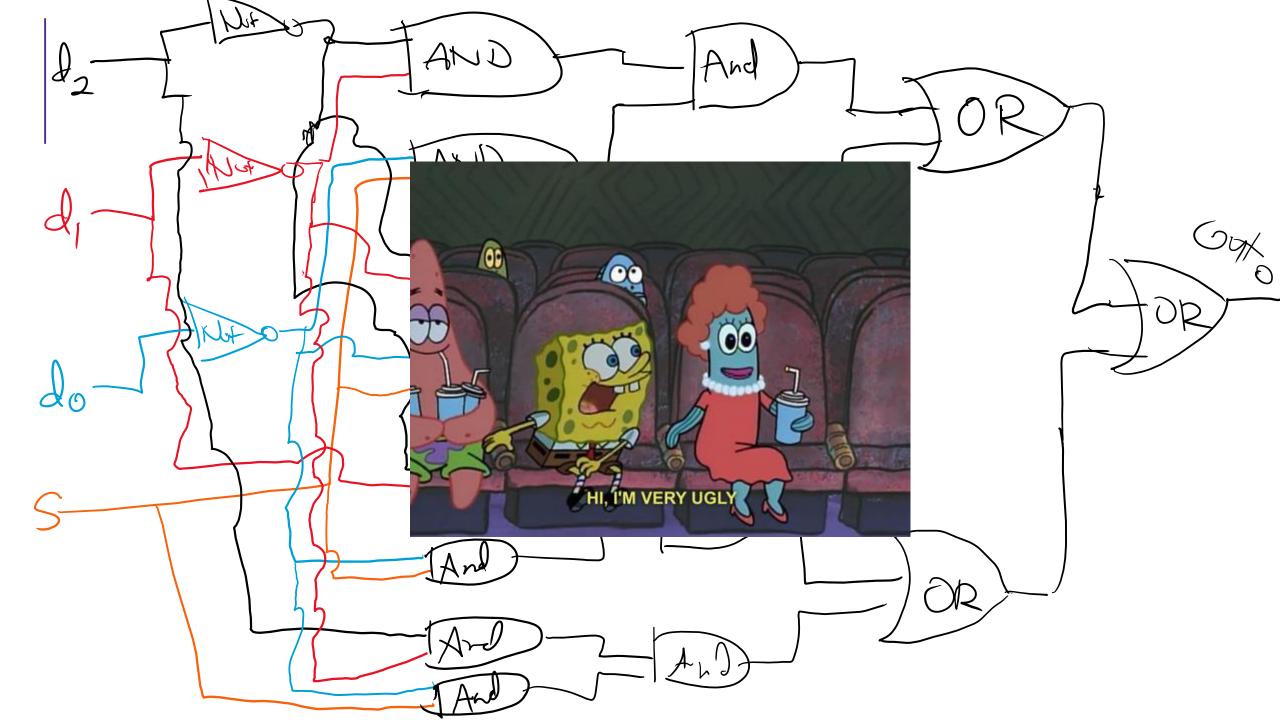

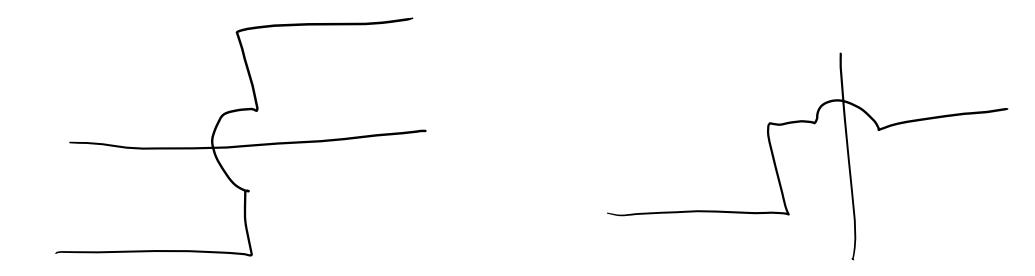
#### WOW that's ugly.


Be careful when wires cross – draw one "jumping over" the other.


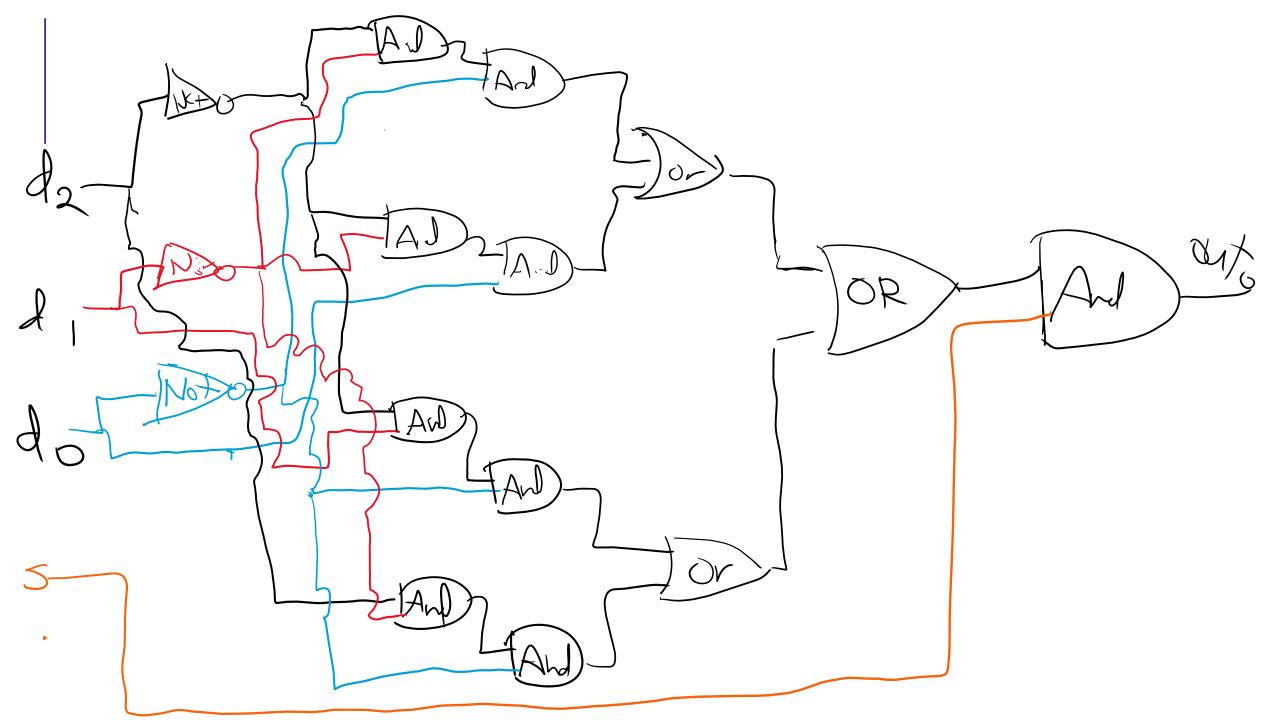
## Can we do better

Maybe the factored version will be better?



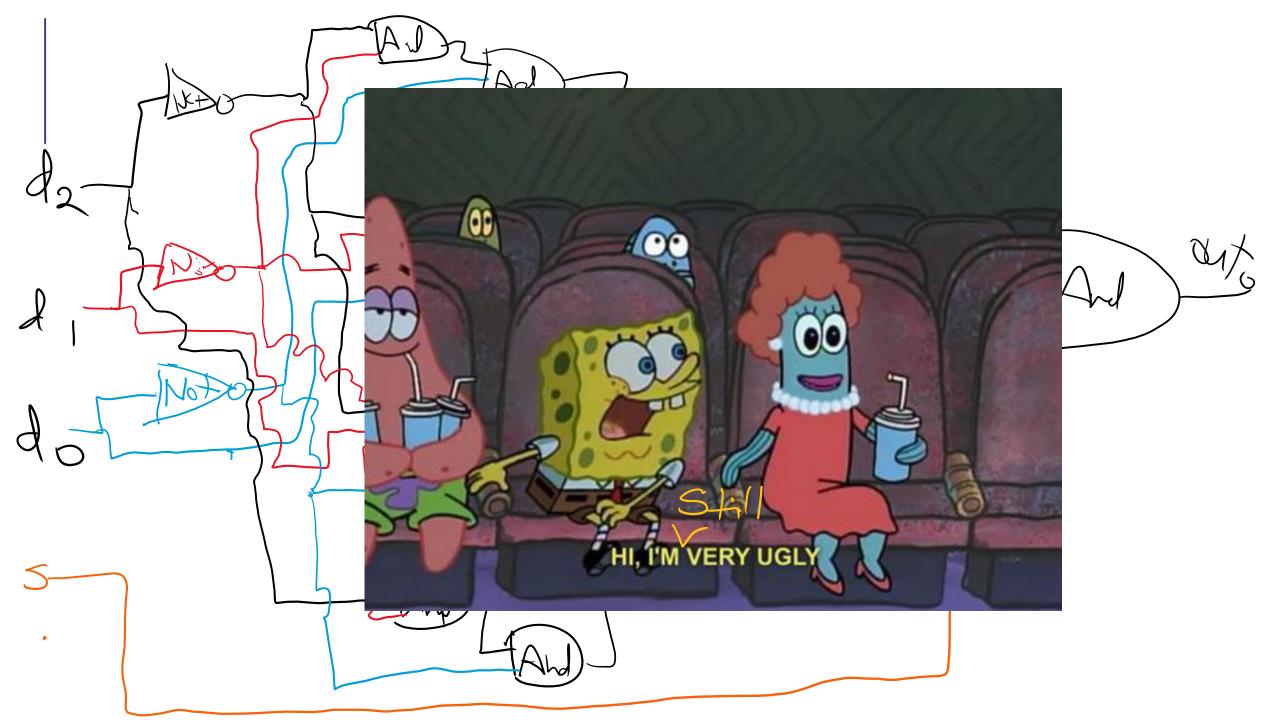


Ehhhhhh, it's a little better?

Part of the problem here is Robbie's art skills.

Part is some layout choices – commuting the terms might make things prettier.

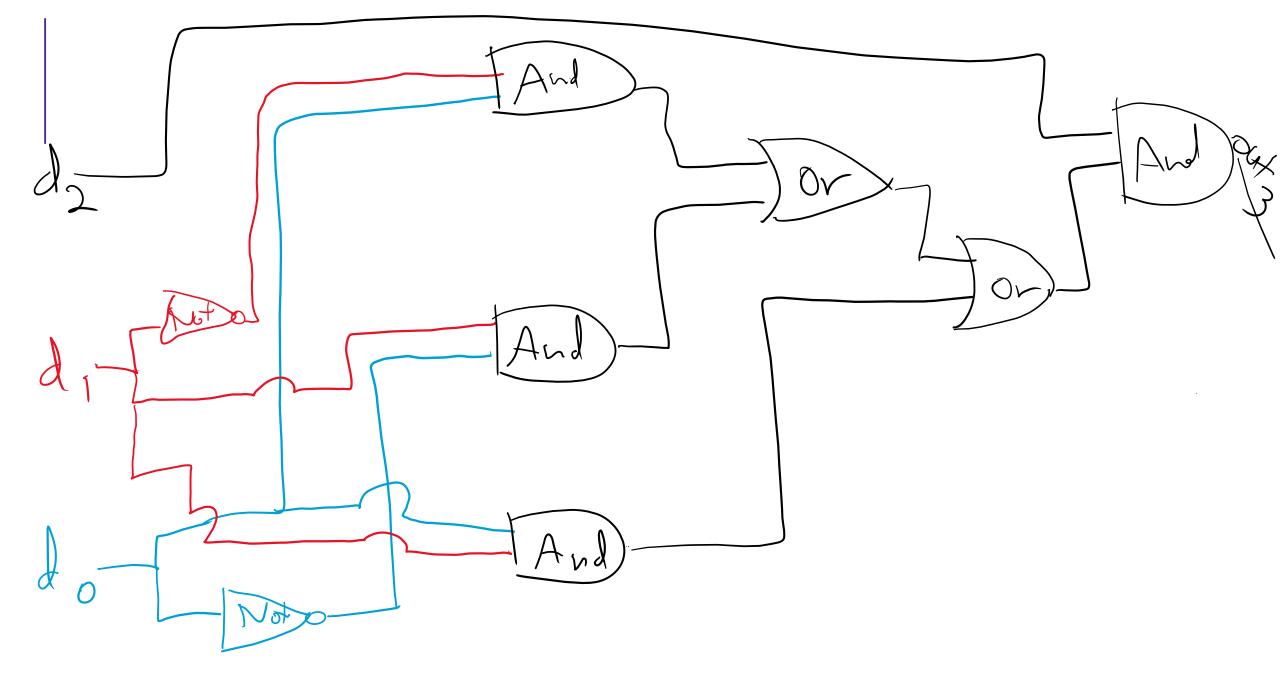Most of the problem is just the circuit is complicated.  $out_3$  is a little better.



### Can we use these for anything?

Sometimes these concrete formulas lead to easier observations.

For example, we might have noticed we factored out s or s' in three of the four, which suggests switching s first.

```
if(talkToSomeone) {
        if ( (day==Monday || day==Tuesday || day==Wednesday || day==Friday) )
 2
 3
            return "office hours";
        else if( day==Thursday)
 4
 5
            return "section";
        else
 6
 7
            return "text a friend";
 8
 9
   else {
10
        if ( (day==Monday || day==Tuesday || day==Wednesday || day==Thursday || day==Friday) )
11
            return "Ed";
12
        else
13
            return "text a friend";
14
```

### Can we use these for anything?

Is this code better? Maybe, maybe not.

It's another tool in your toolkit for thinking about logic Including logic you write in code!

```
if(talkToSomeone) {
 2
        if ( (day==Monday || day==Tuesday || day==Wednesday || day==Friday) )
 3
            return "office hours";
        else if( day==Thursday)
 4
 5
            return "section";
        else
 6
 7
            return "text a friend";
 8
 9
   else {
10
        if ( (day==Monday || day==Tuesday || day==Wednesday || day==Thursday || day==Friday) )
11
            return "Ed";
12
        else
13
            return "text a friend";
14
```

#### Takeaways

Yet another notation for propositions.

These are just more representations – there's only **one** underlying set of rules.

Next time: wrap up digital logic and the tool really represent x > 5.

## Another Proof

Let's prove that  $(p \land q) \rightarrow (q \lor p)$  is a tautology.

Alright, what are we trying to show?

# Another Proof

$$(p \land q) \rightarrow (q \lor p) \equiv \neg (p \land q) \lor (q \lor p) \\ \equiv (\neg p \lor \neg q) \lor (q \lor p) \\ \equiv (\neg p \lor \neg q) \lor (q \lor p) \\ \equiv \neg p \lor (\neg q \lor (q \lor p)) \\ \equiv \neg p \lor ((\neg q \lor q) \lor p) \\ \equiv \neg p \lor ((\neg q \lor q) \lor p) \\ \equiv \neg p \lor ((q \lor \neg q) \lor p) \\ \equiv \neg p \lor ((q \lor \neg q) \lor p) \\ \equiv \neg p \lor (T \lor p)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Law of Implication  
$$= \neg p \lor (p \lor T)$$
 Comparison of the parentheses/just a gut feeling  
$$= p \lor \neg p$$
 Supplify Usitive (blegation for the p, \neg p).

We're done!

# Another Proof

$$(p \land q) \rightarrow (q \lor p) \equiv \neg (p \land q) \lor (q \lor p)$$
Law of implication  
$$\equiv (\neg p \lor \neg q) \lor (q \lor p)$$
DeMorgan's Law  
$$\equiv \neg p \lor (\neg q \lor (q \lor p))$$
Associative  
$$\equiv \neg p \lor ((\neg q \lor q) \lor p)$$
Associative  
$$\equiv \neg p \lor ((q \lor \neg q) \lor p)$$
Commutative  
$$\equiv \neg p \lor (T \lor p)$$
Negation  
$$\equiv \neg p \lor (p \lor T)$$
Commutative  
$$\equiv \neg p \lor p$$
Domination  
$$\equiv p \lor \neg p$$
Commutative  
$$\equiv T$$
Negation