

Review Problem: Basic Verilog

- Write the Verilog for a 2-input gate that is TRUE when an odd number of inputs are true.

// VERILOG FOR $A \oplus B = \bar{A}B + A\bar{B}$

```
module XOR1(x,A,B)
  output x;
  input A,B;
  assign x=(A & ~B) | (~A & B);
endmodule
```

Review Problem: flip-flops

- The following two flip-flops are subtly different, but both useful. The difference in code is shown in bold. What is the difference in their behavior?

```
module D_FF1 (q, d, reset, clk);
    output q;
    input d, reset, clk;
    reg q;

    always @(posedge clk)
    if (reset)
        q <= 0;
    else
        q <= d;

endmodule
```

SYNCHRONOUS RESET
ONLY RESETS ON
CLOCK EDGE

```
module D_FF2 (q, d, reset, clk);
    output q;
    input d, reset, clk;
    reg q;


    always @(posedge clk or posedge reset)
    if (reset)
        q <= 0;
    else
        q <= d;

endmodule
```

ASYNCHRONOUS RESET
WILL RESET AT ANY TIME

Case Study: Seven Segment Display


- Chip to drive digital display

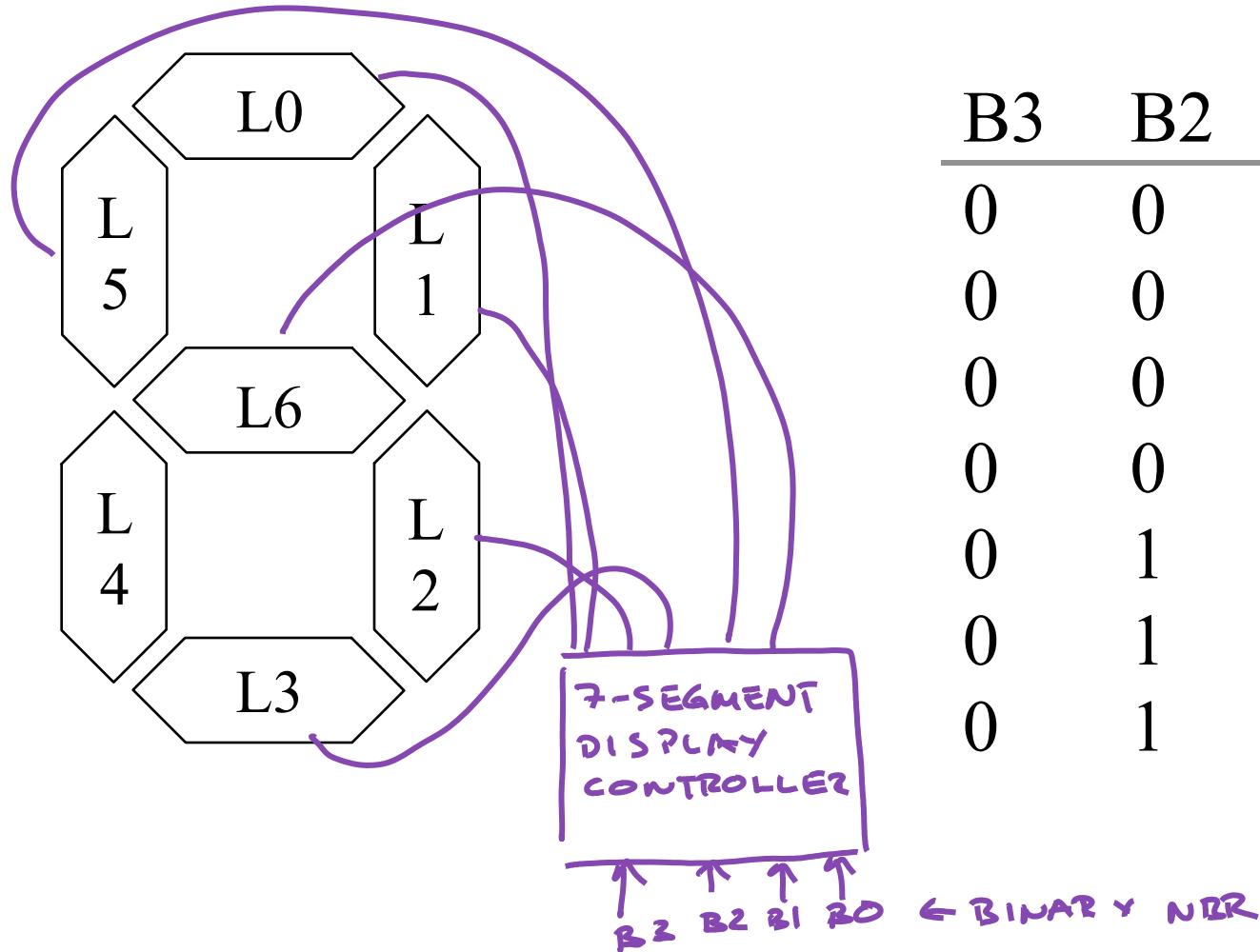


B3	B2	B1	B0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0

Case Study (cont.)

DESIGN EXAMPLE

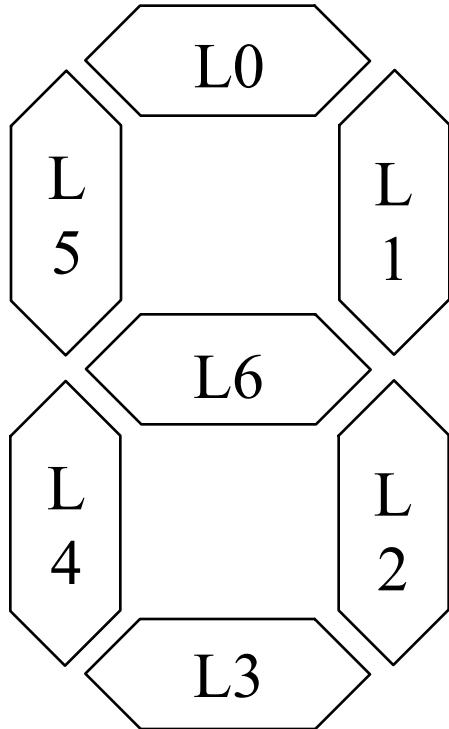

B3	B2	B1	B0	Val	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	0	1	1	0	0	0	0
0	0	1	0	2	1	1	0	1	1	0	1
0	0	1	1	3	1	1	1	1	0	0	1
0	1	0	0	4	0	1	1	0	0	1	1
0	1	0	1	5	1	0	1	1	0	1	1
0	1	1	0	6	1	0	1	1	1	1	1
0	1	1	1	7	1	1	1	0	0	0	0
1	0	0	0	8	1	1	1	1	1	1	1
1	0	0	1	9	1	1	1	1	0	1	1

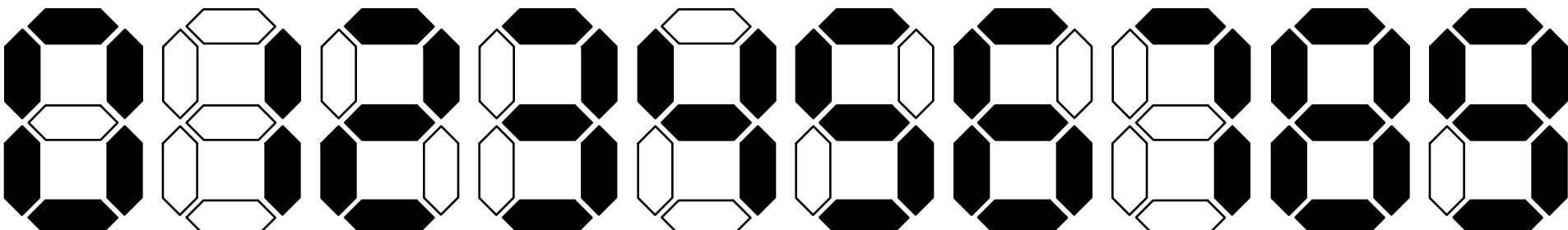

Case Study (cont.)

■ Implement L5:

B3	B2	B1	B0	L5
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1

$$L5 = B_3 + \overline{B_1} \overline{B_0} + B_2 \overline{B_0} + B_2 \overline{B_1}$$

(E.G. FROM K-MAP)

7-seg display in Verilog


■ Verilog RTL: just describe what you want

```
module seg7 (bcd, leds);
    input      [3:0] bcd;
    output reg [6:0] leds;

    always @(*)
        case (bcd)
            // 3210          6543210
            4'b0000: leds = 7'b0111111;
            4'b0001: leds = 7'b00000110;
            4'b0010: leds = 7'b1011011;
            4'b0011: leds = 7'b1001111;
            4'b0100: leds = 7'b1100110;
            4'b0101: leds = 7'b1101101;
            4'b0110: leds = 7'b1111101;
            4'b0111: leds = 7'b0000111;
            4'b1000: leds = 7'b1111111;
            4'b1001: leds = 7'b1101111;
            default: leds = 7'bx;
        endcase
endmodule
```

Review Problem

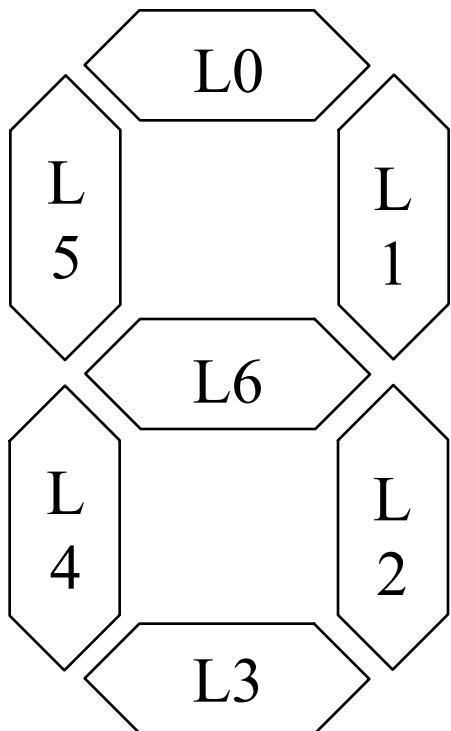- Extend this Verilog code to also show the letter “A” on input pattern 1010 (ten) and “F” on pattern 1111 (fifteen).





$4'b1010: \text{leds} = 7'b1110111;$
 $4'b1111: \text{leds} = 7'b1110001;$

```
module seg7 (bcd, leds);
    input      [3:0] bcd;
    output reg [6:0] leds;


    always @(*)
        case (bcd)
            // BCD []
            // 3210          LEDS []
            // 6543210
            4'b0000: leds = 7'b0111111;
            4'b0001: leds = 7'b00000110;
            4'b0010: leds = 7'b1011011;
            4'b0011: leds = 7'b1001111;
            4'b0100: leds = 7'b1100110;
            4'b0101: leds = 7'b1101101;
            4'b0110: leds = 7'b1111101;
            4'b0111: leds = 7'b00000111;
            4'b1000: leds = 7'b1111111;
            4'b1001: leds = 7'b1101111;
            default: leds = 7'bX;
        endcase
    endmodule
```

Flipflop Realities 1: Gating the Clock

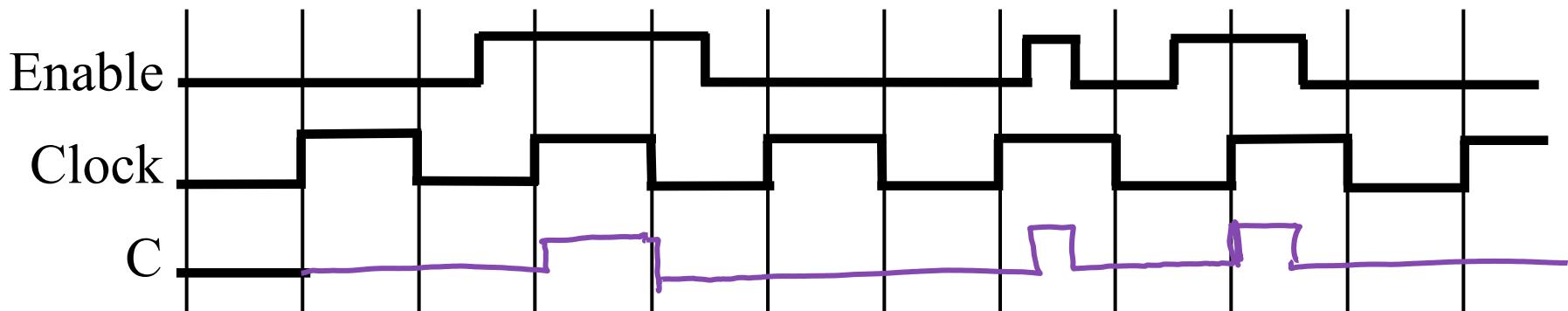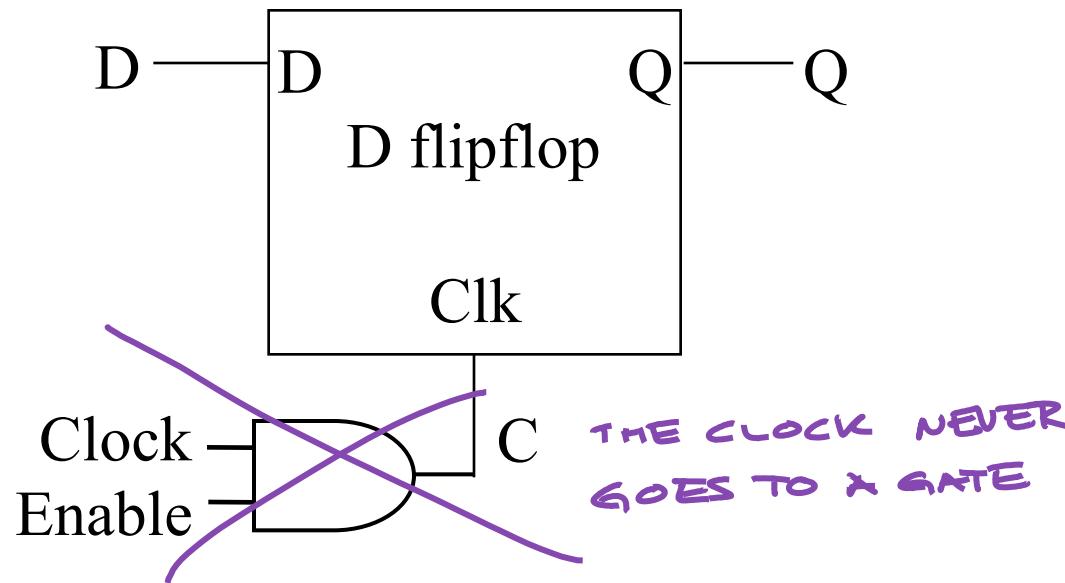


- **NEVER put a logic gate between the clock and DFF's CLK input.**

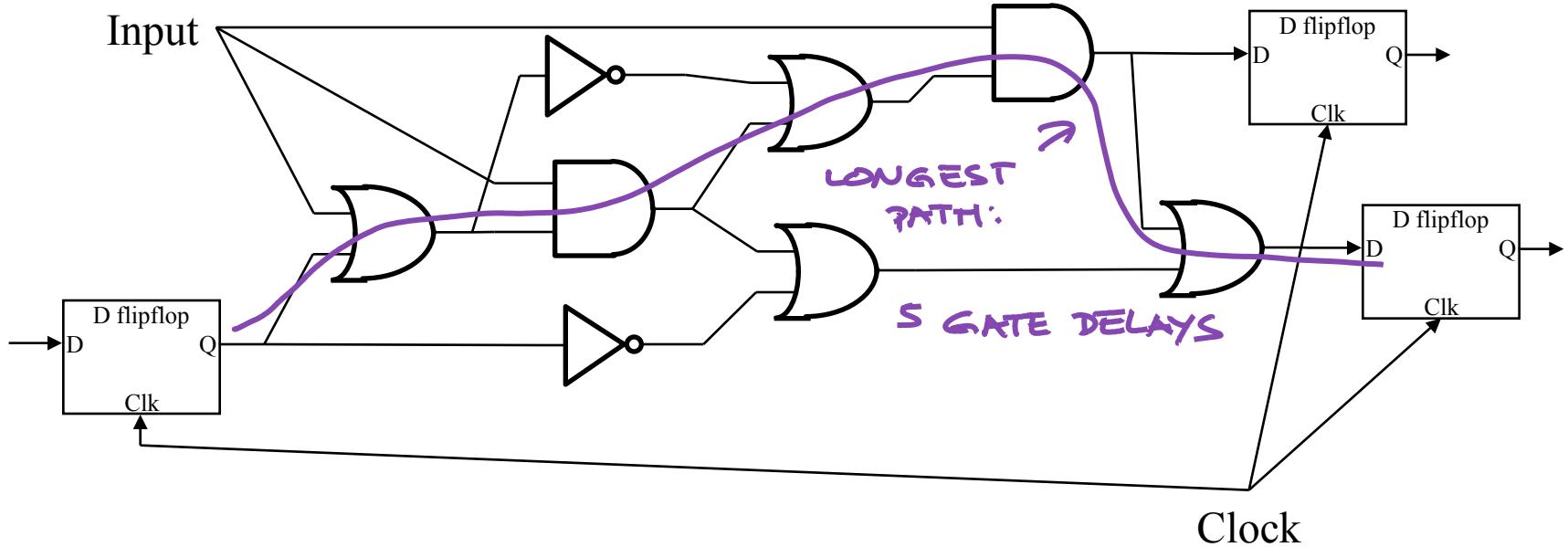Flipflop Realities 2: Clock Period, Applying Stimulus



■ Clock Period?

■ Apply Inputs when?

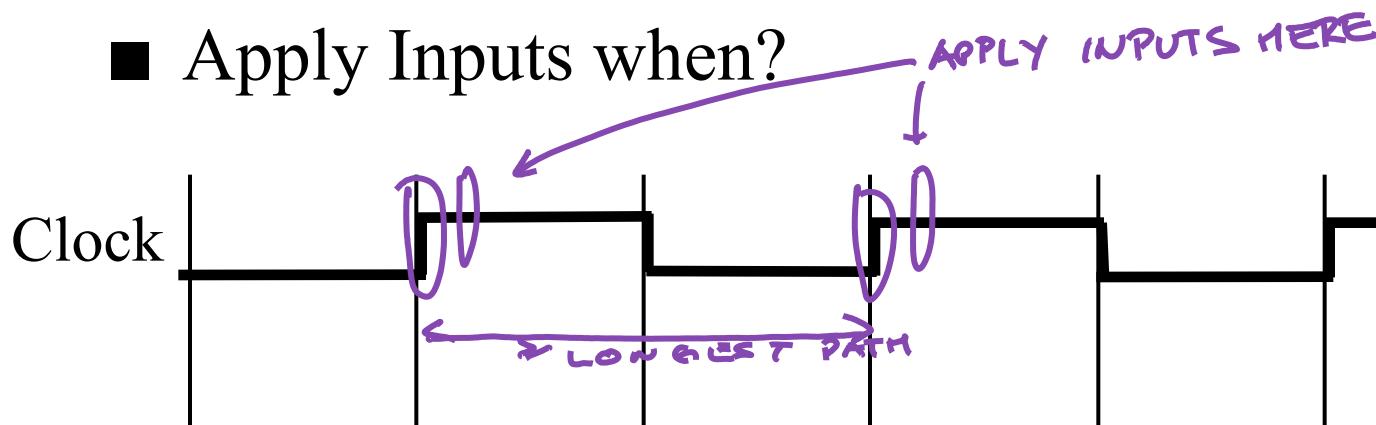


T_{setup} , T_{hold} , Clk->Q

- Flipflops require their inputs be stable for time period around clock edge

T_{setup} : TIME ADDED TO END OF CRITICAL PATH

T_{hold} : DON'T HAVE FAST PATH

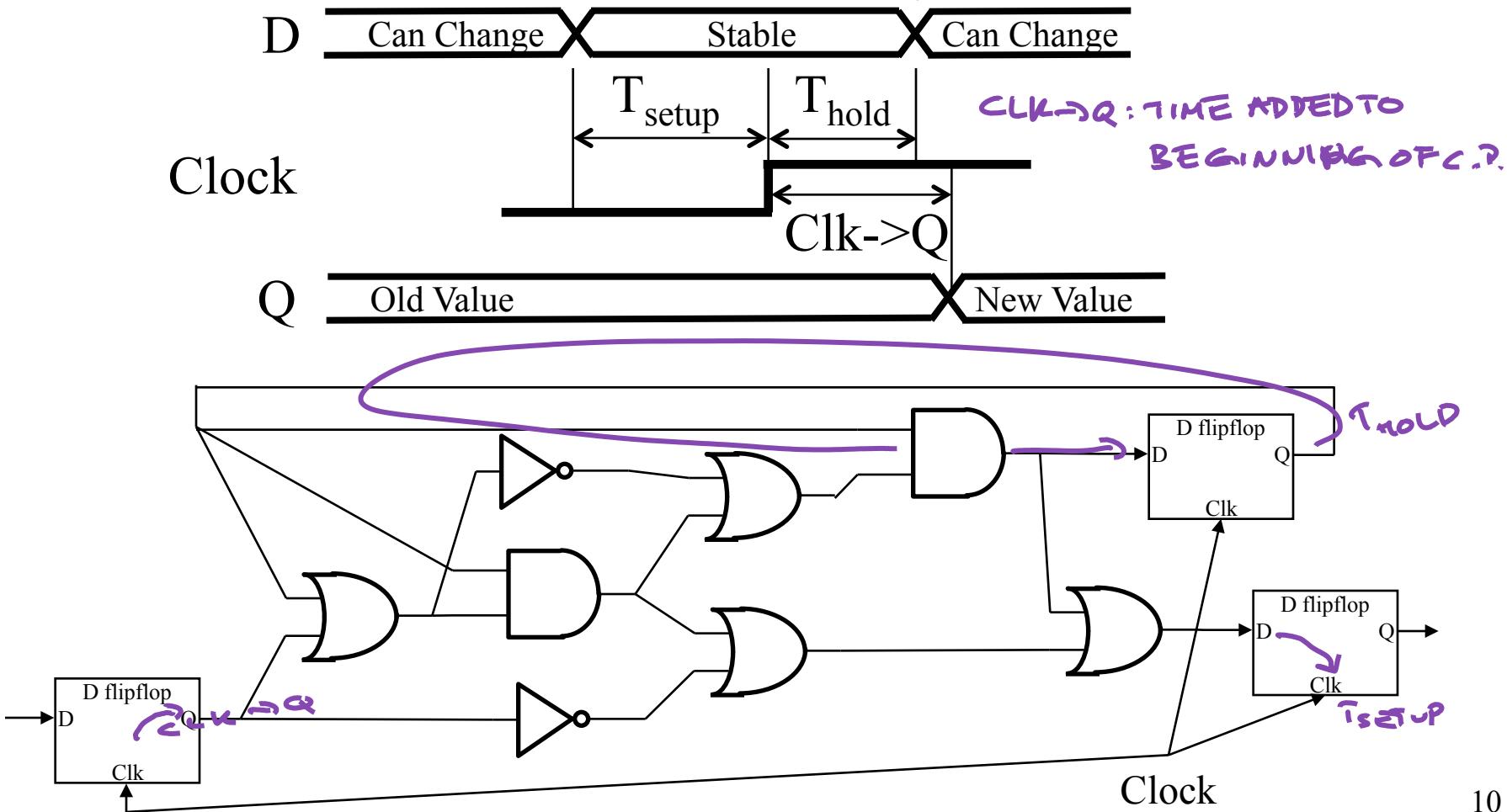


Timing Definitions

- T_{setup} : Time D must be stable BEFORE clock edge
 - Adds to critical path delay
- Clk->Q: Time from clock edge to Q changing
 - Adds to critical path delay
- T_{hold} : Time D must be stable AFTER clock edge
 - Sets minimum path from Q of one DFF to D of another


Flipflop Realities 3: External Inputs

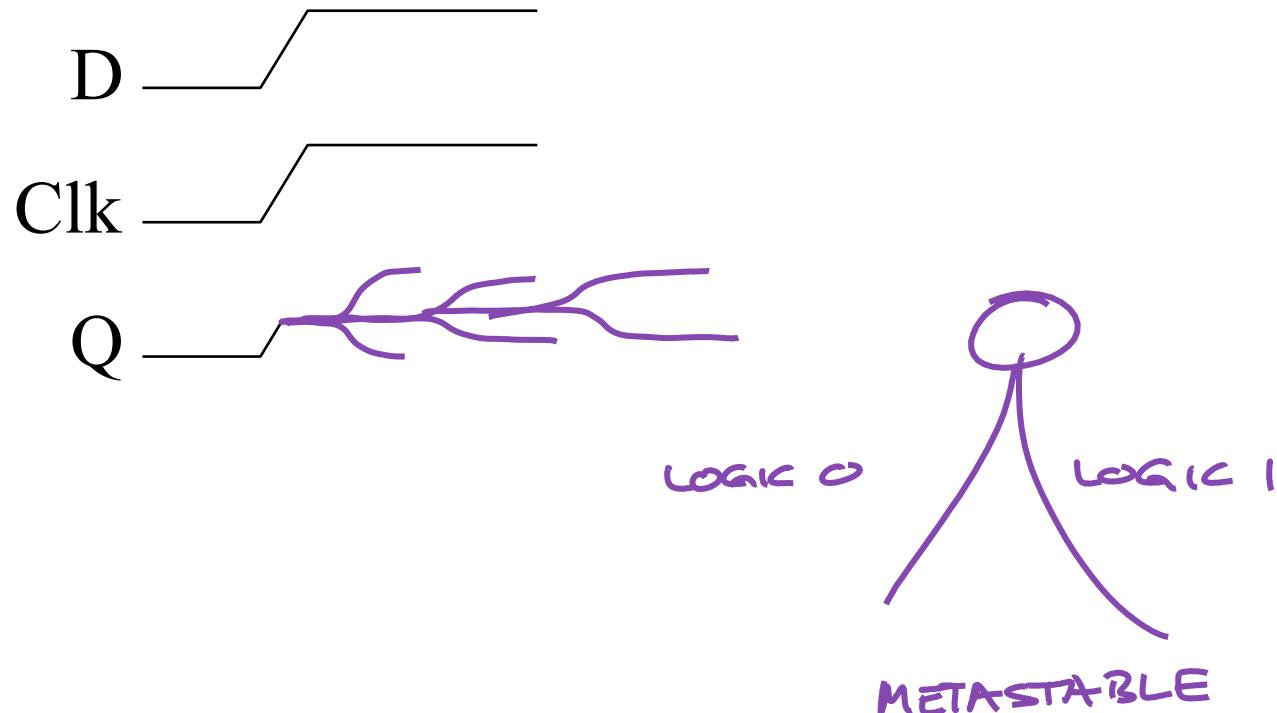- External inputs aren't synchronized to the clock




Dealing with Metastability

■ Single DFF

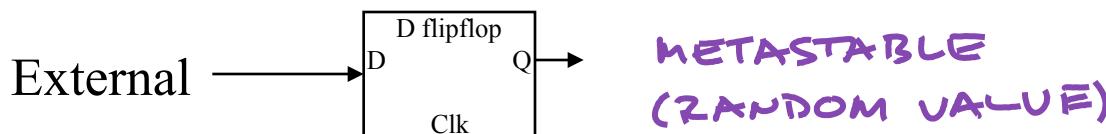

■ 2 DFFs in series

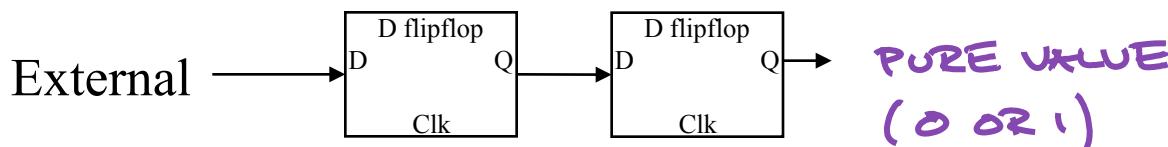

■ 2 DFFs in parallel

