
 
 


Overview

◆ Today

- Finish up with Latches
- State diagrams
- Synchronous Vs Asynchronous Inputs

Latches versus flip-flops

 


behavior is the same **unless** input changes while the clock is high

The SR latch


- ◆ Cross-coupled NOR gates

 - Can set ($S=1, R=0$) or reset ($R=1, S=0$) the output




- ◆ Cross-coupled NAND gates

 - Can set ($S=1, R=0$) or reset ($R=1, S=0$) the output




SR latch behavior

◆ Truth table and timing

 


| S | R | Q |
|---|---|----------|
| 0 | 0 | hold |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | disallow |

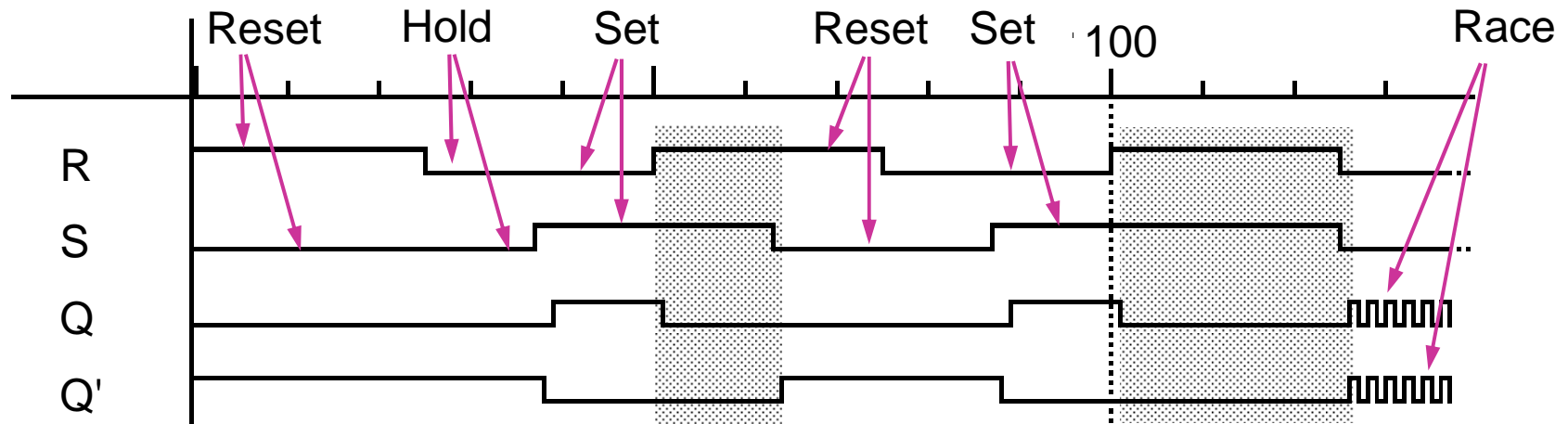

SR latch is glitch sensitive

 - ◆ Static 0 hazards can set/reset latch
 - Glitch on S input sets latch
 - Glitch on R input resets latch



Clear and preset in flip-flops



- ◆ **Clear** and **Preset** set flip-flop to a known state
 - Used at startup, reset
- ◆ **Clear** or **Reset** to a logic 0
 - Synchronous: $Q=0$ when next clock edge arrives
 - Asynchronous: $Q=0$ when reset is asserted
 - ⚡ Doesn't wait for clock
 - ⚡ Quick but dangerous
- ◆ **Preset** or **Set** the state to logic 1
 - Synchronous: $Q=1$ when next clock edge arrives
 - Asynchronous: $Q=1$ when reset is asserted
 - ⚡ Doesn't wait for clock
 - ⚡ Quick but dangerous

State diagrams

- ◆ How do we characterize logic circuits?
 - Combinational circuits: **Truth tables**
 - Sequential circuits: **State diagrams**
- ◆ First draw the states
 - **States** \equiv Unique circuit configurations
- ◆ Second draw the transitions between states
 - **Transitions** \equiv Changes in state caused by inputs

  Example: SR latch



- ◆ Begin by drawing the states
 - States \equiv Unique circuit configurations
 - Possible values for feedback (Q, Q')



Example: SR latch


- ◆ Now draw the state transitions

- Labeling inputs

  

Observed SR latch behavior

 - ◆ The 1–1 state is transitory
 - Either R or S “gets ahead”
 - Latch settles to 0–1 or 1–0 state ambiguously
 - Race condition → non-deterministic transition
 - ↙ Disallow $(R,S) = (1,1)$



System considerations

- ◆ Use edge-triggered flip-flops wherever possible
 - Avoid latches

- ◆ Basic rules for correct timing
 - Clock flip-flops synchronously (all at the same time)
 - ⚡ No flip-flop changes state more than once per clock cycle
 - ⚡ FF propagation delay > hold time
 - Avoid mixing positive-edge triggered and negative-edge triggered flip-flops in the same circuit

Asynchronous inputs

- ◆ Clocked circuits are **synchronous**
 - Circuit changes state only at clock edges
 - Signals (voltages) settle in-between clock edges
- ◆ Unclocked circuits or signals are **asynchronous**
 - No master clock
 - Real-world inputs (e.g. a keypress) are asynchronous
- ◆ Synchronous circuits have asynchronous inputs
 - Reset signal, memory wait, user input, etc.
 - Inputs “bounce”
 - Inputs can change at any time
 - ⚡ We must **synchronize the input** to our clock
 - ⚡ Inputs will violate flip-flop setup/hold times