

## Lecture 21

---

### ◆ Logistics

- HW8 due on Friday, HW9 due a week from today (last one)
- Lab --- make sure you are done before the end of next week.
- Midterm 2: mean 74, median 75, std 15.

### ◆ Last lecture

- Robot ant in maze
- Started on FSM simplification a little bit



### ◆ Today

- More on FSM simplification

## FSM Minimization


---
  
### ◆ Two simple FSMs for odd parity checking



 
## Collapsing States

- ◆ We can make the top machine match the bottom machine by collapsing states  $S_0$  and  $S_2$  onto one state



 
## FSM Design on the Cheap

- ◆ Let's say we start with this FSM for even parity checking


 
## FSM Design on the Cheap

- ◆ Now an enterprising engineer comes along and says, "Hey, we can turn our even parity checker into an odd parity checker by just adding one state."



## Two Methods for FSM Minimization

- ◆ Row matching
  - Easier to do by hand
  - Misses minimization opportunities
- ◆ Implication table
  - Guaranteed to find the most reduced FSM
  - More complicated algorithm (but still relatively easy to write a program to do it)


## A simple problem

---

- ◆ Design a Mealy machine with a single bit input and a single bit output. The machine should output a 0, except once every four cycles, if the previous four inputs matched one of two patterns (0110, 1010)
- ◆ Example input/output trace:  
in:        0010 0110 1100 1010 0011 ...  
out:       0000 0001 0000 0001 0000 ...

## ... and a simple solution

---

 

## Find matching rows

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_7$	$S_8$	0	0
01	$S_4$	$S_9$	$S_{10}$	0	0
10	$S_5$	$S_{11}$	$S_{12}$	0	0
11	$S_6$	$S_{13}$	$S_{14}$	0	0
000	$S_7$	$S_0$	$S_0$	0	0
001	$S_8$	$S_0$	$S_0$	0	0
010	$S_9$	$S_0$	$S_0$	0	0
011	$S_{10}$	$S_0$	$S_0$	1	0
100	$S_{11}$	$S_0$	$S_0$	0	0
101	$S_{12}$	$S_0$	$S_0$	1	0
110	$S_{13}$	$S_0$	$S_0$	0	0
111	$S_{14}$	$S_0$	$S_0$	0	0

CSE370, Lecture 21

9

## Merge the matching rows

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_7$	$S_8$	0	0
01	$S_4$	$S_9$	$S_{10}$	0	0
10	$S_5$	$S_{11}$	$S_{10}$	0	0
11	$S_6$	$S_{13}$	$S_{14}$	0	0
000	$S_7$	$S_0$	$S_0$	0	0
001	$S_8$	$S_0$	$S_0$	0	0
010	$S_9$	$S_0$	$S_0$	0	0
011 or 101	$S_{10}$	$S_0$	$S_0$	1	0
100	$S_{11}$	$S_0$	$S_0$	0	0
110	$S_{13}$	$S_0$	$S_0$	0	0
111	$S_{14}$	$S_0$	$S_0$	0	0

CSE370, Lecture 21

10


## Merge until no more rows match

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_7$	$S_7$	0	0
01	$S_4$	$S_7$	$S_{10}$	0	0
10	$S_5$	$S_7$	$S_{10}$	0	0
11	$S_6$	$S_7$	$S_7$	0	0
Not (011 or 101)	$S_7$	$S_0$	$S_0$	0	0
011 or 101	$S_{10}$	$S_0$	$S_0$	1	0

## The final state transition table

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_4$	$S_3$	0	0
00 or 11	$S_3$	$S_7$	$S_7$	0	0
01 or 10	$S_4$	$S_7$	$S_{10}$	0	0
Not (011 or 101)	$S_7$	$S_0$	$S_0$	0	0
011 or 101	$S_{10}$	$S_0$	$S_0$	1	0


## A more efficient solution

 

CSE370, Lecture 21

13
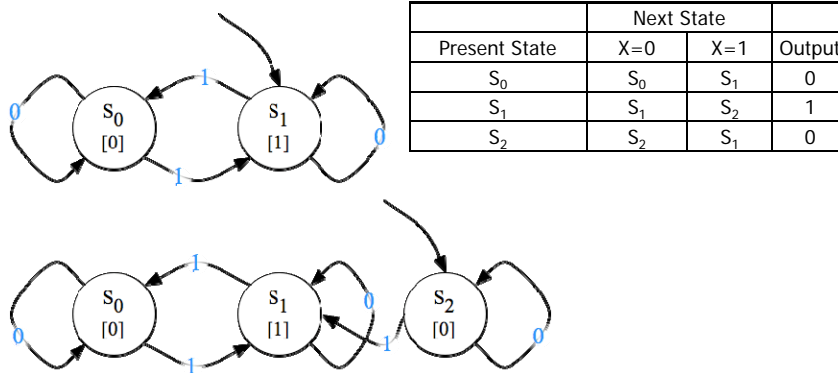
## Simple row matching does not guarantee most reduced state machine




CSE370, Lecture 21


14

## The Implication chart method

- ◆ Here's a slightly funkier FSM

 


## Step 1: Draw the table

 


$s_0$						
$s_1$						
$s_2$						
$s_3$						
$s_4$						
$s_5$						
	$s_0$	$s_1$	$s_2$	$s_3$	$s_4$	$s_5$




## Step 2: Consider the outputs

 


## Step 3: Add transition pairs

 

 
## Step 4 (repeated): Consider transitions




## Final reduced FSM

 

## Odd parity checker revisited

 


Present State	Next State		Output
	X=0	X=1	
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0
S <sub>1</sub>	S <sub>1</sub>	S <sub>2</sub>	1
S <sub>2</sub>	S <sub>2</sub>	S <sub>1</sub>	0

 

## More complex state minimization

### ◆ Multiple input example

 

inputs here


present state	next state				output
	00	01	10	11	
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

symbolic state transition table

## Minimized FSM
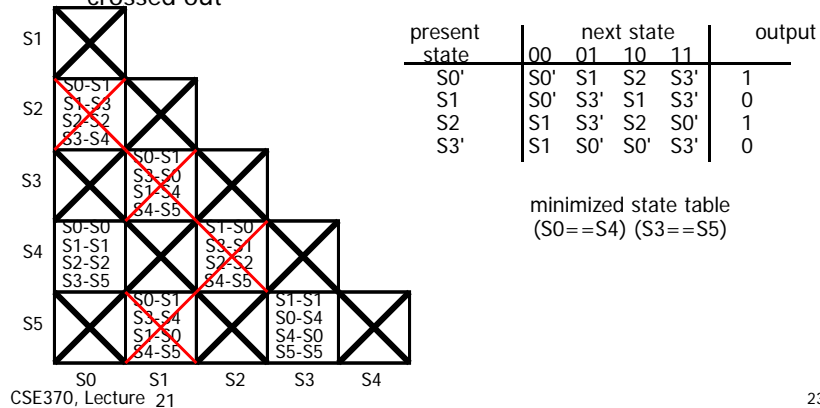
### ◆ Implication chart method

- cross out incompatible states based on outputs
- then cross out more cells if indexed chart entries are already crossed out



## Minimizing incompletely specified FSMs

- ◆ Equivalence of states is transitive when machine is fully specified
- ◆ But its not transitive when don't cares are present


e.g., state output

S0	- 0	S1 is compatible with both S0 and S2
S1	1 -	but S0 and S2 are incompatible
S2	- 1	

- ◆ Hard to determining best grouping of states to yield the smallest number of final states

## Minimizing FSMs isn't always good


- ◆ Two FSMs for 0->1 edge detection

 

CSE370, Lecture 21

25
 
## Minimal state diagram -> not necessarily best circuit



In	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>1</sub> <sup>+</sup>	Q <sub>0</sub> <sup>+</sup>
0	0	0	0	0
0	0	1	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	1	1	1
-	1	0	0	0

$$Q_1^+ = \text{In} \cdot (Q_1 \text{ xor } Q_0)$$


$$Q_0^+ = \text{In} \cdot Q_1' \cdot Q_0'$$

$$\text{Out} = Q_1' \cdot Q_0$$

CSE370, Lecture 21

26
 
## Minimal state diagram -> not necessarily best circuit




In	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>1</sub> <sup>+</sup>	Q <sub>0</sub> <sup>+</sup>
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	1
1	1	0	0	1
1	1	1	1	1

$$Q_1^+ = Q_0$$

$$Q_0^+ = \text{In}$$

$$\text{Out} = Q_1' Q_0$$
 
## Circuit is simpler for non-simplified FSM



## A little perspective

---

- ◆ These kinds of optimizations are what CAD(Computer Aided Design)/EDA(Electronic Design Automation) is all about
- ◆ The interesting problems are almost always computationally intractable to solve optimally
- ◆ People **really** care about the automation of the design of billion-transistor chips