

## Lecture 7

---

- ◆ Logistics
  - Homework 2 due today
  - Homework 3 out today due next Wednesday
  - First midterm a week Friday: Friday Jan 30
    - ↳ Will cover up to the end of Multiplexers/DeMultiplexers
- ◆ Last lecture
  - K-Maps
- ◆ Today
  - Verilog
    - ↳ Structural constructs
    - ↳ Describing combinational circuits

## Summary of two-level combinational-logic

---

- ◆ Logic functions and truth tables
  - AND, OR, Buf, NOT, NAND, NOR, XOR, XNOR
  - Minimal set
- ◆ Axioms and theorems of Boolean algebra
  - Proofs by re-writing
  - Proofs by truth table
- ◆ Gate logic
  - Networks of Boolean functions
  - NAND/NOR conversion and de Morgan's theorem
- ◆ Canonical forms
  - Two-level forms
  - Incompletely specified functions (don't cares)
- ◆ Simplification
  - Two-level simplification (K-maps)

## Solving combinational design problems

---

- ◆ Step 1: Understand the problem
  - Identify the inputs and outputs
  - Draw a truth table
- ◆ Step 2: Simplify the logic
  - Draw a K-map
  - Write a simplified Boolean expression
    - ↳ SOP or POS
    - ↳ Use don't cares
- ◆ Step 3: Implement the design
  - Logic gates and/or
  - Verilog

## Ways of specifying circuits

---

- ◆ Schematics
  - Structural description
  - Describe circuit as interconnected elements
    - ↳ Build complex circuits using hierarchy
      - ◆ Large circuits are unreadable
- ◆ HDLs
  - Hardware description languages
    - ↳ **Not** programming languages
    - ↳ Parallel languages tailored to digital design
  - Synthesize code to produce a circuit

## Hardware description languages (HDLs)

---

- ◆ Abel (~1983)
  - Developed by Data-I/O
  - Targeted to PLDs (programmable logic devices)
  - Limited capabilities (can do state machines)
- ◆ Verilog (~1985)
  - Developed by Gateway (now part of Cadence)
  - **Syntax** similar to C
  - Moved to public domain in 1990
- ◆ VHDL (~1987)
  - DoD (Department of Defence) sponsored
  - **Syntax** similar to Ada


## Verilog versus VHDL

---

- ◆ Both "IEEE standard" languages
- ◆ Most tools support both
- ◆ Verilog is "simpler"
  - Less syntax, fewer constructs
- ◆ VHDL is more structured
  - Can be better for large, complex systems
  - Better modularization
 
## Simulation and synthesis

- ◆ Simulation
  - "Execute" a design to verify correctness
- ◆ Synthesis
  - Generate a physical implementation from HDL code



CSE370, Lecture 7

7

## Simulation and synthesis (con't)

- ◆ Simulation
  - Models what a circuit does
    - ↳ Multiply is "\*" , ignoring implementation options
  - Can include static timing
  - Allows you to test design options
- ◆ Synthesis
  - Converts your code to a netlist
    - ↳ Can simulate synthesized design
  - Tools map your netlist to hardware
- ◆ Simulation and synthesis in the CSE curriculum
  - CSE370: Learn simulation
  - CSE467: Learn synthesis


CSE370, Lecture 7

8
 
## Simulation

- ◆ You provide an environment
  - Using non-circuit constructs
    - ↳ Active-HDL waveforms, Read files, print
  - Using Verilog simulation code
    - ↳ A "test fixture"

Note: We will ignore timing and test benches until later




CSE370, Lecture 7

9
 
## Specifying circuits in Verilog

- ◆ There are three major styles
  - Instances and wires
  - Continuous assignments
  - "always" blocks



"Structural"

```

wire E;
and g1(E,A,B);
not g2(Y,C);
or g3(X,E,Y);
    
```

"Behavioral"

```

wire E;
assign E = A & B;
assign Y = ~C;
assign X = E | Y;
    
```

```

reg E, X, Y;
always @ (A or B or C)
begin
  E = A & B;
  Y = ~C;
  X = E | Y;
end
    
```

CSE370, Lecture 7

10

## Data types

- ◆ Values on a wire
  - 0, 1, x (unknown or conflict), z (tristate or unconnected)
- ◆ Vectors
  - A[3:0] vector of 4 bits: A[3], A[2], A[1], A[0]
    - ↳ Unsigned integer value
    - ↳ Indices **must** be constants
  - Concatenating bits/vectors
    - ↳ e.g. sign extend
      - ◆ B[7:0] = {A[3], A[3], A[3], A[3], A[3:0]};
      - ◆ B[7:0] = {4{A[3]}, A[3:0]};
  - Style: Use a[7:0] = b[7:0] + c[7:0]
    - Not a = b + c;
  - Legal syntax: C = &A[6:7]; // logical and of bits 6 and 7 of A

CSE370, Lecture 7

11

## Data types that do not exist

- ◆ Structures
- ◆ Pointers
- ◆ Objects
- ◆ Recursive types
- ◆ (Remember, Verilog is not C or Java or Lisp or ...!)

CSE370, Lecture 7

12

## Numbers

- ◆ Format: <sign><size><base format><number>
- ◆ 14
  - Decimal number
- ◆ -4'b11
  - 4-bit 2's complement binary of 0011 (is 1101)
- ◆ 12'b0000\_0100\_0110
  - 12 bit binary number ( \_ is ignored)
- ◆ 12'h046
  - 3-digit (12-bit) hexadecimal number
- ◆ Verilog values are unsigned
  - $C[4:0] = A[3:0] + B[3:0]$ ;
    - ↳ if  $A = 0110$  (6) and  $B = 1010$ (-6), then  $C = 10000$  (*not* 00000)
    - ↳ B is zero-padded, *not* sign-extended

CSE370, Lecture 7

13

## Operators

Verilog Operator	Name	Functional Group
[ ]	bit-select or part-select	
( )	parenthesis	
! , ~	logical negation	Logical
& , &&	reduction AND	Bit-wise
,	reduction OR	Reduction
~& , ~	reduction NAND	Reduction
^ , ^~	reduction XOR	Reduction
~^ , ~^~	reduction XNOR	Reduction
+	unary (sign) plus	Arithmetic
-	unary (sign) minus	Arithmetic
{ }	concatenation	Concatenation
{# }	replication	Replication
*, / , %	multiply, divide, modulus	Arithmetic
+, -	binary plus, binary minus	Arithmetic
<< , >>	shift left, shift right	Shift

>	greater than	Relational
>=	greater than or equal to	Relational
<	less than	Relational
<=	less than or equal to	Relational
==	logical equality	Equality
!=	logical inequality	Equality
===	case equality	Equality
!==	case inequality	Equality
&	bit-wise AND	Bit-wise
^	bit-wise XOR	Bit-wise
^~ , ^~^	bit-wise XNOR	Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional

Similar to C operators

CSE370, Lecture 7

14

## Two abstraction mechanisms


- ◆ Modules
  - More structural
  - Heavily used in 370 and "real" Verilog code
- ◆ Functions
  - More behavioral
  - Used to some extent in "real" Verilog, but not much in 370

CSE370, Lecture 7

15
 
## Basic building blocks: Modules

- Instantiated into a design (like macros)
  - ↳ Never called
- Illegal to nest module defs.
- Modules execute in parallel
- Names are case sensitive
- // for comments
- Name can't begin with a number
- Use wires for connections
- and, or, not are keywords
- All keywords are lower case
- Gate declarations (and, or, etc)
  - ↳ List outputs first
  - ↳ Inputs second




```
// first simple example
module smpl (X,Y,A,B,C);
input A,B,C;
output X,Y;
wire E;
and g1(E,A,B);
not g2(X,C);
or g3(X,E,Y);
endmodule
```

CSE370, Lecture 7

16

## Modules are circuit components

- Module has ports
  - ↳ External connections
  - ↳ A,B,C,X,Y in example
- Port types
  - ↳ input
  - ↳ output
  - ↳ inout (tristate)
- Use assign statements for Boolean expressions
  - ↳ and ↔ &
  - ↳ or ↔ |
  - ↳ not ↔ ~

 

```
// previous example as a
// Boolean expression
module smpl2 (X,Y,A,B,C);
input A,B,C;
output X,Y;
assign X = (A&B)|~C;
assign Y = ~C;
endmodule
```


CSE370, Lecture 7

17
 
## Structural Verilog

```
module xor_gate (out,a,b);
input a,b;
output out;
wire abar, bbar, t1, t2;
not inva (abar,a);
not invb (bbar,b);
and and1 (t1,abar,b);
and and2 (t2,bbar,a);
or or1 (out,t1,t2);
endmodule
```

8 basic gates (keywords):  
and, or, nand, nor  
buf, not, xor, xnor




CSE370, Lecture 7

18
 
## Behavioral Verilog

- Describe circuit behavior
  - Not implementation



```
module full_addr (Sum,Cout,A,B,Cin);
  input  A, B, Cin;
  output Sum, Cout;
  assign {Cout, Sum} = A + B + Cin;
endmodule
```

{Cout, Sum} is a concatenation

## Behavioral 4-bit adder

```
module add4 (SUM, OVER, A, B);
  input [3:0] A;
  input [3:0] B;
  output [3:0] SUM;
  output OVER;
  assign {OVER, SUM[3:0]} = A[3:0] + B[3:0];
endmodule
```

"[3:0] A" is a 4-wire bus labeled "A"  
 Bit 3 is the MSB  
 Bit 0 is the LSB

Can also write "[0:3] A"  
 Bit 0 is the MSB  
 Bit 3 is the LSB

Buses are implicitly connected  
 If you write BUS[3:2], BUS[1:0]  
 They become part of BUS[3:0]

## Continuous assignment

- Assignment is continuously evaluated
  - Corresponds to a logic gate
  - Assignments execute in parallel

```
assign A = X | (Y & ~Z);
assign B[3:0] = 4'b01XX;
assign C[15:0] = 16'h00ff;
assign #3 {Cout, Sum[3:0]} = A[3:0] + B[3:0] + Cin;
```

Boolean operators (~ for bit-wise negation)  
 bits can assume four values (0, 1, X, Z)  
 variables can be n-bits wide (MSB:LSB)  
 arithmetic operator  
 Gate delay (used by simulator)  
 multiple assignment (concatenation)

## Example: A comparator

```
module Compare1 (Equal, Alarger, Blarger, A, B);
  input  A, B;
  output Equal, Alarger, Blarger;
  assign Equal = (A & B) | (~A & ~B);
  assign Alarger = (A & ~B);
  assign Blarger = (~A & B);
endmodule
```

- Top-down design and bottom-up design are both okay
- Module ordering doesn't matter because modules execute in parallel

## Comparator example (con't)

```
// Make a 4-bit comparator from 4 1-bit comparators
module Compare4(Equal, Alarger, Blarger, A4, B4);
  input [3:0] A4, B4;
  output Equal, Alarger, Blarger;
  wire e0, e1, e2, e3, A10, A11, A12, A13, B10, B11, B12, B13;

  Compare1 cp0(e0, A10, B10, A4[0], B4[0]);
  Compare1 cp1(e1, A11, B11, A4[1], B4[1]);
  Compare1 cp2(e2, A12, B12, A4[2], B4[2]);
  Compare1 cp3(e3, A13, B13, A4[3], B4[3]);

  assign Equal = (e0 & e1 & e2 & e3);
  assign Alarger = (A13 | (A12 & e3) |
                  (A11 & e3 & e2) |
                  (A10 & e3 & e2 & e1));
  assign Blarger = (~Alarger & ~Equal);
endmodule
```

## Sequential assigns don't make any sense

```
assign A = X | (Y & ~Z);
assign B = W | A;
assign A = Y & Z;
```

"Reusing" a variable on the left side of several assignment statements is not allowed

```
assign A = X | (Y & ~Z);
assign B = W | A;
assign X = B & Z;
```

Cyclic dependencies also are bad

A depends on X  
 which depends on B  
 which depends on A

## Functions

- ◆ Use functions for complex combinational logic

```

module and_gate (out, in1, in2);
  input  in1, in2;
  output out;

  assign out = myfunction(in1, in2);

  function myfunction;
    input in1, in2;
    begin
      myfunction = in1 & in2;
    end
  endfunction
endmodule

```

**Benefit:**  
 Functions force a result  
 ⇒ Compiler will fail if function  
 does not generate a result

CSE370, Lecture 7

25

## Always Blocks

Don't forget variables in this list !!  
 always \*  
 can be used to represent every value change

reg A, B, C;

```

always @ (W or X or Y or Z)
begin
  A = X | (Y & ~Z);
  B = W | A;
  A = Y & Z;
  if (A & B) begin
    B = Z;
    C = W | Y;
  end
end

```

Variables that appear  
 on the left hand side in  
 an always block must  
 be declared as "reg's"

**Sensitivity list:**  
 block is executed  
 each time one of  
 them changes value

Statements in an always  
 block are executed in  
 sequence

All variables must be assigned on  
 every control path!!!  
 (otherwise you get the dreaded  
 "inferred latch")

CSE370, Lecture 7

26

## Sequential Verilog-- Blocking and non-blocking assignments

- ◆ Blocking assignments (Q = A)
  - Variable is assigned immediately
    - ↳ New value is used by subsequent statements
- ◆ Non-blocking assignments (Q <= A)
  - Variable is assigned after all scheduled statements are executed
    - ↳ Value to be assigned is computed but saved for later parallel assignment
  - Usual use: Register assignment
    - ↳ Registers simultaneously take new values after the clock edge
- ◆ Example: Swap

```

always @(posedge CLK)          always @(posedge CLK)
begin                          begin
  temp = B;                    A <= B;
  B = A;                       B <= A;
  A = temp;                    end
end

```

CSE370, Lecture 7

27

## Sequential Verilog-- Assignments- watch out!

- ◆ Blocking versus Non-blocking

```

reg B, C, D;
always @(posedge clk)
begin
  B = A;
  C = B;
  D = C;
end

reg B, C, D;
always @(posedge clk)
begin
  B <= A;
  C <= B;
  D <= C;
end

```



CSE370, Lecture 7

28

## Verilog tips

- ◆ **Do not** write C-code
  - Think hardware, not algorithms
    - ↳ Verilog is **inherently parallel**
    - ↳ Compilers don't map algorithms to circuits well
- ◆ **Do** describe hardware circuits
  - First draw a dataflow diagram
  - Then start coding
- ◆ References
  - Tutorial and reference manual are found in ActiveHDL help
    - ↳ [http://www.cs.washington.edu/education/courses/cse370/09wi/Tutorials/Tutorial\\_3.htm](http://www.cs.washington.edu/education/courses/cse370/09wi/Tutorials/Tutorial_3.htm)
  - "Starter's Guide to Verilog 2001" by Michael Ciletti
    - ↳ copies for borrowing in hardware lab

CSE370, Lecture 7

29