

Lecture 18

Logistics

- HW6 due today
- Midterm 2
 - ◊ Wednesday Feb 25
 - ◊ Review session Tuesday Feb 24, 4:30 in this room, EEB 037
 - ◊ Will cover materials up to today's lecture

Last Lecture

- Counter Finite State Machine
- Timing


Today

- General Finite State Machine (FSM) design

One more counter example: A 5-state counter with D flip flops

- ◆ Counter repeats 5 states in sequence
 - Sequence is 000, 010, 011, 101, 110, 000

Step 1: State diagram

 

Step 2: State transition table Assume D flip-flops

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	X	X	X
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	X	X	X
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	X	X	X

5-state counter (con't)

Step 3: Encode the next state functions

		C		
A	B	0	1	X
0	0	0	0	X
X	1	X	X	1

$C+ = A$

		C			
A	B	1	1	0	X
X	0	X	X	1	


$B+ = B' + A'C'$

		C			
A	B	0	1	0	X
X	1	X	0		

$A+ = BC'$

5-state counter (con't)

Step 4: Implement the design

 


Recall that a D flip flop also produces Q' so A', B', and C' would all be available without any extra inverters

5-state counter (con't)

◆ Is our design robust?

- What if the counter starts in a 111 state?

 Does our counter get stuck in invalid states???



5-state counter (con't)


◆ Back-annotate our design to check it

Fill in state transition table

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

$A+ = BC'$
 $B+ = B' + A'C'$
 $C+ = A$

Draw state diagram

 

The proper methodology is to **design** your counter to be self-starting

Self-starting counters

- ◆ Invalid states should **always** transition to valid states
 - Assures startup
 - Assures bit-error tolerance
- ◆ Design your counters to be self-starting
 - Draw **all** states in the state diagram
 - Fill in the **entire** state-transition table
 - May limit your ability to exploit don't cares
 - ↳ Choose startup transitions that minimize the logic

Finite state machines: more than counters


- ◆ FSM: A system that visits a **finite** number of logically distinct states
- ◆ Counters are simple FSMs
 - Outputs and states are identical
 - Visit states in a fixed sequence without inputs
- ◆ FSMs are typically more complex than counters
 - Outputs can depend on current state and on inputs
 - State sequencing depends on current state and on inputs

FSM design

- Counter design procedure
 1. State diagram
 2. State-transition table
 3. Next-state logic minimization
 4. Implement the design
- FSM design procedure
 1. State diagram
 2. State-transition table
 3. State minimization
 4. State encoding
 5. Next-state logic minimization
 6. Implement the design

 
Example: A vending machine

- ◆ 15 cents for a cup of coffee (yeah, it's subsidized)
- ◆ Doesn't take pennies or quarters
- ◆ Doesn't provide any change



- FSM-design procedure
 1. State diagram
 2. State-transition table
 3. State minimization
 4. State encoding
 5. Next-state logic minimization
 6. Implement the design

 
A vending machine: (conceptual) state diagram



A vending machine: State transition table

present state	inputs		next state	output open
	D	N		
S0	0	0	S0	0
	0	1	S1	0
	1	0	S2	0
S1	1	1	X	X
	0	0	S1	0
	0	1	S3	0
S2	1	0	S4	0
	1	1	X	X
	0	0	S2	0
S3	0	1	S5	0
	1	0	S6	0
	1	1	X	X
S4	0	0	S2	0
	0	1	S5	0
	1	0	S6	0
S5	1	1	X	X
	0	0	S2	0
	0	1	S3	0
S6	1	0	S4	0
	1	1	X	X
	0	0	S2	0
S7	0	0	S7	0
	0	1	S3	0
	1	0	S6	0
S8	1	1	X	X
	0	0	S2	0
	0	1	S3	0

A vending machine: State minimization

 

present state	inputs		next state	output	
	D	N		D1	D0
0¢	0	0	0¢	0	0
	0	1	5¢	0	0
	1	0	10¢	0	0
	1	1	-	-	-
5¢	0	0	5¢	0	0
	0	1	10¢	0	0
	1	0	15¢	0	0
	1	1	-	-	-
10¢	0	0	10¢	0	0
	0	1	15¢	0	0
	1	0	15¢	0	0
	1	1	-	-	-
15¢	0	0	15¢	0	1
	1	1	-	-	-

symbolic state table

CSE370, Lecture 18

13


A vending machine: State encoding

present state		inputs		next state		output	
Q1	Q0	D	N	D1	D0	open	
0	0	0	0	0	0	0	
0	0	0	1	0	1	0	
0	0	1	0	1	0	0	
0	0	1	1	-	-	-	
0	1	0	0	0	1	0	
0	1	0	1	1	0	0	
0	1	1	0	1	1	0	
0	1	1	1	-	-	-	
1	0	0	0	1	0	0	
1	0	0	1	1	1	0	
1	0	1	0	1	1	0	
1	0	1	1	-	-	-	
1	1	-	-	1	1	1	

CSE370, Lecture 18

14

A vending machine: Logic minimization

 

$$D1 = Q1 + D + Q0 N$$


$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$

$$OPEN = Q1 Q0$$

CSE370, Lecture 18

15

A vending machine: Implementation

 

CSE370, Lecture 18

16