

Lecture 27

◆ Logistics

- HW8 due Friday
- Ants problem due Friday
- Lab kit must be returned to Tony by Friday
- Review Sunday 12/7 3pm, Location TBD

◆ Last lecture

- State encoding
 - ▣ One-hot encoding
 - ▣ Output encoding


◆ Today:

- Optimizing FSMs
 - ▣ Pipelining
 - ▣ Retiming
 - ▣ Partitioning

 
Example: Digital combination lock

◆ An output-encoded FSM

- Punch in 3 values in sequence and the door opens
- If there is an error the lock must be reset
- After the door opens the lock must be reset
- Inputs: sequence of number values, reset
- Outputs: door open/close



Design the datapath

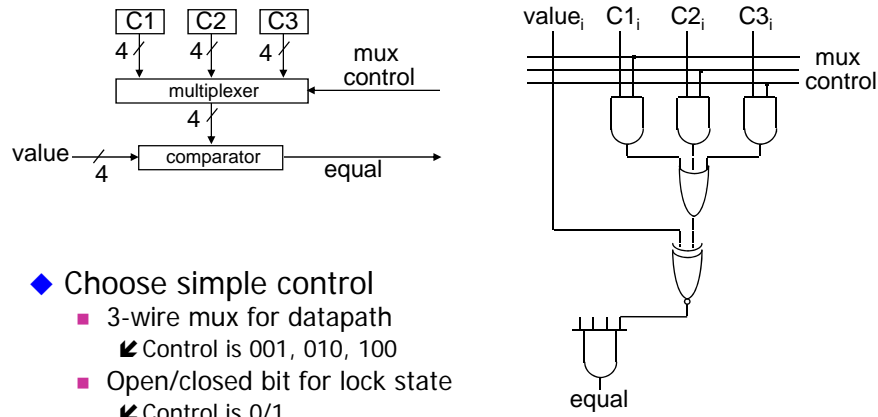


- ◆ Choose simple control
 - 3-wire mux for datapath
 - ☛ Control is 001, 010, 100
 - Open/closed bit for lock state
 - ☛ Control is 0/1

Output encode the FSM

- ◆ FSM outputs
 - Mux control is 100, 010, 001
 - Lock control is 0/1
 - ◆ State are: S0, S1, S2, S3, or ERR
 - Can use 3, 4, or 5 bits to encode
 - Have 4 outputs, so choose 4 bits
 - ☛ Encode mux control and lock control in state bits
 - ☛ Lock control is first bit, mux control is last 3 bits
- S0 = 0001 (lock closed, mux first code)
- S1 = 0010 (lock closed, mux second code)
- S2 = 0100 (lock closed, mux third code)
- S3 = 1000 (lock open)
- ERR = 0000 (error, lock closed)

Encode 4 state bits

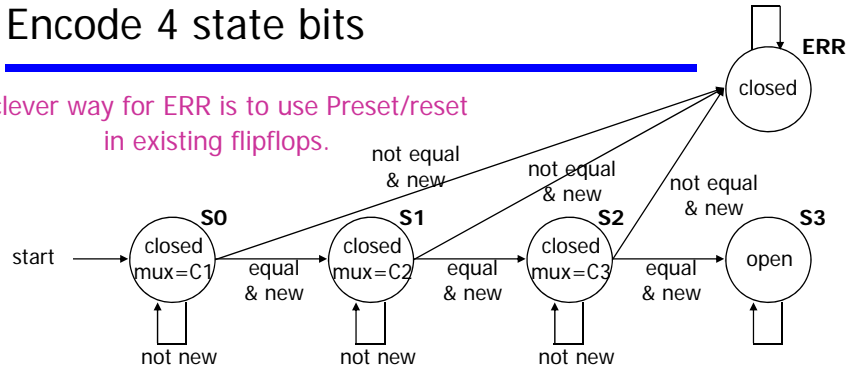A clever way for ERR is to use Preset/reset in existing flipflops.




$$\begin{aligned}
 S_0+ &= S_0N' \\
 S_1+ &= S_0EN + S_1N' \\
 S_2+ &= S_1EN + S_2N' \\
 S_3+ &= S_2EN + S_3
 \end{aligned}$$

$$\begin{aligned}
 \text{Preset}_0 &= \text{start} \\
 \text{Preset}_{1,2,3} &= 0 \\
 \text{Reset}_0 &= \text{start}'(E'N + (Q_0+Q_1+Q_2+Q_3)') \\
 \text{Reset}_{1,2,3} &= \text{start} + (E'N + (Q_0+Q_1+Q_2+Q_3)')
 \end{aligned}$$

$$\begin{aligned}
 D_0 &= Q_0N' \\
 D_1 &= Q_0EN + Q_1N' \\
 D_2 &= Q_1EN + Q_2N' \\
 D_3 &= Q_2EN + Q_3
 \end{aligned}$$
 
$$\begin{aligned}
 \text{Preset}_0 &= \text{start} \\
 \text{Preset}_{1,2,3} &= 0 \\
 \text{Reset}_0 &= \text{start}'(E'N + (Q_0+Q_1+Q_2+Q_3)') \\
 \text{Reset}_{1,2,3} &= \text{start} + (E'N + (Q_0+Q_1+Q_2+Q_3)')
 \end{aligned}$$



FSM design

- FSM-design procedure
 1. State diagram
 2. state-transition table
 3. State minimization
 4. State encoding
 5. Next-state logic minimization
 6. Implement the design

Last topic: more FSM optimization techniques

- ◆ Want to optimize FSM for many reasons beyond state minimization and efficient encoding


- ◆ Additional techniques
 - Pipelining --- allows faster clock speed
 - Retiming --- can reduce registers or change delays
 - Partitioning --- can divide to multiple devices, simpler logic

Pipelining related definitions

- ◆ Latency: Time to perform a computation
 - Data input to data output
- ◆ Throughput: Input or output data rate
 - Typically the clock rate
- ◆ Combinational delays drive performance
 - Define $d \equiv$ delay through slowest combinational stage
 - $n \equiv$ number of stages from input to output
 - Latency $\propto n * d$ (in sec)
 - Throughput $\propto 1/d$ (in Hz)


Pipelining

 - ◆ What?
 - Subdivide combinational logic
 - Add registers between logic
- ◆ Why?
 - Trade latency for throughput
 - **Increased throughput**
 - ↳ Reduce logic delays
 - ↳ Increase clock speed
 - **May increased latency**
 - **Increase circuit utilization**
 - ↳ Simultaneous computations



Pipelining

 - ◆ When?
 - Need throughput more than latency
 - ↳ Signal processing
 - Logic delays > setup/hold times
 - Acyclic logic
- ◆ Where?
 - At natural breaks in the combinational logic
 - Adding registers makes sense




Retiming


- ◆ Pipelining adds registers
 - To increase the clock speed
- ◆ Retiming moves registers around
 - Reschedules computations to optimize performance
 - ↳ Change delay patterns
 - ↳ Reduce register count
 - Without altering functionality

Retiming examples

◆ Reduce register count

 

◆ Change output delays

 

FSM partitioning

◆ Break a large FSM into two or more smaller FSMs

◆ Rationale


- Less states in each partition
 - ✦ Simpler minimization and state assignment
 - ✦ Smaller combinational logic
 - ✦ Shorter critical path
- But more logic overall

◆ Partitions are synchronous

- Same clock!!!


Example: Partition the machine

- ◆ Partition into two halves

 


Introduce idle states

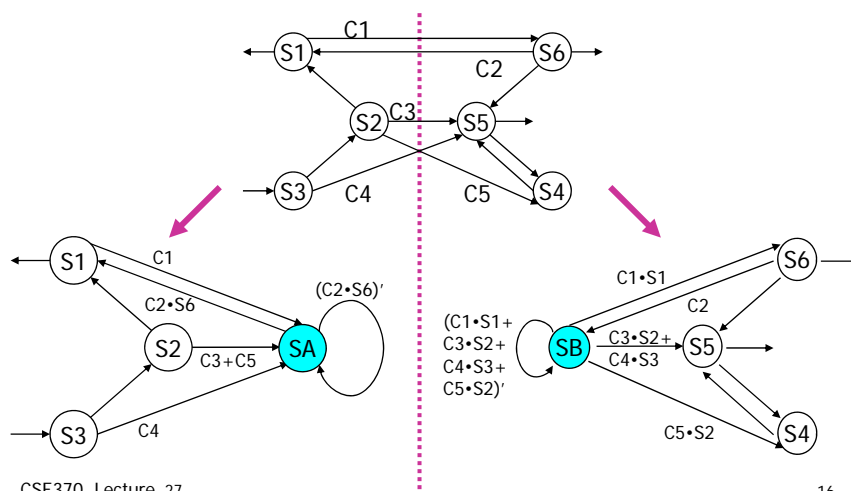- ◆ SA and SB handoff control between machines




Partitioning rules

 Rule #1: Source-state transformation
 Replace by transition to idle state (SA)




 Rule #2: Destination state transformation
 Replace with exit transition from idle state




Partitioning rules (con't)

 Rule #3: Multiple transitions with same source or destination
 Source \Rightarrow Replace by transitions to idle state (SA)
 Destination \Rightarrow Replace with exit transitions from idle state



 Rule #4: Hold condition for idle state
 OR exit conditions and invert




Mealy versus Moore partitions

- ◆ Mealy machines **undesirable**
 - Inputs can affect outputs immediately
 - ✦ "output" can be a handoff to another machine!!!
- ◆ Moore machines **desirable**
 - Input-to-output path always broken by a flip-flop
 - But...may take several clocks for input to propagate to output


Example: Six-state up/down counter

- ◆ Break into 2 parts

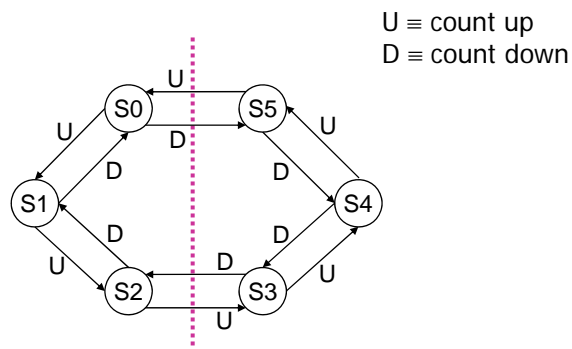

 Example: 6 state up/down counter (con't)

- ◆ Count sequence $S_0, S_1, S_2, S_3, S_4, S_5$
 - S_2 goes to S_A and holds, leaves after S_5
 - S_5 goes to S_B and holds, leaves after S_2
 - Down sequence is similar



Minimize communication between partitions

- ◆ Ideal world: Two machines handoff control
 - Separate I/O, states, etc.
- ◆ Real world: Minimize handoffs and common I/O
 - Minimize number of state bits that cross boundary
 - Merge common outputs



Done!