

Processor Datapath

CSE378

WINTER, 2001

124

Levels in Processor Design

- We can talk about design at a variety of levels (from low to high):
 - Circuit design: transistors, resistors, capacitors, etc. Building gates, flip-flops, etc.
 - Logic design: putting gates (AND, OR, XOR, etc) and flip-flops together to build blocks such as registers, adders, memory. See CSE370.
 - Register transfer level: describes the execution of instructions by showing how information is transferred and manipulated between adders, registers, memory, etc.
 - Processor description: the ISA.
 - System description: includes memory hierarchy, IO, number of processors, etc.

CSE378

WINTER, 2001

125

Register Transfer Perspective


- We'll use either block diagrams or pseudocode to describe the operation/design of a simple processor which implements a subset of the MIPS ISA.
- We'll implement just a subset of the ISA:
 - Memory reference: lw and sw
 - Arithmetic: add, sub, and, or, stli
 - Control: beq, jump
- Key components:
 - Combinational: the output is a function of the inputs (e.g. an adder)
 - Sequential: state is remembered (e.g. a register)

CSE378

WINTER, 2001

126

Data Path and Control Unit

 

- Data path:
 - *Combinational* (ALU) + *Sequential* (Registers, PC, Status)
 - How data moves between components, what operations are performed on data.
- Control unit:
 - Sends signals to data path elements
 - Tells what data to move, where to move it, what ops to perform


CSE378

WINTER, 2001

127

Combinational Elements: ALU

- ALU computes (combinational) output from its two inputs.
- Performs functions needed to execute arithmetic and logical instructions.
- Combinational logic has a "critical path" which determines the length of time needed for the output to stabilize given stable inputs. (These days: ~1ns).

 

CSE378


WINTER, 2001

128


Synchronous Design

- Use a periodic clock, which controls when signals can be read and when they can be written. Values in storage elements can only be updated on clock edges.
- The clock determines when events occur, ie, when signals sent by control unit are obeyed in the datapath.

Changes occur on every clock edge:

 

Changes occur on clock edges when a write signal is asserted (this allows combinational logic to take several cycles):

 


CSE378

WINTER, 2001

129

Building Blocks: Storage elements

- The basic building block is the register.
- Our registers store 32 bits.
- A register will only be written on the clock edge AND when the write control line is asserted.
- It can be read and written on the same clock, but the value read will be the OLD value.

 


CSE378

WINTER, 2001

130

Building Blocks: Register File

 - Register file is an array of registers (32 in MIPS)
- ISA tells us that we should be able to read 2 registers and write 1 register in a given instruction.
- We need to know which registers to read/write, and what data to write.



- Typical access time is around 1ns.


CSE378

WINTER, 2001

131

Memory

 - Memory is like a register file, but much larger and slower.
- Can only read or write one location per cycle.




- Typical access time (for primary memory) is around 50ns. For cache memory it is closer to 5ns.

CSE378

WINTER, 2001

132

Instruction Fetch Datapath

 


- Our implementation will fully execute one instruction per clock cycle: single cycle implementation.
- The PC tells us the read address.
- On each clock edge, a new value for PC will be latched into the PC register.

CSE378

WINTER, 2001

133

Datapath for R-type Instruction

 


- The instruction bits name the read and write regs (rs, rt, rd).
- On the clock edge, the data is read, which moves through the ALU, hopefully in time to be latched into the write port at the next clock edge.

CSE378

WINTER, 2001

134

Datapath for Load/Store

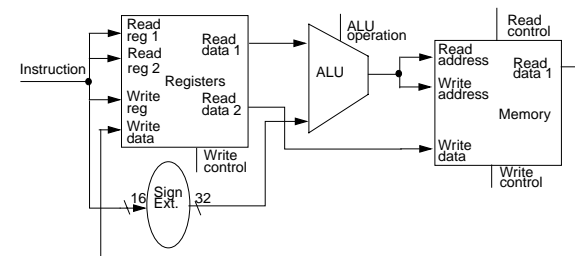


- The instruction bits tell us the registers to use (src/dest and base register) and the 16 bit signed offset.
- We use the ALU to compute the effective address, which is passed along to the data memory.

CSE378

WINTER, 2001

135

Datapath For Branch

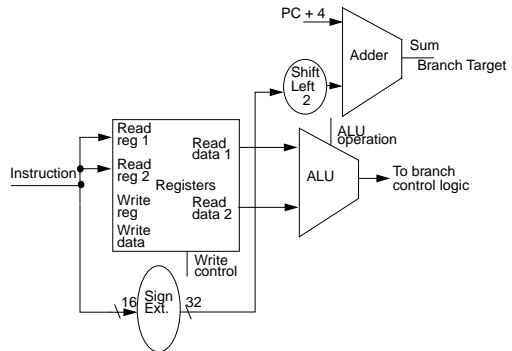


- Question: Why can't we just use the ALU to compute the branch target address?

CSE378


WINTER, 2001

Combinational Elements: (De)Multiplexor

 - Multiplexor (mux) selects the value of one of its inputs to be routed to the output:



- Demultiplexor routes its input to one of its outputs:

 


CSE378

WINTER, 2001

136

137

Combining Memory and R-type

 


- Note that we add 2 muxes:
 - One to select the second ALU input
 - One to select the source for the register writeback (memory or ALU result)

CSE378

WINTER, 2001

Adding Instruction Fetch

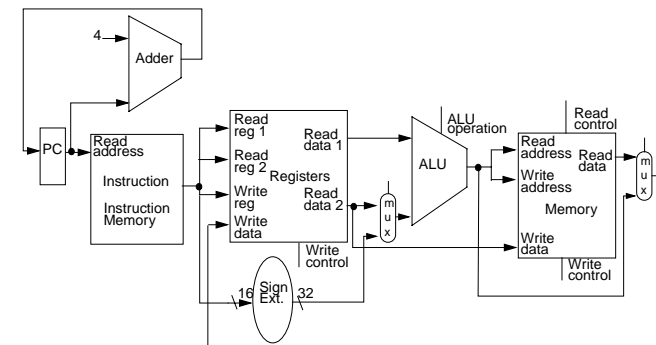


CSE378

WINTER, 2001

138

139

Full Datapath: Adding Branches

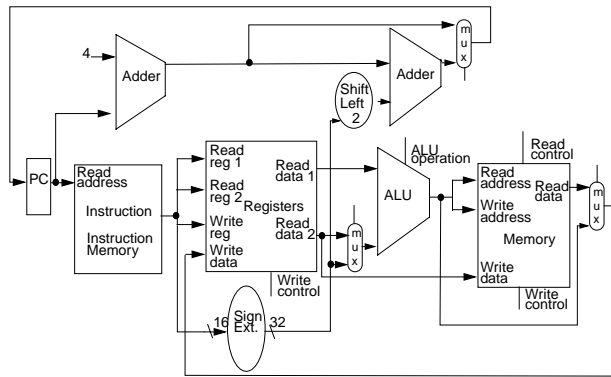

CSE378

WINTER, 2001

140

Processor Control

CSE378

WINTER, 2001

141

Adding Control

- Control Unit:
 - Decodes instruction opcode/function field
 - Sends signals to the data path (muxes, reg file, memories)
- Some controls come directly from the instruction:
 - Register fields indicate which register to read/write
 - Immediate field
- Building the control unit is not that complicated:
 - Input signals (opcode/function) are specified by the ISA
 - Output signals can be identified easily from the opcode
 - We can use PLAs (see CSE370) to build hardwired control units

CSE378

WINTER, 2001

142

Review of Instruction Format

- The opcode lives in bits 31-26
- The two registers to read are always the rs (25-21) and rt (20-16) registers
- For a load/store, we find the base register in the rs field (25-21)
- The 16 bit offset (for branch or load/store) is in 15-0
- The destination register can be in one of two places:
 - Loads: rt field (20-16)
 - R-type: rd field (15-11)
 - This implies we'll need a mux to select between these two fields.

CSE378

WINTER, 2001

143

Where are control signals needed?

- Register File:
 - *RegDst* - selects between *rt* and *rd* field as destination register (different for Load-store than R-type)
 - *RegWrite* - do we want to write a register? (R-type, Load-store)
- ALU:
 - *ALUSrc* - selects between immediate or register value as source for ALU (different for R-type and I-type)
 - Also need to select kind of ALU operation (bits 0-5 is function)
- Memory:
 - *MemWrite* - are we writing memory? (store instructions)
 - *MemRead* - are we reading memory? (load instructions)
 - *MemToReg* - selects between memory value or ALU output as writeback to the register file
- *Branch* - are we branching?

CSE378

WINTER, 2001

144

How are signals asserted?

- Control unit gets the opcode. Decoding yields:
 - Control for the 3 muxes (*RegDst*, *ALUSrc*, *MemToReg*)
 - Signals for read/write memory
 - Signal for register write
 - Signal for branch (ANDed with output of ALU)
 - Signal to ALU Control unit
- We also have a small control unit for the ALU, which takes the signal from the main control unit, together with the *funct* field (5-0) from the instruction.
- We'll focus on the main control unit. The ALU control is similar.

CSE378

WINTER, 2001

145

Examples

- Using the provided figure (5.22), fill in this table which specifies the control signals for the various instructions:

Instr.	opcode bits: 543210	Reg Dst	ALU Src	Mem to Reg	Reg Write	Mem Read	Mem Write	Br
R-format	000000							
lw	100011							
sw	101011							
beq	000100							

CSE378

WINTER, 2001

146

Control Functions

- We can express the functions for the control lines logically:
 - $\text{RegDst} = \text{!op5 AND !op2}$
 - $\text{ALUSrc} = \text{op5}$
 - $\text{MemtoReg} = \text{op5}$
 - $\text{RegWrite} = \text{!op2 AND !op3}$
 - $\text{MemRead} = \text{op5 AND !op3}$
 - $\text{MemWrite} = \text{op5 AND op3}$
 - $\text{Branch} = \text{op2}$
- For our subset instruction set, this minimized logic is fine, but for the full instruction set (64 opcodes), we'd want something more general: We would specify the truth table, and implement it using a PLA.

CSE378

WINTER, 2001

147