

Ways of specifying circuits

◆ Schematic

- ⇒ Structural description
- ⇒ Describe circuit as interconnected elements
 - ◆ Build complex circuits using hierarchy
 - ◆ Large circuits are unreadable

◆ HDLs

- ⇒ Hardware description languages
 - ◆ **Not** programming languages
 - ◆ Parallel languages tailored to digital design
- ⇒ Synthesize code to produce a circuit

Hardware description languages (HDLs)


- ◆ Abel (~1983)
 - ⇒ Developed by Data-I/O
 - ⇒ Targeted to PLDs
 - ⇒ Limited capabilities (can do state machines)
- ◆ Verilog (~1985)
 - ⇒ Developed by Gateway (now part of Cadence)
 - ⇒ Similar to C
- ◆ VHDL (~1987)
 - ⇒ DoD sponsored
 - ⇒ Similar to Ada

Verilog versus VHDL

- ◆ Both “IEEE standard” languages
- ◆ Most tools support both
- ◆ Verilog is “simpler”
 - ⇒ Less syntax, fewer constructs
- ◆ VHDL is structured for large, complex systems
 - ⇒ Better modularization

Simulation versus synthesis

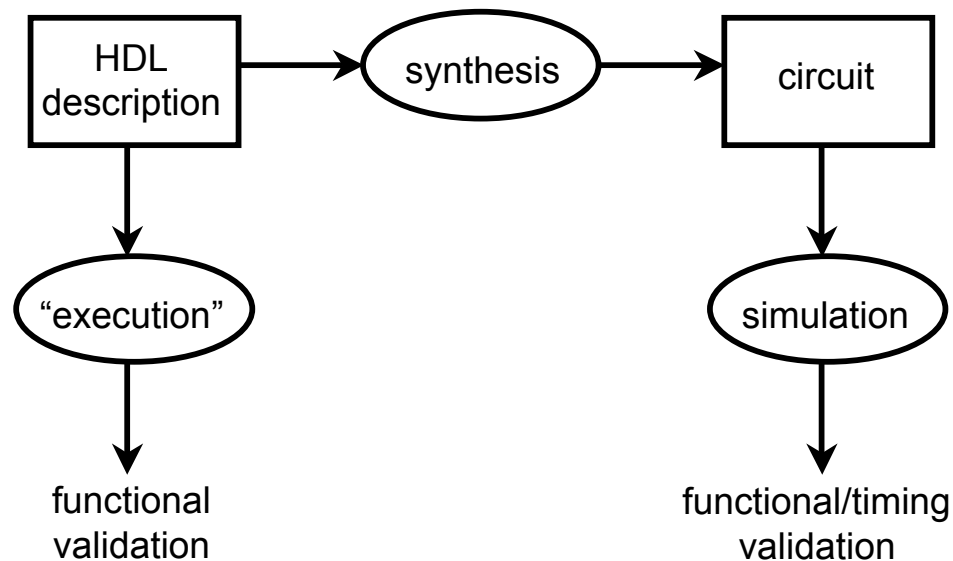- ◆ Early HDLs supported execution/simulation only
 - ⇒ Hand transform code to a schematic
- ◆ Current HDLs support direct synthesis to hardware
 - ⇒ A “synthesizable subset” of the language



Simulation versus synthesis (con't)

◆ Simulation

- ⇒ Models what a circuit does, not how it does it
 - ◆ e.g. multiply
 - Just say “*”, ignoring the implementation possibilities
- ⇒ Includes functions and timing
- ⇒ Allows you to quickly test design options


◆ Synthesis

- ⇒ Converts your code to a netlist
 - ◆ Description of interconnected circuit elements
 - ◆ No timing
- ⇒ Tools map your netlist to hardware

◆ Verilog and VHDL both simulate and synthesize

Simulation

 - ◆ You provide a circuit environment
 - ⇒ Using misc non-circuit constructs
 - ◆ Read files, print, control simulation
 - ⇒ Using Verilog simulation code
 - ◆ A “test fixture”
 - A specification
 - Tests if circuit behavior (I/O) is correct



Structural versus behavioral Verilog

◆ Structural

- ⇒ Describe explicit circuit elements
- ⇒ Describe explicit connections between elements
 - ◆ e.g., logic gates are instantiated and connected to others
- ⇒ Just like schematics, but using text

◆ Behavioral

- ⇒ Describes circuit as algorithms/programs
 - ◆ What a component does
 - ◆ Input/output behavior
- ⇒ Many possible circuits could have same behavior
 - ◆ e.g., different implementation of a Boolean function

Levels of abstraction

- ◆ Verilog supports 4 description levels:

- ⇒ Switch
 - ⇒ Gate
 - ⇒ Dataflow
 - ⇒ Algorithmic
- structural*
- behavioral*

- ◆ Can mix & match levels in a design

- ◆ Designs that combine dataflow and algorithmic constructs and synthesize are called RTL

- ⇒ *Register Transfer Level*

What you will do...

- ◆ Use a synthesizable subset of Verilog
 - ⇒ e.g. no “initial” blocks
 - ⇒ Using structural and “synthesizable” behavioral Verilog
- ◆ **Will** simulate your Verilog code
 - ⇒ Use ActiveHDL
- ◆ **Will** synthesize your code
 - ⇒ Use SimplifyPro
- ◆ **Will** map your netlist
 - ⇒ ISE
- ◆ **Will** simulate your netlist
 - ⇒ After synthesis
 - ⇒ All your code will synthesize (by necessity)

Verilog tips

- ◆ **Do not** write C-code

- ⇒ Don't write algorithms

- ◆ You will not get efficient circuits

- ◆ Compilers don't map algorithms to circuits well

- ◆ **Do** describe hardware circuits

- ⇒ Don't start coding until you have a complete dataflow diagram

- ◆ **References**


- ⇒ <http://www.cs.washington.edu/education/courses/467/99au/admin/HardwareLab.html>

- ⇒ http://www.europa.com/~celiac/ver_edu.html

Modules

- ◆ The basic building block
 - ⇒ Instance into a design
 - ⇒ Illegal to nest module defs
 - ⇒ Example: 4-bit adder
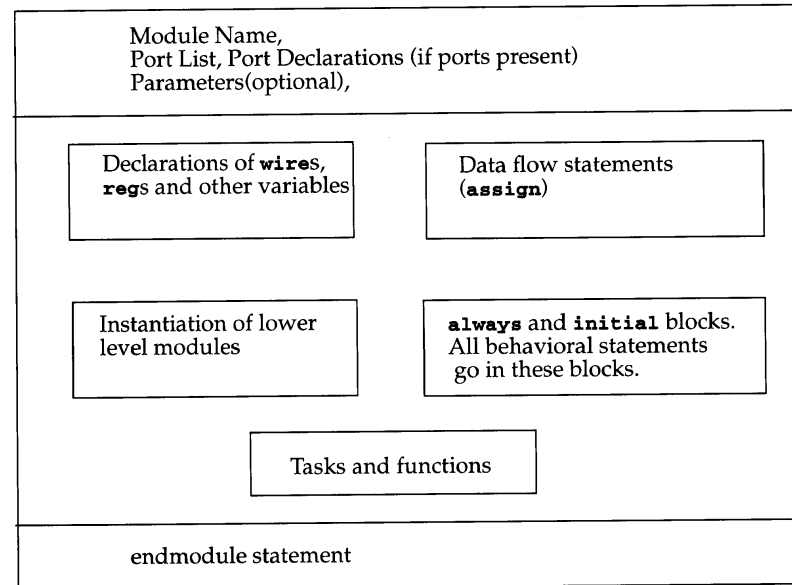
```
module add4 (A, B, SUM, OVER) ;  
  
    input [3:0] A ;  
    input [3:0] B ;  
    output [3:0] SUM ;  
    output OVER ;  
  
    assign {OVER, SUM[3:0]} = A[3:0] + B[3:0] ;  
  
endmodule
```



Modules

- ◆ Modules are circuit components
 - ⇒ “parameter list” is a list of external connections
 - ◆ A list of ports
 - ⇒ Port types: “input”, “output” or “inout”
 - ◆ inout are used on tri-state buses


```
module full_addr (A, B, Cin, S, Cout);  
  input  A, B, Cin;  
  output S, Cout;  
  
  assign {Cout, S} = A + B + Cin;  
endmodule
```

Annotations in the diagram:

- module name** points to `full_addr`
- ports** points to `(A, B, Cin, S, Cout)`
- inputs/outputs** points to `input A, B, Cin;` and `output S, Cout;`

Structural Verilog
 
```
module xor_gate (out, a, b);  
  input      a, b;  
  output     out;  
  wire      abar, bbar, t1, t2;  
  
  inverter  invA (abar, a);  
  inverter  invB (bbar, b);  
  and_gate  and1 (t1, a, bbar);  
  and_gate  and2 (t2, b, abar);  
  or_gate   or1 (out, t1, t2);  
  
endmodule
```



Note: Verilog is case sensitive
□ All keywords are lowercase

Structural full adder

```
module full_addr (A, B, Cin, S, Cout);
    input      A, B, Cin;
    output     S, Cout;

    assign {Cout, S} = A + B + Cin;
endmodule

module adder4 (A, B, Cin, S, Cout);
    input  [3:0] A, B;
    input      Cin;
    output [3:0] S;
    output     Cout;
    wire      C1, C2, C3;

    full_addr fa0 (A[0], B[0], Cin, S[0], C1);
    full_addr fa1 (A[1], B[1], C1, S[1], C2);
    full_addr fa2 (A[2], B[2], C2, S[2], C3);
    full_addr fa3 (A[3], B[3], C3, S[3], Cout);
endmodule
```

Behavioral Verilog

```
module and_gate (out, in1, in2);  
    input        in1, in2;  
    output       out;  
  
    assign out = in1 & in2;  
endmodule
```

Note: AND is a Verilog primitive, so you can also write

```
and and_gate(out, in1, in2);
```

Data types

- ◆ Values on a wire

- ⇒ 0, 1, *x* (don't care), *z* (tristate)

- ◆ Vectors

- ⇒ A[3:0] vector of 4 bits: A[3], A[2], A[1], A[0]

- ◆ An unsigned integer value

- ⇒ Concatenating bits/vectors

- ◆ e.g. sign extend

- B[7:0] = {A[3], A[3], A[3], A[3], A[3:0]};

- B[7:0] = {4{A[3]}, A[3:0]};

- ⇒ Style: Use $a[7:0] = b[7:0] + c$;

- Not* $a = b + c$;

Numbers

- ◆ 14
 - ⇒ Decimal number
- ◆ -14
 - ⇒ 2's complement binary of the decimal number
- ◆ 12'b0000_0100_0110
 - ⇒ 12 bit binary number (_ is ignored)
- ◆ 3'h046
 - ⇒ 12 bit hexadecimal number
- ◆ Verilog values are unsigned
 - ⇒ $C[4:0] = A[3:0] + B[3:0]$;
 - ◆ if $A = 0110$ (6) and $B = 1010$ (-6), then $C = 10000$ (*not* 00000)
 - ◆ B is zero-padded, *not* sign-extended

Operators

Verilog Operator	Name	Functional Group
()	bit-select or part-select	
()	parenthesis	
! ~ & ~& ~ ^ ~^ or ^~	logical negation negation reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{}	concatenation	Concatenation
{{}}	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

> >= < <=	greater than greater than or equal to less than less than or equal to	Relational Relational Relational Relational
== !=	logical equality logical inequality	Equality Equality
=== !==	case equality case inequality	Equality Equality
&	bit-wise AND	Bit-wise
^ ^~ or ~^	bit-wise XOR bit-wise XNOR	Bit-wise Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional

Variables

- ◆ wire
 - ⇒ Connects components together
- ◆ reg
 - ⇒ Saves a value
 - ◆ Part of a behavioral description
 - ◆ Usually corresponds to a wire
 - ⇒ Does *NOT* necessarily become a register when you synthesize
- ◆ The rule
 - ⇒ Declare a variable as reg if it is a target of an assignment statement
 - ◆ Continuous assign doesn't count