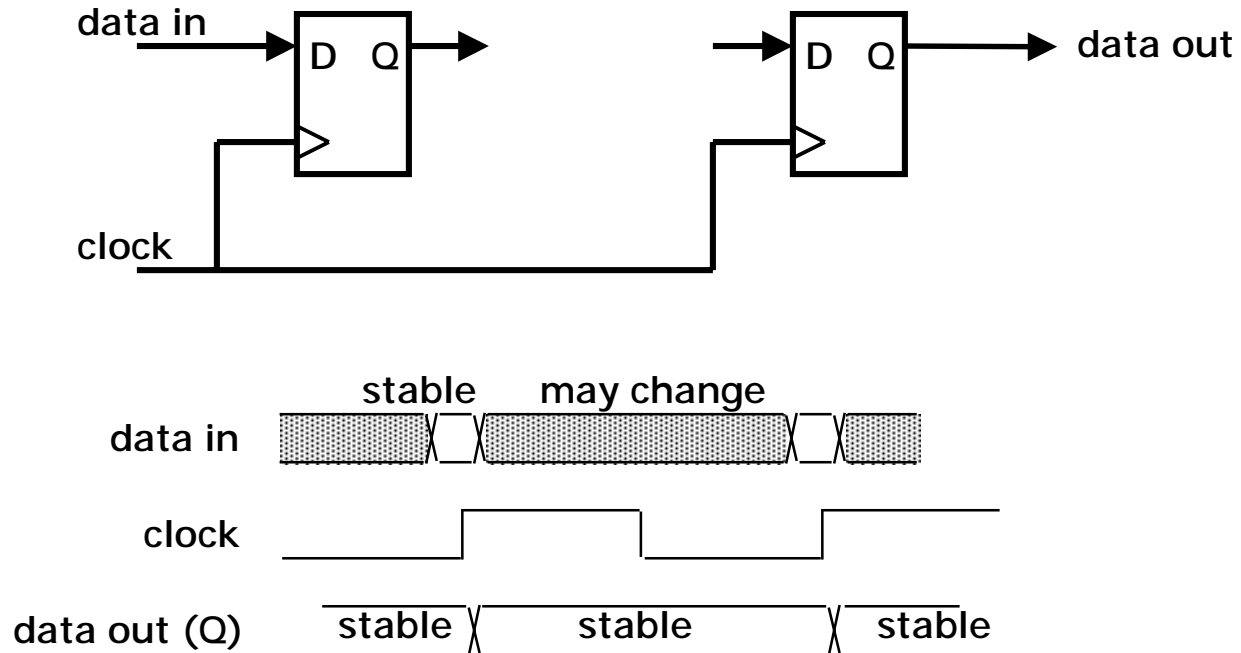



# Registers

- Sample data using clock
- Hold data between clock cycles
- Computation (and delay) occurs between registers



 
# Timing Methodologies (cont'd)

- Definition of terms
  - setup time: minimum time before the clocking event by which the input must be stable ( $T_{su}$ )
  - hold time: minimum time after the clocking event until which the input must remain stable ( $T_h$ )




 there is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized


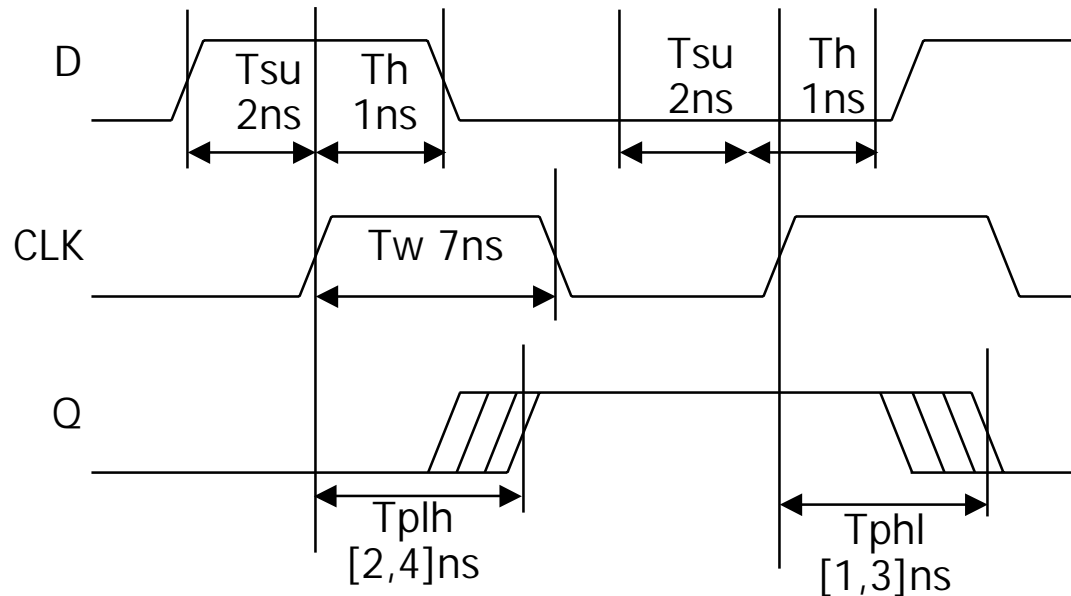
# Typical timing specifications


- Positive edge-triggered D flip-flop
  - setup and hold times
  - minimum clock width
  - propagation delays (low to high, high to low, max and typical)



all measurements are made from the clocking event that is,  
the rising edge of the clock

 
# Synchronous System Model

- Register-to-register operation
- Perform operations during transfer
- Many transfers/operations occur simultaneously



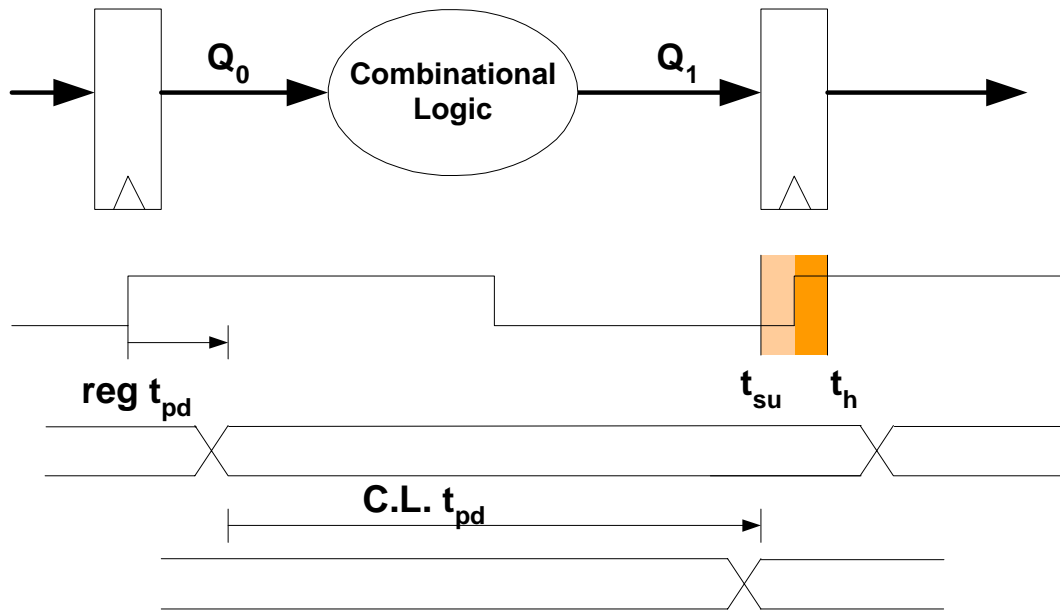
# System Clock Frequency

- Register transfer must fit into one clock cycle
  - $\text{reg } t_{pd} + \text{C.L. } t_{pd} + \text{reg } t_{su} < T_{\text{clk}}$
  - Use maximum delays
  - Find the "critical path"
    - Longest register-register delay



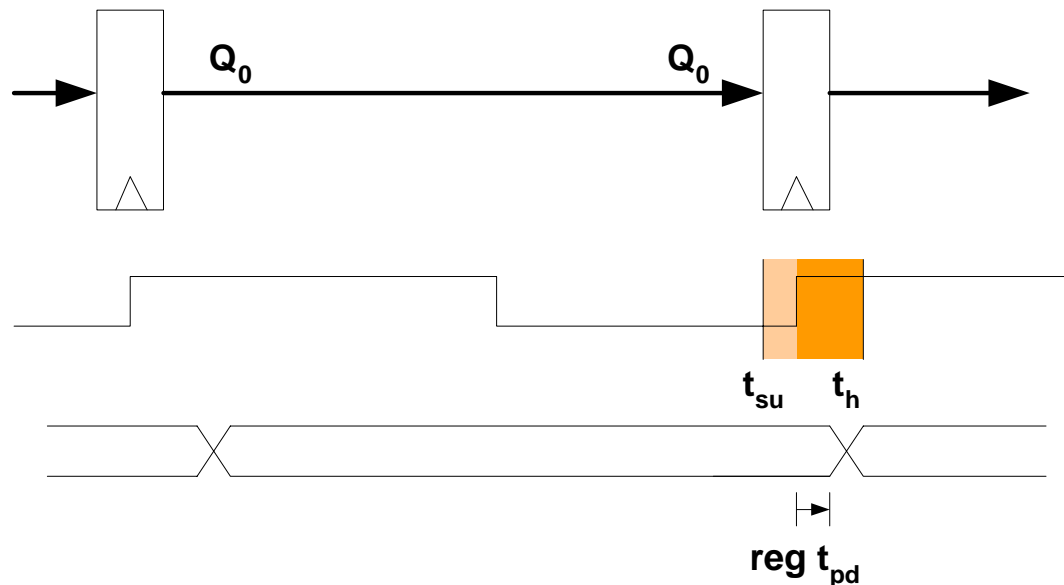
# Short Paths

- Can a path have too little delay?
  - Yes: Hold time can be violated
  - $t_{pd} > t_h$
  - Use min delay (contamination delay)
- Fortunately, most registers have hold time = 0
  - But there can still be a problem! Clock skew...



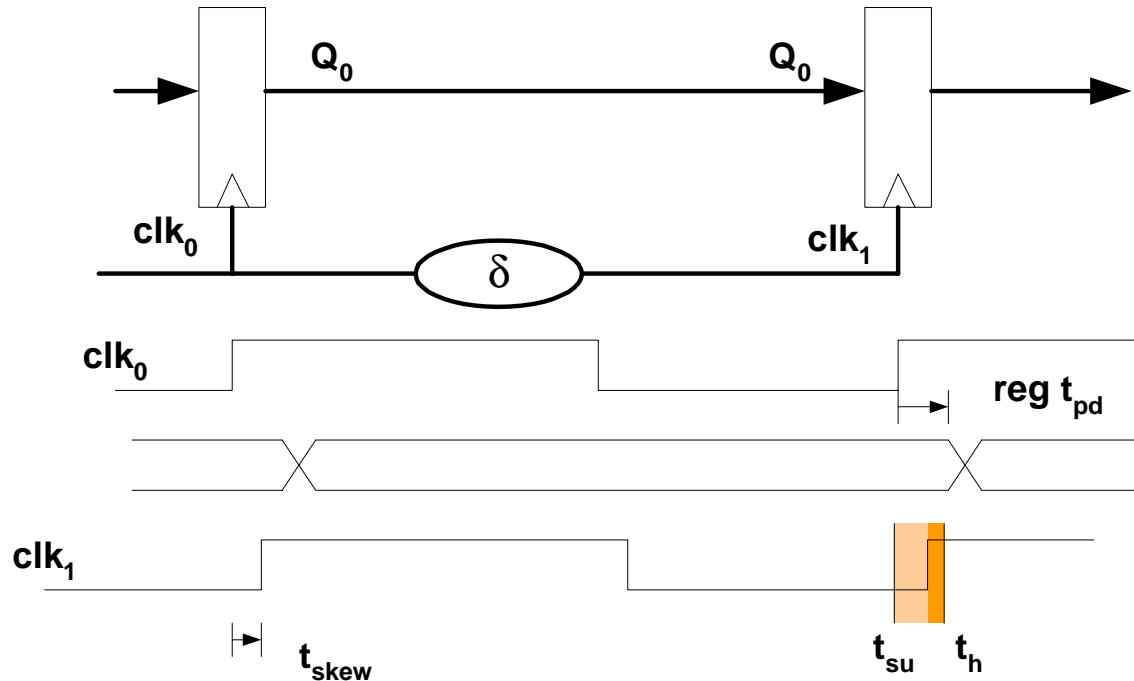
# Clock Skew

- Cannot make clock arrive at registers at the same time
- If skew  $> 0$ :
  - $t_{pd} > t_h + t_{skew}$
  - Clock skew can cause system failure
    - Can you fix this after you've fabbed the chip?


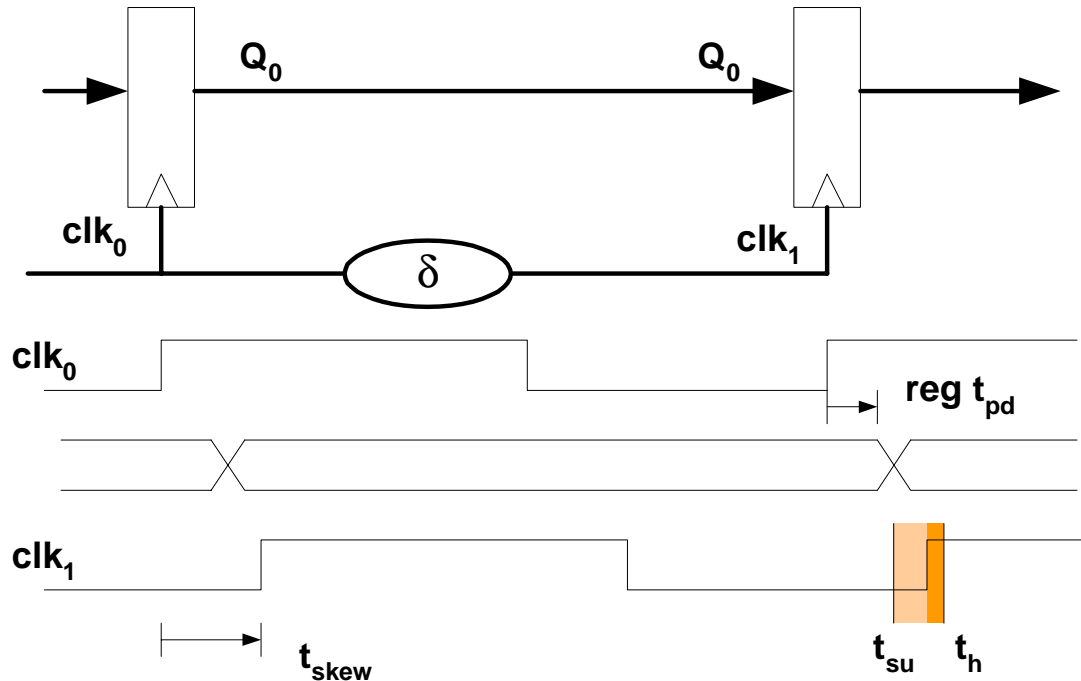
# Clock Skew


- Cannot make clock arrive at registers at the same time
- If skew  $> 0$ :
  - $t_{pd} > t_h + t_{skew}$
  - Clock skew can cause system failure
    - Can you fix this after you've fabbed the chip?






# Clock Skew

- If skew < 0:
  - $t_{clk} > \text{reg } t_{pd} + \text{C.L. } t_{pd} + \text{reg } t_{su} + |t_{skew}|$
  - Can you fix this after fab?

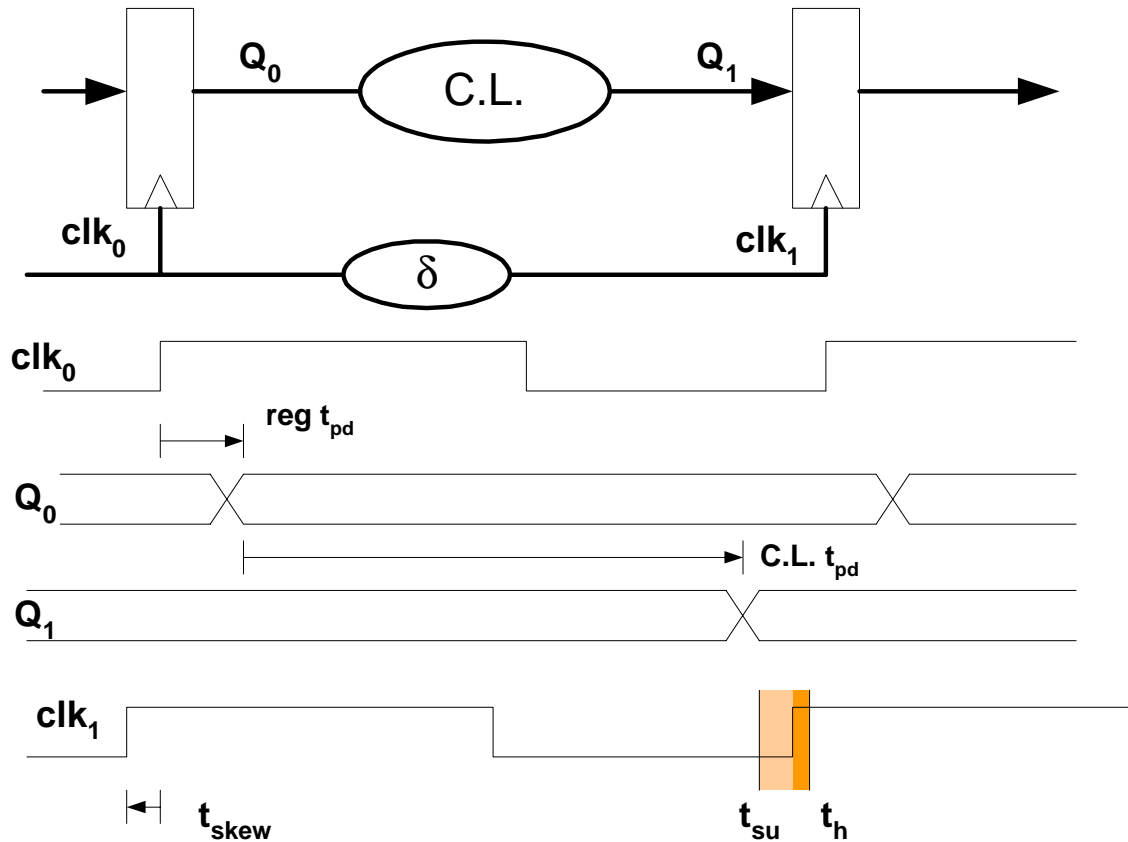

# Clock Skew

- If skew < 0:
  - $t_{clk} > \text{reg } t_{pd} + \text{C.L. } t_{pd} + \text{reg } t_{su} + |t_{skew}|$
  - Can you fix this after fab?

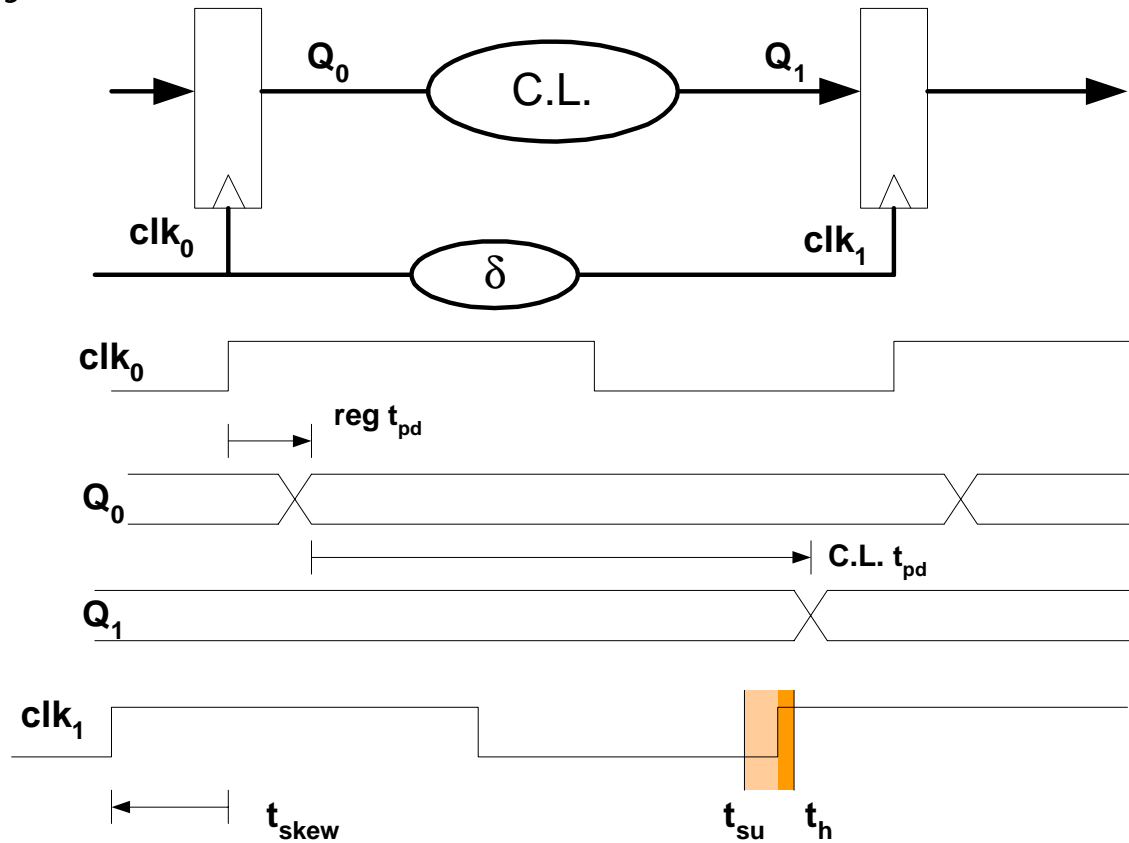


# Clock Skew



- Correct behavior assumes that all storage elements sample at exactly the same time
- Not possible in real systems:
  - clock driven from some central location
  - different wire delay to different points in the circuit
- Problems arise if skew is of the same order as FF contamination delay
- Gets worse as systems get faster (wires don't improve as fast)
  - 1) distribute clock signals against the data flow
  - 2) wire carrying the clock between two communicating components should be as short as possible
  - 3) try to make all wires from the clock generator be the same length => clock tree
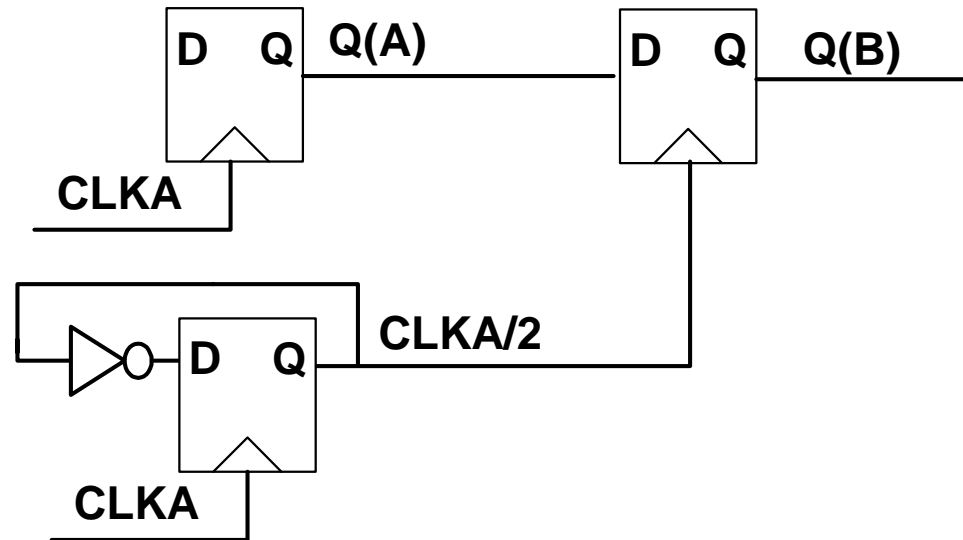
# Nasty Example


- What can go wrong?
- How can you fix it?




# Other Types of Latches and Flip-Flops

- D-FF is ubiquitous
  - simplest design technique, minimizes number of wires
  - preferred in PLDs and FPGAs
  - good choice for data storage register
  - edge-triggered has most straightforward timing constraints
- Historically J-K FF was popular
  - versatile building block, often requires less total logic
  - two inputs require more wiring and logic
  - can always be implemented using D-FF
- Level-sensitive latches in special circumstances
  - popular in VLSI because they can be made very small (4 T)
  - fundamental building block of all other flip-flop types
  - two latches make a D-FF
- Preset and clear inputs are highly desirable
  - System reset


# Comparison of Latches and flip-flops

 

positive  
edge-triggered  
flip-flop

 

 
transparent, flow-through  
(level-sensitive)  
latch





behavior is the same unless input changes  
while the clock is high
 
# What About External Inputs?

- Internal signals are OK
  - Can only change when clock changes
- External signals can change at any time
  - Asynchronous inputs
  - Truly asynchronous
  - Produced by a different clock
- This means register may sample a signal that is changing
  - Violates setup/hold time
  - What happens?




# Sampling external inputs

 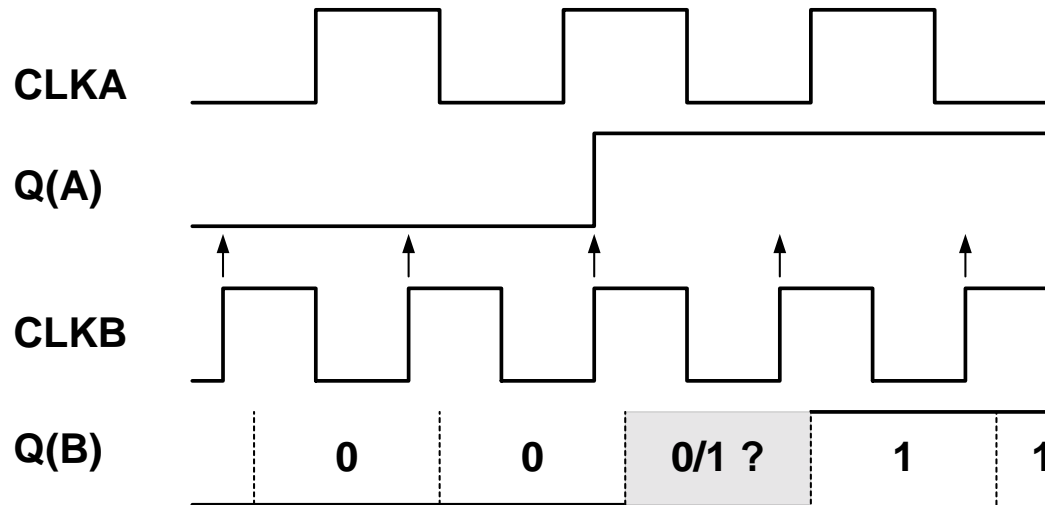



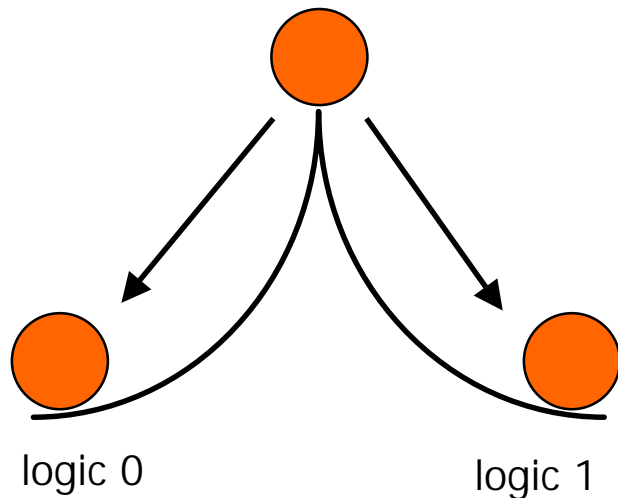
# Synchronization failure

- Occurs when FF input changes close to clock edge
  - the FF may enter a metastable state – neither a logic 0 nor 1 –
  - it may stay in this state an indefinite amount of time
  - this is not likely in practice but has some probability



 small, but non-zero probability that the FF output will get stuck in an in-between state



oscilloscope traces demonstrating synchronizer failure and eventual decay to steady state

# Calculating probability of failure


- For a single synchronizer

$$\text{Mean-Time Between Failure (MTBF)} = \exp ( tr / \tau ) / ( T_0 \times f \times a )$$

where a failure occurs if metastability persists beyond time  $tr$

- $tr$  is the resolution time - extra time in clock period for settling
  - $T_{clk} - (t_{pd} + T_{CL} + t_{setup})$
- $f$  is the frequency of the FF clock
- $a$  is the number of asynchronous input changes per second applied to the FF
- $T_0$  and  $\tau$  are constants that depend on the FF's electrical characteristics (e.g., gain or steepness of curve)
  - example values are  $T_0 = .4s$  and  $\tau = 1.5ns$  (sensitive to temperature, voltage, cosmic rays, etc.).
- Must add probabilities from all synchronizers in system
$$1/MTBF_{system} = \sum 1/MTBF_{synch}$$


# Metastability

 

- Example
  - input changes at 1 MHz
  - system clock of 10MHz, flipflop  $(t_{pd} + t_{setup}) = 5ns$   
 $MTBF = \exp(95ns / 1.5ns) / (.4s \times 10^7 \times 10^6) = 25 \text{ million years}$
  - if we go to 20MHz then:  
 $MTBF = \exp(45ns / 1.5ns) / (.4s \times 2 \times 10^7 \times 10^6) = 1.33 \text{ seconds!}$
  - And we're not even doing any logic!
- Must do the calculations and allow enough time for synchronization


# What does this circuit do?

- What's wrong with this?

 

# What does this circuit do?


- How much better is this?

 

- Can you do better?

 
# Guarding against synchronization failure

- Give the register time to decide
  - Probability of failure cannot be reduced to 0, but it can be reduced
- *Slow down the system clock?*
- *Use very fast technology for synchronizer -> quicker decision?*
- *Cascade two synchronizers?*



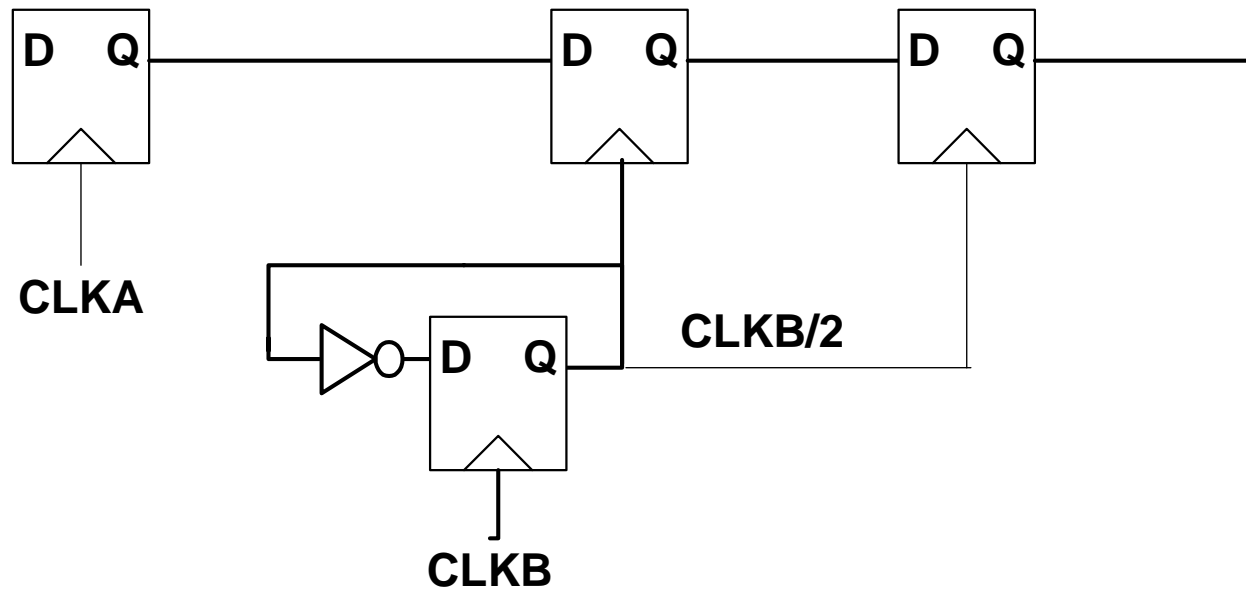
# Stretching the Resolution Time

- Also slows the sample rate and transfer rate


 
# Sampling Rate



- How fast does your sample clock need to be?




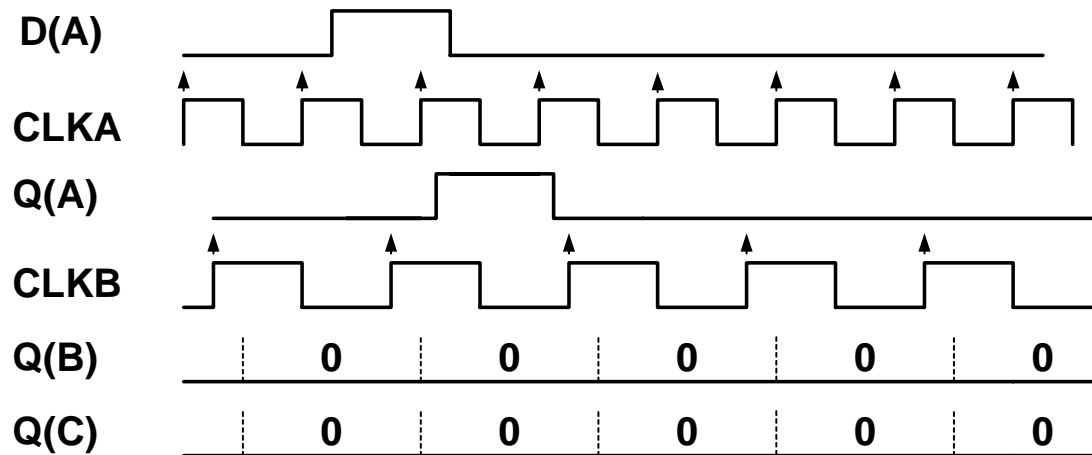 
# Sampling Rate

- How fast does your sample clock need to be?  $f(\text{clkB}) > 2f(\text{clkA})$



# Sampling Rate




- What if sample clock can't go faster?
- If input clock is not available, no solution(?)
- If input clock is available (e.g. video codec)



 
# Another Problem with Asynchronous inputs

- What goes wrong here? (Hint: it's not a metastability thing)
- What is the fix?



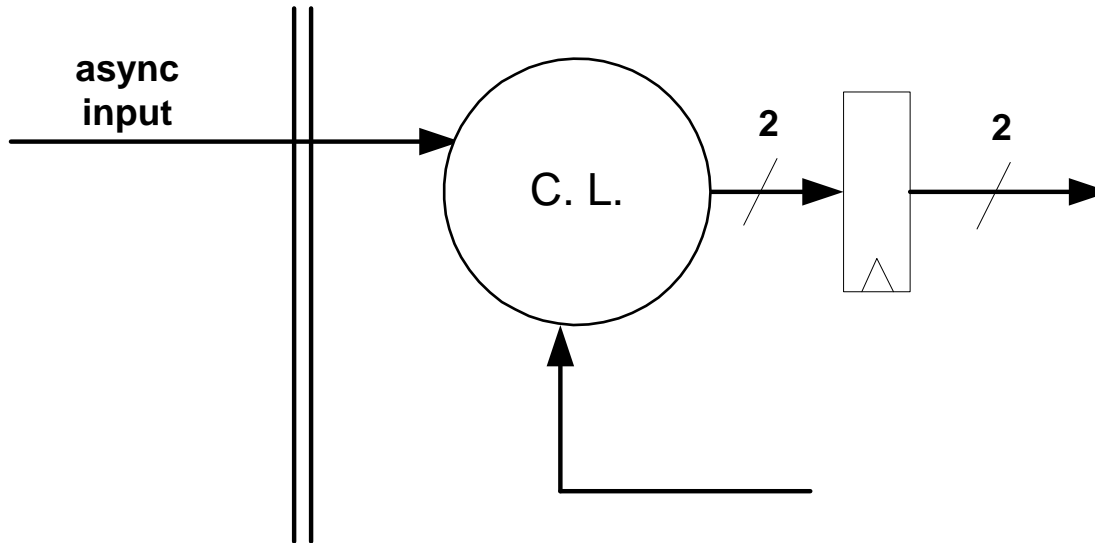
# More Asynchronous inputs

- What is the problem?
- What is the fix?



 
# Important Rule!

- Exactly one register makes the synchronizing decision




 
# More Asynchronous inputs

- Can we input asynchronous data values with several bits?


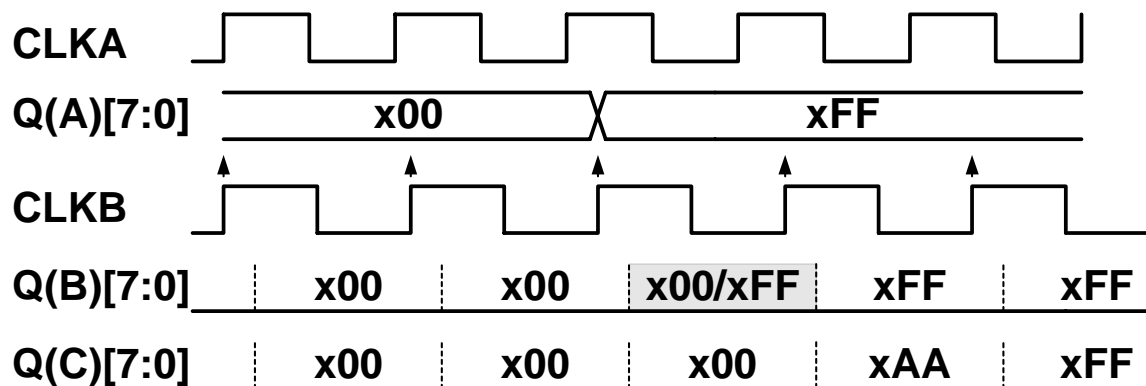 
# More Asynchronous inputs

- How can we input asynchronous data values with several bits?



!!




# What Went Wrong?



- Each bit has a different delay
  - Wire lengths differ
  - Gate thresholds differ
  - Driver speeds are different
  - Register delays are different
    - Rise vs. Fall times
  - Clock skews to register bits
- Bottom line – “data skew” is inevitable
  - aka Bus Skew
  - Longer wires => More skew
- What is the solution??

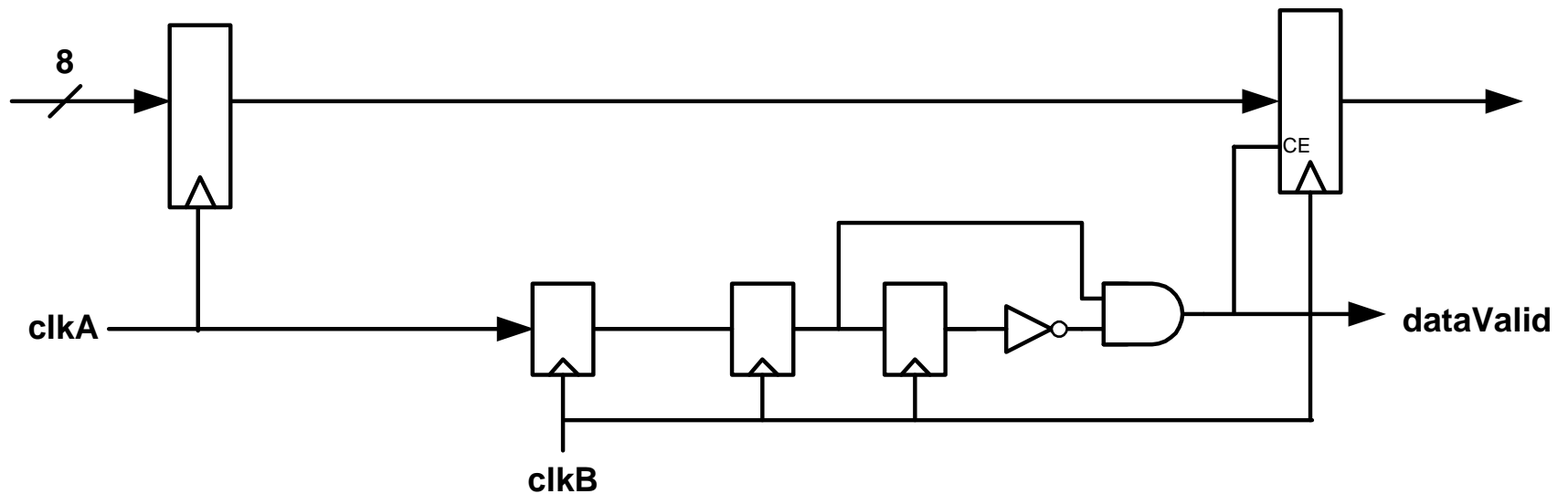
# Sending Multiple Data Bits

- Must send a “clock” with the data
  - Waits until data is stable
  - De-skewing delay
- $f(\text{clkB}) > 2 f(\text{clkA})$



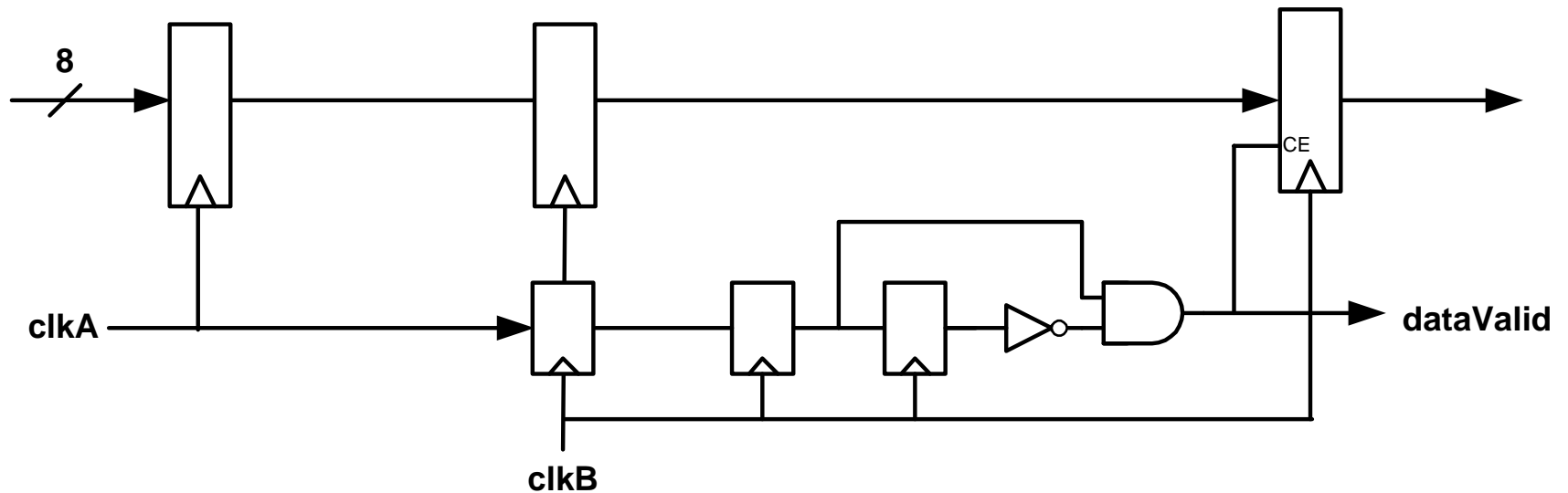
# Sending Multiple Data Bits

- Balancing path delays . . .
- What's wrong with this solution?
- What's the right way to do it?



# Sending Multiple Data Bits

- The right way to do it . . .

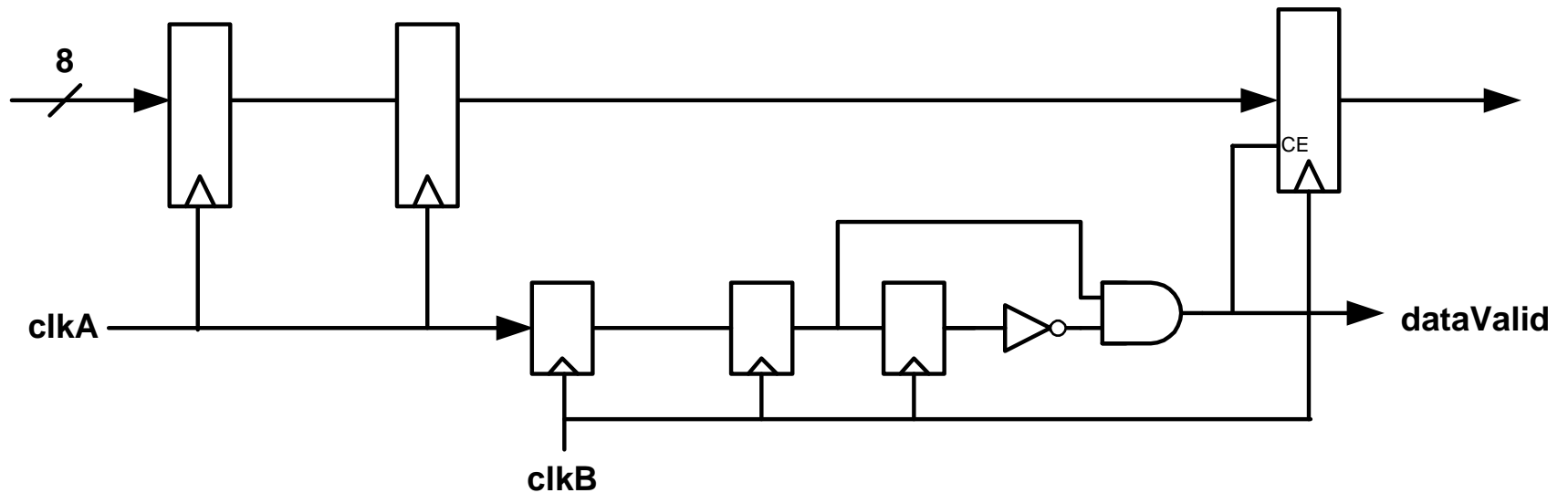

# Sending Multiple Data Bits

- Slightly different alternative . . .

