

Introduction to CMOS VLSI Design

Layout, Fabrication, and Elementary Logic Design


Adapted from Weste & Harris
CMOS VLSI Design

Overview

- ❑ Implementing switches with CMOS transistors
- ❑ How to compute logic functions with switches
- ❑ Fabricating transistors on a silicon wafer and connecting them together


Silicon Lattice

 - ❑ Transistors are built on a silicon substrate
- ❑ Silicon is a Group IV material
- ❑ Forms crystal lattice with bonds to four neighbors




Dopants

 - ❑ Silicon is a semiconductor
- ❑ Pure silicon has no free carriers and conducts poorly
- ❑ Adding dopants increases the conductivity
- ❑ Group V: extra electron (n-type)
- ❑ Group III: missing electron, called hole (p-type)




p-n Junctions

 - ❑ A junction between p-type and n-type semiconductor forms a diode.
- ❑ Current flows only in one direction




anode cathode

 


nMOS Transistor

 - ❑ Four terminals: gate, source, drain, body
- ❑ Gate – oxide – body stack looks like a capacitor
 - Gate and body are conductors
 - SiO_2 (oxide) is a very good insulator




nMOS Operation

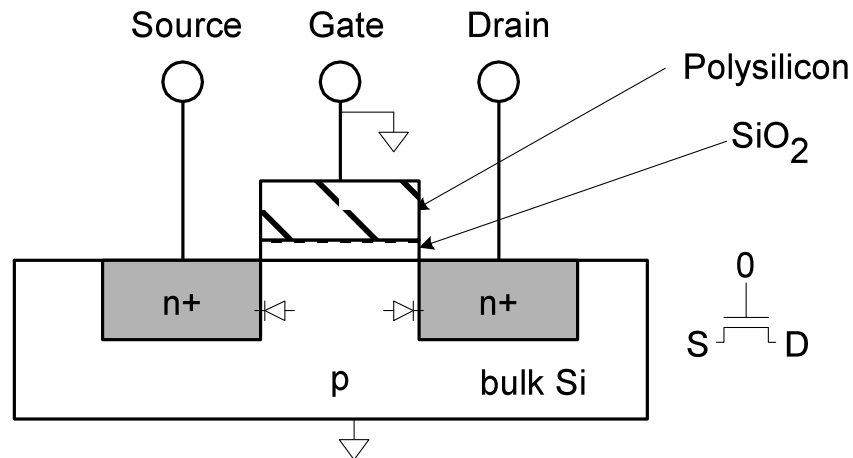- ❑ Body is commonly tied to ground (0 V)
- ❑ When the gate is at a low voltage:
 - Source-body and drain-body diodes are OFF
 - No current flows, transistor is OFF




nMOS Operation

 - When the gate is at a high voltage:
 - Positive charge on gate of MOS capacitor
 - Negative charge attracted to body
 - Inverts a channel under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



pMOS Transistor

 - ❑ Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior




Power Supply Voltage

- ❑ $GND = 0\text{ V}$
- ❑ In 1980's, $V_{DD} = 5\text{V}$
- ❑ V_{DD} has decreased in modern processes
 - High V_{DD} would damage modern tiny transistors
 - Lower V_{DD} saves power
- ❑ $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, \dots$


Transistor Abstraction

 - 3D structure formed by fabrication
- 2D planar “layout” view
- Schematic symbol
- Switch



Transistors as Switches

 - ❑ We can view MOS transistors as electrically controlled switches
- ❑ Voltage at gate controls path from source to drain




Switching Logic


conducts iff
 $a \cdot b$
(0 only)



conducts iff
 $a + b$
(0 only)

 

 
conducts iff
 $a' \cdot b'$ or $(a + b)'$
(1 only)



conducts iff
 $a' + b'$ or $(a \cdot b)'$
(1 only)

Implementation of Logic Gates

□ OR gate

 

a	b	a + b
0	0	0
0	1	1
1	0	1
1	1	1

□ Two problems


- 1) when $a=b=0$, $f(a,b)$ is undefined (floating)
- 2) n- type switches do not conduct 1 well

□ Two solutions

- when $f=0$, connect output to 0v using n-type switches
- when $f=1$, connect output to 1v using p-type switches

Complementary CMOS Gates

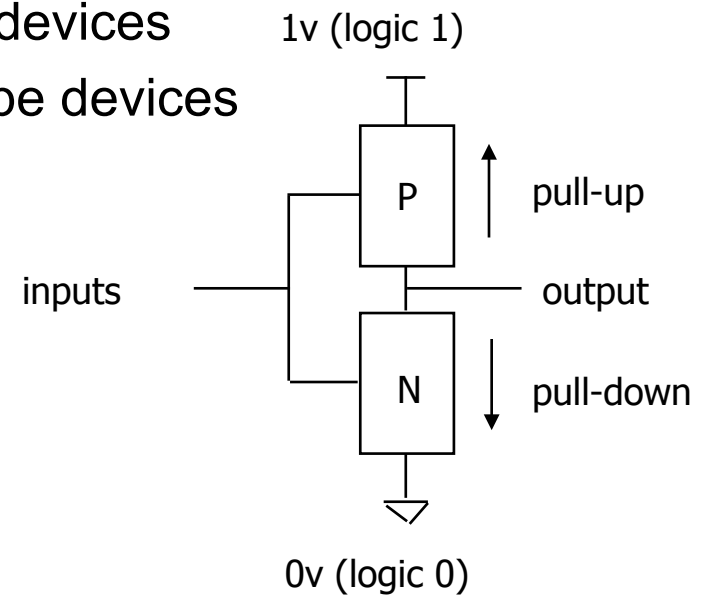- ❑ Pull-up network consisting of p-type devices
- ❑ Pull-down network consisting of n-type devices




- ❑ Example: an inverter

a	a'
0	1
1	0



↑: a'

↓: a

 



CMOS Inverter

A	Y
0	
1	

  



CMOS Inverter

A	Y
0	
1	0

  



CMOS Inverter

A	Y
0	1
1	0

  



CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	
1	0	
1	1	

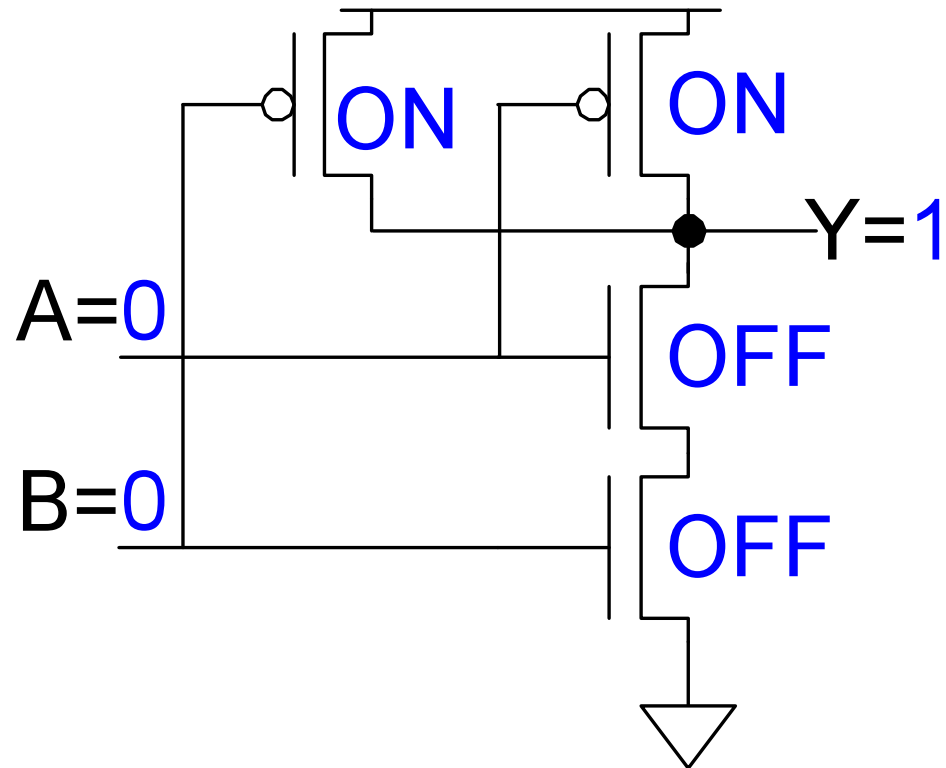 



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	
1	1	

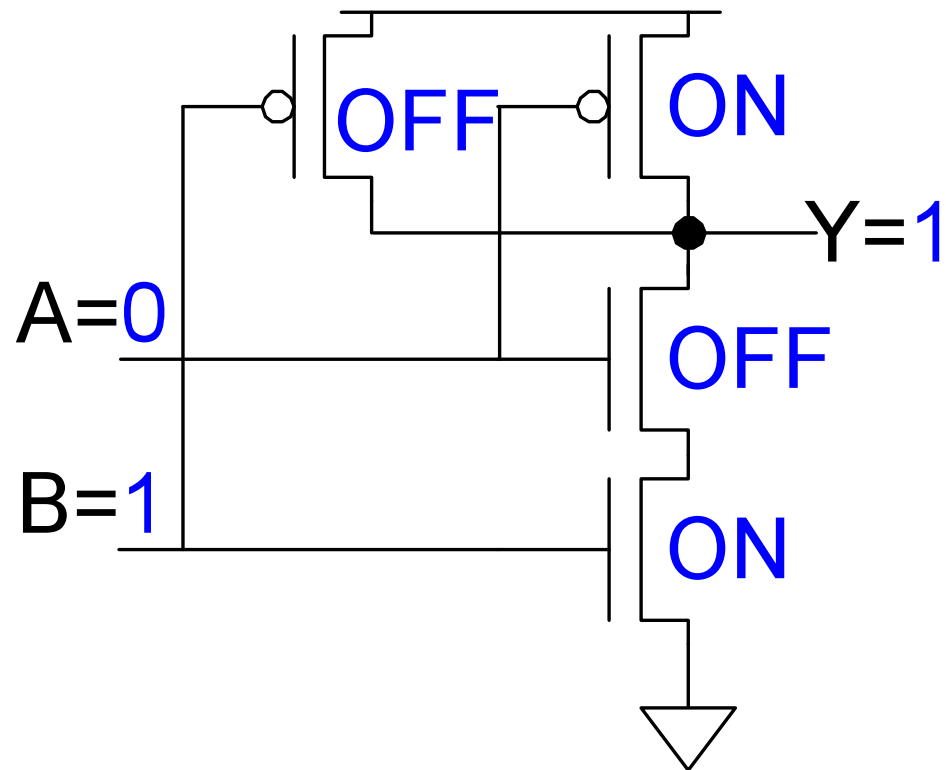 



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	

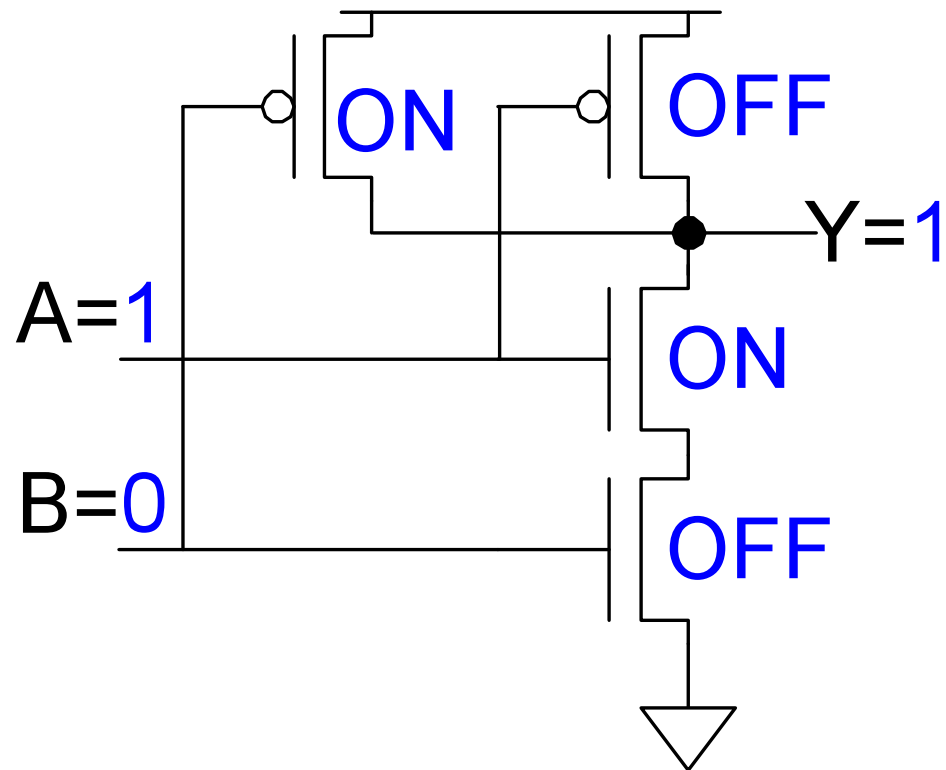 



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

  

CMOS NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

  


3-input NAND Gate

- Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0


3-input NAND Gate

 - ❑ Y pulls low if ALL inputs are 1
- ❑ Y pulls high if ANY input is 0



Switch Logic vs. Gate Logic

- Example: two-input multiplexer

 

$f=a,$ when $s=0$

$f=b,$ when $s=1$


$f=s'a+sb$

Switch Logic vs. Gate Logic

- ❑ Two-input mux with gate logic (14 transistors)




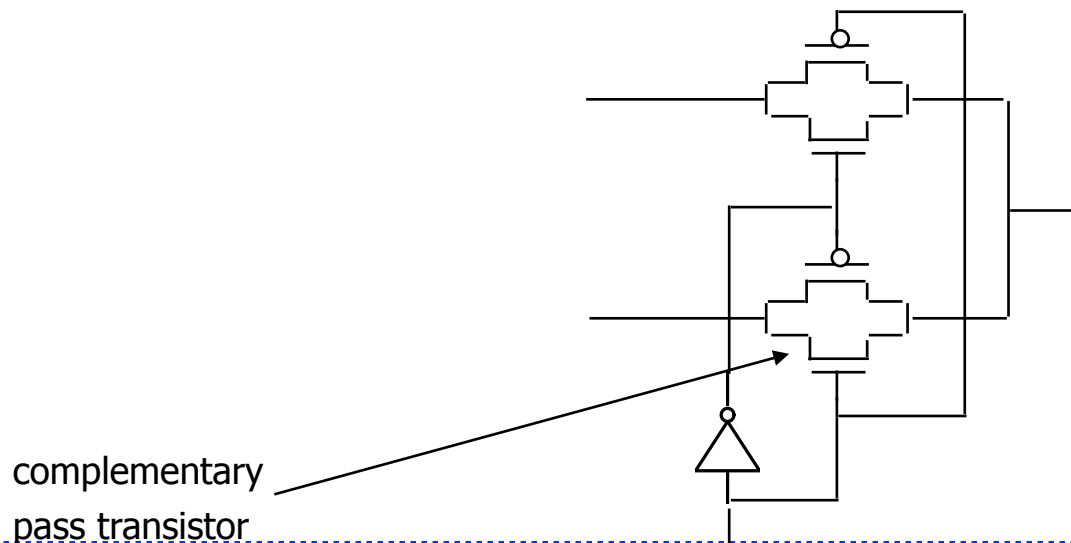- ❑ Two-input mux with switch logic (6 transistors)





Implementing LUTs

 - ❑ Multiplexor logic – simple switch network (a tree)
 - inputs: programming bits
 - controls: inputs to CLB
 - output: function value
- ❑ However, series transistors are slow – $O(n^2)$





Programmable Interconnect

 
 
- ❑ Switches connect wires at intersections
- ❑ Can also be used to segment wire
- ❑ Repeaters needed every so often
 - simple non-inverting buffers (2 inverters)
 - otherwise, too many switches in series slow down signal



Master-Slave Register

  


Dynamic Register

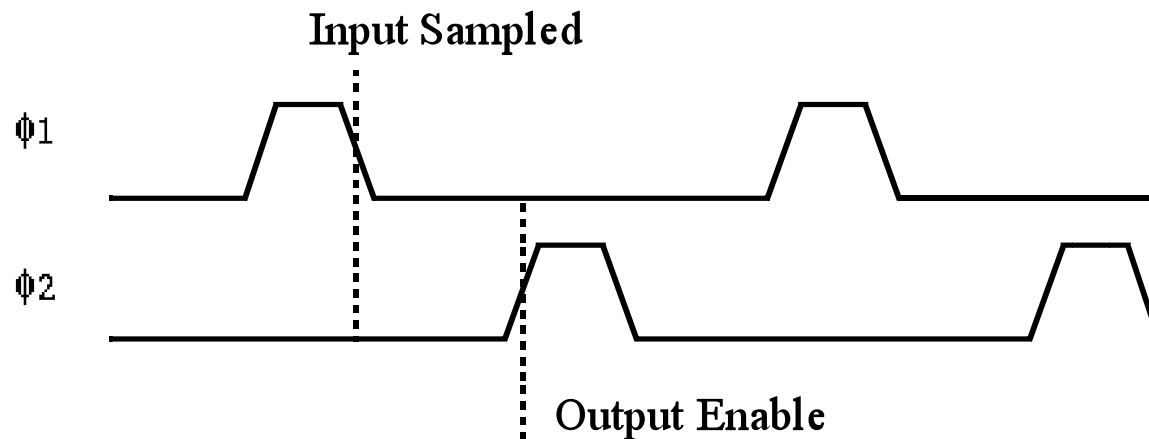 


Latch-Based Design

- ❑ Switches and/or gates compute new values to store on next clock cycle

straightforward implementation

 


 this circuit can use the entire clock cycle – no wasted time - a form of retiming




Static Memory Cell

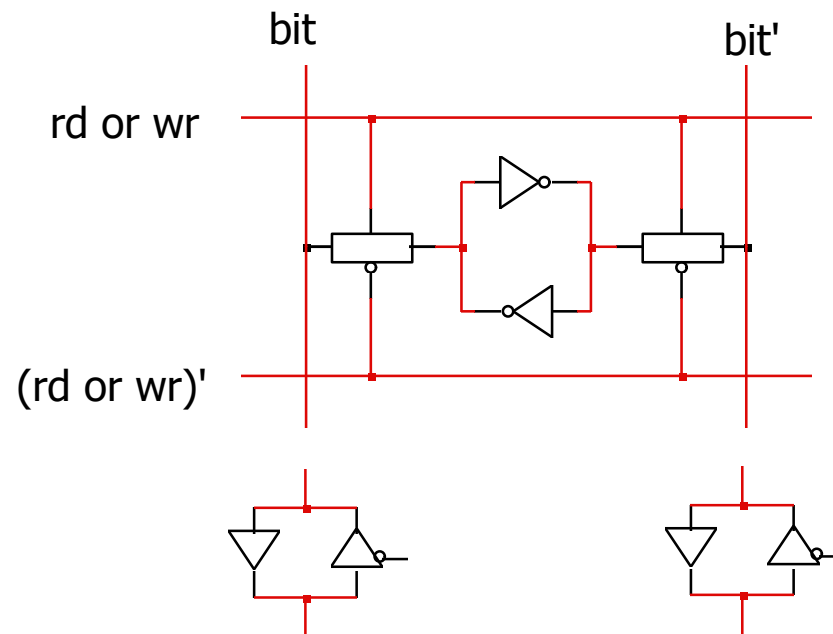- ❑ 8-transistor cell
- ❑ N-transistor only: 6T cell



Dynamic Memory Cell

□ 1-transistor cell

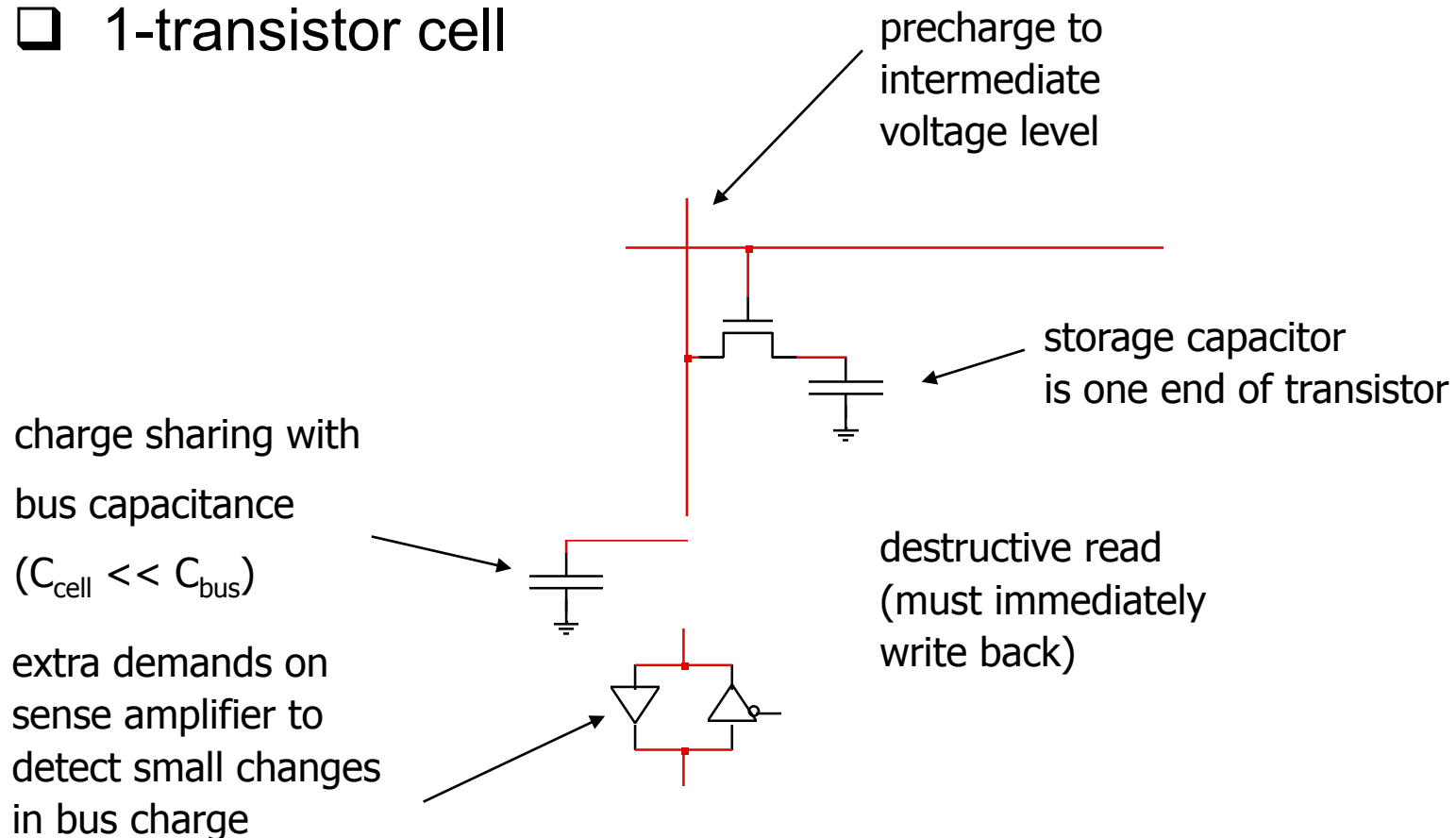


Dynamic storage

- ❑ Capacitor implemented by gate capacitance of transistor
- ❑ No capacitor is perfect
 - charge leaks away through imperfect switches
- ❑ Must be replenished or refreshed
 - 'memory' lasts about 1ms
- ❑ Solution: periodically read the value and write it back

Read-only Memory Cells

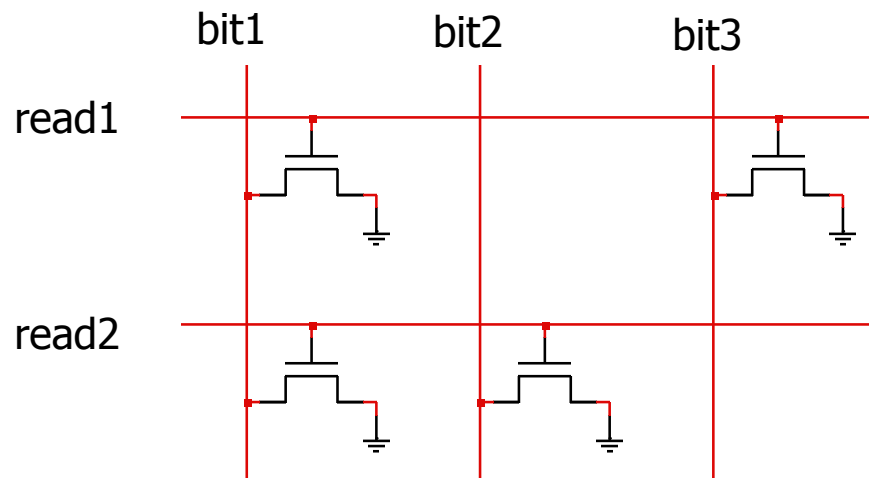
- ❑ To store constants or other invariant data
- ❑ Popular for control implementation



programmable logic array structure
(exploits distributed NOR gate structure)

Multi-ported Register Cells

- Augment 6T cell for more I/O

 






CMOS Fabrication

- ❑ CMOS transistors are fabricated on silicon wafer
- ❑ Lithography process similar to printing press
- ❑ On each step, different materials are deposited or etched
- ❑ Easiest to understand by viewing both top and cross-section of wafer in a simplified manufacturing process

The wafer

 - ❑ Czochralski process
 - Melt silicon at 1425 °C
 - Add impurities (dopants)
 - Spin and pull crystal
- ❑ Slice into wafers
 - 0.25mm to 1.0mm thick
- ❑ Polish one side



    


CMOS VLSI Design

Crystal and wafer



© Kay Chernush


Wand
(a finished 250lb crystal)

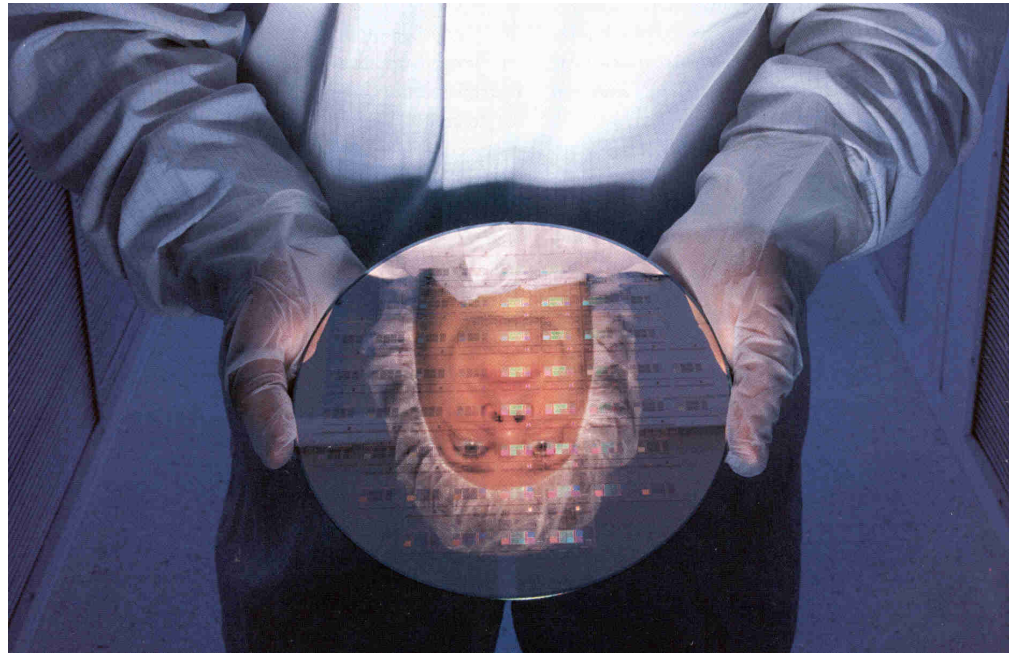

A polished wafer

The mask

 - ❑ Illuminate reticle on wafer
 - Typically 4× reduction
- ❑ Typical image is 25×25mm
 - Limited by focus
- ❑ Step-and repeat across wafer
 - Limited by mechanical alignment



Lithography

- ❑ Patterning is done by exposing photoresist with light
- ❑ Requires many steps per “layer”
- ❑ Example: Implant layer



Grow Oxide Layer




Oxidation Layering

Reference: CMOS VLSI Design

Add Photoresist



Photoresist Application
(Ontrak)

 

Photoresist Coating



Reference: CMOS VLSI Design

Mask




Pattern
Preparation




Reticle
Pattern Preparation

Expose using UV Light

 

Photolithography


Develop and Remove Resist

 

Photoresist Developing

Reference: CMOS VLSI Design

Etch Silicon Dioxide

 

Reference: CMOS VLSI Design


Remove Resist



Photoresist Ashing

Reference: CMOS VLSI Design


Implant Dopant

 

Reference: CMOS VLSI Design


Inverter Cross-section

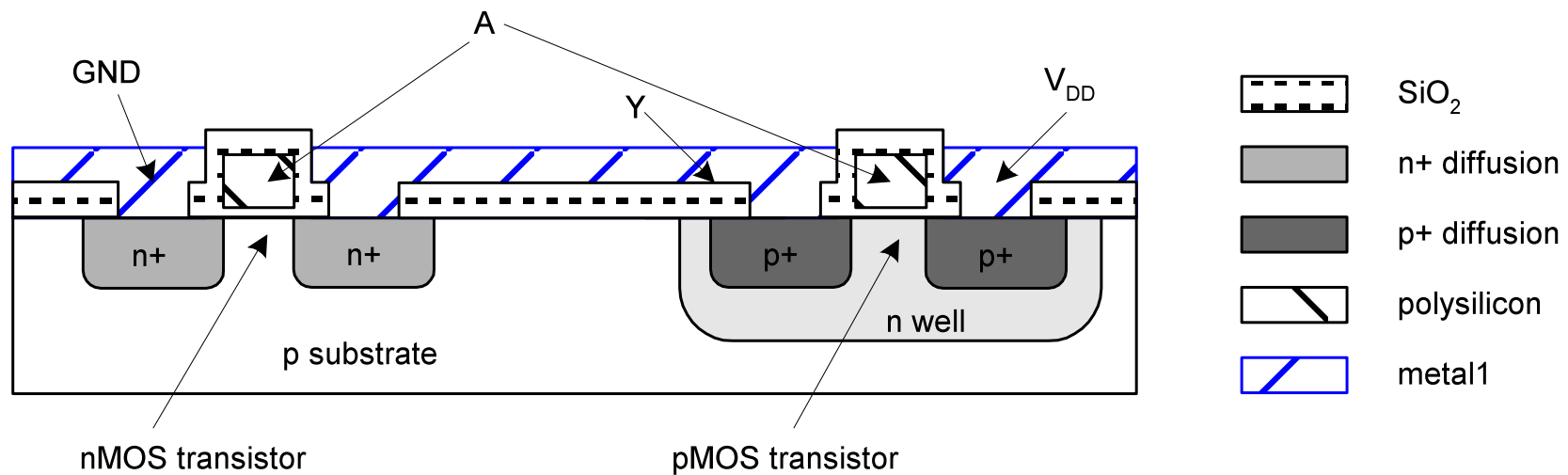- Typically use p-type substrate for nMOS transistor
 - Requires n-well for body of pMOS transistors
 - Several alternatives: SOI, twin-tub, etc.



Inverter Layout

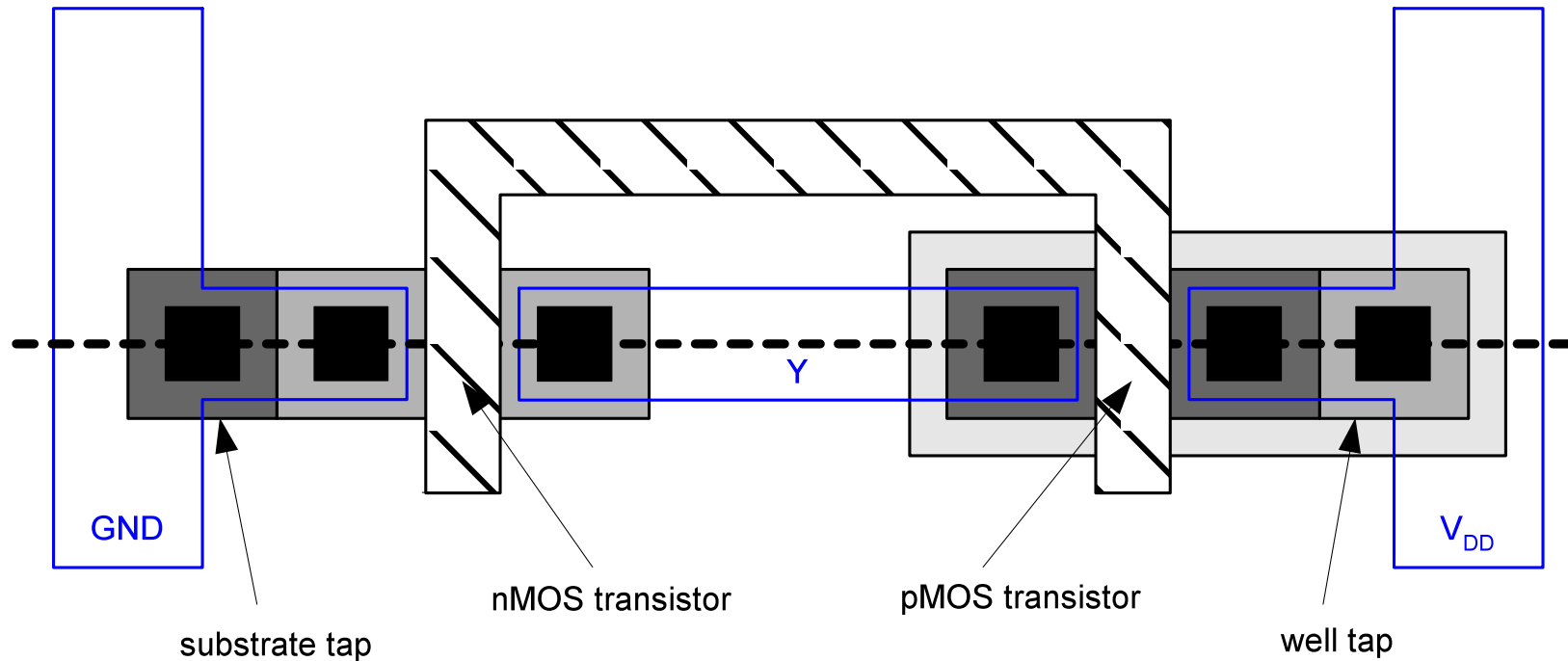
- ❑ Transistors and wires are defined by *masks*
- ❑ Cross-section taken along dashed line




Advanced Metallization - Copper

Dual damascene IC process


- Oxide deposition

 


- Stud lithography and reactive ion etch

 


- Wire lithography and reactive ion etch

 


- Stud and wire metal deposition

 

- Metal chemical-mechanical polish

 

Source: IBM Corp.

 


Copper versus Aluminum


~ 40% lower resistivity

~ 10× less electromigration


A View of Interconnect

 

Package-to-Board Interconnect

 


(a) Through-Hole Mounting

 


(b) Surface Mount

Flip-Chip Bonding

 

Package Types

 

Multi-Chip Modules

