

CSE 311: Foundations of Computing I
Assignment #7
May 17, 2010
due: Monday, May 24, 1:30 p.m.

In problems 1-3, use the Boolean expression notation of Chapter 11, not the propositional logic notation of Chapter 1. For the complement of p , you may use either p' as was done in lecture or \bar{p} as is done in the text.

1. Let $F(x, y, z) = x \oplus y \oplus z$. Be sure to show your work.
 - (a) Express $F(x, y, z)$ in sum-of-products canonical form.
 - (b) Express $F(x, y, z)$ in product-of-sums canonical form.
2. Section 11.2, exercise 14. Explain how this exercise shows that the single operator NAND by itself can be used to express any Boolean function. (Exercise 15 similarly shows that NOR by itself can be used to express any Boolean function.)
3. Figure 9 on page 765 shows a very different implementation of a full adder than was presented in lecture. For this problem, assume that the half adders are implemented as presented in lecture, and not as shown in Figure 8. That is, the top output of each half adder is the XOR of its two inputs, and the bottom output of each half adder is the AND of its two inputs. Each half adder thus consists of just 2 gates, for a total of 5 gates in the full adder of Figure 9, one fewer gate than the full adder presented in lecture.

Show that the resulting full adder computes the correct outputs. There is a subtlety to work out, because if you look carefully you will see that the carry out computed by this circuit does not come out exactly $xy + c_i x + c_i y$ as it should.
4. Section 12.2, exercise 4. For each part, in addition to the output string, give the sequence of states determined by the input string.
5. Construct the state diagram for a finite-state machine that outputs 1 if the input string read so far contains the substring aba , and outputs 0 otherwise. The input alphabet is $\{a, b\}$ and the output alphabet is $\{0, 1\}$.