

CSE311: Quiz Section, 10/06/2011

1. Show that $(p \rightarrow q) \rightarrow r$ and $p \rightarrow (q \rightarrow r)$ are not logically equivalent.
2. Find the sum-of-products expansion of the Boolean function $F(w, x, y, z)$ that has the value 1 if and only if an odd number of w , x , y , and z have value 1.
3. Construct circuits from inverters, AND gates, and OR gates to produce these outputs.
 - (a) $\bar{x} + y$
 - (b) $xyz + \bar{x}y$
 - (c) $(\bar{x} + \bar{y})(\bar{y} + \bar{z})(\bar{x} + \bar{z})$
4. Design a circuit that implements majority voting for five individuals.
5. How many different Boolean functions $F(x, y, z)$ are there such that $F(\bar{x}, \bar{y}, \bar{z}) = F(x, y, z)$ for all values of the Boolean variables x , y , and z ?