

# CSE 311 Foundations of Computing I

Lecture 25  
Circuits for FSMs, Carry-Look-Ahead Adders  
Autumn 2011

## Announcements


- Nice overview of adder circuits at <http://www.aoki.ecei.tohoku.ac.jp/arith/mg/algorithm.html>

## Last lecture highlights

- Languages not recognized by any DFA
  - $\{ 0^n 1^n : n \geq 0 \}$
  - Binary Palindromes
  - Strings of Balanced Parentheses
- Using DFAs for efficient pattern matching

 
## FSMs in Hardware

- Encode the states in binary: e.g. states 0,1,2,3 represented as 000,100,010,001, or as 00,01,10,11.
- Encode the input symbols as binary signals
- Encode the outputs possible as binary signals
- Build combinational logic circuit to compute transition function:



 
## FSMs in Hardware

- Combine with sequential logic for
  - Registers to store bits of state
  - Clock pulse
- At start of clock pulse, current state bits from registers and input signals are released to the circuit
- At end of clock pulse, output bits are produced and next state bits are stored back in the same registers


 
## FSM for binary addition


- Assume that the two integers are  $a_{n-1} \dots a_2 a_1 a_0$  and  $b_{n-1} \dots b_2 b_1 b_0$  and bits arrive together as  $[a_i, b_i]$  then  $[a_1, b_1]$  etc.



[1,1] Generate a carry of 1  
[0,1],[1,0] Propagate a carry of 1 if it was already there

 
## FSM for binary addition using output on edges

- Assume that the two integers are  $a_{n-1}...a_2a_1a_0$  and  $b_{n-1}...b_2b_1b_0$  and bits arrive together as  $[a_i, b_i]$  then  $[a_1, b_1]$  etc.



$[1,1]$  Generate a carry of 1  
 $[0,1],[1,0]$  Propagate a carry of 1 if it was already there

## Example: 1-bit Full Adder

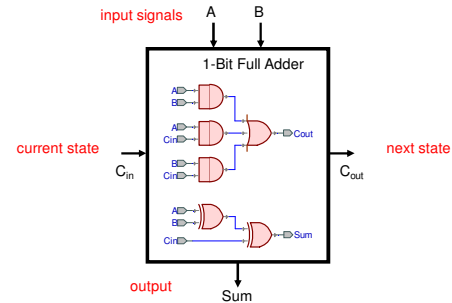

Autumn 2011

CSE 311

8

## FSMs without sequential logic


- What if the entire input bit-strings are available at all once at the start?
  - E.g. 64-bit binary addition
- Don't want to wait for 64 clock cycles to compute the output!
- Suppose all input strings have length  $n$ 
  - Can chain together  $n$  copies of the state transition circuit as one big combinational logic circuit

Autumn 2011

CSE 311

9

## A 2-bit ripple-carry adder

 

Autumn 2011

CSE 311

10

## Problem with Chaining Transition Circuits

- Resulting Boolean circuit is "deep"
- There is a small delay at each gate in a Boolean circuit
  - The clock pulse has to be long enough so that all combinational logic circuits can be evaluated during a single pulse
  - Deep circuits mean slow clock.

Autumn 2011

CSE 311

11

## Speeding things up?

- To go faster, need to work on both 1<sup>st</sup> half and 2<sup>nd</sup> half of the input at once
  - How can you determine action of FSM on 2<sup>nd</sup> half without knowing state reached after reading 1<sup>st</sup> half?

$b_1b_2...b_{n/2} \uparrow b_{n/2+1}...b_{n-1}b_n$   
 what state?

- Idea: Figure out what happens in 2<sup>nd</sup> half for *all* possible values of the middle state at once


Autumn 2011

CSE 311


12

## Transition Function Composition

State	0	1
$s_0$	$s_0$	$s_1$
$s_1$	$s_0$	$s_2$
$s_2$	$s_0$	$s_3$
$s_3$	$s_3$	$s_3$

 

 Transition table gives a function for each input symbol



State reached on input  $b_1 \dots b_n$  is

$$f_{b_n}(f_{b_{n-1}}(\dots(f_{b_2}(f_{b_1}(\text{start})))) \dots) = f_{b_n} \circ f_{b_{n-1}} \circ \dots \circ f_{b_2} \circ f_{b_1}(\text{start})$$

## Transition Function Composition


Constant size 2-level

Boolean logic to

- convert input symbol to bits for transition function



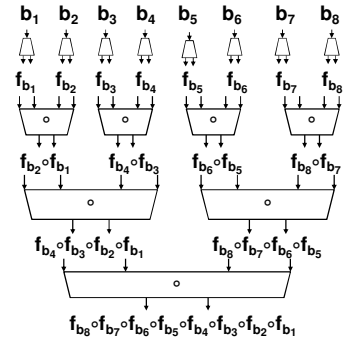- compute composition of two transition functions



Total depth  $2 \log_2 n$   
and size  $\approx n$

## Carry-Look-Ahead Adder

Compute generate  $G_i = a_i \wedge b_i$  [1,1]  
propagate  $P_i = a_i \oplus b_i$  [0,1],[1,0]

These determine transition and output functions

- Carry  $C_i = G_i \vee (P_i \wedge C_{i-1})$  also written  $C_i = G_i + P_i C_{i-1}$
- Sum  $S_i = P_i \oplus C_{i-1}$

Unwinding, we get

$$\begin{aligned} C_0 &= G_0 & C_1 &= G_1 + G_0 P_1 & C_2 &= G_2 + G_1 P_2 + G_0 P_1 P_2 \\ C_3 &= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 \\ C_4 &= G_4 + G_3 P_4 + G_2 P_3 P_4 + G_1 P_2 P_3 P_4 + G_0 P_1 P_2 P_3 P_4 \\ &\text{etc.} \end{aligned}$$

## Carry-Look-Ahead Adder

Compute all generate  $G_i = a_i \wedge b_i$  [1,1]  
propagate  $P_i = a_i \oplus b_i$  [0,1],[1,0]

Then compute all:

$$\begin{aligned} C_0 &= G_0 & C_1 &= G_1 + G_0 P_1 & C_2 &= G_2 + G_1 P_2 + G_0 P_1 P_2 \\ C_3 &= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 \\ C_4 &= G_4 + G_3 P_4 + G_2 P_3 P_4 + G_1 P_2 P_3 P_4 + G_0 P_1 P_2 P_3 P_4 \quad \text{etc.} \end{aligned}$$

Finally, use these to compute

$$\begin{aligned} \text{Sum}_0 &= P_0 & \text{Sum}_1 &= P_1 \oplus C_0 & \text{Sum}_2 &= P_2 \oplus C_1 \\ \text{Sum}_3 &= P_3 \oplus C_2 & \text{Sum}_4 &= P_4 \oplus C_3 & \text{Sum}_5 &= P_5 \oplus C_4 \quad \text{etc} \end{aligned}$$

If all  $C_i$  are computed using 2-level logic, total depth is 4.

## Adders using Composition

Carry-look-ahead circuit for carry  $C_{n-1}$   
has  $2 + 3 + \dots + n = (n+2)(n-1)/2$  gates

- a lot more than ripple-carry adder circuit.

Composition gives an alternative approach

Composition:  $(G,P)$  followed by  $(G',P')$  gives the same effect as  $(G'',P'')$  where

- $G'' = G' \vee (G \wedge P')$  and  $P'' = P' \wedge P$  also written as  $G'' = G' + G P'$  and  $P'' = P' P$

## Adders using Composition

Composition:  $(G,P)$  followed by  $(G',P')$  gives the same effect as  $(G'',P'')$  where

- $G'' = G' \vee (G \wedge P')$  and  $P'' = P' \wedge P$  also written as  $G'' = G' + G P'$  and  $P'' = P' P$

Use this for the circuit component



in transition function composition tree

- Computes  $C_{n-1}$  in depth  $2 \log_2 n$  and size  $\approx n$

- But we need all of  $C_0, C_1, \dots, C_{n-1}$  not just  $C_{n-1}$

## Transition Function Composition

Constant size 2-level Boolean logic to


- convert input symbol to bits for transition function



- compute composition of two transition functions



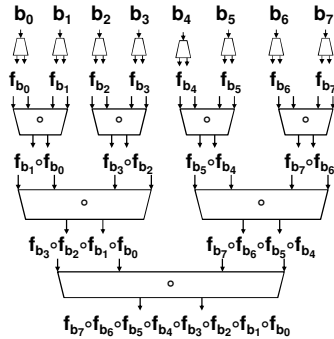Total depth  $2 \log_2 n$  and size  $\approx n$



## Computing all the values


- We need to compute all of

$$\begin{aligned}
 & f_{b_7 \circ f_{b_6 \circ f_{b_5 \circ f_{b_4 \circ f_{b_3 \circ f_{b_2 \circ f_{b_1 \circ f_{b_0}}}}}}} && \text{Already computed} \\
 & f_{b_6 \circ f_{b_5 \circ f_{b_4 \circ f_{b_3 \circ f_{b_2 \circ f_{b_1 \circ f_{b_0}}}}} && = f_{b_6 \circ (f_{b_5 \circ f_{b_4}}) \circ (f_{b_3 \circ f_{b_2 \circ f_{b_1 \circ f_{b_0}}})} \\
 & f_{b_5 \circ f_{b_4 \circ f_{b_3 \circ f_{b_2 \circ f_{b_1 \circ f_{b_0}}}}} && = (f_{b_5 \circ f_{b_4}}) \circ (f_{b_3 \circ f_{b_2 \circ f_{b_1 \circ f_{b_0}}})} \\
 & f_{b_4 \circ f_{b_3 \circ f_{b_2 \circ f_{b_1 \circ f_{b_0}}}}} && = f_{b_4 \circ (f_{b_3 \circ f_{b_2 \circ f_{b_1 \circ f_{b_0}}})} \\
 & f_{b_3 \circ f_{b_2 \circ f_{b_1 \circ f_{b_0}}}} && \text{Already computed} \\
 & f_{b_2 \circ f_{b_1 \circ f_{b_0}}} && = f_{b_2 \circ (f_{b_1 \circ f_{b_0}}) \\
 & f_{b_1 \circ f_{b_0}} && \text{Already computed} \\
 & f_{b_0} && \text{Already computed}
 \end{aligned}$$

## Parallel Prefix Circuit

- The general way of doing this efficiently is called a parallel prefix circuit
  - Designed and analyzed by Michael Fischer and Richard Ladner (University of Washington)
- Uses the adder composition operation that sets  $G'' = G' + G P'$  and  $P'' = P' P$ 
  - we just show it for the part for computing  $P''$  which is a Parallel Prefix AND Circuit

## The Parallel Prefix AND Circuit

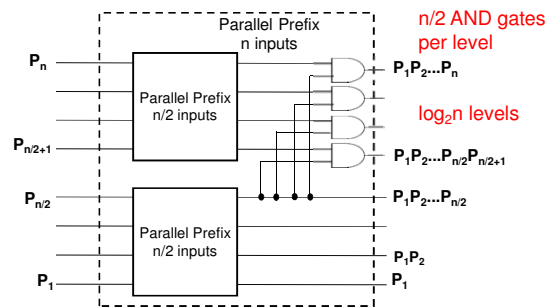

## Parallel Prefix Adder

- Circuit depth  $2 \log_2 n$
- Circuit size  $4 n \log_2 n$
- Actual adder circuits in hardware use combinations of these ideas and more but this gives the basics
- Nice overview of adder circuits at <http://www.aoki.ecei.tohoku.ac.jp/arith/mg/algorithm.html>