

CSE311 Quiz Section: October 4, 2012

1. Carry look-ahead adder.
2. Find the sum-of-products expansion of the Boolean function $F(w, x, y, z)$ that has the value 1 if and only if an odd number of w, x, y, z have value 1.
3. Construct circuits from inverters, AND gates, and OR gates to produce these outputs. Can you simplify any of them? (Note: A bar above an expression means its negation)

(a) $\bar{x} + y$

(b) $xyz + \bar{x}y$

(c) $(\overline{x+y})(\overline{y+z})(\overline{x+z})$

4. Translate English to logical expressions with nested quantifiers.

Both editions: 1.5: 9

Let $L(x,y)$ be the statement "x loves y"

- (a) There is somebody whom everybody loves. (c)
- (b) Nobody loves everybody. (d)
- (c) Everyone loves himself or herself. (i)
- (d) There is someone who loves no one besides himself or herself. (j)