

CSE311 Quiz Section: October 4, 2012

1. Carry look-ahead adder.
2. Find the sum-of-products expansion of the Boolean function $F(w, x, y, z)$ that has the value 1 if and only if an odd number of w, x, y, z have value 1. Standard methodology for sum of products gives us:

$$F(w, x, y, z) = w'xyz + wx'yz + wxy'z + wxyz' + w'x'y'z + w'x'yz' + w'x'y'z' + w'x'y'z'$$

3. Construct circuits from inverters, AND gates, and OR gates to produce these outputs. Can you simplify any of them? (Note: A bar above an expression means its negation)
 - (a) $\bar{x} + y$
 - (b) $xyz + \bar{x}y$

$$xyz + \bar{x}y = y(xz + \bar{x}) = y((x + \bar{x})(z + \bar{x})) = y(1)(z + \bar{x}) = y(\bar{x} + z)$$

where in the second step we used the distributive law.

- (c) $\overline{(x + y)(y + z)(x + z)}$

Let's calculate the negation of this statement. Then by De Morgan's law:

$$\overline{(x + y)(y + z)(x + z)} = \overline{(x + y)} + \overline{(y + z)} + \overline{(x + z)} =$$

$$x + y + y + z + x + z = x + y + z$$

Therefore the initial expression is equal to:

$$\overline{x + y + z}$$

This gives a circuit with 3 gates (2 OR, 1 NOT). If we approached this by just applying De Morgan's law, we would get:

$$\bar{x}\bar{y}\bar{z}$$

and we would need 5 gates for the circuit (3 NOT, 2 AND).

4. Translate English to logical expressions with nested quantifiers.
Both editions: 1.5: 9 **The solution is in the book.**