

# CSE 311 Foundations of Computing I

Lecture 4, Boolean Logic  
Autumn 2012

## Announcements

- Reading assignments
  - Boolean Algebra
    - 12.1 – 12.3 7<sup>th</sup> Edition
    - 11.1 – 11.3 6<sup>th</sup> Edition
    - 10.1 – 10.3 5<sup>th</sup> Edition
  - Predicates and Quantifiers
    - 1.4 7<sup>th</sup> Edition
    - 1.3 5<sup>th</sup> and 6<sup>th</sup> Edition

## Boolean logic

- Combinational logic
  - $output_t = F(input_t)$
- Sequential logic
  - $output_t = F(output_{t-1}, input_t)$ 
    - output dependent on history
    - concept of a time step (clock)
- An algebraic structure consists of
  - a set of elements  $B = \{0, 1\}$
  - binary operations  $\{+, \cdot\}$  (OR, AND)
  - and a unary operation  $\{\prime\}$  (NOT)

## A quick combinational logic example


- Calendar subsystem: number of days in a month (to control watch display)
  - used in controlling the display of a wrist-watch LCD screen
- inputs: month, leap year flag
- outputs: number of days

## Implementation in software

```
integer number_of_days ( month, leap_year_flag) {  
  switch (month) {  
    case 1: return (31);  
    case 2: if (leap_year_flag == 1) then  
      return (29) else return (28);  
    case 3: return (31);  
    ...  
    case 12: return (31);  
    default: return (0);  
  }  
}
```
 
## Implementation as a combinational digital system

- Encoding:
  - how many bits for each input/output?
  - binary number for month
  - four wires for 28, 29, 30, and 31



month	leap	d28	d29	d30	d31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0011	1	0	1	0	0
0100	-	0	0	0	1
0101	-	0	0	1	0
0110	-	0	0	1	0
0111	-	0	0	0	1
1000	-	0	0	0	1
1001	-	0	0	1	0
1010	-	0	0	0	1
1011	-	0	0	1	0
1100	-	0	0	0	1
1101	-	-	-	-	-
1110	-	-	-	-	-
1111	-	-	-	-	-

## Combinational example (cont.)

- Truth-table to logic to switches to gates
  - $d28 = "1 \text{ when month}=0010 \text{ and leap}=0"$
  - $d28 = m8' \cdot m4' \cdot m2 \cdot m1' \cdot \text{leap}'$
  - $d31 = "1 \text{ when month}=0001 \text{ or month}=0011 \text{ or ... month}=1100"$
  - $d31 = (m8' \cdot m4' \cdot m2' \cdot m1) + (m8' \cdot m4' \cdot m2 \cdot m1) + \dots$   
( $m8 \cdot m4 \cdot m2' \cdot m1'$ )
  - $d31 = \text{can we simplify more?}$

month	leap	d28	d29	d30	d31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0011	1	0	1	0	0
0100	-	0	0	0	1
0100	-	0	0	1	0
...					
1100	-	0	0	0	1
1101	-	-	-	-	-
111-	-	-	-	-	-

## Combinational example (cont.)


$$d28 = m8' \cdot m4' \cdot m2 \cdot m1' \cdot \text{leap}'$$

$$d29 = m8' \cdot m4' \cdot m2 \cdot m1' \cdot \text{leap}$$

$$d30 = (m8' \cdot m4 \cdot m2' \cdot m1') + (m8' \cdot m4 \cdot m2 \cdot m1') + (m8 \cdot m4' \cdot m2' \cdot m1) + (m8 \cdot m4' \cdot m2 \cdot m1)$$

$$= (m8' \cdot m4 \cdot m1') + (m8 \cdot m4' \cdot m1)$$
 
$$d31 = (m8' \cdot m4' \cdot m2' \cdot m1) + (m8' \cdot m4' \cdot m2 \cdot m1) + (m8' \cdot m4 \cdot m2' \cdot m1) + (m8' \cdot m4 \cdot m2 \cdot m1) + (m8 \cdot m4' \cdot m2' \cdot m1') + (m8 \cdot m4' \cdot m2 \cdot m1') + (m8 \cdot m4 \cdot m2' \cdot m1')$$




## Combinational logic

- Switches
- Basic logic and truth tables
- Logic functions
- Boolean algebra
- Proofs by re-writing and by perfect induction
 
## Switches: basic element of physical implementations



- Implementing a simple circuit (arrow shows action if wire changes to "1"):



$$Z = A$$
  
## Switches (cont.)

- Compose switches into more complex ones (Boolean functions):



## Transistor networks


- Modern digital systems are designed in CMOS technology
  - MOS stands for Metal-Oxide on Semiconductor
  - C is for complementary because there are both normally-open and normally-closed switches
- MOS transistors act as voltage-controlled switches
  - similar, though easier to work with than relays.

## Multi-input logic gate

- CMOS logic gates are inverting
  - Easy to implement NAND, NOR, NOT while AND, OR, and Buffer are harder




Claude Shannon – 1938

 
 
## Possible logic functions of two variables

- There are 16 possible functions of 2 input variables:
  - in general, there are  $2^{2^n}$  functions of n inputs



## Boolean algebra

- An algebraic structure consists of
  - a set of elements B
  - binary operations { + , • }
  - and a unary operation { ' }
  - such that the following axioms hold:



George Boole – 1854

- the set B contains at least two elements: a, b
  - closure:  $a + b$  is in B
  - commutativity:  $a + b = b + a$
  - associativity:  $a + (b + c) = (a + b) + c$
  - identity:  $a + 0 = a$
  - distributivity:  $a + (b \cdot c) = (a + b) \cdot (a + c)$
  - complementarity:  $a + a' = 1$
- $a \cdot b$  is in B
  - $a \cdot b = b \cdot a$
  - $(a \cdot b) \cdot c = a \cdot (b \cdot c)$
  - $a \cdot 1 = a$
  - $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
  - $a \cdot a' = 0$

## Logic functions and Boolean algebra

Any logic function that can be expressed as a truth table can be written as an expression in Boolean algebra using the operators: ', +, and •

X, Y are Boolean algebra variables

X	Y	X • Y
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	X'	X' • Y'
0	0	1	0
0	1	0	1
1	0	1	0
1	1	0	0

X	Y	X'	Y'	X • Y	X' • Y'	(X • Y) + (X' • Y')
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

$$(X \cdot Y) + (X' \cdot Y') \rightarrow X = Y$$

Boolean expression that is true when the variables X and Y have the same value and false, otherwise

## Axioms and theorems of Boolean algebra

- identity
- $X + 0 = X$
  - $X \cdot 1 = X$
- null
- $X + 1 = 1$
  - $X \cdot 0 = 0$
- idempotency:
- $X + X = X$
  - $X \cdot X = X$
- involution:
- $(X')' = X$
- complementarity:
- $X + X' = 1$
  - $X \cdot X' = 0$
- commutativity:
- $X + Y = Y + X$
  - $X \cdot Y = Y \cdot X$
- associativity:
- $(X + Y) + Z = X + (Y + Z)$
  - $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$
- distributivity:
- $X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$
  - $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$

## Axioms and theorems of Boolean algebra (cont.)

- uniting:
- $X \cdot Y + X \cdot Y' = X$
  - $(X + Y) \cdot (X + Y') = X$
- absorption:
- $X + X \cdot Y = X$
  - $(X + Y') \cdot Y = X \cdot Y$
  - $X \cdot (X + Y) = X$
  - $(X \cdot Y') + Y = X + Y$
- factoring:
- $(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$
  - $X \cdot Y + X' \cdot Z = (X + Z) \cdot (X' + Y)$
- consensus:
- $(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$
  - $(X + Y) \cdot (Y + Z) \cdot (X' + Z) = (X + Y) \cdot (X' + Z)$
- de Morgan's:
- $(X + Y + \dots)' = X' \cdot Y' \cdot \dots$
  - $(X \cdot Y \cdot \dots)' = X' + Y' + \dots$

## Proving theorems (rewriting)

- Using the laws of Boolean algebra:

– e.g., prove the theorem:

$$X \cdot Y + X \cdot Y' = X$$

distributivity (8)  
complementarity (5)  
identity (1D)

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\ &= X \cdot (1) \\ &= X \end{aligned}$$

e.g., prove the theorem:

$$X + X \cdot Y = X$$

identity (1D)  
distributivity (8)  
identity (2)  
identity (1D)

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y \\ &= X \cdot (1 + Y) \\ &= X \cdot (1) \\ &= X \end{aligned}$$

## Proving theorems (perfect induction)

- Using perfect induction (complete truth table):

– e.g., de Morgan's:

$$(X + Y)' = X' \cdot Y'$$

NOR is equivalent to AND with inputs complemented

X	Y	X'	Y'	(X + Y)'	X' · Y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0


$$(X \cdot Y)' = X' + Y'$$

NAND is equivalent to OR with inputs complemented

X	Y	X'	Y'	(X · Y)'	X' + Y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0
 
## A simple example: 1-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out



A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$\begin{aligned} S &= A' B' Cin + A' B Cin' + A B' Cin' + A B Cin \\ Cout &= A' B Cin + A B' Cin + A B Cin' + A B Cin \end{aligned}$$

## Apply the theorems to simplify expressions


- The theorems of Boolean algebra can simplify expressions
- e.g., full adder's carry-out function

$$\begin{aligned} Cout &= A' B Cin + A B' Cin + A B Cin' + A B Cin \\ &= A' B Cin + A B' Cin + A B Cin' + A B Cin + A B Cin \\ &= A' B Cin + A B Cin + A B' Cin + A B Cin' + A B Cin \\ &= (A' + A) B Cin + A B' Cin + A B Cin' + A B Cin \\ &= (1) B Cin + A B' Cin + A B Cin' + A B Cin \\ &= B Cin + A B' Cin + A B Cin' + A B Cin + A B Cin \\ &= B Cin + A B' Cin + A B Cin + A B Cin' + A B Cin \\ &= B Cin + A (B' + B) Cin + A B Cin' + A B Cin \\ &= B Cin + A (1) Cin + A B Cin' + A B Cin \\ &= B Cin + A Cin + A B (Cin' + Cin) \\ &= B Cin + A Cin + A B (1) \\ &= B Cin + A Cin + A B \end{aligned}$$

adding extra terms creates new factoring opportunities
 
## A simple example: 1-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out



A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




$$\begin{aligned} Cout &= B Cin + A Cin + A B \\ S &= A' B' Cin + A' B Cin' + A B' Cin' + A B Cin \\ &= A' (B' Cin + B Cin') + A (B' Cin' + B Cin) \\ &= A' Z + A Z' \\ &= A \text{ xor } Z = A \text{ xor } (B \text{ xor } Cin) \end{aligned}$$

## From Boolean expressions to logic gates

- NOT  $X' \quad \bar{X} \quad \sim X \quad X/ \quad x \rightarrow y$


X	Y
0	1
1	0

 - AND  $X \cdot Y \quad XY \quad X \wedge Y$



X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

- OR  $X + Y \quad X \vee Y$

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

## From Boolean expressions to logic gates (cont'd)

- NAND**

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0
- NOR**

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0
- XOR**  
 $X \oplus Y$ 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$X \text{ xor } Y = X'Y + X'Y'$   
 X or Y but not both  
 ("inequality", "difference")
- XNOR**  
 $X \oplus Y$ 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1


$X \text{ xnor } Y = XY + X'Y'$   
 X and Y are the same  
 ("equality", "coincidence")

Autumn 2012 CSE:311 25
 
## Full adder: Carry-out

Before Boolean minimization  
 $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$


After Boolean minimization  
 $C_{out} = BC_{in} + AC_{in} + AB$



 
## Full adder: Sum

Before Boolean minimization  
 $Sum = A'B'C_{in} + A'B'C_{in}' + AB'C_{in}' + ABC_{in}$

After Boolean minimization  
 $Sum = (A \oplus B) \oplus C_{in}$



## Preview: A 2-bit ripple-carry adder

 

## Mapping truth tables to logic gates

- Given a truth table:
  - Write the Boolean expression
  - Minimize the Boolean expression
  - Draw as gates
  - Map to available gates

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

②  $F = A'BC' + A'BC + AB'C + ABC$   
 $= A'B(C'+C) + AC(B'+B)$   
 $= A'B + AC$

