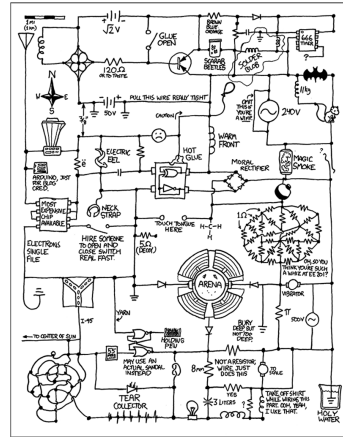


CSE 311: Foundations of Computing

Fall 2013

Lecture 4: Boolean algebra and circuits



announcements

Reading assignment

– Boolean Algebra

12.1 – 12.3 7th Edition

11.1 – 11.3 6th Edition

Homework 1 due today

– Hand in at start of class

Homework 2 available online later today

review: a quick combinational logic example

Calendar subsystem:

of days in a month (to control watch display)

– used in controlling the display of a wrist-watch LCD screen

– **inputs:** month, leap year flag

– **outputs:** number of days

Example: (March, non-leap year) → **31**


review: implementation in software

```
integer number_of_days (month, leap_year_flag){
    switch (month) {
        case 1: return (31);
        case 2: if (leap_year_flag == 1) then
                return (29) else return (28);
        case 3: return (31);
        ...
        case 12: return (31);
        default: return (0);
    }
}
```

review: implementation with combinatorial logic

Encoding:

 - how many bits for each input/output?
- binary number for month
- four wires for 28, 29, 30, and 31



month	leap	d28	d29	d30	d31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0011	1	0	1	0	0
0011	-	0	0	0	1
0100	-	0	0	1	0
0101	-	0	0	0	1
0110	-	0	0	1	0
0111	-	0	0	0	1
1000	-	0	0	0	1
1001	-	0	0	1	0
1010	-	0	0	0	1
1011	-	0	0	1	0
1100	-	0	0	0	1
1101	-	-	-	-	-
1110	-	-	-	-	-
1111	-	-	-	-	-

review: implementation with combinatorial logic

Truth-table to logic to switches to gates

d28 = "1 when month=0010 and leap=0"

$$d28 = m8' \cdot m4' \cdot m2 \cdot m1' \cdot \text{leap}'$$

d31 = "1 when month=0001 or month=0011 or ... month=1100"

$$d31 = (m8' \cdot m4' \cdot m2' \cdot m1) + (m8' \cdot m4' \cdot m2 \cdot m1) + \dots + (m8 \cdot m4 \cdot m2' \cdot m1')$$

d31 = can we simplify more?

month	leap	d28	d29	d30	d31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0011	1	0	1	0	0
0011	-	0	0	0	1
0100	-	0	0	1	0
...					
1100	-	0	0	0	1
1101	-	-	-	-	-
111-	-	-	-	-	-


review: implementation with combinatorial logic

$$d28 = m8' \cdot m4' \cdot m2 \cdot m1' \cdot \text{leap}'$$

$$d29 = m8' \cdot m4' \cdot m2 \cdot m1' \cdot \text{leap}$$

$$d30 = (m8' \cdot m4 \cdot m2' \cdot m1') + (m8' \cdot m4 \cdot m2 \cdot m1') + (m8 \cdot m4' \cdot m2' \cdot m1) + (m8 \cdot m4' \cdot m2 \cdot m1) = (m8' \cdot m4 \cdot m1') + (m8 \cdot m4' \cdot m1)$$
 
$$d31 = (m8' \cdot m4' \cdot m2' \cdot m1) + (m8' \cdot m4' \cdot m2 \cdot m1) + (m8' \cdot m4 \cdot m2' \cdot m1) + (m8' \cdot m4 \cdot m2 \cdot m1) + (m8 \cdot m4' \cdot m2' \cdot m1') + (m8 \cdot m4' \cdot m2 \cdot m1') + (m8 \cdot m4 \cdot m2' \cdot m1')$$




boolean algebra

• Boolean algebra to circuit design

• Boolean algebra

 - a set of elements B containing {0, 1}
- binary operations { + , • }
- and a unary operation { ' }
- such that the following axioms hold:



- | | | |
|---|---------------------------------|---------------------------------|
| 1. the set B contains at least two elements: a, b | | |
| 2. closure: | a + b is in B | a • b is in B |
| 3. commutativity: | a + b = b + a | a • b = b • a |
| 4. associativity: | a + (b + c) = (a + b) + c | a • (b • c) = (a • b) • c |
| 5. identity: | a + 0 = a | a • 1 = a |
| 6. distributivity: | a + (b • c) = (a + b) • (a + c) | a • (b + c) = (a • b) + (a • c) |
| 7. complementarity: | a + a' = 1 | a • a' = 0 |

axioms and theorems of Boolean algebra

identity:

$$1. X + 0 = X$$

$$1D. X \cdot 1 = X$$

null:

$$2. X + 1 = 1$$

$$2D. X \cdot 0 = 0$$

idempotency:

$$3. X + X = X$$

$$3D. X \cdot X = X$$

involution:

$$4. (X')' = X$$

complementarity:

$$5. X + X' = 1$$

$$5D. X \cdot X' = 0$$

commutativity:

$$6. X + Y = Y + X$$

$$6D. X \cdot Y = Y \cdot X$$

associativity:

$$7. (X + Y) + Z = X + (Y + Z)$$

$$7D. (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$$

distributivity:

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

axioms and theorems of Boolean algebra

uniting:

$$9. X \cdot Y + X \cdot Y' = X$$

$$9D. (X + Y) \cdot (X + Y') = X$$

absorption:

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + Y') \cdot Y = X \cdot Y$$

$$11D. (X \cdot Y') + Y = X + Y$$

factoring:

$$12. (X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$$

$$12D. X \cdot Y + X' \cdot Z = (X + Z) \cdot (X' + Y)$$

consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (X' + Z) = (X + Y) \cdot (X' + Z)$$

de Morgan's:

$$14. (X + Y + \dots)' = X' \cdot Y' \cdot \dots$$

$$14D. (X \cdot Y \cdot \dots)' = X' + Y' + \dots$$

proving theorems (rewriting)

Using the laws of Boolean algebra:

prove the theorem:

$$X \cdot Y + X \cdot Y' = X$$

distributivity (8)

$$X \cdot Y + X \cdot Y' = X \cdot (Y + Y')$$

complementarity (5)

$$= X \cdot (1)$$

identity (1D)

$$= X$$

prove the theorem:

$$X + X \cdot Y = X$$

identity (1D)

$$X + X \cdot Y = X \cdot 1 + X \cdot Y$$

distributivity (8)

$$= X \cdot (1 + Y)$$

uniting (2)

$$= X \cdot (1)$$

identity (1D)

$$= X$$

proving theorems (truth table)

Using complete truth table:

For example, de Morgan's Law:


	X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
$(X + Y)' = X' \cdot Y'$	0	0	1	1		
NOR is equivalent to AND	0	1	1	0		
with inputs complemented	1	0	0	1		
	1	1	0	0		

	X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
$(X \cdot Y)' = X' + Y'$	0	0	1	1		
NAND is equivalent to OR	0	1	1	0		
with inputs complemented	1	0	0	1		
	1	1	0	0		

a simple example: 1-bit binary adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$S = A' B' Cin + A' B Cin' + A B' Cin' + A B Cin$$

$$Cout = A' B Cin + A B' Cin + A B Cin' + A B Cin$$

a simple example: 1-bit binary adder

 - **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



$$Cout = A' B Cin + A B' Cin + A B Cin' + A B Cin$$

apply theorems to simplify expressions

The theorems of Boolean algebra can simplify expressions

– e.g., full adder's carry-out function

$$\begin{aligned}
 Cout &= A' B Cin + A B' Cin + A B Cin' + A B Cin \\
 &= A' B Cin + A B' Cin + A B Cin' + \boxed{A B Cin + A B Cin} \\
 &= A' B Cin + A B Cin + A B' Cin + A B Cin' + A B Cin \\
 &= (A' + A) B Cin + A B' Cin + A B Cin' + A B Cin \\
 &= (1) B Cin + A B' Cin + A B Cin' + A B Cin \\
 &= B Cin + A B' Cin + A B Cin' + \boxed{A B Cin + A B Cin} \\
 &= B Cin + A B' Cin + A B Cin + A B Cin' + A B Cin \\
 &= B Cin + A (B' + B) Cin + A B Cin' + A B Cin \\
 &= B Cin + A (1) Cin + A B Cin' + A B Cin \\
 &= B Cin + A Cin + A B (Cin' + Cin) \\
 &= B Cin + A Cin + A B (1) \\
 &= B Cin + A Cin + A B
 \end{aligned}$$

adding extra terms
creates new factoring
opportunities


rewrite using xor gates

$$S = A' B' Cin + A' B Cin' + A B' Cin' + A B Cin$$

a simple example: 1-bit binary adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$\begin{aligned} \text{Cout} &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ \text{S} &= A' B' \text{Cin} + A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin} \end{aligned}$$


$$\begin{aligned} \text{Cout} &= B \text{Cin} + A \text{Cin} + A B \\ \text{S} &= A \text{ xor } (B \text{ xor } \text{Cin}) \end{aligned}$$

recall gates


NOT
 $X' \quad \bar{X} \quad \neg X$

 

 AND
 $X \cdot Y \quad XY \quad X \wedge Y$




OR
 $X + Y \quad X \vee Y$

 


some other gates


NAND
 $\neg(X \wedge Y)$

 


NOR
 $\neg(X \vee Y)$

 


XOR
 $X \oplus Y$

 

XNOR
 $X \leftrightarrow Y, X = Y$

 

a 2-bit ripple-carry adder

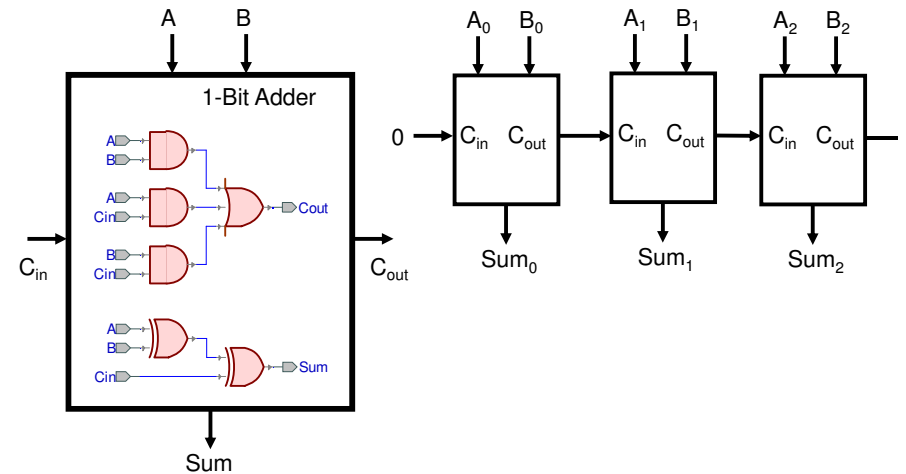

mapping truth tables to logic gates

Given a truth table:

1. Write the Boolean expression
2. Minimize the Boolean expression
3. Draw as gates
4. Map to available gates


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

②

$$F = A'BC' + A'BC + AB'C + ABC$$

$$= A'B(C' + C) + AC(B' + B)$$

$$= A'B + AC$$

 

canonical forms

- Truth table is the unique signature of a Boolean function
- The same truth table can have many gate realizations
 - we've seen this already
 - depends on how good we are at Boolean simplification
- Canonical forms
 - standard forms for a Boolean expression
 - we all come up with the same expression

sum-of-products canonical form

- also known as **Disjunctive Normal Form (DNF)**
- also known as **minterm expansion**

$$F = 001 \quad 011 \quad 101 \quad 110 \quad 111$$

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

sum-of-products canonical form

Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	A'B'C' m0
0	0	1	A'B'C m1
0	1	0	A'BC' m2
0	1	1	A'BC m3
1	0	0	AB'C' m4
1	0	1	AB'C m5
1	1	0	ABC' m6
1	1	1	ABC m7

F in canonical form:

$$F(A, B, C) = \Sigma m(1,3,5,6,7)$$

$$= m1 + m3 + m5 + m6 + m7$$

$$= A'B'C + A'BC + AB'C + ABC' + ABC$$

canonical form \neq minimal form

$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC + ABC'$$

$$= (A'B' + A'B + AB' + AB)C + ABC'$$

$$= ((A' + A)(B' + B))C + ABC'$$

$$= C + ABC'$$

$$= ABC' + C$$

$$= AB + C$$

short-hand notation for minterms of 3 variables

product-of-sums canonical form

- Also known as **Conjunctive Normal Form (CNF)**
- Also known as **maxterm expansion**

					$F =$	000	010	100		
					$F =$	$(A + B + C)$	$(A + B' + C)$	$(A' + B + C)$		

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

product-of-sums canonical form

Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms
0	0	0	A+B+C M0
0	0	1	A+B+C' M1
0	1	0	A+B'+C M2
0	1	1	A+B'+C' M3
1	0	0	A'+B+C M4
1	0	1	A'+B+C' M5
1	1	0	A'+B'+C M6
1	1	1	A'+B'+C' M7

F in canonical form:

$$\begin{aligned}
 F(A, B, C) &= \Pi M(0,2,4) \\
 &= M0 \cdot M2 \cdot M4 \\
 &= (A + B + C) (A + B' + C) (A' + B + C)
 \end{aligned}$$

canonical form \neq minimal form

$$\begin{aligned}
 F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\
 &= (A + B + C) (A + B' + C) \\
 &\quad (A + B + C) (A' + B + C) \\
 &= (A + C) (B + C)
 \end{aligned}$$

short-hand notation for maxterms of 3 variables