## QuickCheck: Gates and Equivalence Solutions (due Thursday, October 2)

## 0. If you turn the paper horizontally, the circuits look like robots (:

(a) Convert each of the following circuits to logical expressions.



Solution:

(i) 
$$((\neg p) \land (p \lor q)) \land \neg \neg q$$

(ii) 
$$\neg p \land (q \land q)$$

(b) Prove that (i) and (ii) are equivalent using a truth table.

Solution:

р	q	$(\neg p \land (p \lor q))$	$(\neg p \land (p \lor q)) \land \neg \neg q$	$ eg p \land (q \land q)$
Т	Т	F	F	F
т	F	F	F	F
F	т	Т	Т	Т
F	F	F	F	F

(c) Prove that (i) and (ii) are equivalent using propositional equivalences. See the back page for a full list of them.

Solution:

$$\begin{array}{ll} (\neg p \land (p \lor q)) \land \neg \neg q \equiv (\neg p \land (p \lor q)) \land q & [\text{Proven in lecture}] \\ \equiv \neg p \land ((p \lor q) \land q) & [\text{Associative}] \\ \equiv \neg p \land (q \land (q \lor p)) & [\text{Commutative twice}] \\ \equiv \neg p \land q & [\text{Absorbtion}] \\ \equiv \neg p \land (q \land q) & [\text{Idempotent}] \end{array}$$

(d) Write (i) and (ii) as expressions in boolean algebra.

Solution:

(i) 
$$(p' \bullet (p + q)) \bullet q'$$

(ii) 
$$p' \bullet (q \bullet q)$$