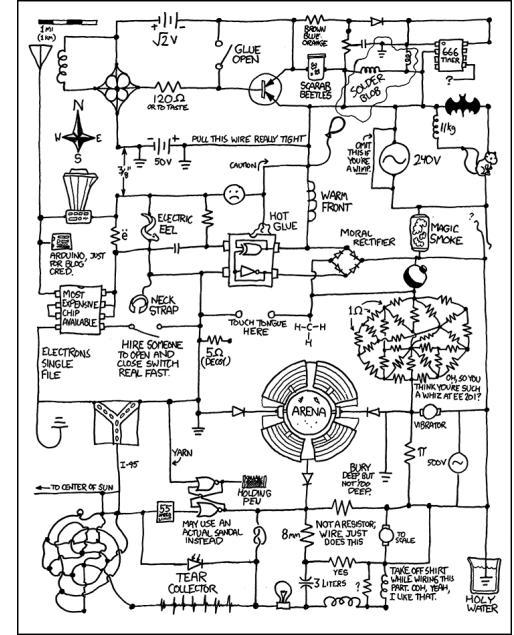


CSE 311



Foundations of Computing I

Fall 2014

Remember, the site is...

<http://tinyurl.com/ynlecture>

Get started on the blue handout!

Recall...in boolean logic,

$A \bullet B$ is A and B

$A + B$ is A or B

A' is not A

Administrivia

Homework 1 Due Today

– Hand in at start of class

Homework 2 Available Online Later Today

A Combinational Logic Example

Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**
Input: (Monday, Section) Output: **1**


Implementation in Software

```
public int classesLeftInMorning(weekday, lecture_flag) {  
    switch (day) {  
        case SUNDAY:  
        case MONDAY:  
            return lecture_flag ? 3 : 1;  
        case TUESDAY:  
        case WEDNESDAY:  
            return lecture_flag ? 2 : 1;  
        case THURSDAY:  
            return lecture_flag ? 1 : 1;  
        case FRIDAY:  
            return lecture_flag ? 1 : 0;  
        case SATURDAY:  
            return lecture_flag ? 0 : 0;  
    }  
}
```

Implementation with Combinational Logic

Encoding:

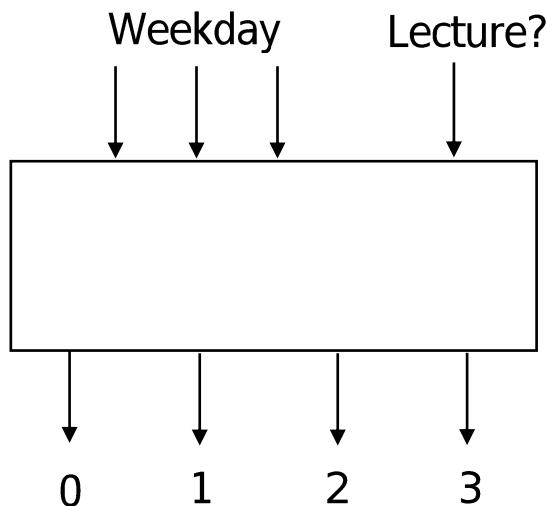- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



Defining Our Inputs!

```
public int classesLeftInMorning(weekday, lecture_flag) {  
    switch (day) {  
        case SUNDAY:  
        case MONDAY:  
            return lecture_flag ? 3 : 1;  
        case TUESDAY:  
        case WEDNESDAY:  
            return lecture_flag ? 2 : 1;  
        case THURSDAY:  
            return lecture_flag ? 1 : 1;  
        case FRIDAY:  
            return lecture_flag ? 1 : 0;  
        case SATURDAY:  
            return lecture_flag ? 0 : 0;  
    }  
}
```

Weekday	Number	Binary
Sunday	0	(000) ₂
Monday	1	(001) ₂
Tuesday	2	(010) ₂
Wednesday	3	(011) ₂
Thursday	4	(100) ₂
Friday	5	(101) ₂
Saturday	6	(110) ₂

Converting to a Truth Table!

Weekday	Number	Binary	Weekday	Lecture?	c0	c1	c2	c3
Sunday	0	(000) ₂	000	0	0	1	0	0
Monday	1	(001) ₂	000	1	0	0	0	1
Tuesday	2	(010) ₂	001	0	0	1	0	0
Wednesday	3	(011) ₂	001	1	0	0	0	1
Thursday	4	(100) ₂	010	0	0	1	0	0
Friday	5	(101) ₂	010	1	0	0	1	0
Saturday	6	(110) ₂	011	0	0	1	0	0
			011	1	0	0	1	0
			100	-	0	1	0	0
			101	0	1	0	0	0
			101	1	0	1	0	0
			110	-	1	0	0	0
			111	-	-	-	-	-

Truth Table to Logic (Part 1)

$c3 = (\text{DAY} == \text{SUN} \text{ and } \text{LEC}) \text{ or } (\text{DAY} == \text{MON} \text{ and } \text{LEC})$

$c3 = (d2 == 0 \text{ && } d1 == 0 \text{ && } d0 == 0 \text{ && } L == 1) \text{ || }$
 $(d2 == 0 \text{ && } d1 == 0 \text{ && } d0 == 1 \text{ && } L == 1)$

$c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L$

DAY	d2	d1	d0	L	c0	c1	c2	c3
SunS	000		0		0	1	0	0
SunL	000		1		0	0	0	1
MonS	001		0		0	1	0	0
MonL	001		1		0	0	0	1
TueS	010		0		0	1	0	0
TueL	010		1		0	0	1	0
WedS	011		0		0	1	0	0
WedL	011		1		0	0	1	0
Thu	100		-		0	1	0	0
FriS	101		0		1	0	0	0
FriL	101		1		0	1	0	0
Sat	110		-		1	0	0	0
-	111		-		-	-	-	-

Truth Table to Logic (Part 2)

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = (\text{DAY} == \text{TUE} \text{ and } \text{LEC}) \text{ or } (\text{DAY} == \text{WED} \text{ and } \text{LEC})$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

DAY	d2	d1	d0	L	c0	c1	c2	c3
SunS	000		0		0	1	0	0
SunL	000		1		0	0	0	1
MonS	001		0		0	1	0	0
MonL	001		1		0	0	0	1
TueS	010		0		0	1	0	0
TueL	010		1		0	0	1	0
WedS	011		0		0	1	0	0
WedL	011		1		0	0	1	0
Thu	100		-		0	1	0	0
FriS	101		0		1	0	0	0
FriL	101		1		0	1	0	0
Sat	110		-		1	0	0	0
-	111		-		-	-	-	-

Truth Table to Logic (Part 3)

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$
$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$


c1 = On your homework for next week!

$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0'$$

DAY	d2	d1	d0	L	c0	c1	c2	c3
SunS	000		0		0	1	0	0
SunL	000		1		0	0	0	1
MonS	001		0		0	1	0	0
MonL	001		1		0	0	0	1
TueS	010		0		0	1	0	0
TueL	010		1		0	0	1	0
Weds	011		0		0	1	0	0
WedL	011		1		0	0	1	0
Thu	100			-	0	1	0	0
FriS	101		0		1	0	0	0
FriL	101		1		0	1	0	0
Sat	110			-	1	0	0	0
-	111			-	-	-	-	-

Logic to Gates
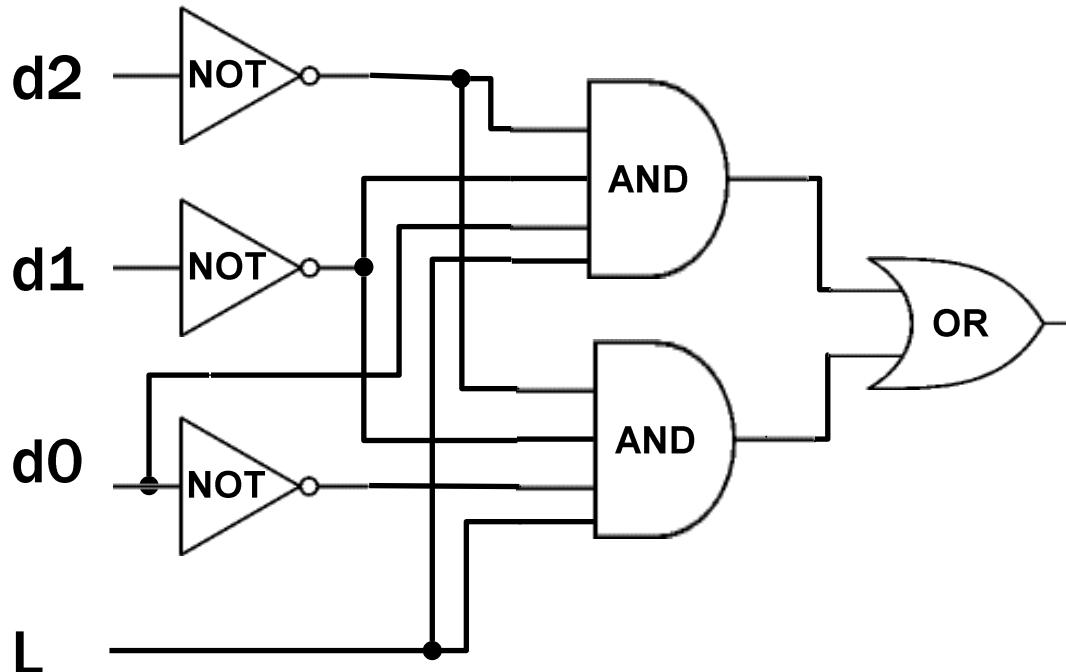
$$c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L$$




Multi-input AND gates

DAY	d2	d1	d0	L	c0	c1	c2	c3
SunS	000		0		0	1	0	0
SunL	000		1		0	0	0	1
MonS	001		0		0	1	0	0
MonL	001		1		0	0	0	1
TueS	010		0		0	1	0	0
TueL	010		1		0	0	1	0
Weds	011		0		0	1	0	0
WedL	011		1		0	0	1	0
Thu	100		-		0	1	0	0
FriS	101		0		1	0	0	0
FriL	101		1		0	1	0	0
Sat	110		-		1	0	0	0
-	111		-		-	-	-	-

CSE 311: Foundations of Computing


Fall 2014

Lecture 4: Boolean Algebra and Circuits

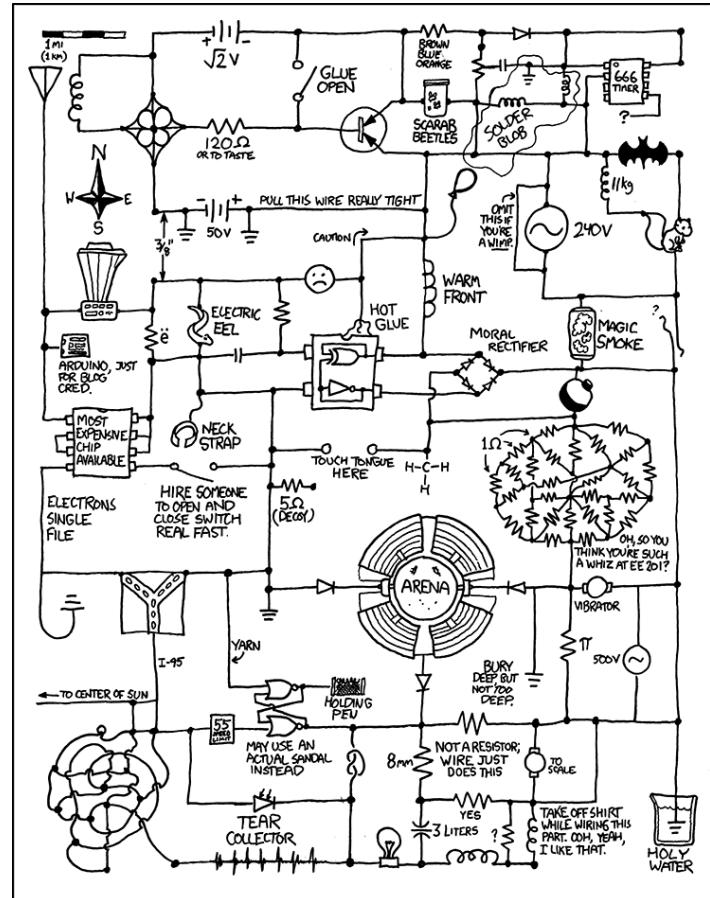

Boolean Algebra

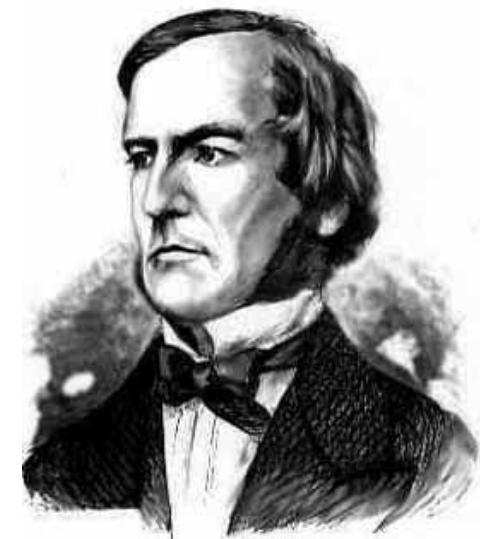- Boolean algebra to circuit design
- Boolean algebra
 - a set of elements B containing {0, 1}
 - binary operations { + , • }
 - and a unary operation { ' }
 - such that the following axioms hold:



1. the set B contains at least two elements: 0, 1

For any a, b, c in B :

2. closure:	$a + b$ is in B	$a \cdot b$ is in B
3. commutativity:	$a + b = b + a$	$a \cdot b = b \cdot a$
4. associativity:	$a + (b + c) = (a + b) + c$	$a \cdot (b \cdot c) = (a \cdot b) \cdot c$
5. identity:	$a + 0 = a$	$a \cdot 1 = a$
6. distributivity:	$a + (b \cdot c) = (a + b) \cdot (a + c)$	$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
7. complementarity:	$a + a' = 1$	$a \cdot a' = 0$

Axioms and Theorems of Boolean Algebra

identity:

$$1. \quad X + 0 = X$$

$$1D. \quad X \cdot 1 = X$$

null:

$$2. \quad X + 1 = 1$$

$$2D. \quad X \cdot 0 = 0$$

idempotency:

$$3. \quad X + X = X$$

$$3D. \quad X \cdot X = X$$

involution:

$$4. \quad (X')' = X$$

complementarity:

$$5. \quad X + X' = 1$$

$$5D. \quad X \cdot X' = 0$$

commutativity:

$$6. \quad X + Y = Y + X$$

$$6D. \quad X \cdot Y = Y \cdot X$$

associativity:

$$7. \quad (X + Y) + Z = X + (Y + Z)$$

$$7D. \quad (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$$

distributivity:

$$8. \quad X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$8D. \quad X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

Axioms and Theorems of Boolean Algebra

uniting:

$$9. X \cdot Y + X \cdot Y' = X$$

$$9D. (X + Y) \cdot (X + Y') = X$$

absorption:

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + Y') \cdot Y = X \cdot Y$$

$$11D. (X \cdot Y') + Y = X + Y$$

factoring:

$$12. (X + Y) \cdot (X' + Z) = \\ X \cdot Z + X' \cdot Y$$

$$12D. X \cdot Y + X' \cdot Z = \\ (X + Z) \cdot (X' + Y)$$

consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = \\ X \cdot Y + X' \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (X' + Z) = \\ (X + Y) \cdot (X' + Z)$$

de Morgan's:

$$14. (X + Y + \dots)' = X' \cdot Y' \cdot \dots$$

$$14D. (X \cdot Y \cdot \dots)' = X' + Y' + \dots$$

Proving Theorems (Rewriting)

Using the laws of Boolean Algebra:

prove the theorem:

$$X \bullet Y + X \bullet Y' = X$$

distributivity (8)

$$X \bullet Y + X \bullet Y' = X \bullet (Y + Y')$$

complementarity (5)

$$= X \bullet (1)$$

identity (1D)

$$= X$$

prove the theorem:

$$X + X \bullet Y = X$$

identity (1D)

$$X + X \bullet Y = X \bullet 1 + X \bullet Y$$

distributivity (8)

$$= X \bullet (1 + Y)$$

uniting (2)

$$= X \bullet (1)$$

identity (1D)

$$= X$$

Proving Theorems (Truth Table)

Using complete truth table:

For example, de Morgan's Law:

$$(X + Y)' = X' \cdot Y'$$

NOR is equivalent to AND
with inputs complemented

X	Y	X'	Y'	(X + Y)'	X' · Y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0


$$(X \cdot Y)' = X' + Y'$$

NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	(X · Y)'	X' + Y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

Simplifying using Boolean algebra

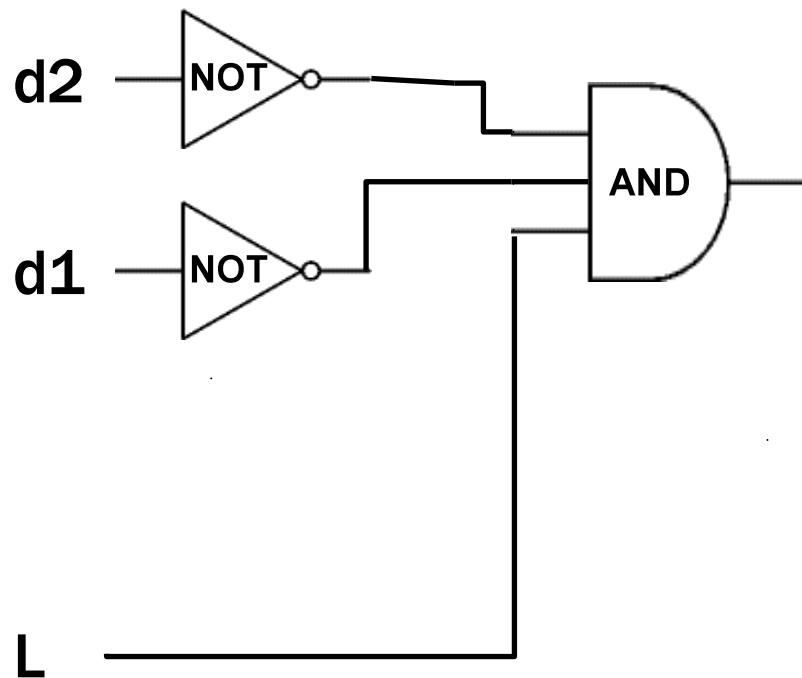
$$\begin{aligned}c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\&= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\&= d2' \cdot d1' \cdot (1) \cdot L \\&= d2' \cdot d1' \cdot L\end{aligned}$$



1-bit Binary Adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

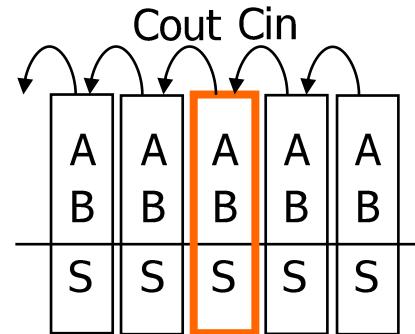

$$S = A' B' \text{Cin} + A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin}$$

$$\text{Cout} = A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin}$$

Apply Theorems to Simplify Expressions

The theorems of Boolean algebra can simplify expressions

- e.g., full adder's carry-out function


$$\begin{aligned}\text{Cout} &= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + \boxed{A B \text{ Cin} + A B \text{ Cin}} \\&= A' B \text{ Cin} + A B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= (A' + A) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= (1) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + \boxed{A B \text{ Cin} + A B \text{ Cin}} \\&= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= B \text{ Cin} + A (B' + B) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= B \text{ Cin} + A (1) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= B \text{ Cin} + A \text{ Cin} + A B (\text{Cin}' + \text{Cin}) \\&= B \text{ Cin} + A \text{ Cin} + A B (1) \\&= B \text{ Cin} + A \text{ Cin} + A B\end{aligned}$$

adding extra terms
creates new factoring
opportunities

Gates Again!

NOT


$$X' \quad \bar{X} \quad \neg X$$

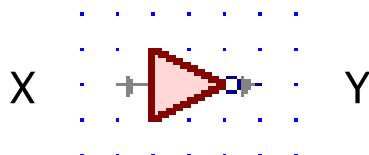

X	Y
0	1
1	0

AND


$$X \cdot Y \quad XY \quad X \wedge Y$$

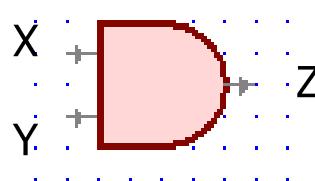

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

OR

$$X + Y \quad X \vee Y$$

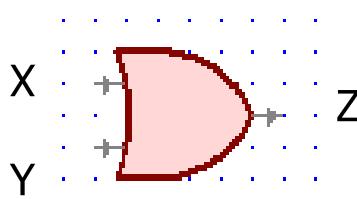


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

More Gates!

NAND


$$\neg(X \wedge Y) \quad (XY)'$$

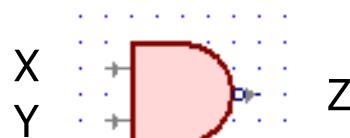

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

NOR


$$\neg(X \vee Y) \quad (X + Y)'$$

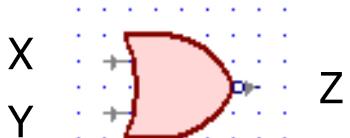

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

XOR


$$X \oplus Y$$

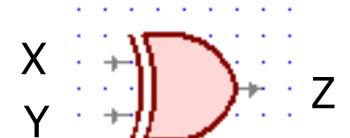

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0


XNOR

$$X \leftrightarrow Y$$

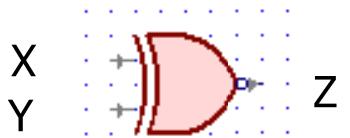

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

A 2-bit Ripple-Carry Adder

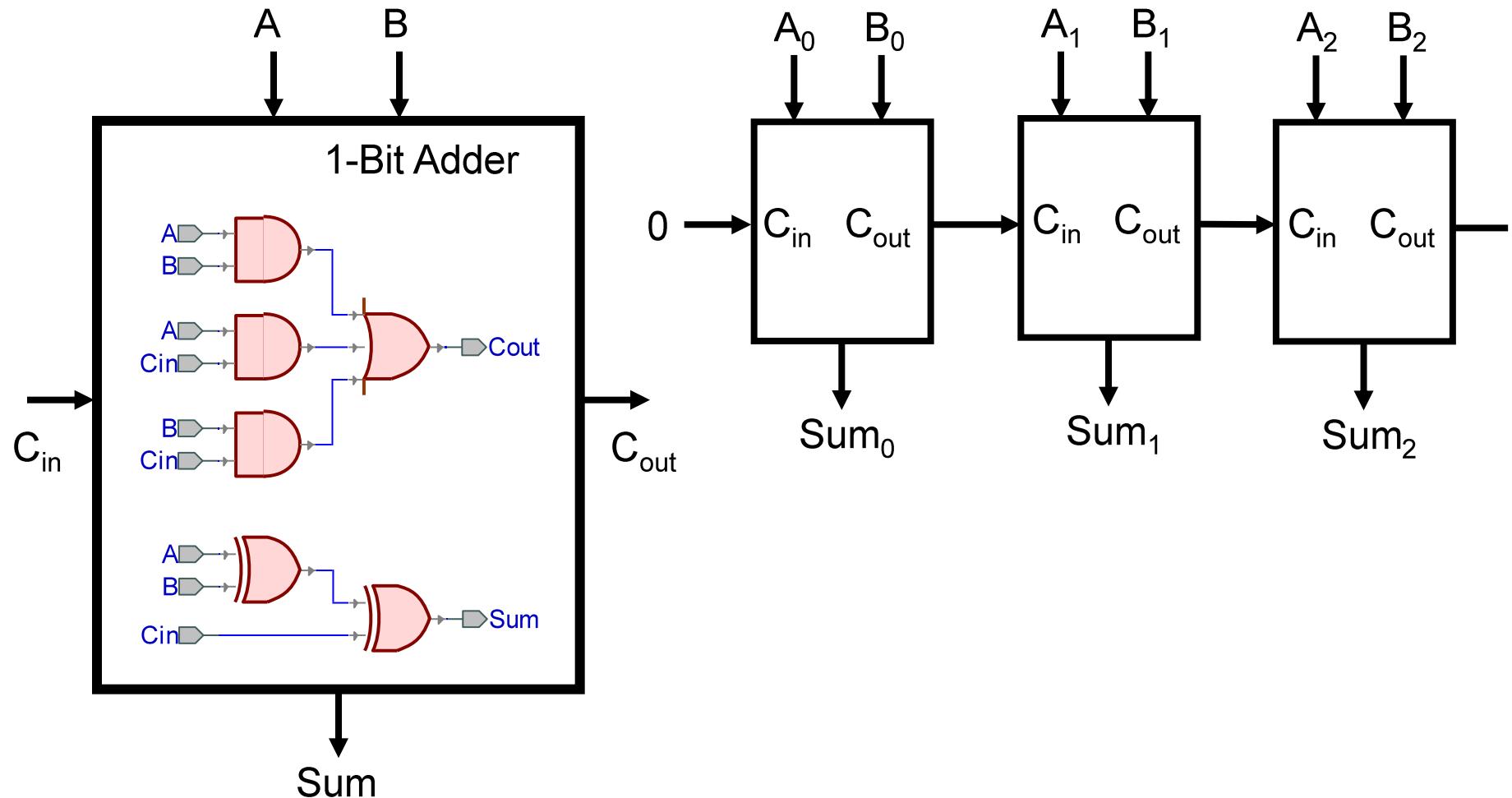

Mapping Truth Tables to Logic Gates

Given a truth table:


1. Write the Boolean expression
2. Minimize the Boolean expression
3. Draw as gates
4. Map to available gates

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


(2)
$$\begin{aligned} F &= A'BC' + A'BC + AB'C + ABC \\ &= A'B(C' + C) + AC(B' + B) \\ &= A'B + AC \end{aligned}$$

(1)

(3)

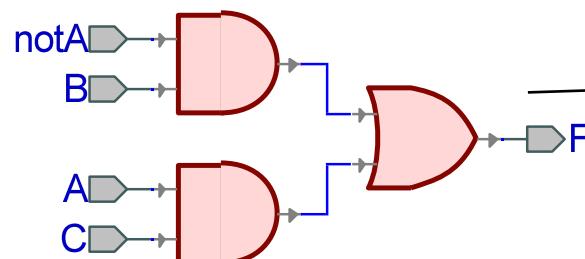

(4)

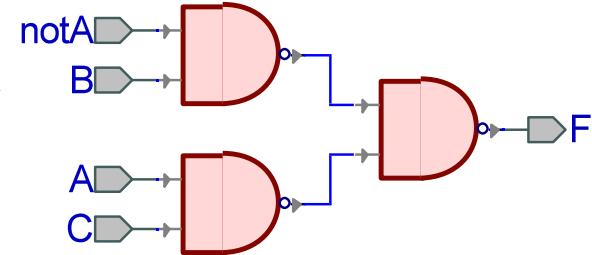

Canonical Forms

- Truth table is the unique signature of a Boolean function
- The same truth table can have many gate realizations
 - we've seen this already
 - depends on how good we are at Boolean simplification
- Canonical forms
 - standard forms for a Boolean expression
 - we all come up with the same expression

Sum-of-Products Canonical Form

- also known as **Disjunctive Normal Form (DNF)**
- also known as **minterm expansion**

			F =	001	011	101	110	111
A	B	C	F	0	1	0	1	0
0	0	0	0	1	0	1	0	1
0	0	1	1	0	1	0	1	0
0	1	0	0	1	0	1	0	1
0	1	1	1	0	1	0	1	0
1	0	0	0	1	0	1	0	1
1	0	1	1	0	1	0	1	0
1	1	0	1	0	1	0	1	0
1	1	1	1	0	1	0	1	0

$F = A'B'C + A'BC + AB'C + ABC' + ABC$

The diagram illustrates the mapping from minterms to terms in the Disjunctive Normal Form (DNF) expression. Five arrows originate from the rows of the truth table where F=1 and point to the corresponding terms in the expression F = A'B'C + A'BC + AB'C + ABC' + ABC. The first arrow points to the term A'B'C (m0), the second to A'BC (m1), the third to AB'C (m2), the fourth to ABC' (m3), and the fifth to ABC (m4).

Sum-of-Products Canonical Form

Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	$A'B'C'$
0	0	1	$A'B'C$
0	1	0	$A'BC'$
0	1	1	$A'BC$
1	0	0	$AB'C'$
1	0	1	$AB'C$
1	1	0	ABC'
1	1	1	ABC

F in canonical form:

$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C \end{aligned}$$

Product-of-Sums Canonical Form

- Also known as **Conjunctive Normal Form (CNF)**
- Also known as **maxterm expansion**

			F	F'
A	B	C		
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F = \overbrace{\quad}^{000} \quad \overbrace{\quad}^{010} \quad \overbrace{\quad}^{100}$

$F = (A + B + C) \quad (A + B' + C) \quad (A' + B + C)$

The diagram shows three arrows originating from the maxterms in the Karnaugh map and pointing to the corresponding terms in the product-of-sums expression. The first arrow points from the top row (000) to the term $(A + B + C)$. The second arrow points from the middle row (010) to the term $(A + B' + C)$. The third arrow points from the bottom row (100) to the term $(A' + B + C)$.

s-o-p, p-o-s, and de Morgan's theorem

Complement of function in sum-of-products form:

$$- F' = A'B'C' + A'BC' + AB'C'$$

Complement again and apply de Morgan's and get the product-of-sums form:

$$- (F')' = (A'B'C' + A'BC' + AB'C)'$$

$$- F = (A + B + C) (A + B' + C) (A' + B + C)$$

Product-of-Sums Canonical Form

Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms
0	0	0	$A+B+C$
0	0	1	$A+B+C'$
0	1	0	$A+B'+C$
0	1	1	$A+B'+C'$
1	0	0	$A'+B+C$
1	0	1	$A'+B+C'$
1	1	0	$A'+B'+C$
1	1	1	$A'+B'+C'$

F in canonical form:

$$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$