 


CSE 311



Foundations of Computing I

Fall 2014

Administrivia

Homework 1 Due Today

- Hand in at start of class

Homework 2 Available Online Later Today

A Combinational Logic Example

Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**

Input: (Monday, Section) Output: **1**


Implementation in Software

```
public int classesLeftInMorning(weekday, lecture_flag) {
    switch (day) {
        case SUNDAY:
        case MONDAY:
            return lecture_flag ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return lecture_flag ? 2 : 1;
        case THURSDAY:
            return lecture_flag ? 1 : 1;
        case FRIDAY:
            return lecture_flag ? 1 : 0;
        case SATURDAY:
            return lecture_flag ? 0 : 0;
    }
}
```

Implementation with Combinational Logic

Encoding:

 - How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



Defining Our Inputs!

```
public int classesLeftInMorning(weekday, lecture_flag) {
    switch (day) {
        case SUNDAY:
        case MONDAY:
            return lecture_flag ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return lecture_flag ? 2 : 1;
        case THURSDAY:
            return lecture_flag ? 1 : 1;
        case FRIDAY:
            return lecture_flag ? 1 : 0;
        case SATURDAY:
            return lecture_flag ? 0 : 0;
    }
}
```

Weekday	Number	Binary
Sunday	0	(000) ₂
Monday	1	(001) ₂
Tuesday	2	(010) ₂
Wednesday	3	(011) ₂
Thursday	4	(100) ₂
Friday	5	(101) ₂
Saturday	6	(110) ₂

Converting to a Truth Table!

Weekday	Number	Binary	Weekday	Lecture?	c0	c1	c2	c3
Sunday	0	(000) ₂	000	0	0	1	0	0
Monday	1	(001) ₂	000	1	0	0	0	1
Tuesday	2	(010) ₂	001	0	0	1	0	0
Wednesday	3	(011) ₂	001	1	0	0	0	1
Thursday	4	(100) ₂	010	0	0	1	0	0
Friday	5	(101) ₂	010	1	0	0	1	0
Saturday	6	(110) ₂	011	0	0	1	0	0
			011	1	0	0	1	0
			100	-	0	1	0	0
			101	0	1	0	0	0
			101	1	0	1	0	0
			110	-	1	0	0	0
			111	-	-	-	-	-

Truth Table to Logic (Part 1)

	DAY	d2	d1	d0	L	c0	c1	c2	c3
	SunS	000	0	0	1	0	1	0	0
	SunL	000	1	0	0	0	0	0	1
	MonS	001	0	0	1	0	0	0	0
c3 = (DAY == SUN and LEC) or (DAY == MON and LEC)	MonL	001	1	0	0	0	0	0	1
	TueS	010	0	0	1	0	0	0	0
c3 = (d2 == 0 && d1 == 0 && d0 == 0 && L == 1) (d2 == 0 && d1 == 0 && d0 == 1 && L == 1)	TueL	010	1	0	0	0	0	1	0
	WedS	011	0	0	1	0	0	0	0
c3 = d2'·d1'·d0'·L + d2'·d1'·d0·L	WedL	011	1	0	0	0	0	1	0
	Thu	100	-	0	1	0	0	0	0
	FriS	101	0	1	0	0	0	0	0
	FriL	101	1	0	1	0	0	0	0
	Sat	110	-	1	0	0	0	0	0
	-	111	-	-	-	-	-	-	-

Truth Table to Logic (Part 2)

$$c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L$$

$$c2 = (\text{DAY} == \text{TUE and LEC}) \text{ or } (\text{DAY} == \text{WED and LEC})$$

$$c2 = d2' \cdot d1 \cdot d0' \cdot L + d2' \cdot d1 \cdot d0 \cdot L$$

DAY	d2	d1	d0	L	c0	c1	c2	c3
SunS	0	0	0	0	0	1	0	0
SunL	0	0	0	1	0	0	0	1
MonS	0	0	1	0	0	1	0	0
MonL	0	0	1	1	0	0	0	1
TueS	0	1	0	0	0	1	0	0
TueL	0	1	0	1	0	0	1	0
WedS	0	1	1	0	0	1	0	0
WedL	0	1	1	1	0	0	1	0
Thu	1	0	-	0	1	0	0	0
FriS	1	0	1	0	1	0	0	0
FriL	1	0	1	1	0	1	0	0
Sat	1	1	-	1	0	0	0	0
-	1	1	-	-	-	-	-	-

Truth Table to Logic (Part 3)

$$c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L$$

$$c2 = d2' \cdot d1 \cdot d0' \cdot L + d2' \cdot d1 \cdot d0 \cdot L$$


$$c1 = \text{On your homework for next week!}$$

$$c0 = d2 \cdot d1' \cdot d0 \cdot L' + d2 \cdot d1 \cdot d0'$$

DAY	d2	d1	d0	L	c0	c1	c2	c3
SunS	0	0	0	0	0	1	0	0
SunL	0	0	0	1	0	0	0	1
MonS	0	0	1	0	0	1	0	0
MonL	0	0	1	1	0	0	0	1
TueS	0	1	0	0	0	1	0	0
TueL	0	1	0	1	0	0	1	0
WedS	0	1	1	0	0	1	0	0
WedL	0	1	1	1	0	0	1	0
Thu	1	0	-	0	1	0	0	0
FriS	1	0	1	0	1	0	0	0
FriL	1	0	1	1	0	1	0	0
Sat	1	1	-	1	0	0	0	0
-	1	1	-	-	-	-	-	-

Logic to Gates
 
$$c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L$$




Multi-input AND gates

DAY	d2	d1	d0	L	c0	c1	c2	c3
SunS	0	0	0	0	0	1	0	0
SunL	0	0	0	1	0	0	0	1
MonS	0	0	1	0	0	1	0	0
MonL	0	0	1	1	0	0	0	1
TueS	0	1	0	0	0	1	0	0
TueL	0	1	0	1	0	0	1	0
WedS	0	1	1	0	0	1	0	0
WedL	0	1	1	1	0	0	1	0
Thu	1	0	-	0	1	0	0	0
FriS	1	0	1	0	1	0	0	0
FriL	1	0	1	1	0	1	0	0
Sat	1	1	-	1	0	0	0	0
-	1	1	-	-	-	-	-	-

CSE 311: Foundations of Computing

Fall 2014

Lecture 4: Boolean Algebra and Circuits

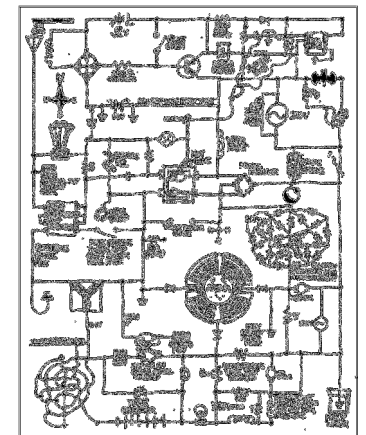


Boolean Algebra

- Boolean algebra to circuit design

- Boolean algebra

 - a set of elements B containing {0, 1}
- binary operations { + , • }
- and a unary operation { ' }
- such that the following axioms hold:



1. the set B contains at least two elements: 0, 1

For any a, b, c in B:

- | | | |
|---------------------|---------------------------------|---------------------------------|
| 2. closure: | a + b is in B | a • b is in B |
| 3. commutativity: | a + b = b + a | a • b = b • a |
| 4. associativity: | a + (b + c) = (a + b) + c | a • (b • c) = (a • b) • c |
| 5. identity: | a + 0 = a | a • 1 = a |
| 6. distributivity: | a + (b • c) = (a + b) • (a + c) | a • (b + c) = (a • b) + (a • c) |
| 7. complementarity: | a + a' = 1 | a • a' = 0 |

Axioms and Theorems of Boolean Algebra

identity:

1. $X + 0 = X$

1D. $X • 1 = X$

null:

2. $X + 1 = 1$

2D. $X • 0 = 0$

idempotency:

3. $X + X = X$

3D. $X • X = X$

involution:

4. $(X')' = X$

complementarity:

5. $X + X' = 1$

5D. $X • X' = 0$

commutatively:

6. $X + Y = Y + X$

6D. $X • Y = Y • X$

associativity:

7. $(X + Y) + Z = X + (Y + Z)$

7D. $(X • Y) • Z = X • (Y • Z)$

distributivity:

8. $X • (Y + Z) = (X • Y) + (X • Z)$

8D. $X + (Y • Z) = (X + Y) • (X + Z)$

Axioms and Theorems of Boolean Algebra

uniting:

9. $X • Y + X • Y' = X$

9D. $(X + Y) • (X + Y') = X$

absorption:

10. $X + X • Y = X$

10D. $X • (X + Y) = X$

11. $(X + Y') • Y = X • Y$

11D. $(X • Y') + Y = X + Y$

factoring:

12. $(X + Y) • (X' + Z) = X • Z + X' • Y$

12D. $X • Y + X' • Z = (X + Z) • (X' + Y)$

consensus:

13. $(X • Y) + (Y • Z) + (X' • Z) = X • Y + X' • Z$

13D. $(X + Y) • (Y + Z) • (X' + Z) = (X + Y) • (X' + Z)$

de Morgan's:

14. $(X + Y + ...) ' = X' • Y' • ...$

14D. $(X • Y • ...) ' = X' + Y' + ...$

Proving Theorems (Rewriting)

Using the laws of Boolean Algebra:

prove the theorem:

$X • Y + X • Y' = X$

distributivity (8)

$X • Y + X • Y' = X • (Y + Y')$

complementarity (5)

$= X • (1)$

identity (1D)

$= X$

prove the theorem:

$X + X • Y = X$

identity (1D)

$X + X • Y = X • 1 + X • Y$

distributivity (8)

$= X • (1 + Y)$

uniting (2)

$= X • (1)$

identity (1D)

$= X$

Proving Theorems (Truth Table)

Using complete truth table:

For example, de Morgan's Law:

$$(X + Y)' = X' \cdot Y'$$

NOR is equivalent to AND
with inputs complemented

X	Y	X'	Y'	(X + Y)'	X' • Y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0


$$(X \cdot Y)' = X' + Y'$$

NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	(X • Y)'	X' + Y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0


Simplifying using Boolean algebra
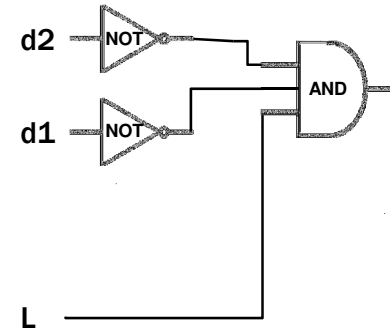
$$\begin{aligned} c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\ &= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\ &= d2' \cdot d1' \cdot (1) \cdot L \\ &= d2' \cdot d1' \cdot L \end{aligned}$$



1-bit Binary Adder

 - **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A' B' Cin + A' B Cin' + A B' Cin' + A B Cin$$

$$Cout = A' B Cin + A B' Cin + A B Cin' + A B Cin$$

Apply Theorems to Simplify Expressions

The theorems of Boolean algebra can simplify expressions

– e.g., full adder's carry-out function


$$\begin{aligned} Cout &= A' B Cin + A B' Cin + A B Cin' + A B Cin \\ &= A' B Cin + A B' Cin + A B Cin' + \boxed{A B Cin + A B Cin} \\ &= A' B Cin + A B Cin + A B' Cin + A B Cin' + A B Cin \\ &= (A' + A) B Cin + A B' Cin + A B Cin' + A B Cin \\ &= (1) B Cin + A B' Cin + A B Cin' + A B Cin \\ &= B Cin + A B' Cin + A B Cin' + \boxed{A B Cin + A B Cin} \\ &= B Cin + A B' Cin + A B Cin + A B Cin' + A B Cin \\ &= B Cin + A (B' + B) Cin + A B Cin' + A B Cin \\ &= B Cin + A (1) Cin + A B Cin' + A B Cin \\ &= B Cin + A Cin + A B (Cin' + Cin) \\ &= B Cin + A Cin + A B (1) \\ &= B Cin + A Cin + A B \end{aligned}$$

adding extra terms
creates new factoring
opportunities

Gates Again!

NOT


$$X' \quad \bar{X} \quad \neg X$$

 

X	Y
0	1
1	0

AND


$$X \cdot Y \quad XY \quad X \wedge Y$$

 

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

OR

$$X + Y \quad X \vee Y$$

 


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

1

More Gates!

NAND


$$\neg(X \wedge Y) \quad (XY)'$$

 

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

NOR


$$\neg(X \vee Y) \quad (X + Y)'$$

 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

XOR


$$X \oplus Y$$

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

$$X \leftrightarrow Y$$

 


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

Slide 22

1

can we omit this slide? we mentioned it on the hw and this feels like info overload?
Adam Blank, 9/27/2014

A 2-bit Ripple-Carry Adder

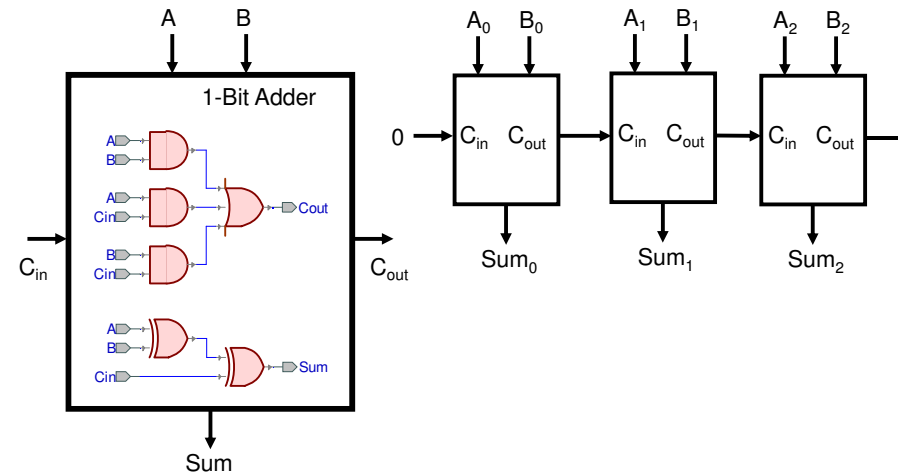

Mapping Truth Tables to Logic Gates

Given a truth table:

1. Write the Boolean expression
2. Minimize the Boolean expression
3. Draw as gates
4. Map to available gates


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

②

$$F = A'BC' + A'BC + AB'C + ABC$$

$$= A'B(C' + C) + AC(B' + B)$$

$$= A'B + AC$$

 

Canonical Forms

- Truth table is the unique signature of a Boolean function
- The same truth table can have many gate realizations
 - we've seen this already
 - depends on how good we are at Boolean simplification
- Canonical forms
 - standard forms for a Boolean expression
 - we all come up with the same expression

Sum-of-Products Canonical Form

- also known as **Disjunctive Normal Form (DNF)**
- also known as **minterm expansion**

$$F = 001 \quad 011 \quad 101 \quad 110 \quad 111$$

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Sum-of-Products Canonical Form

Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	A'B'C'
0	0	1	A'B'C
0	1	0	A'BC'
0	1	1	A'BC
1	0	0	AB'C'
1	0	1	AB'C
1	1	0	ABC'
1	1	1	ABC

F in canonical form:

$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$$

canonical form \neq minimal form

$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC + ABC'$$

$$= (A'B' + A'B + AB' + AB)C + ABC'$$

$$= ((A' + A)(B' + B))C + ABC'$$

$$= C + ABC'$$

$$= ABC' + C$$

$$= AB + C$$

Product-of-Sums Canonical Form

- Also known as **Conjunctive Normal Form (CNF)**
- Also known as **maxterm expansion**

			F =	000	010	100
			F =	(A + B + C)	(A + B' + C)	(A' + B + C)
A	B	C	F	F'		
0	0	0	0	1		
0	0	1	1	0		
0	1	0	0	1		
0	1	1	1	0		
1	0	0	0	1		
1	0	1	1	0		
1	1	0	1	0		
1	1	1	1	0		

s-o-p, p-o-s, and de Morgan's theorem

Complement of function in sum-of-products form:

$$- F' = A'B'C' + A'BC' + AB'C'$$

Complement again and apply de Morgan's and get the product-of-sums form:

$$-(F')' = (A'B'C' + A'BC' + AB'C')'$$

$$- F = (A + B + C) (A + B' + C) (A' + B + C)$$

Product-of-Sums Canonical Form

Sum term (or maxterm)

- **O**Red sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms
0	0	0	A+B+C
0	0	1	A+B+C'
0	1	0	A+B'+C
0	1	1	A+B'+C'
1	0	0	A'+B+C
1	0	1	A'+B+C'
1	1	0	A'+B'+C
1	1	1	A'+B'+C'

F in canonical form:

$$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$