

Homework #1 Due Friday before class.

Please try out Gradescope before then!

(You can submit multiple times, so do a test run on the first homework.)

Office hours now posted on the web page:

TA	Office hours	Room
Evan McCarty	Thu, 3-4pm	CSE 021
Mert Saglam	Tue, 11-12pm	CSE 021
Krista Holden	Thu, 10:30-11:30am	CSE 220
Gunnar Onarheim	Tue, 3-4pm	CSE 021
Ian Turner	Wed, 12-1pm	CSE 218
Junhao (Ian) Zhu	Thu 4-5pm	CSE 021

Sections start this week:

Section	Day/Time	Room
AA Evan	Th, 1230-120	<u>THO</u> 234
AB Mert	Th, 130-220	<u>DEN</u> 217
AC Ian	Th, 230-320	<u>MGH</u> 254
AD Krista	Th, 1130-1220	<u>MGH</u> 251

Class e-mail list, Discussion board

a combinatorial logic example

Sessions of class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: 2
Input: (Monday, Section) Output: 1


implementation in software

```
public int classesLeft (weekday, lecture_flag) {  
    switch Woc (day) {  
        case SUNDAY:  
        case MONDAY:  
            return lecture_flag ? 3 : 1;  
        case TUESDAY:  
        case WEDNESDAY:  
            return lecture_flag ? 2 : 1;  
        case THURSDAY:  
            return lecture_flag ? 1 : 1;  
        case FRIDAY:  
            return lecture_flag ? 1 : 0;  
        case SATURDAY:  
            return lecture_flag ? 0 : 0;  
    }  
}
```

implementation with combinational logic

Encoding:

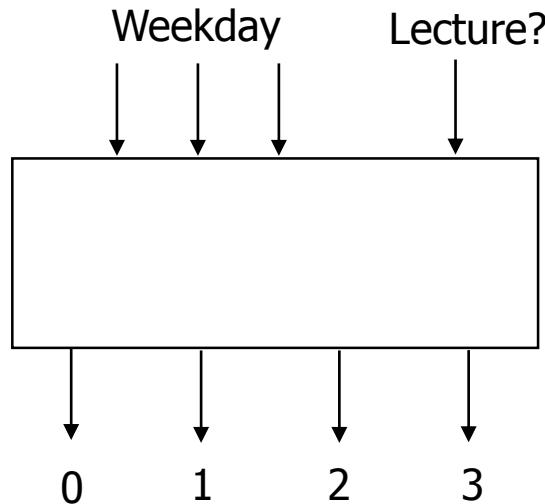- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



defining our inputs

```
public int classesLeft (weekday, lecture_flag) {  
    switch (day) {  
        case SUNDAY:  
        case MONDAY:  
            return lecture_flag ? 3 : 1;  
        case TUESDAY:  
        case WEDNESDAY:  
            return lecture_flag ? 2 : 1;  
        case THURSDAY:  
            return lecture_flag ? 1 : 1;  
        case FRIDAY:  
            return lecture_flag ? 1 : 0;  
        case SATURDAY:  
            return lecture_flag ? 0 : 0;  
    }  
}
```

Weekday	Number	Binary
Sunday	0	(000) ₂
Monday	1	(001) ₂
Tuesday	2	(010) ₂
Wednesday	3	(011) ₂
Thursday	4	(100) ₂
Friday	5	(101) ₂
Saturday	6	(110) ₂

converting to a truth table

Weekday	Number	Binary	Weekday	Lecture?	c0	c1	c2	c3
Sunday	0	(000) ₂	000	0	0	1	0	0
Monday	1	(001) ₂	000	1	0	0	0	1
Tuesday	2	(010) ₂	001	0	0	1	0	0
Wednesday	3	(011) ₂	001	1	0	0	0	1
Thursday	4	(100) ₂	010	0	0	1	0	0
Friday	5	(101) ₂	010	1	0	0	1	0
Saturday	6	(110) ₂	011	0	0	1	0	0
			011	1	0	0	1	0
			100	-	0	1	0	0
			101	0	1	0	0	0
			101	1	0	1	0	0
			110	-	1	0	0	0
			111	-	-	-	-	-

truth table \Rightarrow logic (part one)

$$\begin{aligned} 0 + 1 &= 1 \\ 1 + 1 &= 1 \end{aligned}$$

$$\begin{aligned} 0 \cdot 1 &= 1 \cdot 0 = 0 \\ 1 \cdot 1 &= 1 \quad 0 \cdot 0 = 0 \end{aligned}$$

$c_3 = (\text{DAY} == \text{SUN} \text{ and } \text{LEC}) \text{ or } (\text{DAY} == \text{MON} \text{ and } \text{LEC})$

$c_3 = (d_2 == 0 \text{ \&& } d_1 == 0 \text{ \&& } d_0 == 0 \text{ \&& } L == 1) \text{ || }$
 $(d_2 == 0 \text{ \&& } d_1 == 0 \text{ \&& } d_0 == 1 \text{ \&& } L == 1)$

$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$

DAY	d2d1d0	L	c0	c1	c2	c3
SunS	000	0	0	1	0	0
SunL	000	1	0	0	0	1
MonS	001	0	0	1	0	0
MonL	001	1	0	0	0	1
TueS	010	0	0	1	0	0
TueL	010	1	0	0	1	0
WedS	011	0	0	1	0	0
WedL	011	1	0	0	1	0
Thu	100	-	0	1	0	0
FriS	101	0	1	0	0	0
FriL	101	1	0	1	0	0
Sat	110	-	1	0	0	0
-	111	-	-	-	-	-

truth table ⇒ logic (part two)

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = (\text{DAY} == \text{TUE} \text{ and } \text{LEC}) \text{ or } (\text{DAY} == \text{WED} \text{ and } \text{LEC})$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

DAY	d2d1d0	L	c0	c1	c2	c3
SunS	000	0	0	1	0	0
SunL	000	1	0	0	0	1
MonS	001	0	0	1	0	0
MonL	001	1	0	0	0	1
TueS	010	0	0	1	0	0
TueL	010	1	0	0	1	0
WedS	011	0	0	1	0	0
WedL	011	1	0	0	1	0
Thu	100	-	0	1	0	0
FriS	101	0	1	0	0	0
FriL	101	1	0	1	0	0
Sat	110	-	1	0	0	0
-	111	-	-	-	-	-

truth table \Rightarrow logic (part three)

DAY	d2d1d0	L	c0	c1	c2	c3
SunS	000	0	0	1	0	0
SunL	000	1	0	0	0	1
MonS	001	0	0	1	0	0
MonL	001	1	0	0	0	1
TueS	010	0	0	1	0	0
TueL	010	1	0	0	1	0
WedS	011	0	0	1	0	0
WedL	011	1	0	0	1	0
Thu	100	-	0	1	0	0
FriS	101	0	1	0	0	0
FriL	101	1	0	1	0	0
Sat	110	-	1	0	0	0
-	111	-	-	-	-	-

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$


$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_1 =$$


[you do this one]

$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0'$$

logic \Rightarrow gates

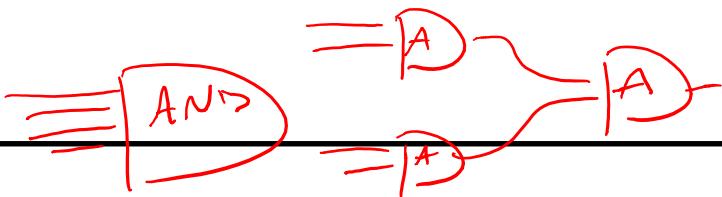
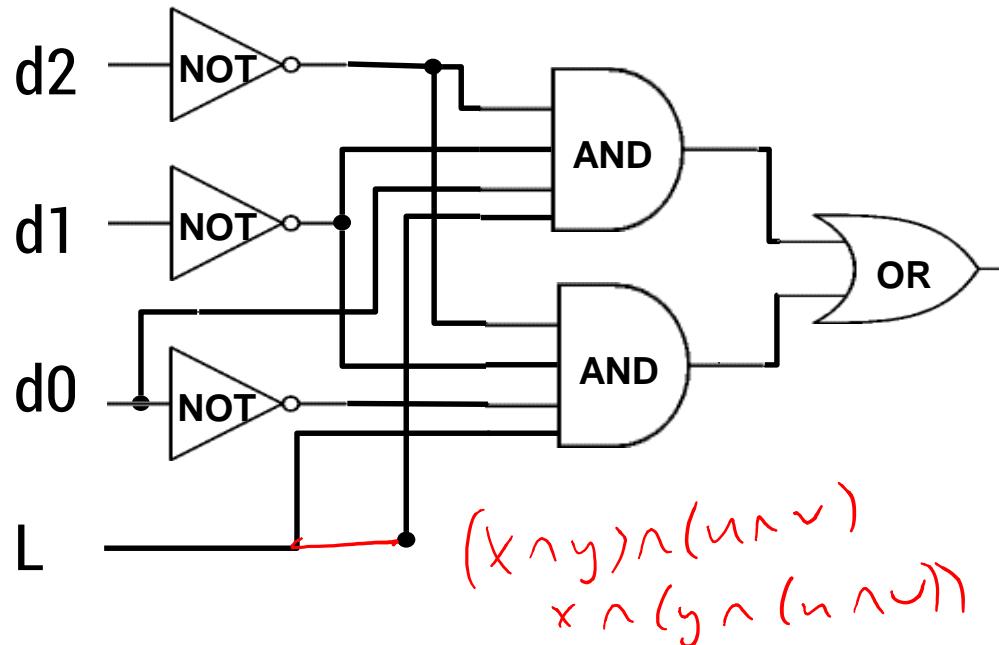
$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$




(multiple input AND gates)

DAY	d2d1d0	L	c0	c1	c2	c3
SunS	000	0	0	1	0	0
SunL	000	1	0	0	0	1
MonS	001	0	0	1	0	0
MonL	001	1	0	0	0	1
TueS	010	0	0	1	0	0
TueL	010	1	0	0	1	0
WedS	011	0	0	1	0	0
WedL	011	1	0	0	1	0
Thu	100	-	0	1	0	0
FriS	101	0	1	0	0	0
FriL	101	1	0	1	0	0
Sat	110	-	1	0	0	0
-	111	-	-	-	-	-

cse 311: foundations of computing

Spring 2015

Lecture 4: Boolean Algebra and Circuits

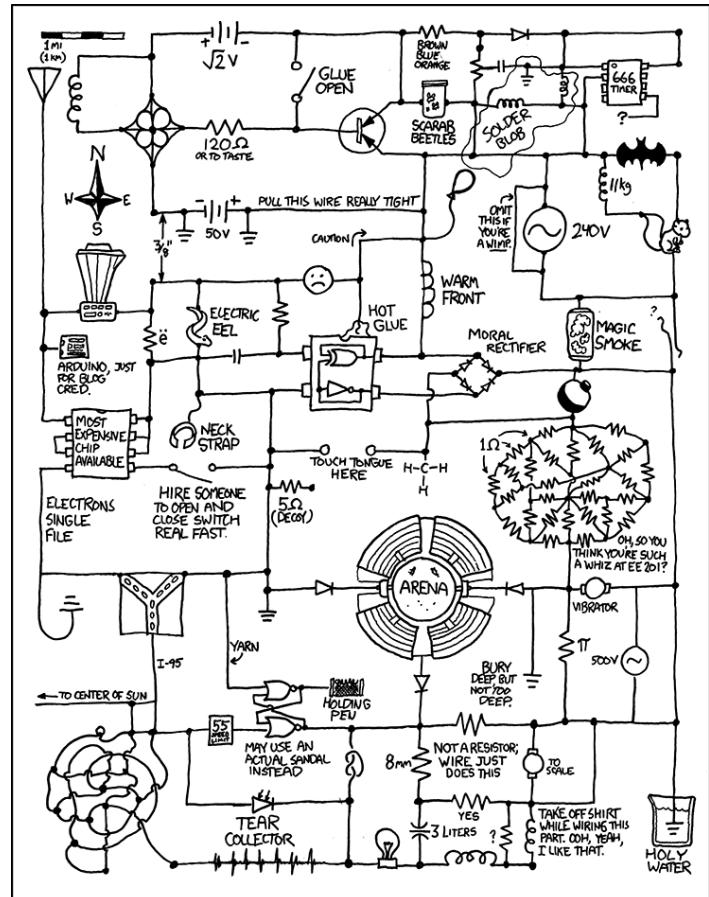

$$X \oplus Y \equiv X'Y + XY'$$

Boolean algebra

- Boolean algebra to circuit design
- Boolean algebra
 - a set of elements B containing $\{0, 1\}$
 - binary operations $\{+, \cdot\}$
 - and a unary operation $\{'\}$
 - such that the following axioms hold:

1. The set B contains at least two elements: $0, 1$



For any a, b, c in B :

2. closure:	$a + b$ is in B	$a \cdot b$ is in B
3. commutativity:	$a + b = b + a$	$a \cdot b = b \cdot a$
4. associativity:	$a + (b + c) = (a + b) + c$	$a \cdot (b \cdot c) = (a \cdot b) \cdot c$
5. identity:	$a + 0 = a$	$a \cdot 1 = a$
6. distributivity:	$a + (b \cdot c) = (a + b) \cdot (a + c)$	$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
7. complementarity:	$a + a' = 1$	$a \cdot a' = 0$

axioms and theorems of Boolean algebra

identity:

$$1. \quad X + 0 = X$$

$$1D. \quad X \cdot 1 = X$$

null:

$$2. \quad X + 1 = 1$$

$$2D. \quad X \cdot 0 = 0$$

idempotency:

$$3. \quad X + X = X$$

$$3D. \quad X \cdot X = X$$

involution:

$$4. \quad (X')' = X$$

complementarity:

$$5. \quad X + X' = 1$$

$$5D. \quad X \cdot X' = 0$$

commutativity:

$$6. \quad X + Y = Y + X$$

$$6D. \quad X \cdot Y = Y \cdot X$$

associativity:

$$7. \quad (X + Y) + Z = X + (Y + Z)$$

$$7D. \quad (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$$

distributivity:

$$8. \quad X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$8D. \quad X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

axioms and theorems of Boolean algebra

uniting:

$$9. X \cdot Y + X \cdot Y' = X$$

$$9D. (X + Y) \cdot (X + Y') = X$$

absorption:

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + Y') \cdot Y = X \cdot Y$$

$$11D. (X \cdot Y') + Y = X + Y$$

factoring:

$$12. (X + Y) \cdot (X' + Z) = \\ X \cdot Z + X' \cdot Y$$

$$12D. X \cdot Y + X' \cdot Z = \\ (X + Z) \cdot (X' + Y)$$

consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = \\ X \cdot Y + X' \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (X' + Z) = \\ (X + Y) \cdot (X' + Z)$$

de Morgan's:

$$14. (X + Y + \dots)' = X' \cdot Y' \cdot \dots$$

$$14D. (X \cdot Y \cdot \dots)' = X' + Y' + \dots$$

proving theorems (rewriting)

Using the laws of Boolean Algebra:

prove the theorem:

distributivity (8)

complementarity (5)

identity (1D)

$$X \bullet Y + X \bullet Y' = X$$

$$\begin{aligned} X \bullet Y + X \bullet Y' &= X \bullet (Y + Y') \\ &= X \bullet (1) \\ &= X \end{aligned}$$

prove the theorem:

identity (1D)

distributivity (8)

uniting (2)

identity (1D)

$$X + X \bullet Y = X$$

$$\begin{aligned} X + X \bullet Y &= X \bullet 1 + X \bullet Y \\ &= X \bullet (1 + Y) \\ &= X \bullet (1) \\ &= X \end{aligned}$$

proving theorems (truth table)

Using complete truth table:

For example, de Morgan's Law:

$$(X + Y)' = X' \cdot Y'$$

NOR is equivalent to AND
with inputs complemented

X	Y	X'	Y'	(X + Y)'	X' · Y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	1	1

Same answers


$$(X \cdot Y)' = X' + Y'$$

NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	(X · Y)'	X' + Y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	1	1


simplifying using Boolean algebra
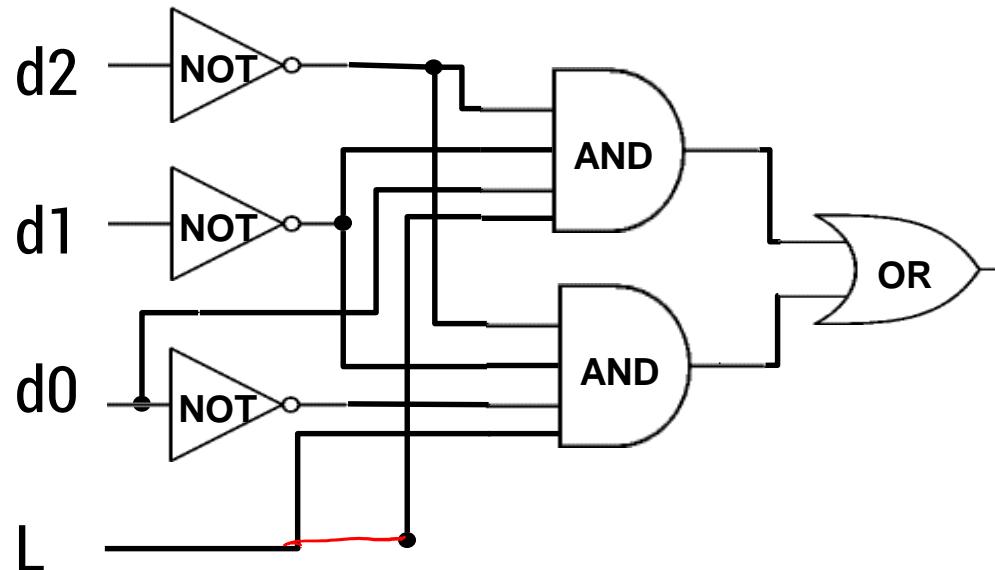
$$\begin{aligned}c_3 &= d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L \\&= d_2' \cdot d_1' \cdot (d_0' + d_0) \cdot L \\&= d_2' \cdot d_1' \cdot (1) \cdot L \\&= d_2' \cdot d_1' \cdot L\end{aligned}$$



simplifying using Boolean algebra

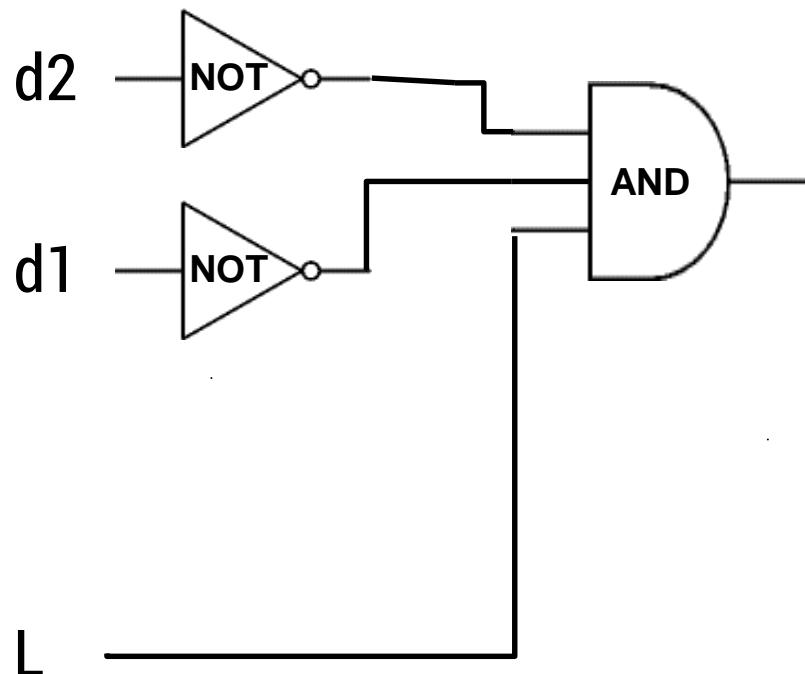
$$\begin{aligned}c_3 &= d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L \\&= d_2' \cdot d_1' \cdot (d_0' + d_0) \cdot L \\&= d_2' \cdot d_1' \cdot (1) \cdot L \\&= d_2' \cdot d_1' \cdot L\end{aligned}$$



1-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	1	0

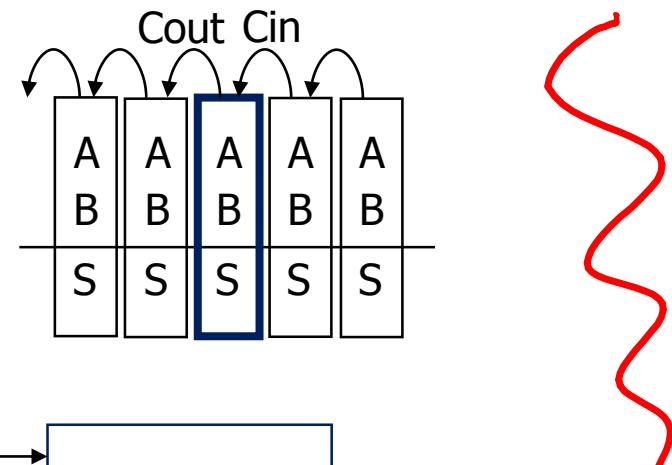


~~1+1=10~~

1-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

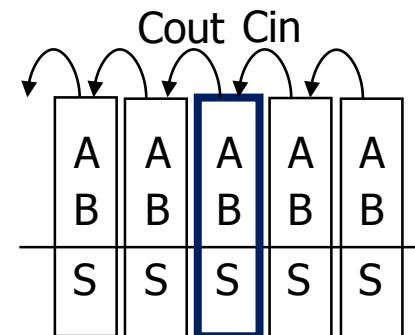

Carry

$$S = (A' B' \text{Cin} + A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin})$$

Cout = A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin}

S



apply theorems to simplify expressions

The theorems of Boolean algebra can simplify expressions

- e.g., full adder's carry-out function


$$\begin{aligned}\text{Cout} &= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + \boxed{A B \text{ Cin} + A B \text{ Cin}} \\ &= A' B \text{ Cin} + A B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= (A' + A) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= (1) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + \boxed{A B \text{ Cin} + A B \text{ Cin}} \\ &= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A (B' + B) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A (1) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A \text{ Cin} + A B (\text{Cin}' + \text{Cin}) \\ &= B \text{ Cin} + A \text{ Cin} + A B (1) \\ &= B \text{ Cin} + A \text{ Cin} + A B\end{aligned}$$

adding extra terms
creates new factoring
opportunities

more gates

NOT


$$X' \quad \bar{X} \quad \neg X$$

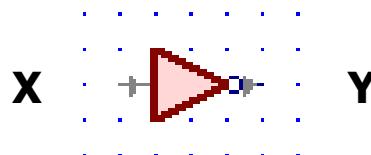

X	Y
0	1
1	0

AND


$$X \cdot Y \quad XY \quad X \wedge Y$$

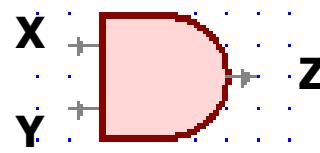

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

OR

$$X + Y \quad X \vee Y$$

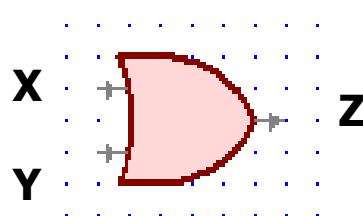


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

more gates

NAND


$$\neg(X \wedge Y) \quad (XY)'$$

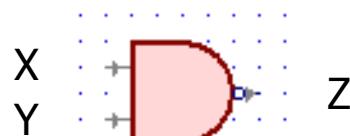

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

NOR

$$\neg(X \vee Y) \quad (X + Y)'$$

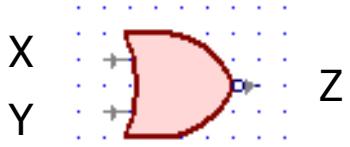


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

XOR

$$X \oplus Y$$

$$X'Y + XY'$$

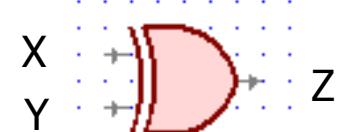


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

XNOR


$$X \leftrightarrow Y$$
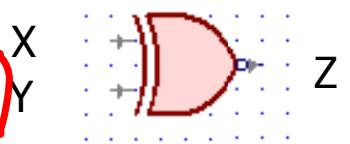
$$\begin{aligned} & (Y' + X)(X' + Y) \\ &= XY + X'Y' \end{aligned}$$



X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

a 2-bit ripple-carry adder

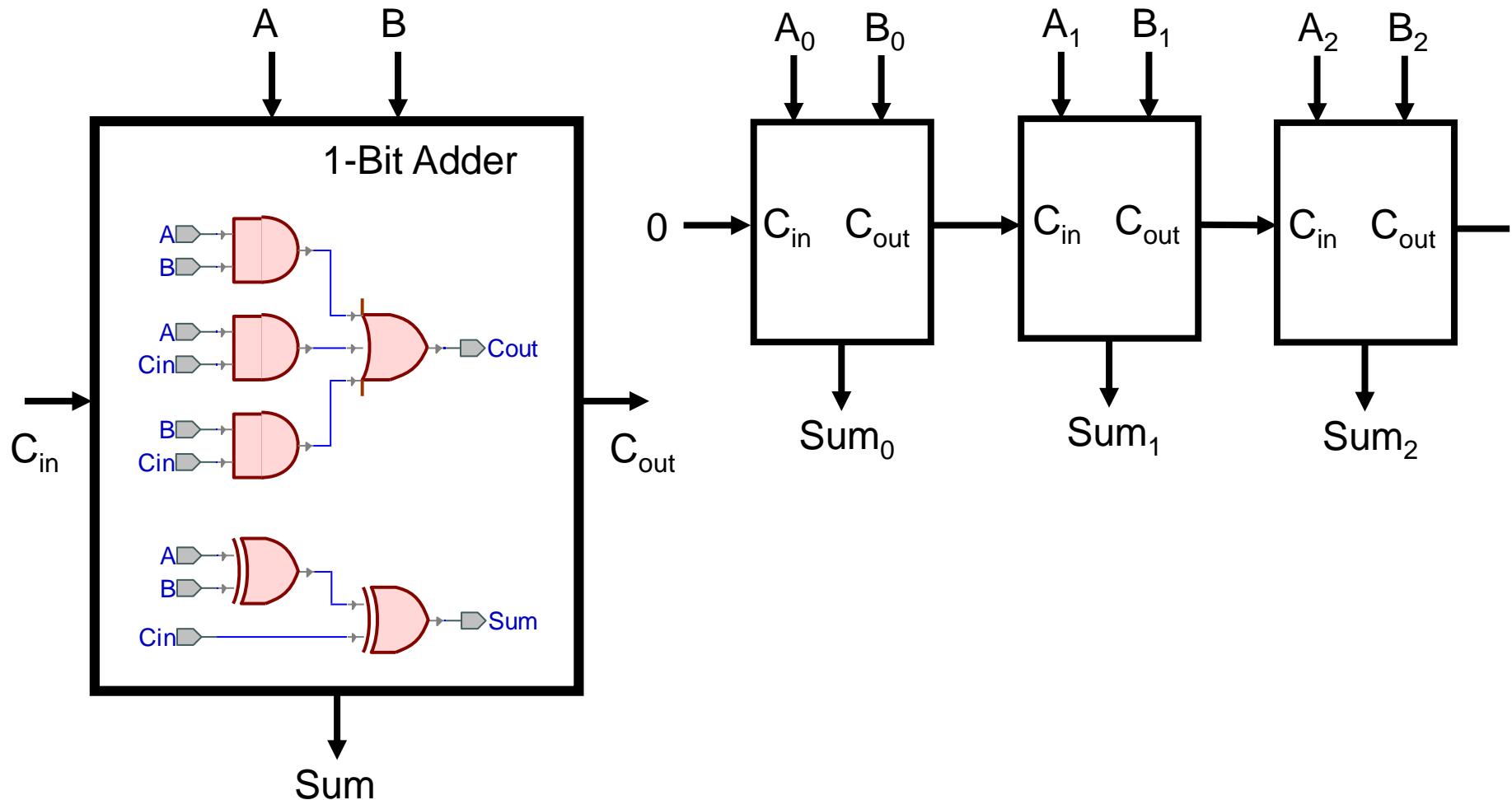

mapping truth tables to logic gates

Given a truth table:


1. Write the Boolean expression
2. Minimize the Boolean expression
3. Draw as gates
4. Map to available gates

(2)
$$\begin{aligned} F &= A'BC' + A'BC + AB'C + ABC \\ &= A'B(C' + C) + AC(B' + B) \\ &= A'B + AC \end{aligned}$$


(1)

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(3)

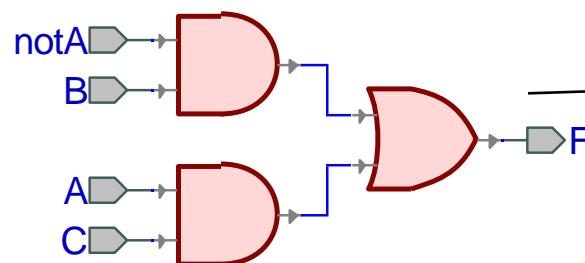

(4)

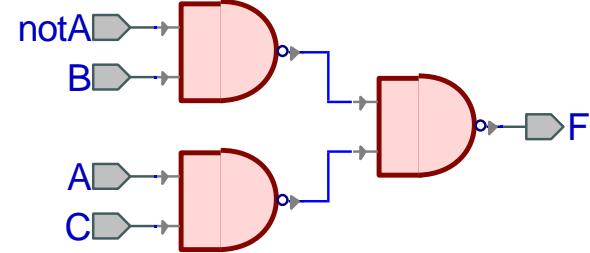

- Truth table is the unique signature of a Boolean function
- The same truth table can have many gate realizations
 - we've seen this already
 - depends on how good we are at Boolean simplification
- Canonical forms
 - standard forms for a Boolean expression
 - we all come up with the same expression

sum-of-products canonical form

- also known as **Disjunctive Normal Form (DNF)**
- also known as **minterm expansion**

			F = 001	011	101	110	111	
			F = A'B'C + A'BC + AB'C + ABC' + ABC					
A	B	C	F	F'				
0	0	0	0	1				
0	0	1	1	0				
0	1	0	0	1				
0	1	1	1	0				
1	0	0	0	1				
1	0	1	1	0				
1	1	0	1	0				
1	1	1	1	0				

The diagram illustrates the mapping from the truth table rows to the sum-of-products expression. Five arrows originate from the rows where F=1 (minterms) and point to the corresponding terms in the expression F = A'B'C + A'BC + AB'C + ABC' + ABC. The first arrow points to A'B'C, the second to A'BC, the third to AB'C, the fourth to ABC', and the fifth to ABC.

sum-of-products canonical form

Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	$A'B'C'$
0	0	1	$A'B'C$
0	1	0	$A'BC'$
0	1	1	$A'BC$
1	0	0	$AB'C'$
1	0	1	$AB'C$
1	1	0	ABC'
1	1	1	ABC

F in canonical form:

$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C \end{aligned}$$

product-of-sums canonical form

- Also known as **Conjunctive Normal Form (CNF)**
- Also known as **maxterm expansion**

			$F = 000$		010		100	
			$F = (A + B + C)$		$(A + B' + C)$		$(A' + B + C)$	
A	B	C	F	F'				
0	0	0	0	1				
0	0	1	1	0				
0	1	0	0	1				
0	1	1	1	0				
1	0	0	0	1				
1	0	1	1	0				
1	1	0	1	0				
1	1	1	1	0				

The diagram shows three arrows originating from the F column of the truth table and pointing to the three terms of the maxterm expansion. The first arrow points to the term $(A + B + C)$, the second to $(A + B' + C)$, and the third to $(A' + B + C)$.

s-o-p, p-o-s, and de Morgan's theorem

Complement of function in sum-of-products form:

- $F' = A'B'C' + A'BC' + AB'C'$

Complement again and apply de Morgan's and
get the product-of-sums form:

- $(F')' = (A'B'C' + A'BC' + AB'C)'$
- $F = (A + B + C) (A + B' + C) (A' + B + C)$

product-of-sums canonical form

Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms
0	0	0	$A+B+C$
0	0	1	$A+B+C'$
0	1	0	$A+B'+C$
0	1	1	$A+B'+C'$
1	0	0	$A'+B+C$
1	0	1	$A'+B+C'$
1	1	0	$A'+B'+C$
1	1	1	$A'+B'+C'$

F in canonical form:

$$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$