

## administrivia

### Homework #1 Due Friday before class.

Please try out Gradescope before then!

(You can submit multiple times, so do a test run on the first homework.)

Office hours now posted on the web page:

TA	Office hours	Room
Evan McCarty	Thu, 3-4pm	CSE 021
Mert Saglam	Tue, 11-12pm	CSE 021
Krista Holden	Thu, 10:30-11:30am	CSE 220
Gunnar Oinarheim	Tue, 3-4pm	CSE 021
Ian Turner	Wed, 12-1pm	CSE 218
Junhao (Jan) Zhu	Thu 4-5pm	CSE 021

Class e-mail list, Discussion board

Sections start this week:

Section	Day/Time	Room
AA Evan	Th, 1230-120	THU 234
AB Mert	Th, 130-220	DEU 217
AC Ian	Th, 230-320	MGH 254
AD Krista	Th, 1130-1220	MGH 251

## a combinatorial logic example

### Sessions of class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- Inputs: Day of the Week, Lecture/Section flag
- Output: Number of sessions left

Examples: Input: (Wednesday,Lecture) Output: 2  
Input: (Monday,Section) Output: 1


## implementation in software

```
public int classesLeft (weekday, lecture_flag) {
    switch (day) {
        case SUNDAY:
        case MONDAY:
            return lecture_flag ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return lecture_flag ? 2 : 1;
        case THURSDAY:
            return lecture_flag ? 1 : 1;
        case FRIDAY:
            return lecture_flag ? 1 : 0;
        case SATURDAY:
            return lecture_flag ? 0 : 0;
    }
}
```

## implementation with combinational logic
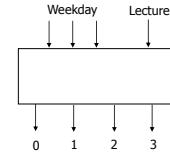
### Encoding:

- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



## defining our inputs

```
public int classesLeft (weekday, lecture_flag) {
    switch (day) {
        case SUNDAY:
        case MONDAY:
            return lecture_flag ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return lecture_flag ? 2 : 1;
        case THURSDAY:
            return lecture_flag ? 1 : 1;
        case FRIDAY:
            return lecture_flag ? 1 : 0;
        case SATURDAY:
            return lecture_flag ? 0 : 0;
    }
}
```

Weekday	Number	Binary
Sunday	0	(000) <sub>2</sub>
Monday	1	(001) <sub>2</sub>
Tuesday	2	(010) <sub>2</sub>
Wednesday	3	(011) <sub>2</sub>
Thursday	4	(100) <sub>2</sub>
Friday	5	(101) <sub>2</sub>
Saturday	6	(110) <sub>2</sub>

## converting to a truth table

Weekday	Number	Binary	Weekday	Lecture?	c0	c1	c2	c3
Sunday	0	(000) <sub>2</sub>	000	0	0	1	0	0
Monday	1	(001) <sub>2</sub>	000	1	0	0	0	1
Tuesday	2	(010) <sub>2</sub>	001	0	0	1	0	0
Wednesday	3	(011) <sub>2</sub>	001	1	0	0	0	1
Thursday	4	(100) <sub>2</sub>	010	0	0	1	0	0
Friday	5	(101) <sub>2</sub>	010	1	0	0	1	0
Saturday	6	(110) <sub>2</sub>	011	0	0	1	0	0
			011	1	0	0	1	0
			100	-	0	1	0	0
			101	0	1	0	0	0
			101	1	0	1	0	0
			110	-	1	0	0	0
			111	-	-	-	-	-

truth table  $\Rightarrow$  logic (part one)

DAY	d2d1d0	L	c0	c1	c2	c3
SunS	000	0	0	1	0	0
SunL	000	1	0	0	0	1
MonS	001	0	0	1	0	0
MonL	001	1	0	0	0	1
TueS	010	0	0	1	0	0
TueL	010	1	0	0	1	0
WedS	011	0	0	1	0	0
WedL	011	1	0	0	1	0
Thu	100	-	0	1	0	0
FriS	101	0	1	0	0	0
FriL	101	1	0	1	0	0
Sat	110	-	1	0	0	0
-	111	-	-	-	-	-

$$c3 = (\text{DAY} == \text{SUN and LEC}) \text{ or } (\text{DAY} == \text{MON and LEC})$$

$$c3 = (d2 == 0 \&\& d1 == 0 \&\& d0 == 0 \&\& L == 1) \text{ || } (d2 == 0 \&\& d1 == 0 \&\& d0 == 1 \&\& L == 1)$$

$$c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L$$

truth table  $\Rightarrow$  logic (part two)

DAY	d2d1d0	L	c0	c1	c2	c3
SunS	000	0	0	1	0	0
SunL	000	1	0	0	0	1
MonS	001	0	0	1	0	0
MonL	001	1	0	0	0	1
TueS	010	0	0	1	0	0
TueL	010	1	0	0	1	0
WedS	011	0	0	1	0	0
WedL	011	1	0	0	1	0
Thu	100	-	0	1	0	0
FriS	101	0	1	0	0	0
FriL	101	1	0	1	0	0
Sat	110	-	1	0	0	0
-	111	-	-	-	-	-

$$c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L$$

$$c2 = (\text{DAY} == \text{TUE and LEC}) \text{ or } (\text{DAY} == \text{WED and LEC})$$

$$c2 = d2' \cdot d1 \cdot d0' \cdot L + d2' \cdot d1 \cdot d0 \cdot L$$

truth table  $\Rightarrow$  logic (part three)

DAY	d2d1d0	L	c0	c1	c2	c3
SunS	000	0	0	1	0	0
SunL	000	1	0	0	0	1
MonS	001	0	0	1	0	0
MonL	001	1	0	0	0	1
TueS	010	0	0	1	0	0
TueL	010	1	0	0	1	0
WedS	011	0	0	1	0	0
WedL	011	1	0	0	1	0
Thu	100	-	0	1	0	0
FriS	101	0	1	0	0	0
FriL	101	1	0	1	0	0
Sat	110	-	1	0	0	0
-	111	-	-	-	-	-

$$c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L$$


$$c2 = d2' \cdot d1 \cdot d0' \cdot L + d2' \cdot d1 \cdot d0 \cdot L$$

c1 =

[you do this one]

$$c0 = d2 \cdot d1' \cdot d0 \cdot L' + d2 \cdot d1 \cdot d0'$$

$$c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L$$

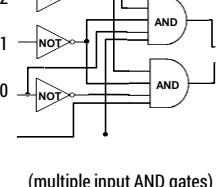
logic  $\Rightarrow$  gates

DAY	d2d1d0	L	c0	c1	c2	c3
SunS	000	0	0	1	0	0
SunL	000	1	0	0	0	1
MonS	001	0	0	1	0	0
MonL	001	1	0	0	0	1
TueS	010	0	0	1	0	0
TueL	010	1	0	0	1	0
WedS	011	0	0	1	0	0
WedL	011	1	0	0	1	0
Thu	100	-	0	1	0	0
FriS	101	0	1	0	0	0
FriL	101	1	0	1	0	0
Sat	110	-	1	0	0	0
-	111	-	-	-	-	-

## cse 311: foundations of computing

## Spring 2015
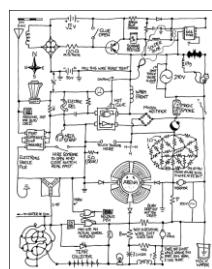
## Lecture 4: Boolean Algebra and Circuits



## Boolean algebra

## • Boolean algebra to circuit design

## • Boolean algebra

- a set of elements B containing {0, 1}
- binary operations {+, ·}
- and a unary operation (')
- such that the following axioms hold:

1. The set B contains at least two elements: 0, 1

For any a, b, c in B:

2. closure:	$a + b$ is in B	$a \cdot b$ is in B
3. commutativity:	$a + b = b + a$	$a \cdot b = b \cdot a$
4. associativity:	$a + (b + c) = (a + b) + c$	$a \cdot (b \cdot c) = (a \cdot b) \cdot c$
5. identity:	$a + 0 = a$	$a \cdot 1 = a$
6. distributivity:	$a + (b \cdot c) = (a + b) \cdot (a + c)$	$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
7. complementarity:	$a + a' = 1$	$a \cdot a' = 0$



## axioms and theorems of Boolean algebra

**identity:**

1.  $X + 0 = X$

1D.  $X \cdot 1 = X$

**null:**

2.  $X + 1 = 1$

2D.  $X \cdot 0 = 0$

**idempotency:**

3.  $X + X = X$

3D.  $X \cdot X = X$

**involution:**

4.  $(X')' = X$

complementarity:

5.  $X \cdot X' = 0$

5D.  $X \cdot X' = 0$

**commutativity:**

6.  $X + Y = Y + X$

6D.  $X \cdot Y = Y \cdot X$

**associativity:**

7.  $(X + Y) + Z = X + (Y + Z)$

7D.  $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$

**distributivity:**

8.  $X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$

8D.  $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$

## axioms and theorems of Boolean algebra

**uniting:**

9.  $X + Y + X \cdot Y' = X$

9D.  $(X + Y) \cdot (X + Y') = X$

**absorption:**

10.  $X + X \cdot Y = X$

10D.  $X \cdot (X + Y) = X$

11.  $(X + Y) \cdot Y = X \cdot Y$

11D.  $(X \cdot Y) + Y = X + Y$

**factoring:**

12.  $(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$

12D.  $X + Y + X' \cdot Z = (X + Z) \cdot (X' + Y)$

**consensus:**

13.  $(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Z + X' \cdot Z$

13D.  $(X + Y) \cdot (Y + Z) \cdot (X' + Z) = (X + Y) \cdot (X' + Z)$

**de Morgan's:**

14.  $(X + Y + \dots)' = X' \cdot Y' \cdot \dots$

14D.  $(X \cdot Y \cdot \dots)' = X' + Y' + \dots$

## proving theorems (rewriting)

**Using the laws of Boolean Algebra:****prove the theorem:**

$$X \cdot Y + X \cdot Y' = X$$

distributivity (8)  
complementarity (5)  
identity (1D)

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\ &= X \cdot (1) \\ &= X \end{aligned}$$

**prove the theorem:**

$$X + X \cdot Y = X$$

identity (1D)  
distributivity (8)  
uniting (2)  
identity (1D)

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y \\ &= X \cdot (1 + Y) \\ &= X \cdot (1) \\ &= X \end{aligned}$$

## proving theorems (truth table)

**Using complete truth table:****For example, de Morgan's Law:**

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0


$(X + Y)' = X' \cdot Y'$   
NOR is equivalent to AND with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$   
NAND is equivalent to OR with inputs complemented

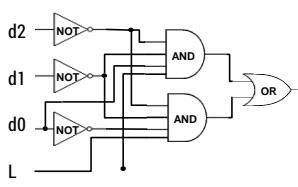
## simplifying using Boolean algebra

$$\begin{aligned} c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\ &= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\ &= d2' \cdot d1' \cdot (1) \cdot L \\ &= d2' \cdot d1' \cdot L \end{aligned}$$


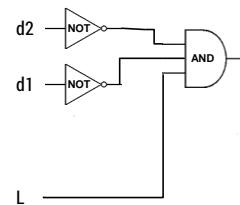
## simplifying using Boolean algebra


$$\begin{aligned} c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\ &= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\ &= d2' \cdot d1' \cdot (1) \cdot L \\ &= d2' \cdot d1' \cdot L \end{aligned}$$



### 1-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out


A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	0
1	0	0	0	1
1	1	0	0	0
1	1	1	1	1

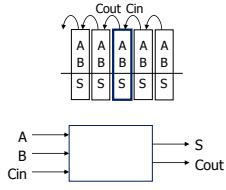

### 1-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

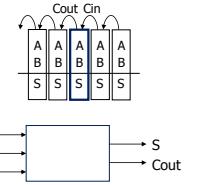

$$S = A' B' Cin + A' B Cin' + A B' Cin' + A B Cin$$

$$Cout = A' B Cin + A B' Cin + A B Cin' + A B Cin$$

### apply theorems to simplify expressions

The theorems of Boolean algebra can simplify expressions

- e.g., full adder's carry-out function


$$\begin{aligned} \text{Cout} &= A' B Cin + A B' Cin + A B Cin' + A B Cin \\ &= A' B Cin + A B' Cin + A B Cin' + A B Cin + A B Cin \\ &= A' B Cin + A B Cin + A B' Cin + A B Cin' + A B Cin \\ &= (A' + A) B Cin + A B' Cin + A B Cin' + A B Cin \\ &= (1) B Cin + A B' Cin + A B Cin' + A B Cin \\ &= B Cin + A B' Cin + A B Cin' + A B Cin + A B Cin \\ &= B Cin + A B' Cin + A B Cin + A B Cin' + A B Cin \\ &= B Cin + A (B + B) Cin + A B Cin' + A B Cin \\ &= B Cin + A (1) Cin + A B Cin' + A B Cin \\ &= B Cin + A Cin + A B (Cin' + Cin) \\ &= B Cin + A Cin + A B (1) \\ &= B Cin + A Cin + A B B \end{aligned}$$

adding extra terms creates new factoring opportunities

### more gates


#### NOT

$$X' \quad \bar{X} \quad \neg X$$

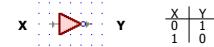


#### AND

$$X \cdot Y \quad XY \quad X \wedge Y$$

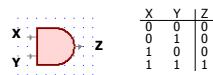


#### OR

$$X + Y \quad X \vee Y$$

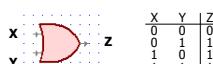

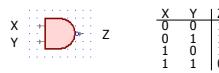
### more gates


**NAND**  
 $\neg(X \wedge Y) \quad (XY)'$



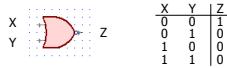
**NOR**  
 $\neg(X \vee Y) \quad (X + Y)'$




**XOR**  
 $X \oplus Y$

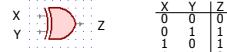


**XNOR**  
 $X \leftrightarrow Y$

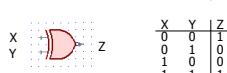

### a 2-bit ripple-carry adder

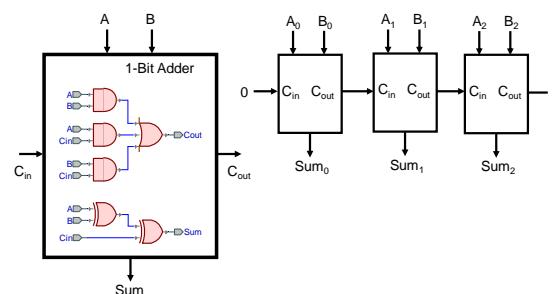

## mapping truth tables to logic gates

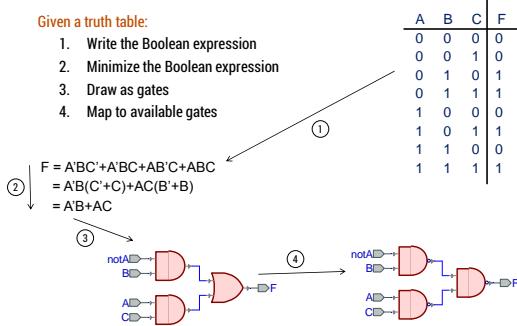


## canonical forms

- Truth table is the unique signature of a Boolean function
- The same truth table can have many gate realizations
  - we've seen this already
  - depends on how good we are at Boolean simplification
- Canonical forms
  - standard forms for a Boolean expression
  - we all come up with the same expression
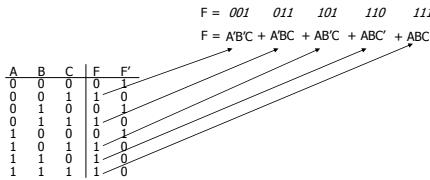
## sum-of-products canonical form

- also known as Disjunctive Normal Form (DNF)
- also known as minterm expansion



## sum-of-products canonical form

### Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)


A	B	C	minterms
0	0	0	$A'B'C'$
0	0	1	$A'B'C$
0	1	0	$A'BC'$
0	1	1	$A'BC$
1	0	0	$AB'C'$
1	0	1	$AB'C$
1	1	0	$ABC'$
1	1	1	$ABC$

### F in canonical form:

$$\begin{aligned} F(A, B, C) &= A'B'C + A'BC + AB'C + ABC' + ABC \\ \text{canonical form} \neq \text{minimal form} \\ F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C \end{aligned}$$
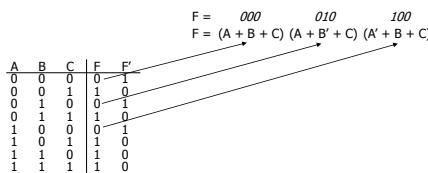
## product-of-sums canonical form

- Also known as Conjunctive Normal Form (CNF)
- Also known as maxterm expansion



## s-o-p, p-o-s, and de Morgan's theorem

### Complement of function in sum-of-products form:

$$- F' = A'B'C' + A'BC' + AB'C'$$

### Complement again and apply de Morgan's and get the product-of-sums form:

$$\begin{aligned} - (F')' &= (A'B'C' + A'BC' + AB'C)' \\ - F &= (A + B + C) (A + B' + C) (A' + B + C) \end{aligned}$$

## product-of-sums canonical form

Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms	F in canonical form:
0	0	0	A+B+C	$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$
0	0	1	A+B+C'	
0	1	0	A+B'+C	
0	1	1	A+B'+C'	canonical form $\neq$ minimal form
1	0	0	A'+B+C	$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$
1	0	1	A'+B+C'	$= (A + B + C) (A + B' + C)$
1	1	0	A'+B+C	$= (A + B + C) (A' + B + C)$
1	1	1	A'+B'+C'	$= (A + C) (B + C)$