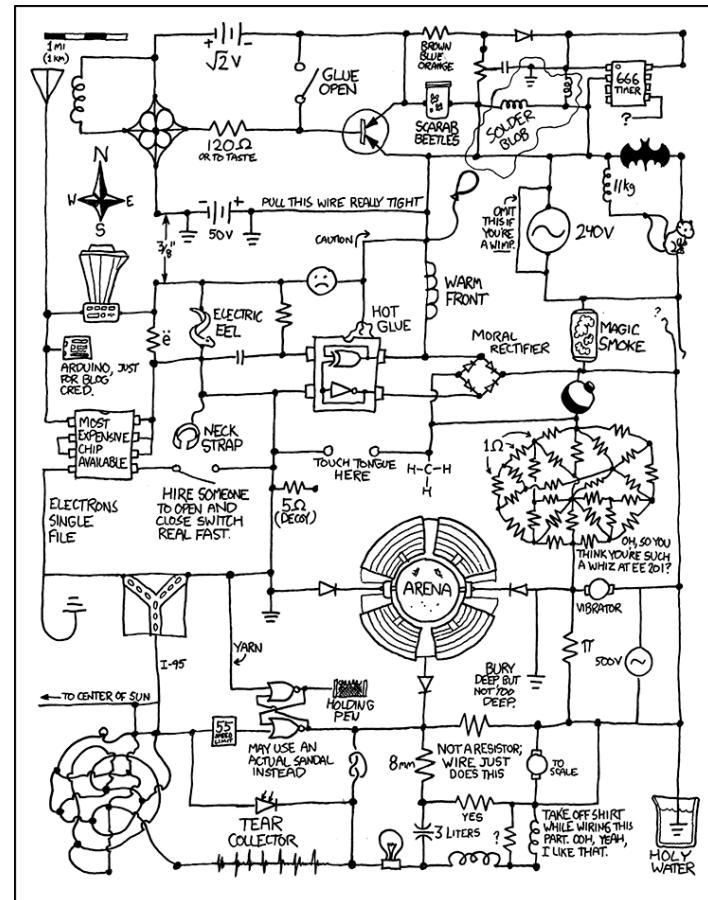


CSE 311: Foundations of Computing

Lecture 4: Boolean Algebra, Circuits, Canonical Forms

Monday 11:30 ~ 12:00

Pal. T 3:00 - 3:30



Boolean Logic

Combinational Logic

- $\text{output} = F(\text{input})$

Sequential Logic

- $\text{output}_t = F(\text{output}_{t-1}, \text{input}_t)$
 - output dependent on history
 - concept of a time step (clock, t)



Boolean Algebra: Another notation for logic consisting of...

- a set of elements $B = \{0, 1\}$
- binary operations $\{ +, \cdot \}$ (OR, AND)
- and a unary operation $\{ ' \}$ (NOT)

$$p \wedge q \quad p \cdot q$$


Boolean Algebra

- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing $\{0, 1\}$
 - binary operations $\{ +, \cdot \}$
 - and a unary operation $\{ '\}$
 - such that the following axioms hold:

For any a, b, c in B :

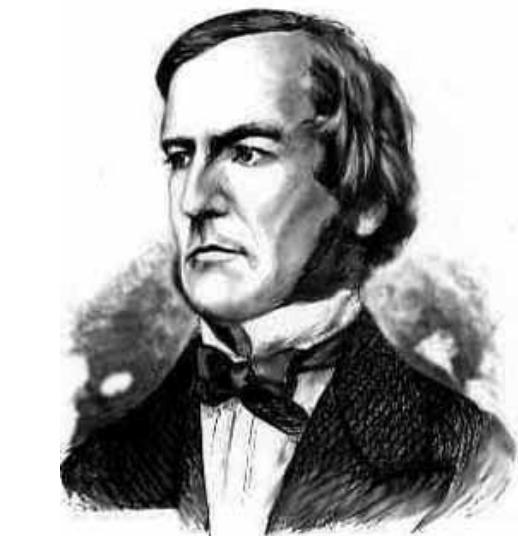1. closure:
2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$$\begin{aligned} a + b &\text{ is in } B \\ a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a &= a \\ (a')' &= a \end{aligned}$$



$$\begin{aligned} a \cdot b &\text{ is in } B \\ a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &\leftarrow= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a &= a \end{aligned}$$

A Combinational Logic Example

Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**
Input: (Monday, Section) Output: **1**


Implementation in Software

```
public int classesLeftInMorning(weekday, lecture_flag) {  
    switch (weekday) {  
        case SUNDAY:  
        case MONDAY:  
            return lecture_flag ? 3 : 1;  
        case TUESDAY:  
        case WEDNESDAY:  
            return lecture_flag ? 2 : 1;  
        case THURSDAY:  
            return lecture_flag ? 1 : 1;  
        case FRIDAY:  
            return lecture_flag ? 1 : 0;  
        case SATURDAY:  
            return lecture_flag ? 0 : 0;  
    }  
}
```

Implementation with Combinational Logic

Encoding:

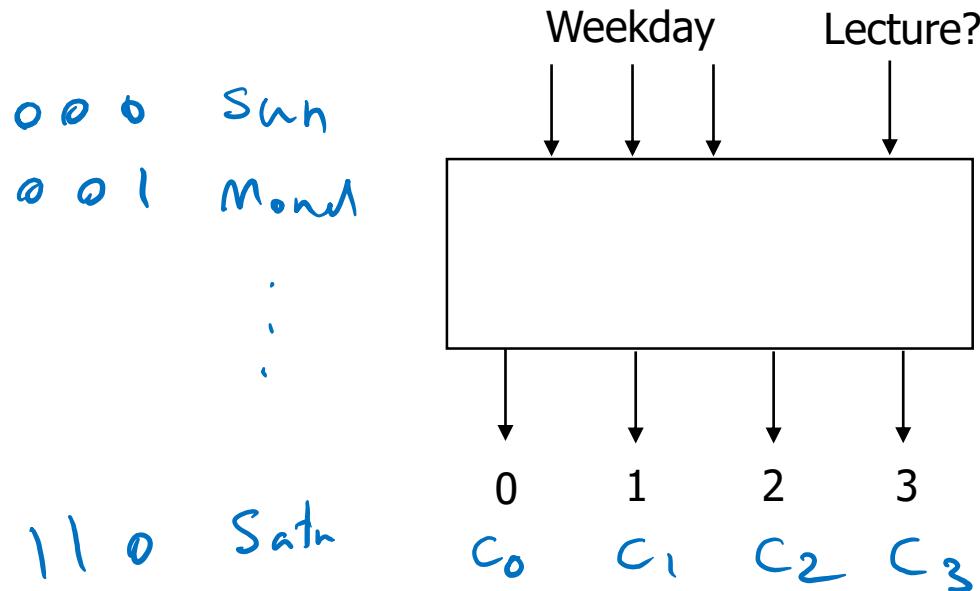- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



Defining Our Inputs!

Weekday Input:

- Binary number for weekday
- Sunday = 0, Monday = 1, ...
- We care about these in binary:

| Weekday | Number | Binary |
|-----------|--------|-----------|
| Sunday | 0 | $(000)_2$ |
| Monday | 1 | $(001)_2$ |
| Tuesday | 2 | $(010)_2$ |
| Wednesday | 3 | $(011)_2$ |
| Thursday | 4 | $(100)_2$ |
| Friday | 5 | $(101)_2$ |
| Saturday | 6 | $(110)_2$ |

Converting to a Truth Table!

```
case SUNDAY or MONDAY:  
    return lecture_flag ? 3 : 1;  
case TUESDAY or WEDNESDAY:  
    return lecture_flag ? 2 : 1;  
case THURSDAY:  
    return lecture_flag ? 1 : 1;  
case FRIDAY:  
    return lecture_flag ? 1 : 0;  
case SATURDAY:  
    return lecture_flag ? 0 : 0;
```

| Weekday | Lecture? | c_0 | c_1 | c_2 | c_3 |
|---------|----------|-------|-------|-------|-------|
| SUN | 000 | 0 | 1 | 0 | 0 |
| SUN | 000 | 0 | 0 | 0 | 1 |
| MON | 001 | 0 | | | |
| MON | 001 | 1 | | | |
| TUE | 010 | 0 | | | |
| TUE | 010 | 1 | | | |
| WED | 011 | 0 | | | |
| WED | 011 | 1 | | | |
| THU | 100 | - | | | |
| FRI | 101 | 0 | | | |
| FRI | 101 | 1 | | | |
| SAT | 110 | - | | | |
| - | 111 | - | | | |

Converting to a Truth Table!

```
case SUNDAY or MONDAY:  
    return lecture_flag ? 3 : 1;  
case TUESDAY or WEDNESDAY:  
    return lecture_flag ? 2 : 1;  
case THURSDAY:  
    return lecture_flag ? 1 : 1;  
case FRIDAY:  
    return lecture_flag ? 1 : 0;  
case SATURDAY:  
    return lecture_flag ? 0 : 0;
```

| Weekday | Lecture? | c_0 | c_1 | c_2 | c_3 |
|---------|----------|-------|-------|-------|-------|
| SUN | 000 | 0 | 1 | 0 | 0 |
| SUN | 000 | 0 | 0 | 0 | 1 |
| MON | 001 | 0 | 1 | 0 | 0 |
| MON | 001 | 1 | → | 0 | 0 |
| TUE | 010 | 0 | 1 | 0 | 0 |
| TUE | 010 | 0 | 0 | 1 | 0 |
| WED | 011 | 0 | 1 | 0 | 0 |
| WED | 011 | 0 | 0 | 1 | 0 |
| THU | 100 | 0 | 1 | 0 | 0 |
| FRI | 101 | 1 | 0 | 0 | 0 |
| FRI | 101 | 0 | 1 | 0 | 0 |
| SAT | 110 | - | 1 | 0 | 0 |
| - | 111 | - | 1 | 0 | 0 |

Truth Table to Logic (Part 1)

| $d_2 d_1 d_0$ | L | c_0 | c_1 | c_2 | c_3 |
|---------------|-----|-------|-------|-------|-------|
| SUN | 000 | 0 | 1 | 0 | 0 |
| SUN | 000 | 1 | 0 | 0 | 1 |
| MON | 001 | 0 | 1 | 0 | 0 |
| MON | 001 | 1 | 0 | 0 | 1 |
| TUE | 010 | 0 | 1 | 0 | 0 |
| TUE | 010 | 1 | 0 | 1 | 0 |
| WED | 011 | 0 | 1 | 0 | 0 |
| WED | 011 | 1 | 0 | 1 | 0 |
| THU | 100 | - | 0 | 1 | 0 |
| FRI | 101 | 0 | 1 | 0 | 0 |
| FRI | 101 | 1 | 0 | 1 | 0 |
| SAT | 110 | - | 1 | 0 | 0 |
| - | 111 | - | 1 | 0 | 0 |

Let's begin by finding an expression for c_3 . To do this, we look at the rows where $c_3 = 1$ (true).

Truth Table to Logic (Part 1)

| $d_2 d_1 d_0$ | L | c_0 | c_1 | c_2 | c_3 |
|---------------|-----|-------|-------|-------|-------|
| SUN | 000 | 0 | 1 | 0 | 0 |
| SUN | 000 | 1 | 0 | 0 | 1 |
| MON | 001 | 0 | 1 | 0 | 0 |
| MON | 001 | 1 | 0 | 0 | 1 |
| TUE | 010 | 0 | 1 | 0 | 0 |
| TUE | 010 | 1 | 0 | 1 | 0 |
| WED | 011 | 0 | 1 | 0 | 0 |
| WED | 011 | 1 | 0 | 1 | 0 |
| THU | 100 | - | 0 | 1 | 0 |
| FRI | 101 | 0 | 1 | 0 | 0 |
| FRI | 101 | 1 | 0 | 1 | 0 |
| SAT | 110 | - | 1 | 0 | 0 |
| - | 111 | - | 1 | 0 | 0 |

DAY == SUN && L == 1

DAY == MON && L == 1

Truth Table to Logic (Part 1)

| $d_2d_1d_0$ | L | c_0 | c_1 | c_2 | c_3 |
|-------------|-----|-------|-------|-------|-------|
| SUN | 000 | 0 | 1 | 0 | 0 |
| SUN | 000 | 1 | 0 | 0 | 1 |
| MON | 001 | 0 | 1 | 0 | 0 |
| MON | 001 | 1 | 0 | 0 | 1 |
| TUE | 010 | 0 | 1 | 0 | 0 |
| TUE | 010 | 1 | 0 | 0 | 1 |
| WED | 011 | 0 | 1 | 0 | 0 |
| WED | 011 | 1 | 0 | 0 | 1 |
| THU | 100 | - | 0 | 1 | 0 |
| FRI | 101 | 0 | 1 | 0 | 0 |
| FRI | 101 | 1 | 0 | 1 | 0 |
| SAT | 110 | - | 1 | 0 | 0 |
| - | 111 | - | 1 | 0 | 0 |

$d_2d_1d_0 == 000 \& L == 1$

$d_2d_1d_0 == 001 \& L == 1$

Substituting DAY for the binary representation.

Truth Table to Logic (Part 1)

| $d_2d_1d_0$ | L | c_0 | c_1 | c_2 | c_3 |
|-------------|---|-------|-------|-------|-------|
| SUN 000 | 0 | 0 | 1 | 0 | 0 |
| SUN 000 | 1 | 0 | 0 | 0 | 1 |
| MON 001 | 0 | 0 | 1 | 0 | 0 |
| MON 001 | 1 | 0 | 0 | 0 | 1 |
| TUE 010 | 0 | 0 | 1 | 0 | 0 |
| TUE 010 | 1 | 0 | 0 | 1 | 0 |
| WED 011 | 0 | 0 | 1 | 0 | 0 |
| WED 011 | 1 | 0 | 0 | 1 | 0 |
| THU 100 | - | 0 | 1 | 0 | 0 |
| FRI 101 | 0 | 1 | 0 | 0 | 0 |
| FRI 101 | 1 | 0 | 1 | 0 | 0 |
| SAT 110 | - | 1 | 0 | 0 | 0 |
| - 111 | - | 1 | 0 | 0 | 0 |

→ $d_2 == 0 \&& d_1 == 0 \&& d_0 == 0 \&& L == 1$

→ $d_2 == 0 \&& d_1 == 0 \&& d_0 == 1 \&& L == 1$

Splitting up the bits of the day;
so, we can write a formula.

Truth Table to Logic (Part 1)

| | $d_2 d_1 d_0$ | L | c_0 | c_1 | c_2 | c_3 |
|-----|---------------|---|-------|-------|-------|-------|
| SUN | 000 | 0 | 0 | 1 | 0 | 0 |
| SUN | 000 | 1 | 0 | 0 | 0 | 1 |
| MON | 001 | 0 | 0 | 1 | 0 | 0 |
| MON | 001 | 1 | 0 | 0 | 0 | 1 |
| TUE | 010 | 0 | 0 | 1 | 0 | 0 |
| TUE | 010 | 1 | 0 | 0 | 1 | 0 |
| WED | 011 | 0 | 0 | 1 | 0 | 0 |
| WED | 011 | 1 | 0 | 0 | 1 | 0 |
| THU | 100 | - | 0 | 1 | 0 | 0 |
| FRI | 101 | 0 | 1 | 0 | 0 | 0 |
| FRI | 101 | 1 | 0 | 1 | 0 | 0 |
| SAT | 110 | - | 1 | 0 | 0 | 0 |
| - | 111 | - | 1 | 0 | 0 | 0 |

$$d_2 = 0 \quad \neg d_2 \wedge \neg d_1 \wedge \neg d_0 \wedge L$$

$$d_2' \cdot d_1' \cdot d_0' \cdot L$$

+

$$d_2' \cdot d_1' \cdot d_0 \cdot L$$

Replacing with
Boolean Algebra...

Truth Table to Logic (Part 1)

| $d_2 d_1 d_0$ | L | c_0 | c_1 | c_2 | c_3 |
|---------------|---|-------|-------|-------|-------|
| SUN 000 | 0 | 0 | 1 | 0 | 0 |
| SUN 000 | 1 | 0 | 0 | 0 | 1 |
| MON 001 | 0 | 0 | 1 | 0 | 0 |
| MON 001 | 1 | 0 | 0 | 0 | 1 |
| TUE 010 | 0 | 0 | 1 | 0 | 0 |
| TUE 010 | 1 | 0 | 0 | 1 | 0 |
| WED 011 | 0 | 0 | 1 | 0 | 0 |
| WED 011 | 1 | 0 | 0 | 1 | 0 |
| THU 100 | - | 0 | 1 | 0 | 0 |
| FRI 101 | 0 | 1 | 0 | 0 | 0 |
| FRI 101 | 1 | 0 | 1 | 0 | 0 |
| SAT 110 | - | 1 | 0 | 0 | 0 |
| - 111 | - | 1 | 0 | 0 | 0 |

Either situation causes c_3 to be true. So, we “or” them.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Truth Table to Logic (Part 2)

| | $d_2 d_1 d_0$ | L | c_0 | c_1 | c_2 | c_3 | $c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$ |
|-----|---------------|---|-------|-------|-------|-------|--|
| SUN | 000 | 0 | 0 | 1 | 0 | 0 | |
| SUN | 000 | 1 | 0 | 0 | 0 | 1 | |
| MON | 001 | 0 | 0 | 1 | 0 | 0 | |
| MON | 001 | 1 | 0 | 0 | 0 | 1 | |
| TUE | 010 | 0 | 0 | 1 | 0 | 0 | |
| TUE | 010 | 1 | 0 | 0 | 1 | 0 | $d_2 = 0 \quad d_1 = 1 \quad d_0 = 0, L = 1$ |
| WED | 011 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1 \cdot d_0 \cdot L$ |
| WED | 011 | 1 | 0 | 0 | 1 | 0 | $d_2' \cdot d_1 \cdot d_0 \cdot L = c_2$ |
| THU | 100 | - | 0 | 1 | 0 | 0 | |
| FRI | 101 | 0 | 1 | 0 | 0 | 0 | |
| FRI | 101 | 1 | 0 | 1 | 0 | 0 | |
| SAT | 110 | - | 1 | 0 | 0 | 0 | |
| - | 111 | - | 1 | 0 | 0 | 0 | |

Now, we do c_2 .

$$d_2 = 0 \quad d_1 = 1 \quad d_0 = 0, L = 1$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L = c_2$$

$$d_2' \cdot d_1 \cdot L = c_2$$

Truth Table to Logic (Part 3)

| $d_2 d_1 d_0$ | L | c_0 | c_1 | c_2 | c_3 | |
|---------------|---|-------|-------|-------|-------|---------------------------------------|
| SUN 000 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1' \cdot d_0' \cdot L'$ |
| SUN 000 | 1 | 0 | 0 | 0 | 1 | |
| MON 001 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1' \cdot d_0 \cdot L'$ |
| MON 001 | 1 | 0 | 0 | 0 | 1 | |
| TUE 010 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1 \cdot d_0' \cdot L'$ |
| TUE 010 | 1 | 0 | 0 | 1 | 0 | |
| WED 011 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1 \cdot d_0 \cdot L'$ |
| WED 011 | 1 | 0 | 0 | 1 | 0 | |
| THU 100 | - | 0 | 1 | 0 | 0 | ??? $d_2 \cdot d_1' \cdot d_0'$ |
| FRI 101 | 0 | 1 | 0 | 0 | 0 | |
| FRI 101 | 1 | 0 | 1 | 0 | 0 | $d_2 \cdot d_1' \cdot d_0 \cdot L$ |
| SAT 110 | - | 1 | 0 | 0 | 0 | |
| - 111 | - | 1 | 0 | 0 | 0 | |

Now, we do c_1 :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

| $d_2 d_1 d_0$ | L | c_0 | c_1 | c_2 | c_3 | |
|---------------|---|-------|-------|-------|-------|---------------------------------------|
| SUN 000 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1' \cdot d_0' \cdot L'$ |
| SUN 000 | 1 | 0 | 0 | 0 | 1 | |
| MON 001 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1' \cdot d_0 \cdot L'$ |
| MON 001 | 1 | 0 | 0 | 0 | 1 | |
| TUE 010 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1 \cdot d_0' \cdot L'$ |
| TUE 010 | 1 | 0 | 0 | 1 | 0 | |
| WED 011 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1 \cdot d_0 \cdot L'$ |
| WED 011 | 1 | 0 | 0 | 1 | 0 | |
| THU 100 | - | 0 | 1 | 0 | 0 | $d_2 \cdot d_1' \cdot d_0'$ |
| FRI 101 | 0 | 1 | 0 | 0 | 0 | |
| FRI 101 | 1 | 0 | 1 | 0 | 0 | $d_2 \cdot d_1' \cdot d_0 \cdot L$ |
| SAT 110 | - | 1 | 0 | 0 | 0 | |
| - 111 | - | 1 | 0 | 0 | 0 | |

Now, we do c_1 :

$$d_2' \cdot d_1' \cdot d_0' \cdot L'$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L'$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L'$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L'$$

$$d_2 \cdot d_1' \cdot d_0'$$

$$d_2 \cdot d_1' \cdot d_0 \cdot L$$

No matter what L is,
we always say it's 1.
So, we don't need L
in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2 \cdot d_1 \cdot d_0' \cdot L + d_2 \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

| $d_2 d_1 d_0$ | L | c_0 | c_1 | c_2 | c_3 | |
|---------------|---|-------|-------|-------|-------|---------------------------------------|
| SUN 000 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1' \cdot d_0' \cdot L'$ |
| SUN 000 | 1 | 0 | 0 | 0 | 1 | |
| MON 001 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1' \cdot d_0 \cdot L'$ |
| MON 001 | 1 | 0 | 0 | 0 | 1 | |
| TUE 010 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1 \cdot d_0' \cdot L'$ |
| TUE 010 | 1 | 0 | 0 | 1 | 0 | |
| WED 011 | 0 | 0 | 1 | 0 | 0 | $d_2' \cdot d_1 \cdot d_0 \cdot L'$ |
| WED 011 | 1 | 0 | 0 | 1 | 0 | |
| THU 100 | - | 0 | 1 | 0 | 0 | $d_2 \cdot d_1' \cdot d_0'$ |
| FRI 101 | 0 | 1 | 0 | 0 | 0 | |
| FRI 101 | 1 | 0 | 1 | 0 | 0 | $d_2 \cdot d_1' \cdot d_0 \cdot L$ |
| SAT 110 | - | 1 | 0 | 0 | 0 | |
| - 111 | - | 1 | 0 | 0 | 0 | |

Now, we do c_1 :

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2 \cdot d_1 \cdot d_0' \cdot L + d_2 \cdot d_1 \cdot d_0 \cdot L$$

No matter what L is,
we always say it's 1.
So, we don't need L
in the expression.

Truth Table to Logic (Part 4)

| | $d_2 d_1 d_0$ | L | c_0 | c_1 | c_2 | c_3 | |
|-----|---------------|---|-------|-------|-------|-------|--|
| SUN | 000 | 0 | 0 | 1 | 0 | 0 | $c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' +$ $d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' +$ $d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$ |
| SUN | 000 | 1 | 0 | 0 | 0 | 1 | $c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$ |
| MON | 001 | 0 | 0 | 1 | 0 | 0 | $c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$ |
| MON | 001 | 1 | 0 | 0 | 0 | 1 | |
| TUE | 010 | 0 | 0 | 1 | 0 | 0 | |
| TUE | 010 | 1 | 0 | 0 | 1 | 0 | |
| WED | 011 | 0 | 0 | 1 | 0 | 0 | |
| WED | 011 | 1 | 0 | 0 | 1 | 0 | |
| THU | 100 | - | 0 | 1 | 0 | 0 | |
| FRI | 101 | 0 | 1 | 0 | 0 | 0 | $d_2 \cdot d_1' \cdot d_0 \cdot L'$ |
| FRI | 101 | 1 | 0 | 1 | 0 | 0 | |
| SAT | 110 | - | 1 | 0 | 0 | 0 | $d_2 \cdot d_1 \cdot d_0'$ |
| - | 111 | - | 1 | 0 | 0 | 0 | $d_2 \cdot d_1 \cdot d_0$ |

Finally, we do c_0 :

Truth Table to Logic (Part 4)


$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0$$

$$c_1 = d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

→ $c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$

Here's c_3 as a circuit:

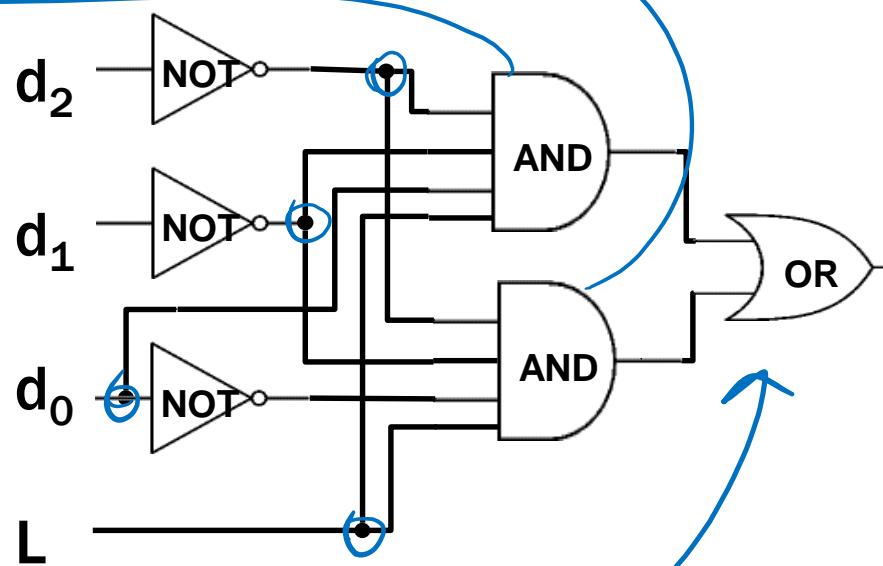

Boolean Algebra

- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing $\{0, 1\}$
 - binary operations $\{ +, \cdot \}$
 - and a unary operation $\{ '\}$
 - such that the following axioms hold:

For any a, b, c in B :

| | | |
|---------------------|---|---|
| 1. closure: | $a + b$ is in B | $a \cdot b$ is in B |
| 2. commutativity: | $a + b = b + a$ | $a \cdot b = b \cdot a$ |
| 3. associativity: | $a + (b + c) = (a + b) + c$ | $a \cdot (b \cdot c) = (a \cdot b) \cdot c$ |
| 4. distributivity: | $a + (b \cdot c) = (a + b) \cdot (a + c)$ | $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$ |
| 5. identity: | $a + 0 = a$ | $a \cdot 1 = a$ |
| 6. complementarity: | $a + a' = 1$ | $a \cdot a' = 0$ |
| 7. null: | $a + 1 = 1$ | $a \cdot 0 = 0$ |
| 8. idempotency: | $a + a = a$ | $a \cdot a = a$ |
| 9. involution: | $(a')' = a$ | |



Simplification using Boolean Algebra

→ uniting:

$$10. \quad a \cdot b + a \cdot b' = a$$

$$10D. \quad (a + b) \cdot (a + b') = a$$

→ absorption:

$$11. \quad a + a \cdot b = a$$

$$11D. \quad a \cdot (a + b) = a$$

$$12. \quad (a + b') \cdot b = a \cdot b$$

$$12D. \quad (a \cdot b') + b = a + b$$

factoring:

$$13. \quad (a + b) \cdot (a' + c) = \\ a \cdot c + a' \cdot b$$

$$13D. \quad a \cdot b + a' \cdot c = \\ (a + c) \cdot (a' + b)$$

consensus:

$$14. \quad (a \cdot b) + (b \cdot c) + (a' \cdot c) = \\ a \cdot b + a' \cdot c$$

$$14D. \quad (a + b) \cdot (b + c) \cdot (a' + c) = \\ (a + b) \cdot (a' + c)$$

de Morgan's:

$$15. \quad (a + b + \dots)' = a' \cdot b' \cdot \dots$$

$$15D. \quad (a \cdot b \cdot \dots)' = a' + b' + \dots$$

Proving Theorems

- 2. commutativity:
- 3. associativity:
- 4. distributivity:
- 5. identity:
- 6. complementarity:
- 7. null:
- 8. idempotency:
- 9. involution:

$$\begin{aligned} a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a = a & \\ (a')' = a & \end{aligned}$$

$$\begin{aligned} a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a = a & \end{aligned}$$

Using the laws of Boolean Algebra:

prove the Uniting theorem:

$$X \cdot Y + X \cdot Y' = X$$

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \text{ distrib} \\ &= X \cdot 1 \text{ complem} \\ &= X \text{ identity} \end{aligned}$$

prove the Absorption theorem:

$$(X) + (X \cdot Y) = X$$

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y \text{ identity} \\ &= X \cdot (1 + Y) \text{ dist.} \\ &= X \cdot 1 \text{ Null} \\ &= X \text{ identity} \end{aligned}$$

Proving Theorems

- 2. commutativity:
- 3. associativity:
- 4. distributivity:
- 5. identity:
- 6. complementarity:
- 7. null:
- 8. idempotency:
- 9. involution:

$$\begin{aligned} a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a &= a \\ (a')' &= a \end{aligned}$$

$$\begin{aligned} a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a &= a \end{aligned}$$

Using the laws of Boolean Algebra:

prove the Uniting theorem:

$$X \cdot Y + X \cdot Y' = X$$

distributivity

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\ &= X \cdot 1 \\ &= X \end{aligned}$$

complementarity

identity

prove the theorem:

$$X + X \cdot Y = X$$

identity

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y \\ &= X \cdot (1 + Y) \\ &= X \cdot (Y + 1) \\ &= X \cdot 1 \\ &= X \end{aligned}$$

distributivity

commutativity

null

identity

Proving Theorems

Using complete truth table:

For example, de Morgan's Law:

$$(X + Y)' = X' \cdot Y'$$

NOR is equivalent to AND
with inputs complemented

| X | Y | X' | Y' | (X + Y)' | X' · Y' |
|---|---|----|----|----------|---------|
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |

$$(X \cdot Y)' = X' + Y'$$


NAND is equivalent to OR
with inputs complemented

| X | Y | X' | Y' | (X · Y)' | X' + Y' |
|---|---|----|----|----------|---------|
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 |

Simplifying using Boolean Algebra

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$
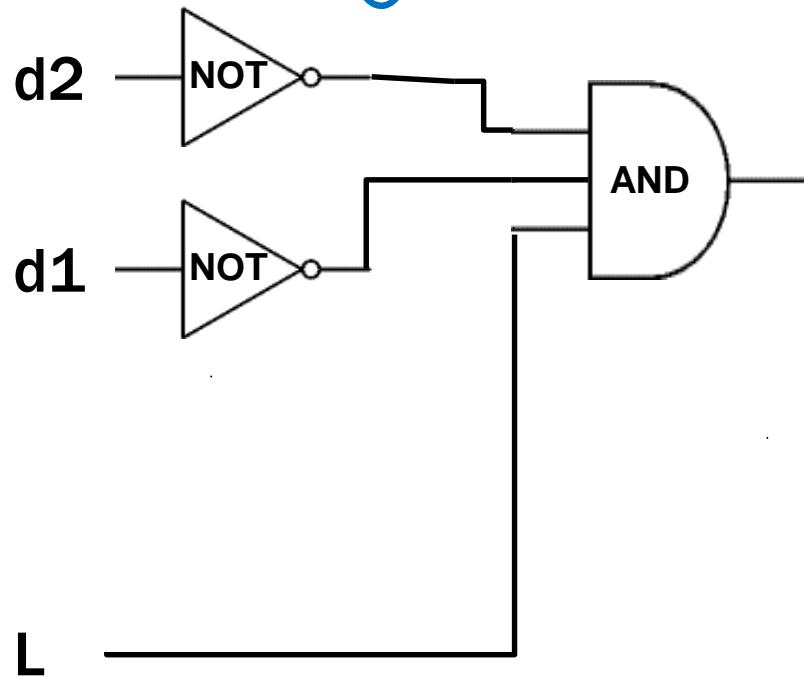
$$\begin{aligned} &= d_2' \cdot d_1' \cdot (d_0' + d_0) \cdot L && \text{dist} \\ &= d_2' \cdot d_1' \cdot 1 \cdot L && \text{comp } 1 \\ &= d_2' \cdot d_1' \cdot L && \text{idn by} \end{aligned}$$



1-bit Binary Adder

$$\begin{array}{r} A \\ + B \\ \hline S \end{array}$$

(C_{OUT})

$0 + 0 = 0$ (with $C_{OUT} = 0$)

$0 + 1 = 1$ (with $C_{OUT} = 0$)

$1 + 0 = 1$ (with $C_{OUT} = 0$)

$1 + 1 = 0$ (with $C_{OUT} = 1$)

\sum *Count*

1-bit Binary Adder

| | |
|-------------|-----------------------------------|
| A | $0 + 0 = 0$ (with $C_{OUT} = 0$) |
| <u>+ B</u> | $0 + 1 = 1$ (with $C_{OUT} = 0$) |
| S | $1 + 0 = 1$ (with $C_{OUT} = 0$) |
| (C_{OUT}) | $1 + 1 = 0$ (with $C_{OUT} = 1$) |


Idea: To chain these together, let's add a carry-in

1-bit Binary Adder

| | |
|-------------|-----------------------------------|
| A | $0 + 0 = 0$ (with $C_{OUT} = 0$) |
| <u>+ B</u> | $0 + 1 = 1$ (with $C_{OUT} = 0$) |
| S | $1 + 0 = 1$ (with $C_{OUT} = 0$) |
| (C_{OUT}) | $1 + 1 = 0$ (with $C_{OUT} = 1$) |

Idea: To chain these together, let's add a carry-in

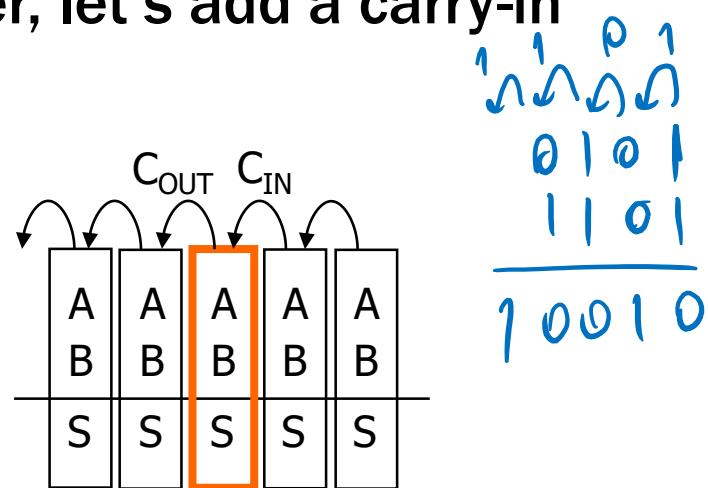
$$\begin{array}{r} (C_{IN}) \\ A \\ + B \\ \hline S \\ (C_{OUT}) \end{array}$$



1-bit Binary Adder


- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out

| A | B | C _{IN} | C _{OUT} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

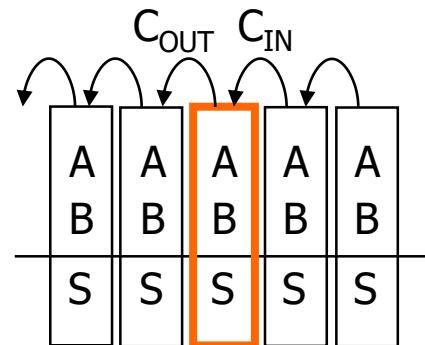

1-bit Binary Adder

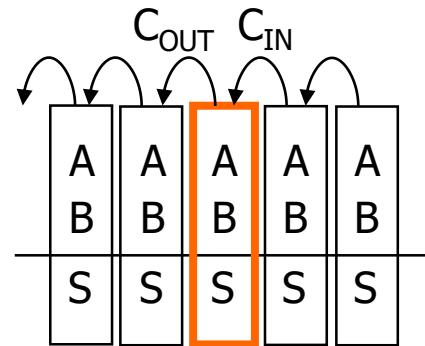- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



| A | B | C _{IN} | C _{OUT} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Derive an expression for S

$$A' \cdot B' \cdot C_{IN}$$

$$A' \cdot B \cdot C_{IN}'$$


$$A \cdot B' \cdot C_{IN}'$$

$$A \cdot B \cdot C_{IN}$$

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

1-bit Binary Adder

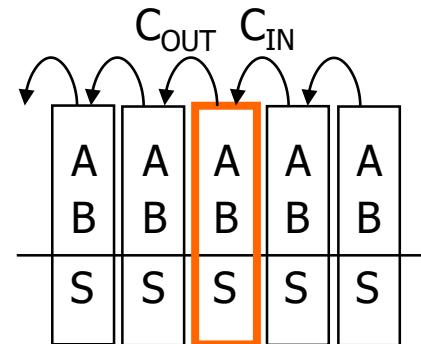- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



| A | B | C _{IN} | C _{OUT} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Derive an expression for C_{OUT}


$$\begin{aligned} & \text{A}' \cdot B \cdot C_{IN} \\ & \text{A} \cdot B' \cdot C_{IN} \\ & \text{A} \cdot B \cdot C_{IN}' \\ & \text{A} \cdot B \cdot C_{IN} \end{aligned}$$

$$C_{OUT} = \text{A}' \cdot B \cdot C_{IN} + \text{A} \cdot B' \cdot C_{IN} + \text{A} \cdot B \cdot C_{IN}' + \text{A} \cdot B \cdot C_{IN}$$

$$S = \text{A}' \cdot B' \cdot C_{IN} + \text{A}' \cdot B \cdot C_{IN}' + \text{A} \cdot B' \cdot C_{IN}' + \text{A} \cdot B \cdot C_{IN}$$

1-bit Binary Adder

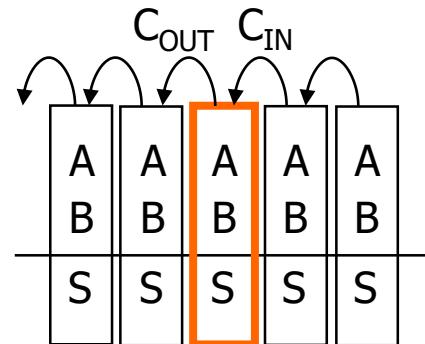- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



| A | B | C_{IN} | C_{OUT} | S |
|---|---|----------|-----------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

Apply Theorems to Simplify Expressions


The theorems of Boolean algebra can simplify expressions

- e.g., full adder's carry-out function

$$\begin{aligned} \text{Cout} &= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + \boxed{A B \text{ Cin}} + \boxed{A B \text{ Cin}} \\ &= A' B \text{ Cin} + A B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= (A' + A) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= (1) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + \boxed{A B \text{ Cin}} + \boxed{A B \text{ Cin}} \\ &= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A (B' + B) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A (1) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A \text{ Cin} + A B (\text{Cin}' + \text{Cin}) \\ &= B \text{ Cin} + A \text{ Cin} + A B (1) \\ &= B \text{ Cin} + A \text{ Cin} + A B \end{aligned}$$

adding extra terms
creates new factoring
opportunities

A 2-bit Ripple-Carry Adder

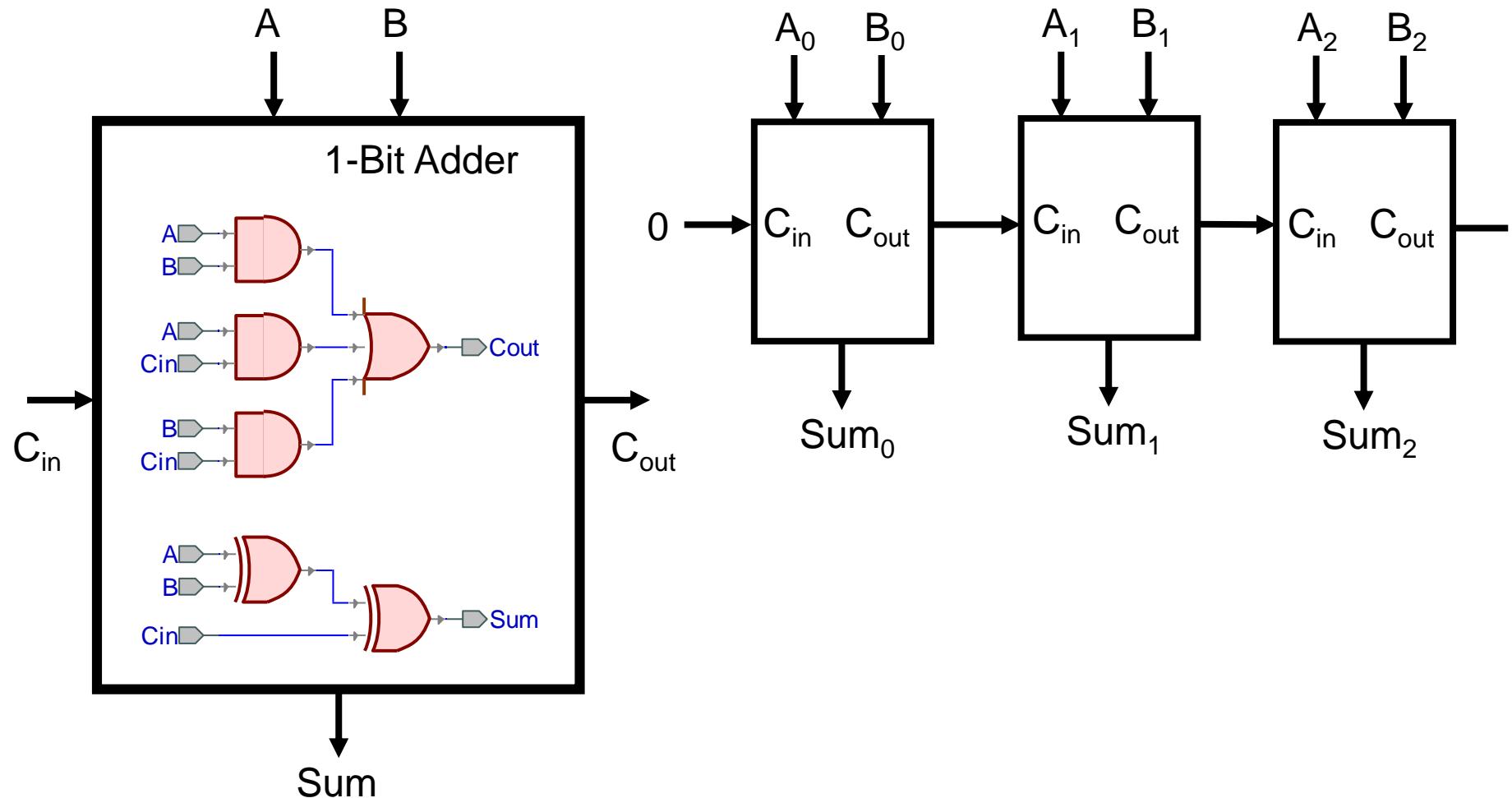

Mapping Truth Tables to Logic Gates


Given a truth table:

1. Write the Boolean expression
2. Minimize the Boolean expression
3. Draw as gates
4. Map to available gates


| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

(1)
$$\begin{aligned} F &= A'BC' + A'BC + AB'C + ABC \\ &= A'B(C' + C) + AC(B' + B) \\ &= A'B + AC \end{aligned}$$

(2)

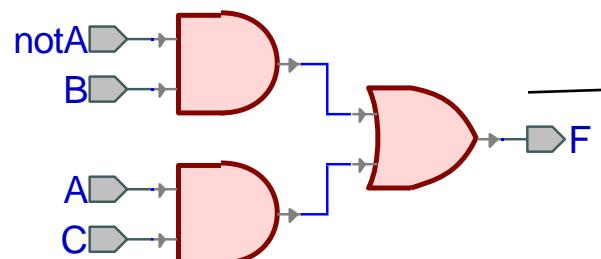

(4)

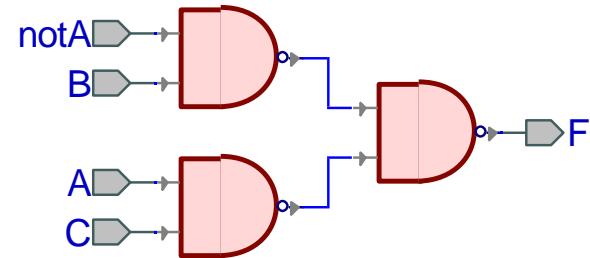

Canonical Forms

- Truth table is the **unique signature** of a Boolean Function
- The same truth table can have many gate realizations
 - We've seen this already
 - Depends on how good we are at Boolean simplification
- Canonical forms
 - Standard forms for a Boolean expression
 - We all come up with the same expression

Sum-of-Products Canonical Form

- AKA **Disjunctive Normal Form (DNF)**
- AKA **Minterm Expansion**

(3)

Add the minterms together

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

(1)
Read T rows off
truth table

001

(2)
Convert to
Boolean Algebra

$A'B'C$

011

$A'BC$

101

$AB'C$


110

ABC'

111

ABC

F

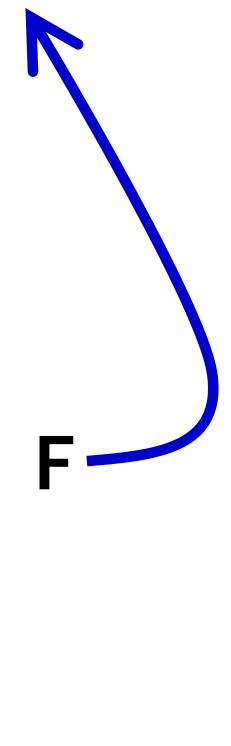

Sum-of-Products Canonical Form

Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

| A | B | C | minterms |
|---|---|---|----------|
| 0 | 0 | 0 | $A'B'C'$ |
| 0 | 0 | 1 | $A'B'C$ |
| 0 | 1 | 0 | $A'BC'$ |
| 0 | 1 | 1 | $A'BC$ |
| 1 | 0 | 0 | $AB'C'$ |
| 1 | 0 | 1 | $AB'C$ |
| 1 | 1 | 0 | ABC' |
| 1 | 1 | 1 | ABC |

F in canonical form:

$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C \end{aligned}$$

Product-of-Sums Canonical Form

- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**

④

Multiply the maxterms together

$F =$

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

① Read F rows off
truth table

② Negate all
bits

③ Convert to
Boolean Algebra

F

Product-of-Sums Canonical Form

- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

① Read F rows off
truth table

1

000

② Negate all
bits

2

111

4

Multiply the maxterms together

$$F = (A + B + C)(A + B' + C)(A' + B + C)$$

③ Convert to
Boolean Algebra

3

$A + B + C$

010

101

$A + B' + C$

100

011

$A' + B + C$

F

1

Product-of-Sums: Why does this procedure work?

Useful Facts:

- We know $(F')' = F$
- We know how to get a **minterm** expansion for F'

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$$F' = A'B'C' + A'BC' + AB'C'$$

Product-of-Sums: Why does this procedure work?

Useful Facts:

- We know $(F')' = F$
- We know how to get a **minterm expansion** for F'

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$$F' = A'B'C' + A'BC' + AB'C'$$

Taking the complement of both sides...

$$(F')' = (A'B'C' + A'BC' + AB'C)'$$

And using DeMorgan/Comp....

$$F = (A'B'C')' (A'BC')' (AB'C')'$$

$$F = (A + B + C)(A + B' + C)(A' + B + C)$$

Product-of-Sums Canonical Form

Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

| A | B | C | maxterms |
|---|---|---|------------|
| 0 | 0 | 0 | $A+B+C$ |
| 0 | 0 | 1 | $A+B+C'$ |
| 0 | 1 | 0 | $A+B'+C$ |
| 0 | 1 | 1 | $A+B'+C'$ |
| 1 | 0 | 0 | $A'+B+C$ |
| 1 | 0 | 1 | $A'+B+C'$ |
| 1 | 1 | 0 | $A'+B'+C$ |
| 1 | 1 | 1 | $A'+B'+C'$ |

F in canonical form:

$$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$