



Foundations of Computing I

Pre-Lecture Problem

Do it! Do it now! What are you waiting for? ☺

Use Logical Equivalences to show

$$p \wedge ((p \rightarrow q) \vee (p \rightarrow r)) \equiv (r \vee q) \wedge p$$

Identity $p \wedge T \equiv p$ $p \vee F \equiv p$	Domination $p \vee T \equiv T$ $p \wedge F \equiv F$	Idempotency $p \vee p \equiv p$ $p \wedge p \equiv p$
Commutativity $p \vee q \equiv q \vee p$ $p \wedge q \equiv q \wedge p$	Associativity $(p \vee q) \vee r \equiv p \vee (q \vee r)$ $(p \wedge q) \wedge r \equiv p \wedge (q \wedge r)$	Distributivity $p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$ $p \vee (q \wedge r) \equiv (p \vee q) \wedge (p \vee r)$
Absorption $p \vee (p \wedge q) \equiv p$ $p \wedge (p \vee q) \equiv p$	Negation $p \vee \neg p \equiv T$ $p \wedge \neg p \equiv F$	DeMorgan's Laws $\neg(p \vee q) \equiv \neg p \wedge \neg q$ $\neg(p \wedge q) \equiv \neg p \vee \neg q$
Double Negation $\neg\neg p \equiv p$	Law of Implication $p \rightarrow q \equiv \neg p \vee q$	Contrapositive $p \rightarrow q \equiv \neg q \rightarrow \neg p$

A Combinational Logic Example

Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**
 Input: (Monday, Section) Output: **1**


Implementation in Software

```
public int classesLeftInMorning(weekday, lecture_flag) {
    switch (weekday) {
        case SUNDAY:
        case MONDAY:
            return lecture_flag ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return lecture_flag ? 2 : 1;
        case THURSDAY:
            return lecture_flag ? 1 : 1;
        case FRIDAY:
            return lecture_flag ? 1 : 0;
        case SATURDAY:
            return lecture_flag ? 0 : 0;
    }
}
```

Implementation with Combinational Logic

Encoding:

 - How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



Defining Our Inputs!

Weekday Input:

- Binary number for weekday
- Sunday = 0, Monday = 1, ...
- We care about these in binary:

Weekday	Number	Binary
Sunday	0	(000) ₂
Monday	1	(001) ₂
Tuesday	2	(010) ₂
Wednesday	3	(011) ₂
Thursday	4	(100) ₂
Friday	5	(101) ₂
Saturday	6	(110) ₂

Converting to a Truth Table!

```

case SUNDAY or MONDAY:
    return lecture_flag ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return lecture_flag ? 2 : 1;
case THURSDAY:
    return lecture_flag ? 1 : 1;
case FRIDAY:
    return lecture_flag ? 1 : 0;
case SATURDAY:
    return lecture_flag ? 0 : 0;
    
```

Weekday	Lecture?	c ₀	c ₁	c ₂	c ₃	
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Truth Table to Logic (Part 1)

d ₂ d ₁ d ₀	L	c ₀	c ₁	c ₂	c ₃	
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Let's begin by finding an expression for c₃. To do this, we look at the rows where c₃ = 1 (true).

Truth Table to Logic (Part 1)

d ₂ d ₁ d ₀	L	c ₀	c ₁	c ₂	c ₃	
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

DAY == SUN && L == 1

DAY == MON && L == 1

Truth Table to Logic (Part 1)

d ₂ d ₁ d ₀	L	c ₀	c ₁	c ₂	c ₃	
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

d₂d₁d₀ == 000 && L == 1

d₂d₁d₀ == 001 && L == 1

Substituting DAY for the binary representation.

Truth Table to Logic (Part 1)

d ₂ d ₁ d ₀	L	c ₀	c ₁	c ₂	c ₃	
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

d₂ == 0 && d₁ == 0 && d₀ == 0 && L == 1

d₂ == 0 && d₁ == 0 && d₀ == 1 && L == 1

Splitting up the bits of the day; so, we can write a formula.

Truth Table to Logic (Part 1)

d ₂ d ₁ d ₀	L	c ₀	c ₁	c ₂	c ₃	
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

d₂' · d₁' · d₀' · L

d₂' · d₁' · d₀ · L

Replacing with Boolean Algebra...

Truth Table to Logic (Part 1)

	d_2, d_1, d_0	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2' \cdot d_1' \cdot d_0' \cdot L$
 $d_2' \cdot d_1' \cdot d_0 \cdot L$
 Either situation causes c_3 to be true. So, we "or" them.
 $c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$

Truth Table to Logic (Part 2)

	d_2, d_1, d_0	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
 Now, we do c_2 .

Truth Table to Logic (Part 3)

	d_2, d_1, d_0	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Now, we do c_2 :
 $d_2' \cdot d_1' \cdot d_0' \cdot L$
 $d_2' \cdot d_1' \cdot d_0 \cdot L$
 $d_2' \cdot d_1 \cdot d_0' \cdot L$
 $d_2' \cdot d_1 \cdot d_0 \cdot L$
 $d_2 \cdot d_1' \cdot d_0' \cdot L$
 $d_2 \cdot d_1' \cdot d_0 \cdot L$
 No matter what L is, we always say it's 1. So, we don't need L in the expression.
 $c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
 $c_2 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
 $c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' \cdot L' + d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' \cdot L' + d_2 \cdot d_1 \cdot d_0 \cdot L'$


Truth Table to Logic (Part 4)

	d_2, d_1, d_0	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' \cdot L' + d_2 \cdot d_1' \cdot d_0 \cdot L'$
 $c_2 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
 $c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
 Finally, we do c_0 :
 $d_2 \cdot d_1' \cdot d_0' \cdot L'$
 $d_2 \cdot d_1' \cdot d_0'$
 $d_2 \cdot d_1' \cdot d_0$


Truth Table to Logic (Part 4)

$c_0 = d_2 \cdot d_1' \cdot d_0' \cdot L' + d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' \cdot L'$
 $c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' \cdot L' + d_2 \cdot d_1' \cdot d_0 \cdot L'$
 $c_2 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
 $c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$

 

CSE 311: Foundations of Computing

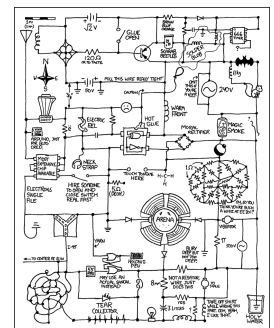
Lecture 4: Boolean Algebra, Circuits, Canonical Forms



1-bit Binary Adder


A	0 + 0 = 0 (with $C_{OUT} = 0$)
+ B	0 + 1 = 1 (with $C_{OUT} = 0$)
S	1 + 0 = 1 (with $C_{OUT} = 0$)
(C_{OUT})	1 + 1 = 0 (with $C_{OUT} = 1$)

 Idea: To chain these together, let's add a carry-in



1-bit Binary Adder

 - Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out




A	B	C_{IN}	C_{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



1-bit Binary Adder

 - Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out




A	B	C_{IN}	C_{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Derive an expression for S

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

1-bit Binary Adder

 - Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out




A	B	C_{IN}	C_{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Derive an expression for C_{OUT}

$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

1-bit Binary Adder

 - Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out



A	B	C_{IN}	C_{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$


Apply Theorems to Simplify Expressions

- The theorems of Boolean algebra can simplify expressions
- e.g., full adder's carry-out function

$$\begin{aligned} C_{out} &= A' B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= A' B C_{in} + A B' C_{in} + A B C_{in}' + \boxed{A B C_{in}} + A B C_{in} \\ &= A' B C_{in} + A B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= (A' + A) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= (1) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A B' C_{in} + A B C_{in}' + \boxed{A B C_{in}} + A B C_{in} \\ &= B C_{in} + A B' C_{in} + A B C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A (B' + B) C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A (1) C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A C_{in} + A B (C_{in}' + C_{in}) \\ &= B C_{in} + A C_{in} + A B (1) \\ &= B C_{in} + A C_{in} + A B \end{aligned}$$

adding extra terms creates new factoring opportunities

A 2-bit Ripple-Carry Adder

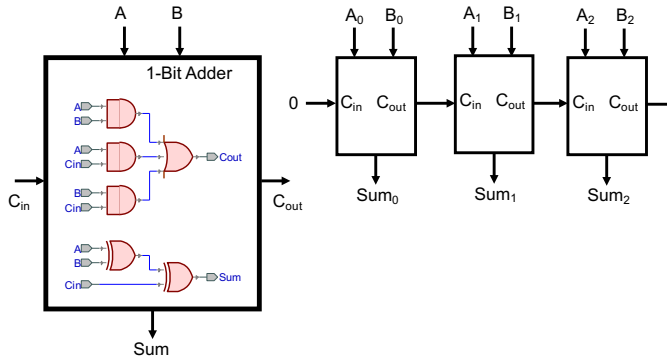

Mapping Truth Tables to Logic Gates

Given a truth table:

1. Write the Boolean expression
2. Minimize the Boolean expression
3. Draw as gates
4. Map to available gates

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$\begin{aligned}
 F &= A'BC' + A'BC + AB'C + ABC \\
 &= A'B(C'+C) + AC(B'+B) \\
 &= A'B + AC
 \end{aligned}$$

