



# CSE 311 Lecture 04: Boolean Algebra

Emina Torlak and Kevin Zatloukal

# Topics

## Equivalence and proofs

A brief review of [Lecture 03](#).

## Boolean algebra

A notation for combinational circuits.

## Simplification and proofs

Optimizing circuits and proving theorems.


# Equivalence and proofs

A brief review of [Lecture 03](#).

# Equivalence via truth tables and proofs

$A \equiv B$  is an **assertion** that two propositions  $A$  and  $B$  have the same truth values in all possible cases.

$A \equiv B$  and  $(A \leftrightarrow B) \equiv \text{T}$  have the same meaning.

  
tautology

**Checking equivalence has many real-world applications.**

Verification, optimization, and more!

**There are two ways to check equivalence of propositional formulas.**

Brute-force: compare their truth tables.

Proof-based: apply equivalences to transform one into the other.

# Boolean algebra

A notation for combinational circuits.

# Recall the relationship between logic and circuits ...

Digital circuits implement propositional logic:

- T corresponds to 1 or high voltage.
- F corresponds to 0 or low voltage.

Digital circuits are functions that

- take values 0/1 as inputs and produce 0/1 as output;
- $out = F(input)$ , where  $F$  is built out of wires and gates; and
- every bit of output is computed from some bits of the input.

# Recall the relationship between logic and circuits ...

Digital circuits implement propositional logic:

- T corresponds to 1 or high voltage.
- F corresponds to 0 or low voltage.

Digital circuits are functions that

- take values 0/1 as inputs and produce 0/1 as output;
- $out = F(input)$ , where  $F$  is built out of wires and gates; and
- every bit of output is computed from some bits of the input.

We call these types of digital circuits *combinational logic circuits*.

There are other kinds of digital circuits (called *sequential circuits*) but we'll focus on combinational circuits in this course.

# Boolean algebra is a notation for combinational logic

Think of it as a notation for propositional logic used in circuit design.

Boolean algebra consists of the following elements and operations:

- a set of elements  $B = \{0, 1\}$ ,
- binary operations  $\{+, \cdot\}$ ,
- a unary operation  $\{ '\}$ .

These correspond to the truth values  $\{F, T\}$ , and the logical connectives  $\vee, \wedge, \neg$ .



# Boolean algebra is a notation for combinational logic

Think of it as a notation for propositional logic used in circuit design.

Boolean algebra consists of the following elements and operations:

- a set of elements  $B = \{0, 1\}$ ,
- binary operations  $\{+, \cdot\}$ ,
- a unary operation  $\{ '\}$ .

These correspond to the truth values  $\{F, T\}$ , and the logical connectives  $\vee, \wedge, \neg$ .

Boolean operations satisfy the following axioms for any  $a, b, c \in B$ :

## Closure

$$a + b \in B$$

$$a \cdot b \in B$$

## Commutativity

$$a + b = b + a$$

$$a \cdot b = b \cdot a$$

## Associativity

$$a + (b + c) = (a + b) + c$$

$$a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

## Distributivity

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

## Identity

$$a + 0 = a$$

$$a \cdot 1 = a$$

## Complementarity

$$a + a' = 1$$

$$a \cdot a' = 0$$

## Null

$$a + 1 = 1$$

$$a \cdot 0 = 0$$

## Idempotency

$$a + a = a$$

$$a \cdot a = a$$

## Involution

$$(a')' = a$$

## Example: from **spec** to code to logic to circuits

Suppose that we want to compute the number of lectures or sections remaining *at the start* of a given day of the week.

## Example: from **spec** to code to logic to circuits

Suppose that we want to compute the number of lectures or sections remaining *at the start* of a given day of the week.

The function for this computation has the following signature:

- **Inputs:** day of the week (integers from 0 to 6), lecture flag (boolean).
- **Output:** number of sessions left (integer from 0 to 3).

# Example: from **spec** to code to logic to circuits

Suppose that we want to compute the number of lectures or sections remaining *at the start* of a given day of the week.

The function for this computation has the following signature:

- **Inputs:** day of the week (integers from 0 to 6), lecture flag (boolean).
- **Output:** number of sessions left (integer from 0 to 3).

Here are some examples of the function's input/output behavior:

- Input: (Wednesday, Lecture), Output: 2
- Input: (Monday, Section), Output: 1

How would you implement this function in Java?

# From spec to code ...

```
public class Sessions {  
  
    public static int classesLeft(int day, boolean lecture) {  
        switch (day) {  
            case 0: // SUNDAY  
            case 1: // MONDAY  
                return lecture ? 3 : 1;  
            case 2: // TUESDAY  
            case 3: // WEDNESDAY  
                return lecture ? 2 : 1;  
            case 4: // THURSDAY  
                return lecture ? 1 : 1;  
            case 5: // FRIDAY  
                return lecture ? 1 : 0;  
            default: //case 6: // SATURDAY  
                return lecture ? 0 : 0;  
        }  
    }  
  
    public static void main(String []args){  
        System.out.println("(W, L) -> " + classesLeft(3,true));  
        System.out.println("(M, S) -> " + classesLeft(1,false));  
    }  
}
```

# From spec to **code** ...

```
public class Sessions {  
  
    public static int classesLeft(int day, boolean lecture) {  
        switch (day) {  
            case 0: // SUNDAY  
            case 1: // MONDAY  
                return lecture ? 3 : 1;  
            case 2: // TUESDAY  
            case 3: // WEDNESDAY  
                return lecture ? 2 : 1;  
            case 4: // THURSDAY  
                return lecture ? 1 : 1;  
            case 5: // FRIDAY  
                return lecture ? 1 : 0;  
            default: //case 6: // SATURDAY  
                return lecture ? 0 : 0;  
        }  
    }  
  
    public static void main(String []args){  
        System.out.println("(W, L) -> " + classesLeft(3,true));  
        System.out.println("(M, S) -> " + classesLeft(1,false));  
    }  
}
```

Suppose that we need this function run *really* fast ...

# From spec to **code** ...

```
public class Sessions {  
  
    public static int classesLeft(int day, boolean lecture) {  
        switch (day) {  
            case 0: // SUNDAY  
            case 1: // MONDAY  
                return lecture ? 3 : 1;  
            case 2: // TUESDAY  
            case 3: // WEDNESDAY  
                return lecture ? 2 : 1;  
            case 4: // THURSDAY  
                return lecture ? 1 : 1;  
            case 5: // FRIDAY  
                return lecture ? 1 : 0;  
            default: //case 6: // SATURDAY  
                return lecture ? 0 : 0;  
        }  
    }  
  
    public static void main(String []args){  
        System.out.println("(W, L) -> " + classesLeft(3,true));  
        System.out.println("(M, S) -> " + classesLeft(1,false));  
    }  
}
```

Suppose that we need this function run *really* fast ... To do that, we'll implement a custom circuit (hardware accelerator!).

# From code to combinational logic ...

Recall the signature of our function:

- **Inputs:** day of the week (integers from 0 to 6), lecture flag (boolean).
- **Output:** number of sessions left (integer from 0 to 3).

How many bits for each input/output?




# From code to combinational logic ...

Recall the signature of our function:

- **Inputs:** day of the week (integers from 0 to 6), lecture flag (boolean).
- **Output:** number of sessions left (integer from 0 to 3).


How many bits for each input/output?

 - **Inputs:** 3 bits for day of the week, 1 bit for the lecture flag.
- **Output:** 2 bits for the number of sessions left.


 
# From code to combinational logic via a truth table


```
switch (day) {  
  case 0: // SUNDAY  
  case 1: // MONDAY  
    return lecture ? 3 : 1;  
  case 2: // TUESDAY  
  case 3: // WEDNESDAY  
    return lecture ? 2 : 1;  
  case 4: // THURSDAY  
    return lecture ? 1 : 1;  
  case 5: // FRIDAY  
    return lecture ? 1 : 0;  
  default: // SATURDAY etc.  
    return lecture ? 0 : 0;  
}
```



Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	
SUN	000	1	
MON	001	0	
MON	001	1	
TUE	010	0	
TUE	010	1	
WED	011	0	
WED	011	1	
THU	100	0	
THU	100	1	
FRI	101	0	
FRI	101	1	
SAT	110	0	
SAT	110	1	
-	111	0	
-	111	1	
 
# From code to combinational logic via a truth table


```
switch (day) {  
  case 0: // SUNDAY  
  case 1: // MONDAY  
    return lecture ? 3 : 1;  
  case 2: // TUESDAY  
  case 3: // WEDNESDAY  
    return lecture ? 2 : 1;  
  case 4: // THURSDAY  
    return lecture ? 1 : 1;  
  case 5: // FRIDAY  
    return lecture ? 1 : 0;  
  default: // SATURDAY etc.  
    return lecture ? 0 : 0;  
}
```



Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	
MON	001	1	
TUE	010	0	
TUE	010	1	
WED	011	0	
WED	011	1	
THU	100	0	
THU	100	1	
FRI	101	0	
FRI	101	1	
SAT	110	0	
SAT	110	1	
-	111	0	
-	111	1	
 
# From code to combinational logic via a truth table


```
switch (day) {  
  case 0: // SUNDAY  
  case 1: // MONDAY  
    return lecture ? 3 : 1;  
  case 2: // TUESDAY  
  case 3: // WEDNESDAY  
    return lecture ? 2 : 1;  
  case 4: // THURSDAY  
    return lecture ? 1 : 1;  
  case 5: // FRIDAY  
    return lecture ? 1 : 0;  
  default: // SATURDAY etc.  
    return lecture ? 0 : 0;  
}
```



Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	
TUE	010	1	
WED	011	0	
WED	011	1	
THU	100	0	
THU	100	1	
FRI	101	0	
FRI	101	1	
SAT	110	0	
SAT	110	1	
-	111	0	
-	111	1	
 
# From code to combinational logic via a truth table


```
switch (day) {  
  case 0: // SUNDAY  
  case 1: // MONDAY  
    return lecture ? 3 : 1;  
  case 2: // TUESDAY  
  case 3: // WEDNESDAY  
    return lecture ? 2 : 1;  
  case 4: // THURSDAY  
    return lecture ? 1 : 1;  
  case 5: // FRIDAY  
    return lecture ? 1 : 0;  
  default: // SATURDAY etc.  
    return lecture ? 0 : 0;  
}
```



Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	
WED	011	1	
THU	100	0	
THU	100	1	
FRI	101	0	
FRI	101	1	
SAT	110	0	
SAT	110	1	
-	111	0	
-	111	1	
 
# From code to combinational logic via a truth table


```
switch (day) {  
  case 0: // SUNDAY  
  case 1: // MONDAY  
    return lecture ? 3 : 1;  
  case 2: // TUESDAY  
  case 3: // WEDNESDAY  
    return lecture ? 2 : 1;  
  case 4: // THURSDAY  
    return lecture ? 1 : 1;  
  case 5: // FRIDAY  
    return lecture ? 1 : 0;  
  default: // SATURDAY etc.  
    return lecture ? 0 : 0;  
}
```



Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	
THU	100	1	
FRI	101	0	
FRI	101	1	
SAT	110	0	
SAT	110	1	
-	111	0	
-	111	1	
 
# From code to combinational logic via a truth table


```
switch (day) {  
  case 0: // SUNDAY  
  case 1: // MONDAY  
    return lecture ? 3 : 1;  
  case 2: // TUESDAY  
  case 3: // WEDNESDAY  
    return lecture ? 2 : 1;  
  case 4: // THURSDAY  
    return lecture ? 1 : 1;  
  case 5: // FRIDAY  
    return lecture ? 1 : 0;  
  default: // SATURDAY etc.  
    return lecture ? 0 : 0;  
}
```



Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	
FRI	101	1	
SAT	110	0	
SAT	110	1	
-	111	0	
-	111	1	
 
# From code to combinational logic via a truth table

```
switch (day) {  
  case 0: // SUNDAY  
  case 1: // MONDAY  
    return lecture ? 3 : 1;  
  case 2: // TUESDAY  
  case 3: // WEDNESDAY  
    return lecture ? 2 : 1;  
  case 4: // THURSDAY  
    return lecture ? 1 : 1;  
  case 5: // FRIDAY  
    return lecture ? 1 : 0;  
  default: // SATURDAY etc.  
    return lecture ? 0 : 0;  
}
```




Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	
SAT	110	1	
-	111	0	
-	111	1	


 
# From code to combinational logic via a truth table


```
switch (day) {  
  case 0: // SUNDAY  
  case 1: // MONDAY  
    return lecture ? 3 : 1;  
  case 2: // TUESDAY  
  case 3: // WEDNESDAY  
    return lecture ? 2 : 1;  
  case 4: // THURSDAY  
    return lecture ? 1 : 1;  
  case 5: // FRIDAY  
    return lecture ? 1 : 0;  
  default: // SATURDAY etc.  
    return lecture ? 0 : 0;  
}
```



Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	
-	111	1	
 
# From code to combinational logic via a truth table

```
switch (day) {  
  case 0: // SUNDAY  
  case 1: // MONDAY  
    return lecture ? 3 : 1;  
  case 2: // TUESDAY  
  case 3: // WEDNESDAY  
    return lecture ? 2 : 1;  
  case 4: // THURSDAY  
    return lecture ? 1 : 1;  
  case 5: // FRIDAY  
    return lecture ? 1 : 0;  
  default: // SATURDAY etc.  
    return lecture ? 0 : 0;  
}
```



Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

# From code to **combinational logic** via a truth table: $c_1$

Day	$d_2d_1d_0$	$L$	$c_1c_0$
SUN	000	0	01
<b>SUN</b>	<b>000</b>	<b>1</b>	<b>11</b>
MON	001	0	01
<b>MON</b>	<b>001</b>	<b>1</b>	<b>11</b>
TUE	010	0	01
<b>TUE</b>	<b>010</b>	<b>1</b>	<b>10</b>
WED	011	0	01
<b>WED</b>	<b>011</b>	<b>1</b>	<b>10</b>
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

To find an expression for  $c_1$ , look at the rows where  $c_1 = 1$ .

- $d_2d_1d_0 == 000 \ \&\& \ L == 1$
- $d_2d_1d_0 == 001 \ \&\& \ L == 1$
- $d_2d_1d_0 == 010 \ \&\& \ L == 1$
- $d_2d_1d_0 == 011 \ \&\& \ L == 1$

# From code to **combinational logic** via a truth table: $c_1$

Day	$d_2d_1d_0$	$L$	$c_1c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

To find an expression for  $c_1$ , look at the rows where  $c_1 = 1$ .

- $d_2d_1d_0 == 000 \ \&\& \ L == 1$
- $d_2d_1d_0 == 001 \ \&\& \ L == 1$
- $d_2d_1d_0 == 010 \ \&\& \ L == 1$
- $d_2d_1d_0 == 011 \ \&\& \ L == 1$

Split up the bits of the day to get a formula for each row.

- $d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$
- $d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$
- $d_2 == 0 \ \&\& \ d_1 == 1 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$
- $d_2 == 0 \ \&\& \ d_1 == 1 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$

# From code to **combinational logic** via a truth table: $c_1$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
<b>SUN</b>	<b>000</b>	<b>1</b>	<b>11</b>
MON	001	0	01
<b>MON</b>	<b>001</b>	<b>1</b>	<b>11</b>
TUE	010	0	01
<b>TUE</b>	<b>010</b>	<b>1</b>	<b>10</b>
WED	011	0	01
<b>WED</b>	<b>011</b>	<b>1</b>	<b>10</b>
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

To find an expression for  $c_1$ , look at the rows where  $c_1 = 1$ .

- $d_2 d_1 d_0 == 000 \ \&\& \ L == 1$
- $d_2 d_1 d_0 == 001 \ \&\& \ L == 1$
- $d_2 d_1 d_0 == 010 \ \&\& \ L == 1$
- $d_2 d_1 d_0 == 011 \ \&\& \ L == 1$

Split up the bits of the day to get a formula for each row.

- $d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$
- $d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$
- $d_2 == 0 \ \&\& \ d_1 == 1 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$
- $d_2 == 0 \ \&\& \ d_1 == 1 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$

Translate to Boolean algebra to get an expression for  $c_1$ .

- $d_2' \cdot d_1' \cdot d_0' \cdot L$
- $d_2' \cdot d_1' \cdot d_0 \cdot L$
- $d_2' \cdot d_1 \cdot d_0' \cdot L$
- $d_2' \cdot d_1 \cdot d_0 \cdot L$

# From code to **combinational logic** via a truth table: $c_1$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
<b>SUN</b>	<b>000</b>	<b>1</b>	<b>11</b>
MON	001	0	01
<b>MON</b>	<b>001</b>	<b>1</b>	<b>11</b>
TUE	010	0	01
<b>TUE</b>	<b>010</b>	<b>1</b>	<b>10</b>
WED	011	0	01
<b>WED</b>	<b>011</b>	<b>1</b>	<b>10</b>
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

To find an expression for  $c_1$ , look at the rows where  $c_1 = 1$ .

- $d_2 d_1 d_0 == 000 \ \&\& \ L == 1$
- $d_2 d_1 d_0 == 001 \ \&\& \ L == 1$
- $d_2 d_1 d_0 == 010 \ \&\& \ L == 1$
- $d_2 d_1 d_0 == 011 \ \&\& \ L == 1$

Split up the bits of the day to get a formula for each row.

- $d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$
- $d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$
- $d_2 == 0 \ \&\& \ d_1 == 1 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$
- $d_2 == 0 \ \&\& \ d_1 == 1 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$

Translate to Boolean algebra to get an expression for  $c_1$ .

- $d'_2 \cdot d'_1 \cdot d'_0 \cdot L$
- $d'_2 \cdot d'_1 \cdot d_0 \cdot L$
- $d'_2 \cdot d_1 \cdot d'_0 \cdot L$
- $d'_2 \cdot d_1 \cdot d_0 \cdot L$

$$c_1 = d'_2 \cdot d'_1 \cdot d'_0 \cdot L + d'_2 \cdot d'_1 \cdot d_0 \cdot L + d'_2 \cdot d_1 \cdot d'_0 \cdot L + d'_2 \cdot d_1 \cdot d_0 \cdot L$$

# From code to **combinational logic** via a truth table: $c_0$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L$$

Now we repeat this process to get  $c_0$ .

$$c_0 =$$

# From code to **combinational logic** via a truth table: $c_0$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L$$

Now we repeat this process to get  $c_0$ .

$$c_0 = d_2' \cdot d_1' \cdot d_0' \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0' \cdot L +$$



# From code to **combinational logic** via a truth table: $c_0$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L$$

Now we repeat this process to get  $c_0$ .

$$c_0 = d_2' \cdot d_1' \cdot d_0' \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

# From code to **combinational logic** via a truth table: $c_0$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L$$

Now we repeat this process to get  $c_0$ .

$$c_0 = d_2' \cdot d_1' \cdot d_0' \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L' +$$

# From code to **combinational logic** via a truth table: $c_0$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L$$

Now we repeat this process to get  $c_0$ .

$$c_0 = d_2' \cdot d_1' \cdot d_0' \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L' +$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L' +$$

# From code to **combinational logic** via a truth table: $c_0$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L$$

Now we repeat this process to get  $c_0$ .

$$c_0 = d_2' \cdot d_1' \cdot d_0' \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L' +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L +$$

$$d_2 \cdot d_1' \cdot d_0' \cdot L' +$$

$$d_2 \cdot d_1' \cdot d_0' \cdot L +$$

# From code to **combinational logic** via a truth table: $c_0$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L$$

Now we repeat this process to get  $c_0$ .

$$c_0 = d_2' \cdot d_1' \cdot d_0' \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L' +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L +$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L' +$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L' +$$

$$d_2 \cdot d_1' \cdot d_0' \cdot L' +$$

$$d_2 \cdot d_1' \cdot d_0' \cdot L +$$


$$d_2 \cdot d_1' \cdot d_0 \cdot L$$

# From combinational logic to circuits

$$\begin{aligned}c_0 = & d_2' \cdot d_1' \cdot d_0' \cdot L' + \\ & d_2' \cdot d_1' \cdot d_0' \cdot L + \\ & d_2' \cdot d_1' \cdot d_0 \cdot L' + \\ & d_2' \cdot d_1' \cdot d_0 \cdot L + \\ & d_2' \cdot d_1 \cdot d_0' \cdot L' + \\ & d_2' \cdot d_1 \cdot d_0' \cdot L + \\ & d_2 \cdot d_1' \cdot d_0' \cdot L' + \\ & d_2 \cdot d_1' \cdot d_0' \cdot L + \\ & d_2 \cdot d_1' \cdot d_0 \cdot L\end{aligned}$$

$$\begin{aligned}c_1 = & d_2' \cdot d_1' \cdot d_0' \cdot L + \\ & d_2' \cdot d_1' \cdot d_0 \cdot L + \\ & d_2' \cdot d_1 \cdot d_0' \cdot L + \\ & d_2' \cdot d_1 \cdot d_0 \cdot L\end{aligned}$$

Here is  $c_1$  as a circuit ...

 

# What can we do with the logic encoding?

Create hardware implementations!

And perform program verification ...

**Example: verify that `classesLeft` returns 3 only if `lecture` is true.**

$$\begin{aligned}
 c_0 = & d_2' \cdot d_1' \cdot d_0' \cdot L' + & c_1 = & d_2' \cdot d_1' \cdot d_0' \cdot L + \\
 & d_2' \cdot d_1' \cdot d_0' \cdot L + & & d_2' \cdot d_1' \cdot d_0' \cdot L + \\
 & d_2' \cdot d_1' \cdot d_0 \cdot L' + & & d_2' \cdot d_1 \cdot d_0' \cdot L + \\
 & d_2' \cdot d_1' \cdot d_0 \cdot L + & & d_2' \cdot d_1 \cdot d_0 \cdot L \\
 & d_2' \cdot d_1 \cdot d_0' \cdot L' + & & \\
 & d_2' \cdot d_1 \cdot d_0 \cdot L' + & & \\
 & d_2 \cdot d_1' \cdot d_0' \cdot L' + & & \\
 & d_2 \cdot d_1' \cdot d_0' \cdot L + & & \\
 & d_2 \cdot d_1' \cdot d_0 \cdot L & &
 \end{aligned}$$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00

# What can we do with the logic encoding?

Create hardware implementations!

And perform program verification ...

**Example: verify that `classesLeft` returns 3 only if `lecture` is true.**

Check that  $c_1 \wedge c_0 \rightarrow L \equiv \top$ .

$$\begin{aligned}
 c_0 = & d_2' \cdot d_1' \cdot d_0' \cdot L' + & c_1 = & d_2' \cdot d_1' \cdot d_0' \cdot L + \\
 & d_2' \cdot d_1' \cdot d_0' \cdot L + & & d_2' \cdot d_1' \cdot d_0' \cdot L + \\
 & d_2' \cdot d_1' \cdot d_0 \cdot L' + & & d_2' \cdot d_1 \cdot d_0' \cdot L + \\
 & d_2' \cdot d_1' \cdot d_0 \cdot L + & & d_2' \cdot d_1 \cdot d_0 \cdot L \\
 & d_2' \cdot d_1 \cdot d_0' \cdot L' + & & \\
 & d_2' \cdot d_1 \cdot d_0 \cdot L' + & & \\
 & d_2 \cdot d_1' \cdot d_0' \cdot L' + & & \\
 & d_2 \cdot d_1' \cdot d_0' \cdot L + & & \\
 & d_2 \cdot d_1' \cdot d_0 \cdot L & &
 \end{aligned}$$

Day	$d_2 d_1 d_0$	$L$	$c_1 c_0$
SUN	000	0	01
SUN	000	1	11
MON	001	0	01
MON	001	1	11
TUE	010	0	01
TUE	010	1	10
WED	011	0	01
WED	011	1	10
THU	100	0	01
THU	100	1	01
FRI	101	0	00
FRI	101	1	01
SAT	110	0	00
SAT	110	1	00
-	111	0	00
-	111	1	00



# Simplification and proofs

Optimizing circuits and proving theorems.

# So far, we've used the basics of Boolean algebra ...

Boolean algebra consists of the following elements and operations:

- a set of elements  $B = \{0, 1\}$ ,
- binary operations  $\{+, \cdot\}$ ,
- a unary operation  $\{ '\}$ .

These correspond to the truth values  $\{F, T\}$ , and the logical connectives  $\vee, \wedge, \neg$ .

Boolean operations satisfy the following axioms for any  $a, b, c \in B$ :

## Closure

$$a + b \in B$$

$$a \cdot b \in B$$

## Commutativity

$$a + b = b + a$$

$$a \cdot b = b \cdot a$$

## Associativity

$$a + (b + c) = (a + b) + c$$

$$a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

## Distributivity

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

## Identity

$$a + 0 = a$$

$$a \cdot 1 = a$$

## Complementarity

$$a + a' = 1$$

$$a \cdot a' = 0$$

## Null

$$a + 1 = 1$$

$$a \cdot 0 = 0$$

## Idempotency

$$a + a = a$$

$$a \cdot a = a$$

## Involution

$$(a')' = a$$

# We can use the basics to prove some useful theorems

## Uniting

$$a \cdot b + a \cdot b' = a$$

$$(a + b) \cdot (a + b') = a$$

## Absorption

$$a + a \cdot b = a$$

$$a \cdot (a + b) = a$$

$$(a + b') \cdot b = a \cdot b$$

$$(a \cdot b') + b = a + b$$

## Factoring

$$(a + b) \cdot (a' + c) = a \cdot c + a' \cdot b$$

$$a \cdot b + a' \cdot c = (a + c) \cdot (a' + b)$$

## Consensus

$$(a \cdot b) + (b \cdot c) + (a' \cdot c) = a \cdot b + a' \cdot c$$

$$(a + b) \cdot (b + c) \cdot (a' + c) = (a + b) \cdot (a' + c)$$

## DeMorgan's

$$(a + b + \dots)' = a' \cdot b' \cdot \dots$$

$$(a \cdot b \cdot \dots)' = a' + b' + \dots$$

# Example: proving theorems using the axioms

Uniting

$$\begin{aligned} X \cdot Y + X \cdot Y' &= \\ &= \\ &= X \end{aligned}$$

Absorption

$$\begin{aligned} X + X \cdot Y &= \\ &= \\ &= \\ &= \\ &= X \end{aligned}$$

**Closure**

$$\begin{aligned} a + b &\in B \\ a \cdot b &\in B \end{aligned}$$

**Commutativity**

$$\begin{aligned} a + b &= b + a \\ a \cdot b &= b \cdot a \end{aligned}$$

**Associativity**

$$\begin{aligned} a + (b + c) &= (a + b) + c \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \end{aligned}$$

**Distributivity**

$$\begin{aligned} a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \end{aligned}$$

**Identity**

$$\begin{aligned} a + 0 &= a \\ a \cdot 1 &= a \end{aligned}$$

**Complementarity**

$$\begin{aligned} a + a' &= 1 \\ a \cdot a' &= 0 \end{aligned}$$

**Null**

$$\begin{aligned} a + 1 &= 1 \\ a \cdot 0 &= 0 \end{aligned}$$

**Idempotency**

$$\begin{aligned} a + a &= a \\ a \cdot a &= a \end{aligned}$$

**Involution**

$$(a')' = a$$

# Example: proving theorems using the axioms

Uniting

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') && \text{Distributivity} \\ &= \\ &= X \end{aligned}$$

Absorption

$$\begin{aligned} X + X \cdot Y &= \\ &= \\ &= \\ &= \\ &= X \end{aligned}$$

**Closure**

$$\begin{aligned} a + b &\in B \\ a \cdot b &\in B \end{aligned}$$

**Commutativity**

$$\begin{aligned} a + b &= b + a \\ a \cdot b &= b \cdot a \end{aligned}$$

**Associativity**

$$\begin{aligned} a + (b + c) &= (a + b) + c \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \end{aligned}$$

**Distributivity**

$$\begin{aligned} a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \end{aligned}$$

**Identity**

$$\begin{aligned} a + 0 &= a \\ a \cdot 1 &= a \end{aligned}$$

**Complementarity**

$$\begin{aligned} a + a' &= 1 \\ a \cdot a' &= 0 \end{aligned}$$

**Null**

$$\begin{aligned} a + 1 &= 1 \\ a \cdot 0 &= 0 \end{aligned}$$

**Idempotency**

$$\begin{aligned} a + a &= a \\ a \cdot a &= a \end{aligned}$$

**Involution**

$$(a')' = a$$

# Example: proving theorems using the axioms

Uniting

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') && \text{Distributivity} \\ &= X \cdot 1 && \text{Complementarity} \\ &= X \end{aligned}$$

Absorption

$$\begin{aligned} X + X \cdot Y &= \\ &= \\ &= \\ &= \\ &= X \end{aligned}$$

Closure

$$\begin{aligned} a + b &\in B \\ a \cdot b &\in B \end{aligned}$$

Commutativity

$$\begin{aligned} a + b &= b + a \\ a \cdot b &= b \cdot a \end{aligned}$$

Associativity

$$\begin{aligned} a + (b + c) &= (a + b) + c \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \end{aligned}$$

Distributivity

$$\begin{aligned} a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \end{aligned}$$

Identity

$$\begin{aligned} a + 0 &= a \\ a \cdot 1 &= a \end{aligned}$$

Complementarity

$$\begin{aligned} a + a' &= 1 \\ a \cdot a' &= 0 \end{aligned}$$

Null

$$\begin{aligned} a + 1 &= 1 \\ a \cdot 0 &= 0 \end{aligned}$$

Idempotency

$$\begin{aligned} a + a &= a \\ a \cdot a &= a \end{aligned}$$

Involution

$$(a')' = a$$

# Example: proving theorems using the axioms

Uniting

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') && \text{Distributivity} \\ &= X \cdot 1 && \text{Complementarity} \\ &= X && \text{Identity} \end{aligned}$$

Absorption

$$\begin{aligned} X + X \cdot Y &= \\ &= \\ &= \\ &= \\ &= X \end{aligned}$$

Closure

$$\begin{aligned} a + b &\in B \\ a \cdot b &\in B \end{aligned}$$

Commutativity

$$\begin{aligned} a + b &= b + a \\ a \cdot b &= b \cdot a \end{aligned}$$

Associativity

$$\begin{aligned} a + (b + c) &= (a + b) + c \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \end{aligned}$$

Distributivity

$$\begin{aligned} a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \end{aligned}$$

Identity

$$\begin{aligned} a + 0 &= a \\ a \cdot 1 &= a \end{aligned}$$

Complementarity

$$\begin{aligned} a + a' &= 1 \\ a \cdot a' &= 0 \end{aligned}$$

Null

$$\begin{aligned} a + 1 &= 1 \\ a \cdot 0 &= 0 \end{aligned}$$

Idempotency

$$\begin{aligned} a + a &= a \\ a \cdot a &= a \end{aligned}$$

Involution

$$(a')' = a$$

# Example: proving theorems using the axioms

Uniting

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') && \text{Distributivity} \\ &= X \cdot 1 && \text{Complementarity} \\ &= X && \text{Identity} \end{aligned}$$

Absorption

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y && \text{Identity} \\ &= \\ &= \\ &= \\ &= X \end{aligned}$$

Closure

$$\begin{aligned} a + b &\in B \\ a \cdot b &\in B \end{aligned}$$

Commutativity

$$\begin{aligned} a + b &= b + a \\ a \cdot b &= b \cdot a \end{aligned}$$

Associativity

$$\begin{aligned} a + (b + c) &= (a + b) + c \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \end{aligned}$$

Distributivity

$$\begin{aligned} a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \end{aligned}$$

Identity

$$\begin{aligned} a + 0 &= a \\ a \cdot 1 &= a \end{aligned}$$

Complementarity

$$\begin{aligned} a + a' &= 1 \\ a \cdot a' &= 0 \end{aligned}$$

Null

$$\begin{aligned} a + 1 &= 1 \\ a \cdot 0 &= 0 \end{aligned}$$

Idempotency

$$\begin{aligned} a + a &= a \\ a \cdot a &= a \end{aligned}$$

Involution

$$(a')' = a$$



# Example: proving theorems using the axioms

Uniting

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') && \text{Distributivity} \\ &= X \cdot 1 && \text{Complementarity} \\ &= X && \text{Identity} \end{aligned}$$

Absorption

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y && \text{Identity} \\ &= X \cdot (1 + Y) && \text{Distributivity} \\ &= \\ &= \\ &= X \end{aligned}$$

Closure

$$\begin{aligned} a + b &\in B \\ a \cdot b &\in B \end{aligned}$$

Commutativity

$$\begin{aligned} a + b &= b + a \\ a \cdot b &= b \cdot a \end{aligned}$$

Associativity

$$\begin{aligned} a + (b + c) &= (a + b) + c \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \end{aligned}$$

Distributivity

$$\begin{aligned} a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \end{aligned}$$

Identity

$$\begin{aligned} a + 0 &= a \\ a \cdot 1 &= a \end{aligned}$$

Complementarity

$$\begin{aligned} a + a' &= 1 \\ a \cdot a' &= 0 \end{aligned}$$

Null

$$\begin{aligned} a + 1 &= 1 \\ a \cdot 0 &= 0 \end{aligned}$$

Idempotency

$$\begin{aligned} a + a &= a \\ a \cdot a &= a \end{aligned}$$

Involution

$$(a')' = a$$

# Example: proving theorems using the axioms

Uniting

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') && \text{Distributivity} \\ &= X \cdot 1 && \text{Complementarity} \\ &= X && \text{Identity} \end{aligned}$$

Absorption

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y && \text{Identity} \\ &= X \cdot (1 + Y) && \text{Distributivity} \\ &= X \cdot (Y + 1) && \text{Commutativity} \\ &= && \\ &= X && \end{aligned}$$

Closure

$$\begin{aligned} a + b &\in B \\ a \cdot b &\in B \end{aligned}$$

Distributivity

$$\begin{aligned} a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \end{aligned}$$

Null

$$\begin{aligned} a + 1 &= 1 \\ a \cdot 0 &= 0 \end{aligned}$$

Commutativity

$$\begin{aligned} a + b &= b + a \\ a \cdot b &= b \cdot a \end{aligned}$$

Identity

$$\begin{aligned} a + 0 &= a \\ a \cdot 1 &= a \end{aligned}$$

Idempotency

$$\begin{aligned} a + a &= a \\ a \cdot a &= a \end{aligned}$$

Associativity

$$\begin{aligned} a + (b + c) &= (a + b) + c \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \end{aligned}$$

Complementarity

$$\begin{aligned} a + a' &= 1 \\ a \cdot a' &= 0 \end{aligned}$$

Involution

$$(a')' = a$$

# Example: proving theorems using the axioms

Uniting

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') && \text{Distributivity} \\ &= X \cdot 1 && \text{Complementarity} \\ &= X && \text{Identity} \end{aligned}$$

Absorption

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y && \text{Identity} \\ &= X \cdot (1 + Y) && \text{Distributivity} \\ &= X \cdot (Y + 1) && \text{Commutativity} \\ &= X \cdot 1 && \text{Null} \\ &= X \end{aligned}$$

Closure

$$\begin{aligned} a + b &\in B \\ a \cdot b &\in B \end{aligned}$$

Distributivity

$$\begin{aligned} a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \end{aligned}$$

Null

$$\begin{aligned} a + 1 &= 1 \\ a \cdot 0 &= 0 \end{aligned}$$

Commutativity

$$\begin{aligned} a + b &= b + a \\ a \cdot b &= b \cdot a \end{aligned}$$

Identity

$$\begin{aligned} a + 0 &= a \\ a \cdot 1 &= a \end{aligned}$$

Idempotency

$$\begin{aligned} a + a &= a \\ a \cdot a &= a \end{aligned}$$

Associativity

$$\begin{aligned} a + (b + c) &= (a + b) + c \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \end{aligned}$$

Complementarity

$$\begin{aligned} a + a' &= 1 \\ a \cdot a' &= 0 \end{aligned}$$

Involution

$$(a')' = a$$

# Example: proving theorems using the axioms

Uniting

$$\begin{aligned}
 X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') && \text{Distributivity} \\
 &= X \cdot 1 && \text{Complementarity} \\
 &= X && \text{Identity}
 \end{aligned}$$

Absorption

$$\begin{aligned}
 X + X \cdot Y &= X \cdot 1 + X \cdot Y && \text{Identity} \\
 &= X \cdot (1 + Y) && \text{Distributivity} \\
 &= X \cdot (Y + 1) && \text{Commutativity} \\
 &= X \cdot 1 && \text{Null} \\
 &= X && \text{Identity}
 \end{aligned}$$

Closure

$$\begin{aligned}
 a + b &\in B \\
 a \cdot b &\in B
 \end{aligned}$$

Distributivity

$$\begin{aligned}
 a + (b \cdot c) &= (a + b) \cdot (a + c) \\
 a \cdot (b + c) &= (a \cdot b) + (a \cdot c)
 \end{aligned}$$

Null

$$\begin{aligned}
 a + 1 &= 1 \\
 a \cdot 0 &= 0
 \end{aligned}$$

Commutativity

$$\begin{aligned}
 a + b &= b + a \\
 a \cdot b &= b \cdot a
 \end{aligned}$$

Identity

$$\begin{aligned}
 a + 0 &= a \\
 a \cdot 1 &= a
 \end{aligned}$$

Idempotency

$$\begin{aligned}
 a + a &= a \\
 a \cdot a &= a
 \end{aligned}$$

Associativity

$$\begin{aligned}
 a + (b + c) &= (a + b) + c \\
 a \cdot (b \cdot c) &= (a \cdot b) \cdot c
 \end{aligned}$$

Complementarity

$$\begin{aligned}
 a + a' &= 1 \\
 a \cdot a' &= 0
 \end{aligned}$$

Involution

$$(a')' = a$$

# Example: proving theorems using truth tables

## DeMorgan's law

$$(X + Y)' = X' \cdot Y'$$

NOR is equivalent to AND with inputs complemented

$X$	$Y$	$X'$	$Y'$	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

## DeMorgan's law

$$(X \cdot Y)' = X' + Y'$$

NAND is equivalent to OR with inputs complemented

$X$	$Y$	$X'$	$Y'$	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

# Example: simplifying (circuits) using Boolean algebra

$$\begin{aligned}c_1 &= d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L + d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L && \text{(from classesLeft)} \\ &= \dots && \text{(HW2)} \\ &= d_2' \cdot L && \text{(HW2)}\end{aligned}$$

## Closure

$$\begin{aligned}a + b &\in B \\ a \cdot b &\in B\end{aligned}$$

## Commutativity

$$\begin{aligned}a + b &= b + a \\ a \cdot b &= b \cdot a\end{aligned}$$

## Associativity

$$\begin{aligned}a + (b + c) &= (a + b) + c \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c\end{aligned}$$

## Distributivity

$$\begin{aligned}a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c)\end{aligned}$$

## Identity

$$\begin{aligned}a + 0 &= a \\ a \cdot 1 &= a\end{aligned}$$

## Complementarity

$$\begin{aligned}a + a' &= 1 \\ a \cdot a' &= 0\end{aligned}$$

## Null

$$\begin{aligned}a + 1 &= 1 \\ a \cdot 0 &= 0\end{aligned}$$

## Idempotency

$$\begin{aligned}a + a &= a \\ a \cdot a &= a\end{aligned}$$


## Involution

$$(a')' = a$$
 
# Example: simplifying (circuits) using Boolean algebra

$$\begin{aligned}c_1 &= d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L + d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L && \text{(from classesLeft)} \\ &= \dots && \text{(HW2)} \\ &= d_2' \cdot L && \text{(HW2)}\end{aligned}$$

Here is the simplified  $c_1$  circuit ...



# Summary

**Boolean algebra is a notation for combinational circuits.**

It consists of elements  $\{0, 1\}$  and operations  $\{+, \cdot, '\}$ .

The operations satisfy the axioms of Boolean algebra.

**We can translate specs to code to logic and to circuits for faster implementation in hardware, and program verification.**

**We can use axioms of Boolean algebra and truth tables to prove useful theorems, and simplify and optimize combinational circuits.**