 


# CSE 311: Foundations of Computing

---

## Lecture 4: Boolean Algebra, Circuits, Canonical Forms



# Boolean Logic

---

## Combinational Logic

- output =  $F(\text{input})$

## Sequential Logic

- $\text{output}_t = F(\text{output}_{t-1}, \text{input}_t)$ 
  - output dependent on history
  - concept of a time step (clock,  $t$ )




## Boolean Algebra: Another notation for logic consisting of...

- a set of elements  $B = \{0, 1\}$
- binary operations  $\{ + , \cdot \}$  (OR, AND)
- and a unary operation  $\{ ' \}$  (NOT)
 
# Boolean Algebra

---

- Usual notation used in circuit design
- Boolean algebra
  - a set of elements  $B$  containing  $\{0, 1\}$
  - binary operations  $\{ + , \cdot \}$
  - and a unary operation  $\{ ' \}$
  - such that the following axioms hold:



For any  $a, b, c$  in  $B$ :

1. closure:  $a + b$  is in  $B$
2. commutativity:  $a + b = b + a$
3. associativity:  $a + (b + c) = (a + b) + c$
4. distributivity:  $a + (b \cdot c) = (a + b) \cdot (a + c)$
5. identity:  $a + 0 = a$
6. complementarity:  $a + a' = 1$
7. null:  $a + 1 = 1$
8. idempotency:  $a + a = a$
9. involution:  $(a')' = a$

- $a \cdot b$  is in  $B$
- $a \cdot b = b \cdot a$
- $a \cdot (b \cdot c) = (a \cdot b) \cdot c$
- $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
- $a \cdot 1 = a$
- $a \cdot a' = 0$
- $a \cdot 0 = 0$
- $a \cdot a = a$

# A Combinational Logic Example

---

## Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**

Input: (Monday, Section) Output: **1**

# Implementation in Software

---


```
public int classesLeftInMorning(weekday, lecture_flag) {
    switch (weekday) {
        case SUNDAY:
        case MONDAY:
            return lecture_flag ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return lecture_flag ? 2 : 1;
        case THURSDAY:
            return lecture_flag ? 1 : 1;
        case FRIDAY:
            return lecture_flag ? 1 : 0;
        case SATURDAY:
            return lecture_flag ? 0 : 0;
    }
}
```

# Implementation with Combinational Logic

---
 
## Encoding:

- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



# Defining Our Inputs!

---

## Weekday Input:

- Binary number for weekday
- Sunday = 0, Monday = 1, ...
- We care about these in binary:

Weekday	Number	Binary
Sunday	0	$(000)_2$
Monday	1	$(001)_2$
Tuesday	2	$(010)_2$
Wednesday	3	$(011)_2$
Thursday	4	$(100)_2$
Friday	5	$(101)_2$
Saturday	6	$(110)_2$

# Converting to a Truth Table!

---

```
case SUNDAY or MONDAY:
    return lecture_flag ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return lecture_flag ? 2 : 1;
case THURSDAY:
    return lecture_flag ? 1 : 1;
case FRIDAY:
    return lecture_flag ? 1 : 0;
case SATURDAY:
    return lecture_flag ? 0 : 0;
```

Weekday	Lecture?	c <sub>0</sub>	c <sub>1</sub>	c <sub>2</sub>	c <sub>3</sub>
SUN	000	0			
SUN	000	1			
MON	001	0			
MON	001	1			
TUE	010	0			
TUE	010	1			
WED	011	0			
WED	011	1			
THU	100	-			
FRI	101	0			
FRI	101	1			
SAT	110	-			
-	111	-			



# Converting to a Truth Table!

---

```

case SUNDAY or MONDAY:
    return lecture_flag ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return lecture_flag ? 2 : 1;
case THURSDAY:
    return lecture_flag ? 1 : 1;
case FRIDAY:
    return lecture_flag ? 1 : 0;
case SATURDAY:
    return lecture_flag ? 0 : 0;

```

Weekday	Lecture?	c <sub>0</sub>	c <sub>1</sub>	c <sub>2</sub>	c <sub>3</sub>
SUN	000	0	1	0	0
SUN	000	0	0	0	1
MON	001	0	1	0	0
MON	001	0	0	0	1
TUE	010	0	1	0	0
TUE	010	0	0	1	0
WED	011	0	1	0	0
WED	011	0	0	1	0
THU	100	0	1	0	0
FRI	101	1	0	0	0
FRI	101	0	1	0	0
SAT	110	1	0	0	0
-	111	1	0	0	0

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Let's begin by finding an expression for  $c_3$ . To do this, we look at the rows where  $c_3 = 1$  (true).

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

→ DAY == SUN && L == 1

→ DAY == MON && L == 1

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2d_1d_0 == 000 \ \&\& \ L == 1$

$d_2d_1d_0 == 001 \ \&\& \ L == 1$

Substituting DAY for the binary representation.

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$

$d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$

Splitting up the bits of the day;  
so, we can write a formula.

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2' \cdot d_1' \cdot d_0' \cdot L$

$d_2' \cdot d_1' \cdot d_0 \cdot L$

Replacing with  
Boolean Algebra...

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$d_2' \cdot d_1' \cdot d_0' \cdot L$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L$$

Either situation causes  $c_3$  to be true. So, we "or" them.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 2)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Now, we do  $c_2$ .





# Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	→
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	→
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	→
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	→
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	→
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	→
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	???
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

No matter what L is, we always say it's 1. So, we don't need L in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 3)

	$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

No matter what L is, we always say it's 1. So, we don't need L in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 4)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Finally, we do  $c_0$ :

$$d_2 \cdot d_1' \cdot d_0 \cdot L'$$

$$d_2 \cdot d_1 \cdot d_0'$$

$$d_2 \cdot d_1 \cdot d_0$$

# Truth Table to Logic (Part 4)

---


$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Here's  $c_3$  as a circuit:

 

# Boolean Algebra

---

- Usual notation used in circuit design
- Boolean algebra
  - a set of elements  $B$  containing  $\{0, 1\}$
  - binary operations  $\{ + , \cdot \}$
  - and a unary operation  $\{ ' \}$
  - such that the following axioms hold:



For any  $a, b, c$  in  $B$ :

1. closure:

$$a + b \text{ is in } B$$

2. commutativity:

$$a + b = b + a$$

3. associativity:

$$a + (b + c) = (a + b) + c$$

4. distributivity:

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

5. identity:

$$a + 0 = a$$

6. complementarity:

$$a + a' = 1$$

7. null:

$$a + 1 = 1$$

8. idempotency:

$$a + a = a$$

9. involution:

$$(a')' = a$$

$a \cdot b$  is in  $B$

$$a \cdot b = b \cdot a$$

$$a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

$$a \cdot 1 = a$$

$$a \cdot a' = 0$$

$$a \cdot 0 = 0$$

$$a \cdot a = a$$

# Simplification using Boolean Algebra

---

## uniting:

$$10. a \cdot b + a \cdot b' = a$$

$$10D. (a + b) \cdot (a + b') = a$$

## absorption:

$$11. a + a \cdot b = a$$

$$11D. a \cdot (a + b) = a$$

$$12. (a + b') \cdot b = a \cdot b$$

$$12D. (a \cdot b') + b = a + b$$

## factoring:

$$13. (a + b) \cdot (a' + c) = \\ a \cdot c + a' \cdot b$$

$$13D. a \cdot b + a' \cdot c = \\ (a + c) \cdot (a' + b)$$

## consensus:

$$14. (a \cdot b) + (b \cdot c) + (a' \cdot c) = \\ a \cdot b + a' \cdot c$$

$$14D. (a + b) \cdot (b + c) \cdot (a' + c) = \\ (a + b) \cdot (a' + c)$$

## de Morgan's:

$$15. (a + b + \dots)' = a' \cdot b' \cdot \dots$$

$$15D. (a \cdot b \cdot \dots)' = a' + b' + \dots$$



# Proving Theorems

---

- 2. commutativity:
- 3. associativity:
- 4. distributivity:
- 5. identity:
- 6. complementarity:
- 7. null:
- 8. idempotency:
- 9. involution:

$$\begin{aligned}a + b &= b + a \\a + (b + c) &= (a + b) + c \\a + (b \cdot c) &= (a + b) \cdot (a + c) \\a + 0 &= a \\a + a' &= 1 \\a + 1 &= 1 \\a + a &= a \\(a')' &= a\end{aligned}$$

$$\begin{aligned}a \cdot b &= b \cdot a \\a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\a \cdot 1 &= a \\a \cdot a' &= 0 \\a \cdot 0 &= 0 \\a \cdot a &= a\end{aligned}$$

## Using the laws of Boolean Algebra:

prove the Uniting theorem:

$$X \cdot Y + X \cdot Y' = X$$

$$X \cdot Y + X \cdot Y' =$$

prove the Absorption theorem:

$$X + X \cdot Y = X$$

$$X + X \cdot Y =$$

# Proving Theorems

---

2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$$\begin{aligned}a + b &= b + a \\a + (b + c) &= (a + b) + c \\a + (b \cdot c) &= (a + b) \cdot (a + c) \\a + 0 &= a \\a + a' &= 1 \\a + 1 &= 1 \\a + a &= a \\(a')' &= a\end{aligned}$$

$$\begin{aligned}a \cdot b &= b \cdot a \\a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\a \cdot 1 &= a \\a \cdot a' &= 0 \\a \cdot 0 &= 0 \\a \cdot a &= a\end{aligned}$$

## Using the laws of Boolean Algebra:

**prove the Uniting theorem:**

$$X \cdot Y + X \cdot Y' = X$$

distributivity  
complementarity  
identity

$$\begin{aligned}X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\&= X \cdot 1 \\&= X\end{aligned}$$

**prove the theorem:**

$$X + X \cdot Y = X$$

identity  
distributivity  
commutativity  
null  
identity

$$\begin{aligned}X + X \cdot Y &= X \cdot 1 + X \cdot Y \\&= X \cdot (1 + Y) \\&= X \cdot (Y + 1) \\&= X \cdot 1 \\&= X\end{aligned}$$

# Proving Theorems

---

## Using truth table:

For example, de Morgan's Law:

$(X + Y)' = X' \cdot Y'$   
NOR is equivalent to AND  
with inputs complemented

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0


$(X \cdot Y)' = X' + Y'$   
NAND is equivalent to OR  
with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0
 
# Simplifying using Boolean Algebra

---

$$\begin{aligned}c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\ &= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\ &= d2' \cdot d1' \cdot 1 \cdot L \\ &= d2' \cdot d1' \cdot L\end{aligned}$$



# 1-bit Binary Adder

---

A	$0 + 0 = 0$ (with $C_{OUT} = 0$ )
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$ )
S	$1 + 0 = 1$ (with $C_{OUT} = 0$ )
( $C_{OUT}$ )	$1 + 1 = 0$ (with $C_{OUT} = 1$ )

# 1-bit Binary Adder

---

A	$0 + 0 = 0$ (with $C_{OUT} = 0$ )
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$ )
S	$1 + 0 = 1$ (with $C_{OUT} = 0$ )
( $C_{OUT}$ )	$1 + 1 = 0$ (with $C_{OUT} = 1$ )



**Idea: To chain these together, let's add a carry-in**

# 1-bit Binary Adder

---

A	$0 + 0 = 0$ (with $C_{OUT} = 0$ )
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$ )
S	$1 + 0 = 1$ (with $C_{OUT} = 0$ )
( $C_{OUT}$ )	$1 + 1 = 0$ (with $C_{OUT} = 1$ )

  
Idea: To chain these together, let's add a carry-in


 
# 1-bit Binary Adder

---

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out




A	B	C <sub>IN</sub>	C <sub>OUT</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1





 
# 1-bit Binary Adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C <sub>IN</sub>	C <sub>OUT</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Derive an expression for S

 

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$
 
# 1-bit Binary Adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C <sub>IN</sub>	C <sub>OUT</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Derive an expression for C<sub>OUT</sub>


$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

The diagram shows the derivation of the carry-out expression. The truth table is used to identify the conditions where C<sub>OUT</sub> is 1. These conditions are: (A=0, B=1, C<sub>IN</sub>=1), (A=1, B=0, C<sub>IN</sub>=1), (A=1, B=1, C<sub>IN</sub>=0), and (A=1, B=1, C<sub>IN</sub>=1). The corresponding Boolean expressions are: A' · B · C<sub>IN</sub>, A · B' · C<sub>IN</sub>, A · B · C<sub>IN</sub>', and A · B · C<sub>IN</sub>. These are summed to form the final expression for C<sub>OUT</sub>.

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$
 
# 1-bit Binary Adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	$C_{IN}$	$C_{OUT}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

# Apply Theorems to Simplify Expressions

---

The theorems of Boolean algebra can simplify expressions


– e.g., full adder's carry-out function

$$\begin{aligned} \text{Cout} &= A' B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= A' B C_{in} + A B' C_{in} + A B C_{in}' + \boxed{A B C_{in} + A B C_{in}} \\ &= A' B C_{in} + A B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= (A' + A) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= (1) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A B' C_{in} + A B C_{in}' + \boxed{A B C_{in} + A B C_{in}} \\ &= B C_{in} + A B' C_{in} + A B C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A (B' + B) C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A (1) C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A C_{in} + A B (C_{in}' + C_{in}) \\ &= B C_{in} + A C_{in} + A B (1) \\ &= B C_{in} + A C_{in} + A B \end{aligned}$$

adding extra terms  
creates new factoring  
opportunities

# A 2-bit Ripple-Carry Adder

---

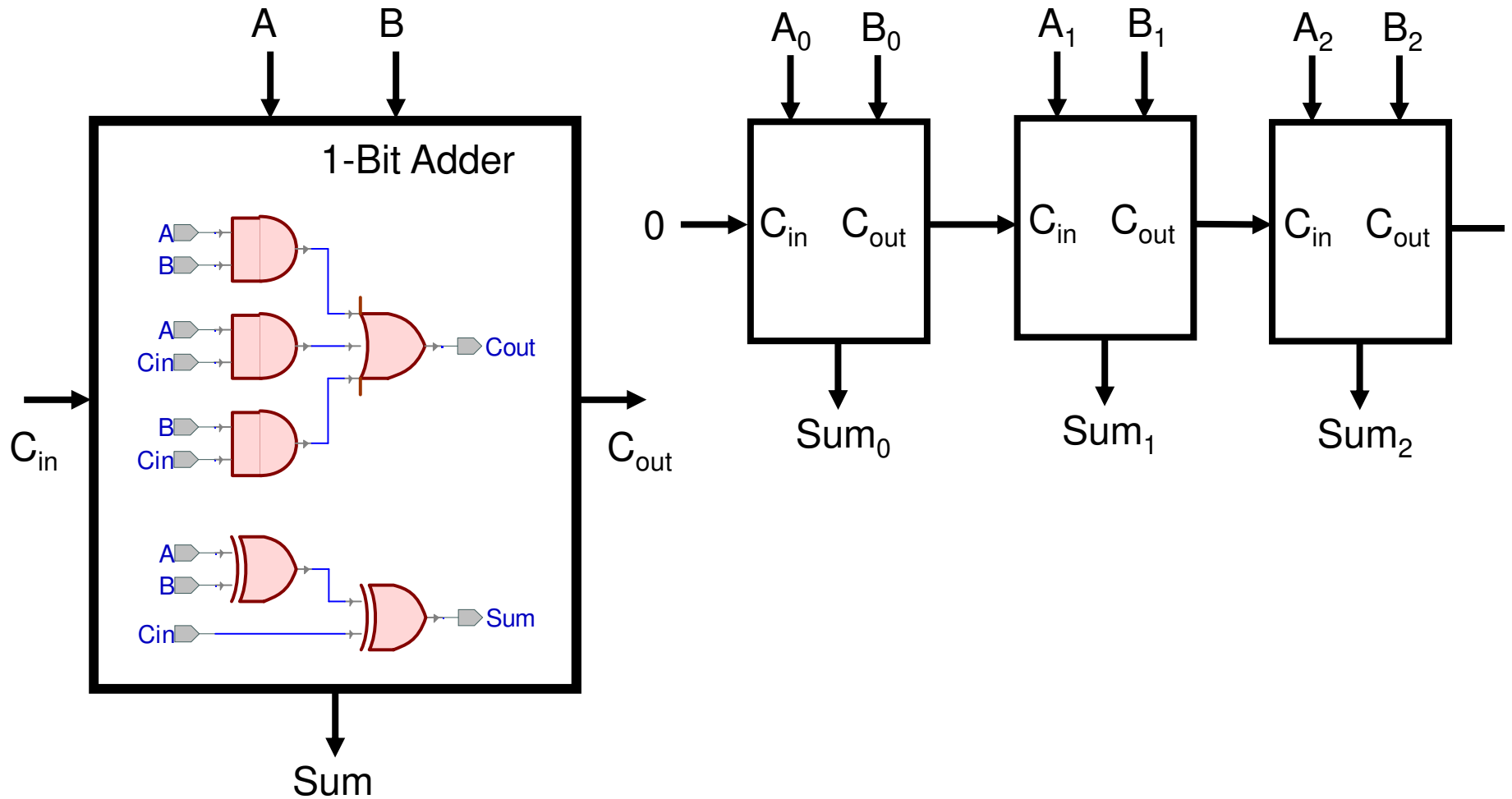

# Mapping Truth Tables to Logic Gates

Given a truth table:

1. Write the Boolean expression
2. Minimize the Boolean expression
3. Draw as gates
4. Map to available gates


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

①


②

$$\begin{aligned} F &= A'BC' + A'BC + AB'C + ABC \\ &= A'B(C' + C) + AC(B' + B) \\ &= A'B + AC \end{aligned}$$

③

 

④

 

# Canonical Forms

---

- **Truth table is the unique signature of a Boolean Function**
- **The same truth table can have many gate realizations**
  - We've seen this already
  - Depends on how good we are at Boolean simplification
- **Canonical forms**
  - Standard forms for a Boolean expression
  - We all come up with the same expression


# Sum-of-Products Canonical Form

- AKA **Disjunctive Normal Form (DNF)**
- AKA **Minterm Expansion**

③

Add the minterms together

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

 



# Sum-of-Products Canonical Form

---

## Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	$A'B'C'$
0	0	1	$A'B'C$
0	1	0	$A'BC'$
0	1	1	$A'BC$
1	0	0	$AB'C'$
1	0	1	$AB'C$
1	1	0	$ABC'$
1	1	1	$ABC$

**F in canonical form:**


$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$$

**canonical form  $\neq$  minimal form**

$$\begin{aligned} F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C \end{aligned}$$

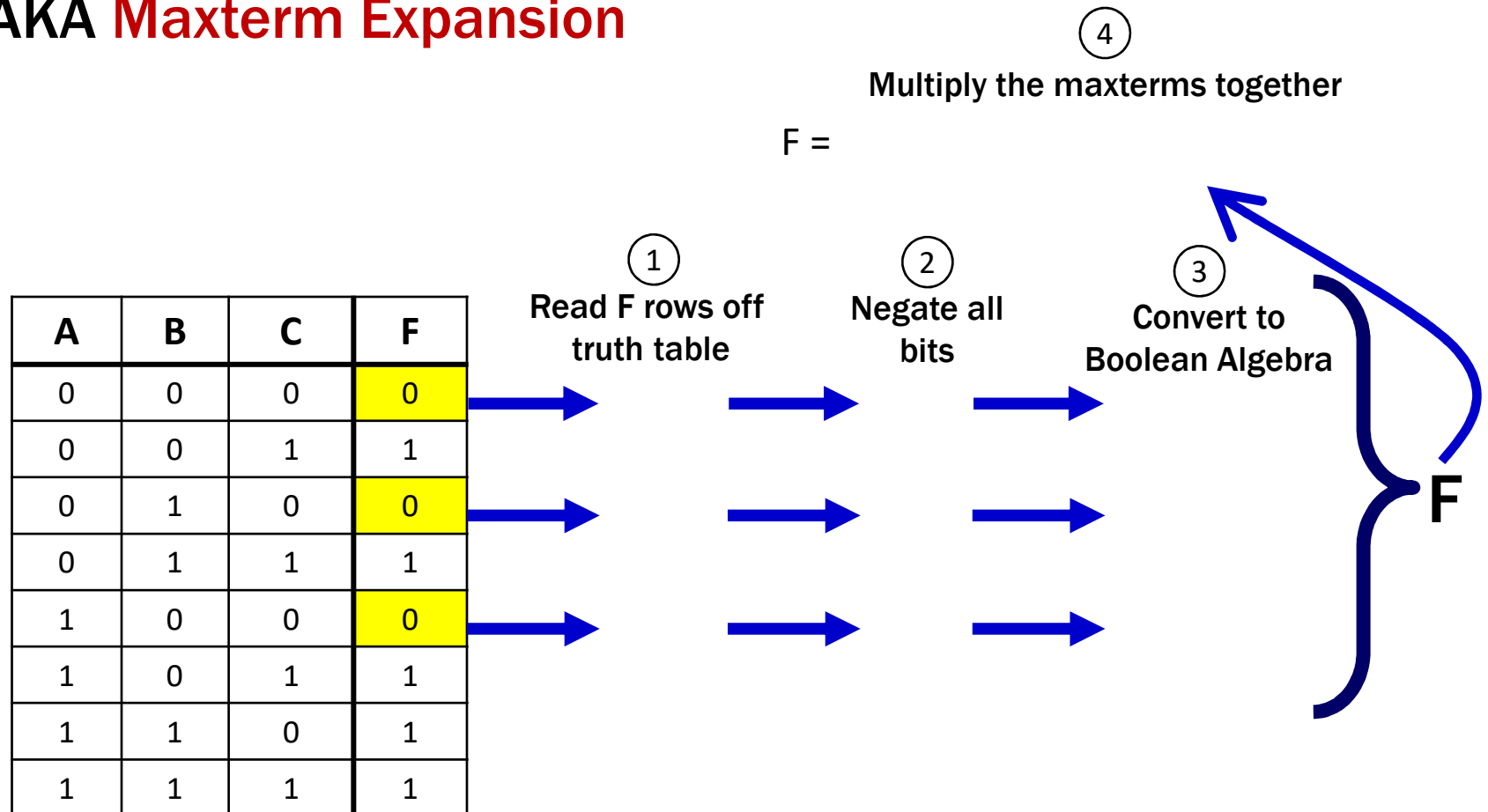
# Product-of-Sums Canonical Form

- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**


 
# Product-of-Sums Canonical Form

- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**




# Product-of-Sums: Why does this procedure work?

---

## Useful Facts:

- We know  $(F')' = F$
- We know how to get a minterm expansion for  $F'$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

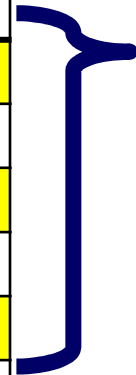
$$F' = A'B'C' + A'BC' + AB'C'$$

# Product-of-Sums: Why does this procedure work?

---

## Useful Facts:

- We know  $(F')' = F$
- We know how to get a minterm expansion for  $F'$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


$$F' = A'B'C' + A'BC' + AB'C'$$

Taking the complement of both sides...

$$(F')' = (A'B'C' + A'BC' + AB'C')'$$

And using DeMorgan/Comp....

$$F = (A'B'C')' (A'BC')' (AB'C')'$$

$$F = (A + B + C)(A + B' + C)(A' + B + C)$$

# Product-of-Sums Canonical Form

---

## Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms
0	0	0	$A+B+C$
0	0	1	$A+B+C'$
0	1	0	$A+B'+C$
0	1	1	$A+B'+C'$
1	0	0	$A'+B+C$
1	0	1	$A'+B+C'$
1	1	0	$A'+B'+C$
1	1	1	$A'+B'+C'$

**F in canonical form:**

$$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$$

**canonical form  $\neq$  minimal form**

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$