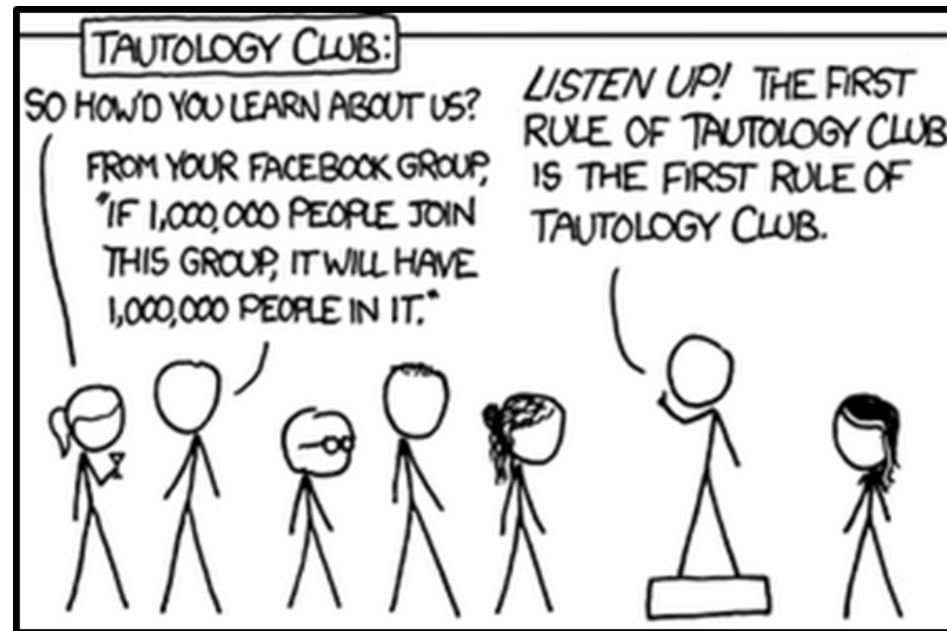


CSE 311: Foundations of Computing

Lecture 4: Boolean Algebra, Circuits, Canonical Forms



Boolean Logic

Combinational Logic

- output = $F(\text{input})$

Sequential Logic

- $\text{output}_t = F(\text{output}_{t-1}, \text{input}_t)$
 - output dependent on history
 - concept of a time step (clock, t)




Boolean Algebra: Another notation for logic consisting of...

- a set of elements $B = \{0, 1\}$
- binary operations $\{ + , \cdot \}$ (OR, AND)
- and a unary operation $\{ ' \}$ (NOT)

Boolean Algebra

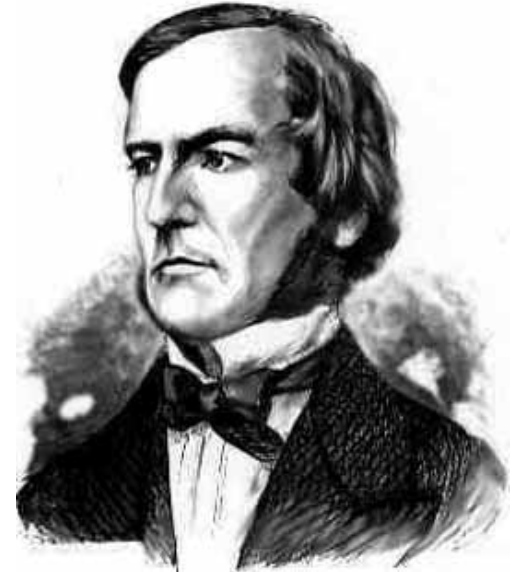- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing $\{0, 1\}$
 - binary operations $\{ + , \cdot \}$
 - and a unary operation $\{ ' \}$
 - such that the following axioms hold:



For any a, b, c in B :

- | | |
|---------------------|---|
| 1. closure: | $a + b$ is in B |
| 2. commutativity: | $a + b = b + a$ |
| 3. associativity: | $a + (b + c) = (a + b) + c$ |
| 4. distributivity: | $a + (b \cdot c) = (a + b) \cdot (a + c)$ |
| 5. identity: | $a + 0 = a$ |
| 6. complementarity: | $a + a' = 1$ |
| 7. null: | $a + 1 = 1$ |
| 8. idempotency: | $a + a = a$ |
| 9. involution: | $(a')' = a$ |

- | |
|---|
| $a \cdot b$ is in B |
| $a \cdot b = b \cdot a$ |
| $a \cdot (b \cdot c) = (a \cdot b) \cdot c$ |
| $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$ |
| $a \cdot 1 = a$ |
| $a \cdot a' = 0$ |
| $a \cdot 0 = 0$ |
| $a \cdot a = a$ |

A Combinational Logic Example

Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**

Input: (Monday, Section) Output: **1**


Implementation in Software

```
public int classesLeftInMorning(weekday, lecture_flag) {
    switch (weekday) {
        case SUNDAY:
        case MONDAY:
            return lecture_flag ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return lecture_flag ? 2 : 1;
        case THURSDAY:
            return lecture_flag ? 1 : 1;
        case FRIDAY:
            return lecture_flag ? 1 : 0;
        case SATURDAY:
            return lecture_flag ? 0 : 0;
    }
}
```

Implementation with Combinational Logic

Encoding:

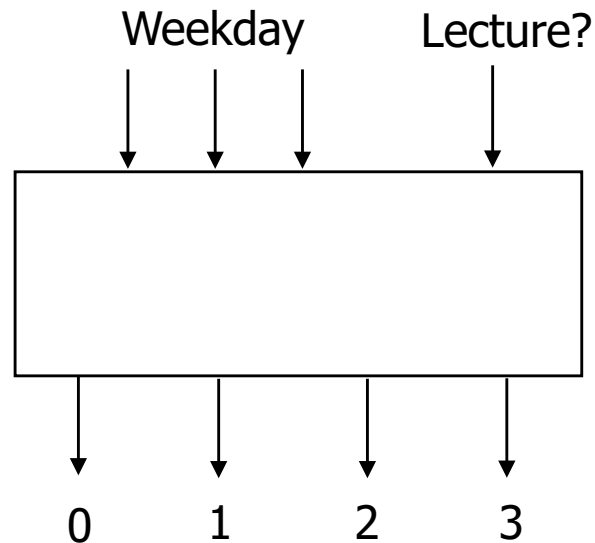- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



Defining Our Inputs!

Weekday Input:

- Binary number for weekday
- Sunday = 0, Monday = **1**, ...
- We care about these in binary:

Weekday	Number	Binary
Sunday	0	$(000)_2$
Monday	1	$(001)_2$
Tuesday	2	$(010)_2$
Wednesday	3	$(011)_2$
Thursday	4	$(100)_2$
Friday	5	$(101)_2$
Saturday	6	$(110)_2$

Converting to a Truth Table!

```
case SUNDAY or MONDAY:
    return lecture_flag ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return lecture_flag ? 2 : 1;
case THURSDAY:
    return lecture_flag ? 1 : 1;
case FRIDAY:
    return lecture_flag ? 1 : 0;
case SATURDAY:
    return lecture_flag ? 0 : 0;
```

	Weekday	Lecture?	c₀	c₁	c₂	c₃
	SUN	000	0			
	SUN	000	1			
	MON	001	0			
	MON	001	1			
	TUE	010	0			
	TUE	010	1			
	WED	011	0			
	WED	011	1			
	THU	100	-			
	FRI	101	0			
	FRI	101	1			
	SAT	110	-			
	-	111	-			

Converting to a Truth Table!

```
case SUNDAY or MONDAY:
    return lecture_flag ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return lecture_flag ? 2 : 1;
case THURSDAY:
    return lecture_flag ? 1 : 1;
case FRIDAY:
    return lecture_flag ? 1 : 0;
case SATURDAY:
    return lecture_flag ? 0 : 0;
```

Weekday		Lecture?	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0


Truth Table to Logic (Part 1)


	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Let's begin by finding an expression for c_3 . To do this, we look at the rows where $c_3 = 1$ (true).

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

 DAY == SUN && L == 1

 DAY == MON && L == 1

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2d_1d_0 == 000 \ \&\& \ L == 1$

$d_2d_1d_0 == 001 \ \&\& \ L == 1$

Substituting DAY for the binary representation.

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$

$d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$

Splitting up the bits of the day;
so, we can write a formula.

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$d_2' \cdot d_1' \cdot d_0' \cdot L$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L$$

Replacing with
Boolean Algebra...

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$\rightarrow d_2' \cdot d_1' \cdot d_0' \cdot L$$

$$\rightarrow d_2' \cdot d_1' \cdot d_0 \cdot L$$

Either situation causes c_3 to be true. So, we "or" them.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Truth Table to Logic (Part 2)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Now, we do c_2 .



Truth Table to Logic (Part 3)

Now, we do c_1 :

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	???
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do c_1 :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do c_1 :

No matter what L is, we always say it's 1. So, we don't need L in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do c_1 :

No matter what L is, we always say it's 1. So, we don't need L in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

Truth Table to Logic (Part 4)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Finally, we do c_0 :

→ $d_2 \cdot d_1' \cdot d_0 \cdot L'$

→ $d_2 \cdot d_1 \cdot d_0'$

→ $d_2 \cdot d_1 \cdot d_0$

Truth Table to Logic (Part 4)


$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$


$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Here's c_3 as a circuit:

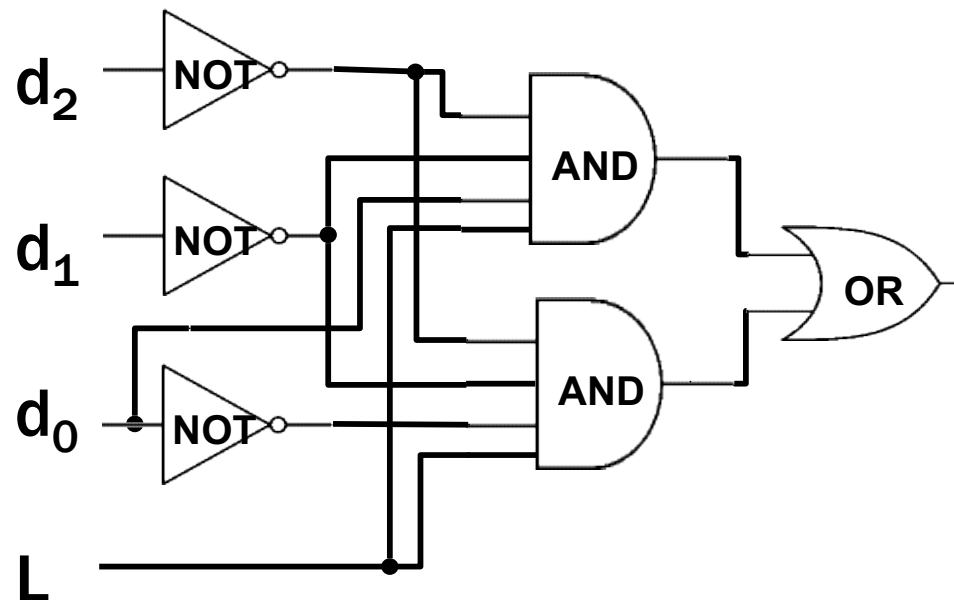

Boolean Algebra

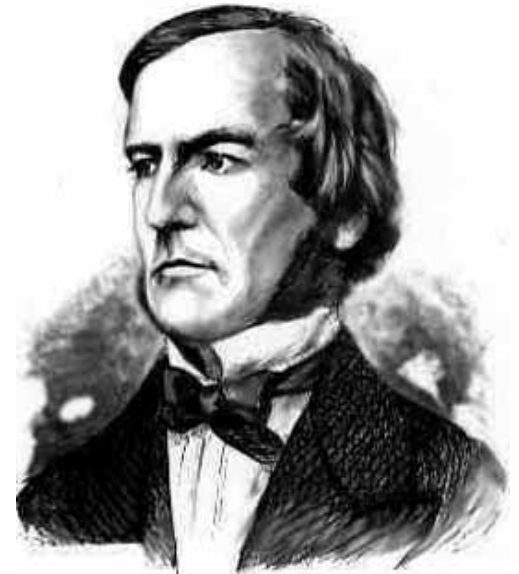- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing $\{0, 1\}$
 - binary operations $\{ + , \cdot \}$
 - and a unary operation $\{ ' \}$
 - such that the following axioms hold:



For any a, b, c in B :

- | | |
|---------------------|---|
| 1. closure: | $a + b$ is in B |
| 2. commutativity: | $a + b = b + a$ |
| 3. associativity: | $a + (b + c) = (a + b) + c$ |
| 4. distributivity: | $a + (b \cdot c) = (a + b) \cdot (a + c)$ |
| 5. identity: | $a + 0 = a$ |
| 6. complementarity: | $a + a' = 1$ |
| 7. null: | $a + 1 = 1$ |
| 8. idempotency: | $a + a = a$ |
| 9. involution: | $(a')' = a$ |

- | |
|---|
| $a \cdot b$ is in B |
| $a \cdot b = b \cdot a$ |
| $a \cdot (b \cdot c) = (a \cdot b) \cdot c$ |
| $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$ |
| $a \cdot 1 = a$ |
| $a \cdot a' = 0$ |
| $a \cdot 0 = 0$ |
| $a \cdot a = a$ |

Simplification using Boolean Algebra

uniting:

$$10. a \cdot b + a \cdot b' = a$$

$$10D. (a + b) \cdot (a + b') = a$$

absorption:

$$11. a + a \cdot b = a$$

$$11D. a \cdot (a + b) = a$$

$$12. (a + b') \cdot b = a \cdot b$$

$$12D. (a \cdot b') + b = a + b$$

factoring:

$$13. (a + b) \cdot (a' + c) = \\ a \cdot c + a' \cdot b$$

$$13D. a \cdot b + a' \cdot c = \\ (a + c) \cdot (a' + b)$$

consensus:

$$14. (a \cdot b) + (b \cdot c) + (a' \cdot c) = \\ a \cdot b + a' \cdot c$$

$$14D. (a + b) \cdot (b + c) \cdot (a' + c) = \\ (a + b) \cdot (a' + c)$$

de Morgan's:

$$15. (a + b + \dots)' = a' \cdot b' \cdot \dots$$

$$15D. (a \cdot b \cdot \dots)' = a' + b' + \dots$$

Proving Theorems

2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$$\begin{aligned}a + b &= b + a \\a + (b + c) &= (a + b) + c \\a + (b \cdot c) &= (a + b) \cdot (a + c) \\a + 0 &= a \\a + a' &= 1 \\a + 1 &= 1 \\a + a &= a \\(a')' &= a\end{aligned}$$

$$\begin{aligned}a \cdot b &= b \cdot a \\a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\a \cdot 1 &= a \\a \cdot a' &= 0 \\a \cdot 0 &= 0 \\a \cdot a &= a\end{aligned}$$

Using the laws of Boolean Algebra:

prove the **Uniting theorem**:

$$X \cdot Y + X \cdot Y' = X$$

$$X \cdot Y + X \cdot Y' =$$

prove the **Absorption theorem**:

$$X + X \cdot Y = X$$

$$X + X \cdot Y =$$

Proving Theorems

2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$$\begin{aligned}a + b &= b + a \\a + (b + c) &= (a + b) + c \\a + (b \cdot c) &= (a + b) \cdot (a + c) \\a + 0 &= a \\a + a' &= 1 \\a + 1 &= 1 \\a + a &= a \\(a')' &= a\end{aligned}$$

$$\begin{aligned}a \cdot b &= b \cdot a \\a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\a \cdot 1 &= a \\a \cdot a' &= 0 \\a \cdot 0 &= 0 \\a \cdot a &= a\end{aligned}$$

Using the laws of Boolean Algebra:

prove the Uniting theorem:

$$X \cdot Y + X \cdot Y' = X$$

distributivity
complementarity
identity

$$\begin{aligned}X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\&= X \cdot 1 \\&= X\end{aligned}$$

prove the theorem:

$$X + X \cdot Y = X$$

identity
distributivity
commutativity
null
identity

$$\begin{aligned}X + X \cdot Y &= X \cdot 1 + X \cdot Y \\&= X \cdot (1 + Y) \\&= X \cdot (Y + 1) \\&= X \cdot 1 \\&= X\end{aligned}$$

Proving Theorems

Using truth table:

For example, de Morgan's Law:

$(X + Y)' = X' \cdot Y'$
NOR is equivalent to AND
with inputs complemented

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

Simplifying using Boolean Algebra

$$\begin{aligned}c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\ &= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\ &= d2' \cdot d1' \cdot 1 \cdot L \\ &= d2' \cdot d1' \cdot L\end{aligned}$$

