 


CSE 311: Foundations of Computing

Lecture 4: Boolean Algebra, Circuits, Canonical Forms



Last Class

- More combinational logic gates
 - NAND, NOR, XOR, XNOR
- Proofs of Logical Equivalence
 - e.g.

$(p \wedge q) \rightarrow (q \vee p)$ is a tautology

$$\begin{aligned}
 (p \wedge q) \rightarrow (q \vee p) &\equiv \neg(p \wedge q) \vee (q \vee p) \\
 &\equiv (\neg p \vee \neg q) \vee (q \vee p) \\
 &\equiv \neg p \vee (\neg q \vee (q \vee p)) \\
 &\equiv \neg p \vee ((\neg q \vee q) \vee p) \\
 &\equiv \neg p \vee (p \vee (\neg q \vee q)) \\
 &\equiv (\neg p \vee p) \vee (\neg q \vee q) \\
 &\equiv (p \vee \neg p) \vee (q \vee \neg q) \\
 &\equiv \mathbf{T} \vee \mathbf{T} \\
 &\equiv \mathbf{T}
 \end{aligned}$$

Associative
– $(p \vee q) \vee r \equiv p \vee (q \vee r)$
– $(p \wedge q) \wedge r \equiv p \wedge (q \wedge r)$
Distributive
– $p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$
– $p \vee (q \wedge r) \equiv (p \vee q) \wedge (p \vee r)$
Absorption
– $p \vee (p \wedge q) \equiv p$
– $p \wedge (p \vee q) \equiv p$
Negation
– $p \vee \neg p \equiv \mathbf{T}$
– $p \wedge \neg p \equiv \mathbf{F}$

- Law of Implication
- DeMorgan
- Associative
- Associative
- Commutative
- Associative
- Commutative (twice)
- Negation (twice)
- Domination/Identity

Identity
– $p \wedge \mathbf{T} \equiv p$
– $p \vee \mathbf{F} \equiv p$
Domination
– $p \vee \mathbf{T} \equiv \mathbf{T}$
– $p \wedge \mathbf{F} \equiv \mathbf{F}$
Idempotent
– $p \vee p \equiv p$
– $p \wedge p \equiv p$
Commutative
– $p \vee q \equiv q \vee p$
– $p \wedge q \equiv q \wedge p$

Boolean Logic: Circuits

4 up

Combinational Logic


- output = F(input)

Sequential Logic

- $\text{output}_t = F(\text{output}_{t-1}, \text{input}_t)$
 - output dependent on history
 - concept of a time step (clock, t)

CSE
369

CSE 369

 

Boolean Algebra: Another notation for logic consisting of...

- a set of elements $B = \{0, 1\}$
- binary operations $\{ +, \cdot \}$ (OR, AND)
- and a unary operation $\{ ' \}$ (NOT)

Boolean Algebra

- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing {0, 1}
 - binary operations { + , • }
 - and a unary operation { ' }
 - such that the following axioms hold:



For any a, b, c in B:

1. closure:
2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$a + b$ is in B

$$a + b = b + a$$

$$a + (b + c) = (a + b) + c$$

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$a + 0 = a$$

$$a + a' = 1$$

$$a + 1 = 1$$

$$a + a = a$$

$$(a')' = a$$

$a \cdot b$ is in B

$$a \cdot b = b \cdot a$$

$$a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

$$a \cdot 1 = a$$

$$a \cdot a' = 0$$

$$a \cdot 0 = 0$$

$$a \cdot a = a$$

A Combinational Logic Example

Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**

Input: (Monday, Section) Output: **1**


Implementation in Software

```
public int classesLeftInMorning(weekday, lecture_flag) {
    switch (weekday) {
        case SUNDAY:
        case MONDAY:
            return lecture_flag ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return lecture_flag ? 2 : 1;
        case THURSDAY:
            return lecture_flag ? 1 : 1;
        case FRIDAY:
            return lecture_flag ? 1 : 0;
        case SATURDAY:
            return lecture_flag ? 0 : 0;
    }
}
```

Implementation with Combinational Logic

Encoding:

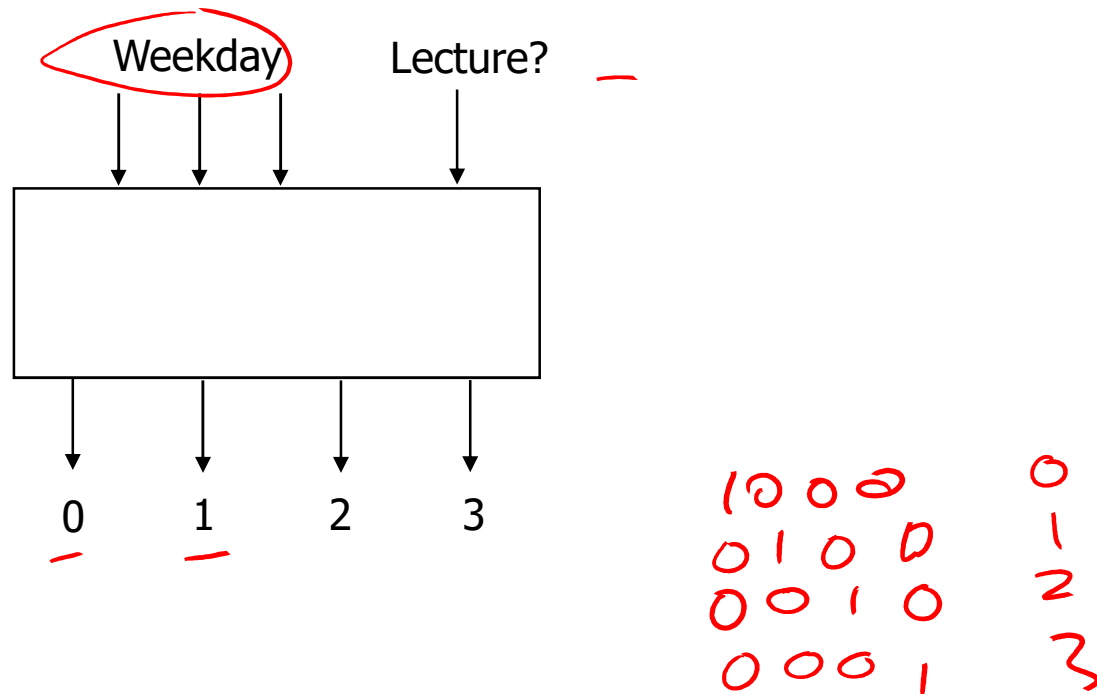- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output (called “1-hot” encoding)



Defining Our Inputs!

Weekday Input:

- Binary number for weekday
- Sunday = 0, Monday = 1, ...
- We care about these in binary:

Weekday	Number	Binary
Sunday	0	$(000)_2$
Monday	1	$(001)_2$
Tuesday	2	$(010)_2$
Wednesday	3	$(011)_2$
Thursday	4	$(100)_2$
Friday	5	$(101)_2$
Saturday	6	$(110)_2$

Converting to a Truth Table!

```

case SUNDAY or MONDAY:
    return lecture_flag ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return lecture_flag ? 2 : 1;
case THURSDAY:
    return lecture_flag ? 1 : 1;
case FRIDAY:
    return lecture_flag ? 1 : 0;
case SATURDAY:
    return lecture_flag ? 0 : 0;

```

Weekday	Lecture?	c ₀	c ₁	c ₂	c ₃
SUN	<u>000</u>				
SUN	000				
MON	001				
MON	001				
TUE	010				
TUE	010	0	0	1	0
WED	011				
WED	011	0	0	1	0
THU	100				
FRI	101				
FRI	101				
SAT	110				
-	111				

Converting to a Truth Table!

```
case SUNDAY or MONDAY:
    return lecture_flag ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return lecture_flag ? 2 : 1;
case THURSDAY:
    return lecture_flag ? 1 : 1;
case FRIDAY:
    return lecture_flag ? 1 : 0;
case SATURDAY:
    return lecture_flag ? 0 : 0;
```

Weekday	Lecture?	c ₀	c ₁	c ₂	c ₃
SUN	000	0	1	0	0
SUN	000	0	0	0	1
MON	001	0	1	0	0
MON	001	0	0	0	1
TUE	010	0	1	0	0
TUE	010	0	0	1	0
WED	011	0	1	0	0
WED	011	0	0	1	0
THU	100	0	1	0	0
FRI	101	1	0	0	0
FRI	101	0	1	0	0
SAT	110	1	0	0	0
-	111	1	0	0	0

Truth Table to Logic (Part 1)


	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0


Let's begin by finding an expression for c_3 . To do this, we look at the rows where $c_3 = 1$ (true).

$$c_3 = \text{"DAY=SUN"} \cdot L + \text{"DAY=MON"} \cdot L$$

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0


DAY == SUN && L == 1


DAY == MON && L == 1

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2d_1d_0 == 000 \ \&\& \ L == 1$

$d_2d_1d_0 == 001 \ \&\& \ L == 1$

Substituting DAY with the binary representation.

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$d_2' \cdot d_1' \cdot d_0' \cdot L$$

$$d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$$

$$d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$$

Splitting up the bits of the day;
so, we can write a formula.

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$\underline{d_2' \cdot d_1' \cdot d_0' \cdot L}$$

$$\underline{d_2' \cdot d_1' \cdot d_0 \cdot L}$$

Replacing with
Boolean Algebra...

Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$d_2' \cdot d_1' \cdot d_0' \cdot L$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L$$

Either situation causes c_3 to be true. So, we "or" them.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Truth Table to Logic (Part 2)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Now, we do c_2 .

DAY = TUE & L = 1
 $d_2' \cdot d_1 \cdot d_0' \cdot L$

+ $d_2' \cdot d_1 \cdot d_0 \cdot L$

$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$

Truth Table to Logic (Part 3)

	$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Now, we do c_1 :

$$d_2' \cdot d_1' \cdot d_0' \cdot L'$$

$$+$$

$$-$$

$$-$$

$$-$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	???
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do c_1 :

$d_2 \cdot d_1' \cdot d_0'$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

	$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do c_1 :

No matter what L is, we always say it's 1. So, we don't need L in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

	$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do c_1 :

No matter what L is, we always say it's 1. So, we don't need L in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

Truth Table to Logic (Part 4)

	$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Finally, we do c_0 :

$$d_2 \cdot d_1' \cdot d_0 \cdot L'$$

$$d_2 \cdot d_1 \cdot d_0'$$

$$d_2 \cdot d_1 \cdot d_0$$

Truth Table to Logic (Part 4)


$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Here's c_3 as a circuit:

 

connected
not connected

Boolean Algebra

- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing $\{0, 1\}$
 - binary operations $\{ + , \cdot \}$
 - and a unary operation $\{ ' \}$
 - such that the following axioms hold:



For any a, b, c in B :

- | | |
|---------------------|---|
| 1. closure: | $a + b$ is in B |
| 2. commutativity: | $a + b = b + a$ |
| 3. associativity: | $a + (b + c) = (a + b) + c$ |
| 4. distributivity: | $a + (b \cdot c) = (a + b) \cdot (a + c)$ |
| 5. identity: | $a + 0 = a$ |
| 6. complementarity: | $a + a' = 1$ |
| 7. null: | $a + 1 = 1$ |
| 8. idempotency: | $a + a = a$ |
| 9. involution: | $(a')' = a$ |

- | |
|---|
| $a \cdot b$ is in B |
| $a \cdot b = b \cdot a$ |
| $a \cdot (b \cdot c) = (a \cdot b) \cdot c$ |
| $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$ |
| $a \cdot 1 = a$ |
| $a \cdot a' = 0$ |
| $a \cdot 0 = 0$ |
| $a \cdot a = a$ |

Simplification using Boolean Algebra

uniting:

$$10. a \cdot b + a \cdot b' = a$$

$$10D. (a + b) \cdot (a + b') = a$$

absorption:

$$11. a + a \cdot b = a$$

$$11D. a \cdot (a + b) = a$$

$$12. (a + b') \cdot b = a \cdot b$$

$$12D. (a \cdot b') + b = a + b$$

factoring:

$$13. (a + b) \cdot (a' + c) = \\ a \cdot c + a' \cdot b$$

$$13D. a \cdot b + a' \cdot c = \\ (a + c) \cdot (a' + b)$$

consensus:

$$14. (a \cdot b) + (b \cdot c) + (a' \cdot c) = \\ a \cdot b + a' \cdot c$$

$$14D. (a + b) \cdot (b + c) \cdot (a' + c) = \\ (a + b) \cdot (a' + c)$$

de Morgan's:

$$15. (a + b + \dots)' = a' \cdot b' \cdot \dots$$

$$15D. (a \cdot b \cdot \dots)' = a' + b' + \dots$$

Proving Theorems

- 2. commutativity:
- 3. associativity:
- 4. distributivity:
- 5. identity:
- 6. complementarity:
- 7. null:
- 8. idempotency:
- 9. involution:

$$\begin{aligned}a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a &= a \\ (a')' &= a\end{aligned}$$

$$\begin{aligned}a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a &= a\end{aligned}$$

Using the laws of Boolean Algebra:

prove the Uniting theorem:

$$X \cdot Y + X \cdot Y' = X$$

$$\begin{aligned}X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \text{ dist} \\ &= X \cdot 1 \text{ compl} \\ &= X \text{ ident}\end{aligned}$$

prove the Absorption theorem:

$$X + X \cdot Y = X$$

$$\begin{aligned}X + X \cdot Y &= X \cdot 1 + X \cdot Y \text{ ident} \\ &= X \cdot (1 + Y) \text{ dist} \\ &= X \cdot (Y + 1) \text{ un} \\ &= X \cdot 1 \text{ nul} \\ &= X \text{ id}\end{aligned}$$

Proving Theorems

2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$$\begin{aligned}a + b &= b + a \\a + (b + c) &= (a + b) + c \\a + (b \cdot c) &= (a + b) \cdot (a + c) \\a + 0 &= a \\a + a' &= 1 \\a + 1 &= 1 \\a + a &= a \\(a')' &= a\end{aligned}$$

$$\begin{aligned}a \cdot b &= b \cdot a \\a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\a \cdot 1 &= a \\a \cdot a' &= 0 \\a \cdot 0 &= 0 \\a \cdot a &= a\end{aligned}$$

Using the laws of Boolean Algebra:

prove the Uniting theorem:

$$X \cdot Y + X \cdot Y' = X$$

distributivity
complementarity
identity

$$\begin{aligned}X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\&= X \cdot 1 \\&= X\end{aligned}$$

prove the theorem:

$$X + X \cdot Y = X$$

identity
distributivity
commutativity
null
identity

$$\begin{aligned}X + X \cdot Y &= X \cdot 1 + X \cdot Y \\&= X \cdot (1 + Y) \\&= X \cdot (Y + 1) \\&= X \cdot 1 \\&= X\end{aligned}$$

Proving Theorems

Using truth table:

For example, de Morgan's Law:

$(X + Y)' = X' \cdot Y'$
NOR is equivalent to AND
with inputs complemented



X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

Simplifying using Boolean Algebra
  
$$\begin{aligned}c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\ &= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\ &\hat{=} d2' \cdot d1' \cdot 1 \cdot L \\ &= d2' \cdot d1' \cdot L\end{aligned}$$



1-bit Binary Adder

<u>A</u>		$0 + 0 = \underline{0}$ (with $C_{OUT} = 0$)
+ <u>B</u>		$0 + 1 = \underline{1}$ (with $C_{OUT} = 0$)
<u>S</u>		$1 + 0 = \underline{1}$ (with $C_{OUT} = 0$)
(C_{OUT})		$1 + 1 = \underline{0}$ (with $C_{OUT} = 1$)

|

1-bit Binary Adder



A	$0 + 0 = 0$ (with $C_{OUT} = 0$)
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$)
S	$1 + 0 = 1$ (with $C_{OUT} = 0$)
(C_{OUT})	$1 + 1 = 0$ (with $C_{OUT} = 1$)

Idea: To chain these together, let's add a carry-in

1-bit Binary Adder

A	$0 + 0 = 0$ (with $C_{OUT} = 0$)
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$)
S	$1 + 0 = 1$ (with $C_{OUT} = 0$)
(C_{OUT})	$1 + 1 = 0$ (with $C_{OUT} = 1$)

  
Idea: To chain these together, let's add a carry-in



1-bit Binary Adder


A	$0 + 0 = 0$ (with $C_{OUT} = 0$)
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$)
S	$1 + 0 = 1$ (with $C_{OUT} = 0$)
(C_{OUT})	$1 + 1 = 0$ (with $C_{OUT} = 1$)

 Idea: To chain these together, let's add a carry-in



1-bit Binary Adder

 - **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out




A	B	C _{IN}	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

↑
↑
↑



1-bit Binary Adder

 
- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



My 2/12 outputs

A	B	C_{IN}	C_{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Derive an expression for S

 

$$S = \underline{A' \cdot B' \cdot C_{IN}} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

1-bit Binary Adder

 - **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C_{IN}	C_{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Derive an expression for C_{OUT}


$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

The diagram shows four blue arrows pointing from the rows of the truth table to the terms in the equation above. The first arrow points from the row (0, 1, 1) to $A' \cdot B \cdot C_{IN}$. The second arrow points from the row (1, 0, 1) to $A \cdot B' \cdot C_{IN}$. The third arrow points from the row (1, 1, 0) to $A \cdot B \cdot C_{IN}'$. The fourth arrow points from the row (1, 1, 1) to $A \cdot B \cdot C_{IN}$. A large blue curly bracket groups these four terms together, pointing to the final equation.

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

1-bit Binary Adder

 - **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C _{IN}	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

Apply Theorems to Simplify Expressions


The theorems of Boolean algebra can simplify expressions

– e.g., full adder's carry-out function

$$\begin{aligned} \text{Cout} &= A' B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= A' B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} + A B C_{in} \\ &= A' B C_{in} + A B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= (A' + A) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= (1) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} + A B C_{in} \\ &= B C_{in} + A B' C_{in} + A B C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A (B' + B) C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A (1) C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A C_{in} + A B (C_{in}' + C_{in}) \\ &= B C_{in} + A C_{in} + A B (1) \\ &= B C_{in} + A C_{in} + A B \end{aligned}$$

adding extra terms
creates new factoring
opportunities

Multi-bit Ripple-Carry Adder

 

Mapping Truth Tables to Logic Gates





Given a truth table:

1. Write the Boolean expression
2. Minimize the Boolean expression
3. Draw as gates
4. Map to available gates

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

②
    
$$\begin{aligned} F &= A'BC' + A'BC + AB'C + ABC \\ &= A'B(C' + C) + AC(B' + B) \\ &= A'B + AC \end{aligned}$$



Canonical Forms

- **Truth table is the unique signature of a Boolean Function**
- **The same truth table can have many gate realizations**
 - We've seen this already
 - Depends on how good we are at Boolean simplification
- **Canonical forms**
 - Standard forms for a Boolean expression
 - We all come up with the same expression


Sum-of-Products Canonical Form

- AKA **Disjunctive Normal Form (DNF)**
- AKA **Minterm Expansion**

③

Add the minterms together

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

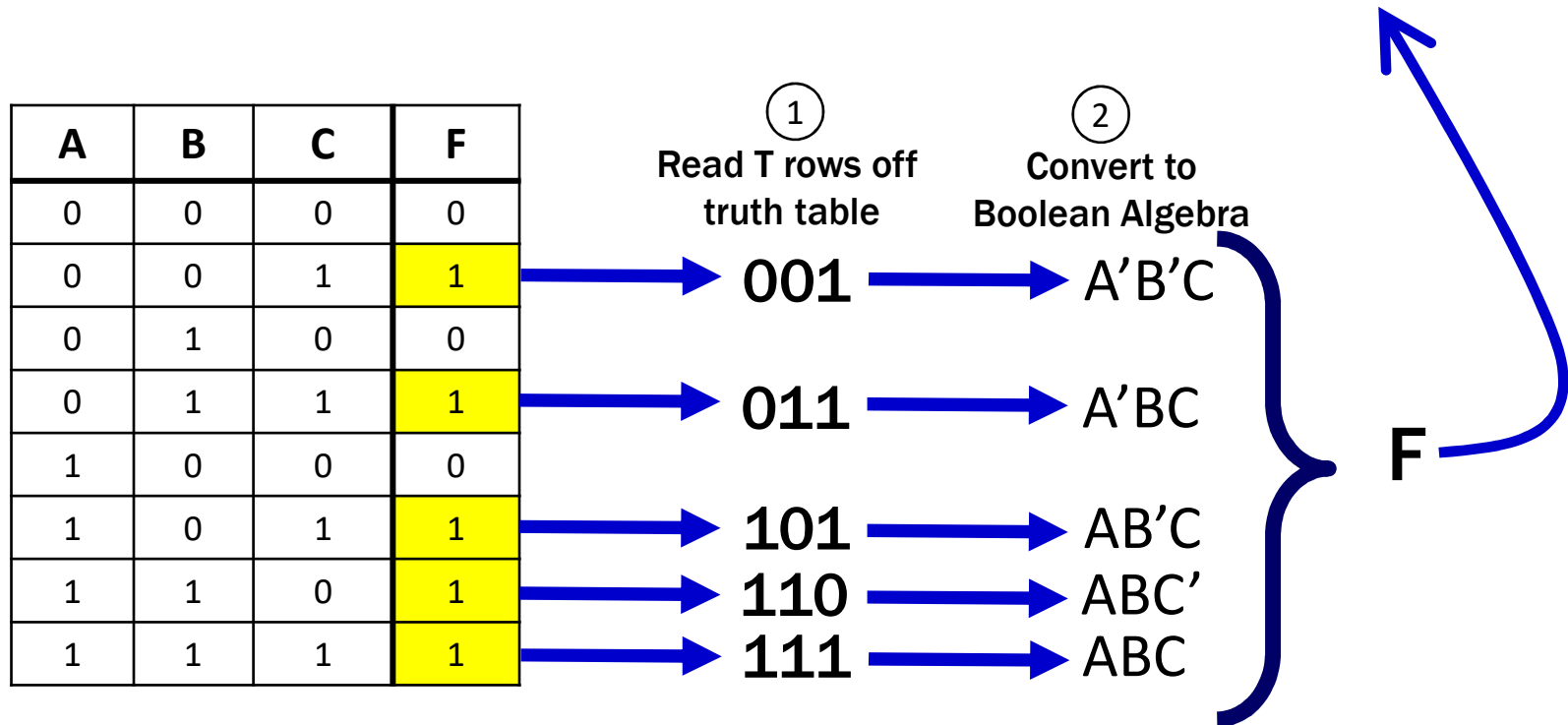

Sum-of-Products Canonical Form

Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	$A'B'C'$
0	0	1	$A'B'C$
0	1	0	$A'BC'$
0	1	1	$A'BC$
1	0	0	$AB'C'$
1	0	1	$AB'C$
1	1	0	ABC'
1	1	1	ABC

F in canonical form:


$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C \end{aligned}$$


Product-of-Sums Canonical Form

 - AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**



Product-of-Sums Canonical Form

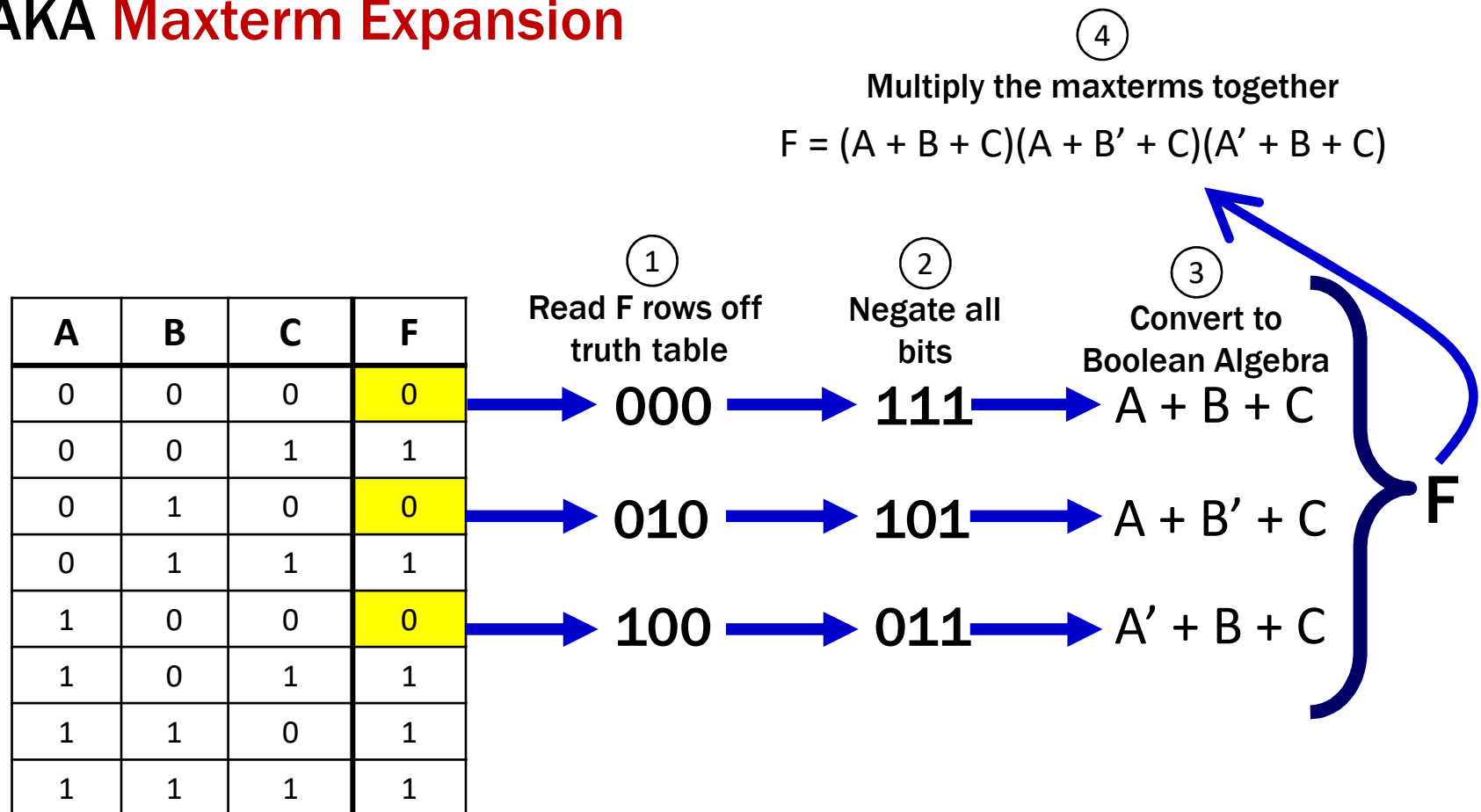- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**




Product-of-Sums: Why does this procedure work?

Useful Facts:

- We know $(F')' = F$
- We know how to get a minterm expansion for F'

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

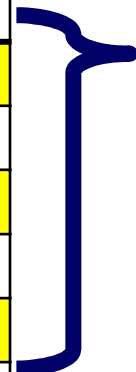
$$F' = A'B'C' + A'BC' + AB'C'$$

Product-of-Sums: Why does this procedure work?

Useful Facts:

- We know $(F')' = F$
- We know how to get a minterm expansion for F'

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


$$F' = A'B'C' + A'BC' + AB'C'$$

Taking the complement of both sides...

$$(F')' = (A'B'C' + A'BC' + AB'C')'$$

And using DeMorgan/Comp....

$$F = (A'B'C')' (A'BC')' (AB'C')'$$

$$F = (A + B + C)(A + B' + C)(A' + B + C)$$

Product-of-Sums Canonical Form

Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms
0	0	0	$A+B+C$
0	0	1	$A+B+C'$
0	1	0	$A+B'+C$
0	1	1	$A+B'+C'$
1	0	0	$A'+B+C$
1	0	1	$A'+B+C'$
1	1	0	$A'+B'+C$
1	1	1	$A'+B'+C'$

F in canonical form:

$$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$