

# Number Systems

---

- Readings: 3-3.3.3, 3.3.5
- Problem: Implement simple pocket calculator
- Need: Display, adders & subtractors, inputs
  - Display: Seven segment displays
  - Inputs: Switches
- Missing: Way to implement numbers in binary



- Approach: From decimal to binary numbers  
(and back)

# Arithmetic Operations

Decimal:

$$\begin{array}{r} 5 \ 7 \ 8 \ 9 \ 2 \\ + 7 \ 8 \ 9 \ 5 \ 6 \\ \hline \end{array}$$

Binary:

$$\begin{array}{r} 1 \ 0 \ 1 \ 0 \ 1 \ 1 \\ + 0 \ 1 \ 0 \ 0 \ 1 \ 0 \\ \hline 1 \ 1 \ 1 \ 1 \ 1 \ 0 \ 0 \end{array}$$

Decimal:

$$\begin{array}{r} 5 \ 7 \ 8 \ 9 \ 2 \\ - 3 \ 2 \ 9 \ 4 \ 6 \\ \hline \end{array}$$

Binary:

$$\begin{array}{r} 1 \ 0 \ 1 \ 0 \ 0 \ 1 \ 1 \ 0 \\ - 0 \ 0 \ 1 \ 1 \ 0 \ 1 \ 1 \ 1 \\ \hline 0 \ 1 \ 1 \ 0 \ 1 \ 1 \ 1 \ 1 \end{array}$$

# Arithmetic Operations (cont.)

---

Decimal:

$$\begin{array}{r} 2 \ 0 \ 1 \\ * \ 2 \ 1 \ 4 \\ \hline \end{array}$$


Binary:

$$\begin{array}{r} 1 \ 0 \ 0 \ 1 \\ * \ 1 \ 0 \ 1 \ 1 \\ \hline 1 \ 0 \ 0 \ 1 \\ 1 \ 0 \ 0 \ 1 - \\ 0 \ 0 \ 0 \ 0 - - \\ 1 \ 0 \ 1 \ 1 - - - \\ \hline 1 \ 1 \ 0 \ 0 \ 1 \ 1 \end{array}$$


# Half Adder

$A_i$	$B_i$	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

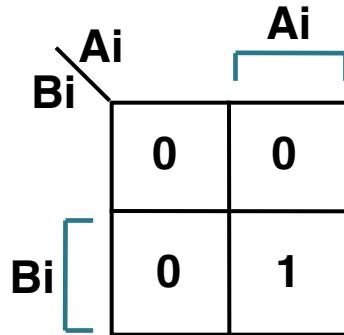
*(Handwritten annotations: 'AND' under the Carry column, 'XOR' under the Sum column)*



$$\text{Carry} = A_i B_i$$

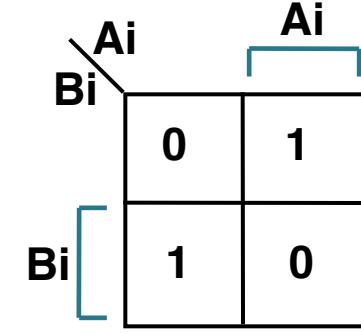
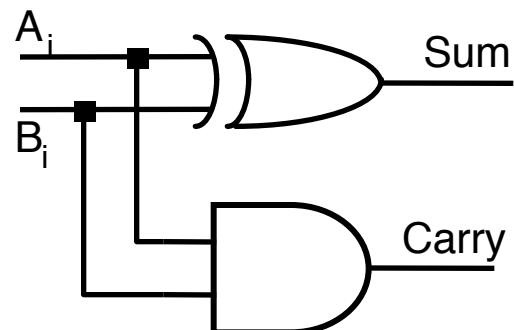
$$\begin{aligned}\text{Sum} &= \bar{A}_i B_i + A_i \bar{B}_i \\ &= A_i \oplus B_i\end{aligned}$$



Half-adder Schematic



# Full Adder

---

A	B	Cl	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C_{OUT} = AB + AC_{IN} + BC_{IN}$$

$$S = A \oplus B \oplus C$$

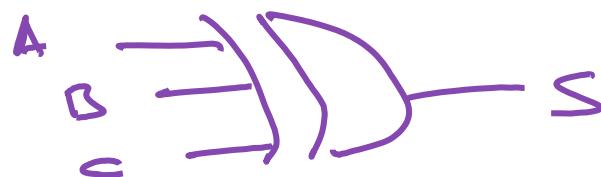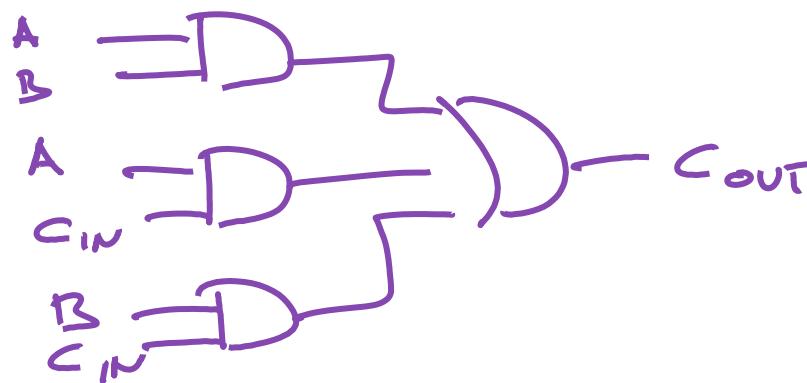


# Full Adder Implementation

---

# Multi-Bit Addition

" RIPPLE - CARRY ADDER "

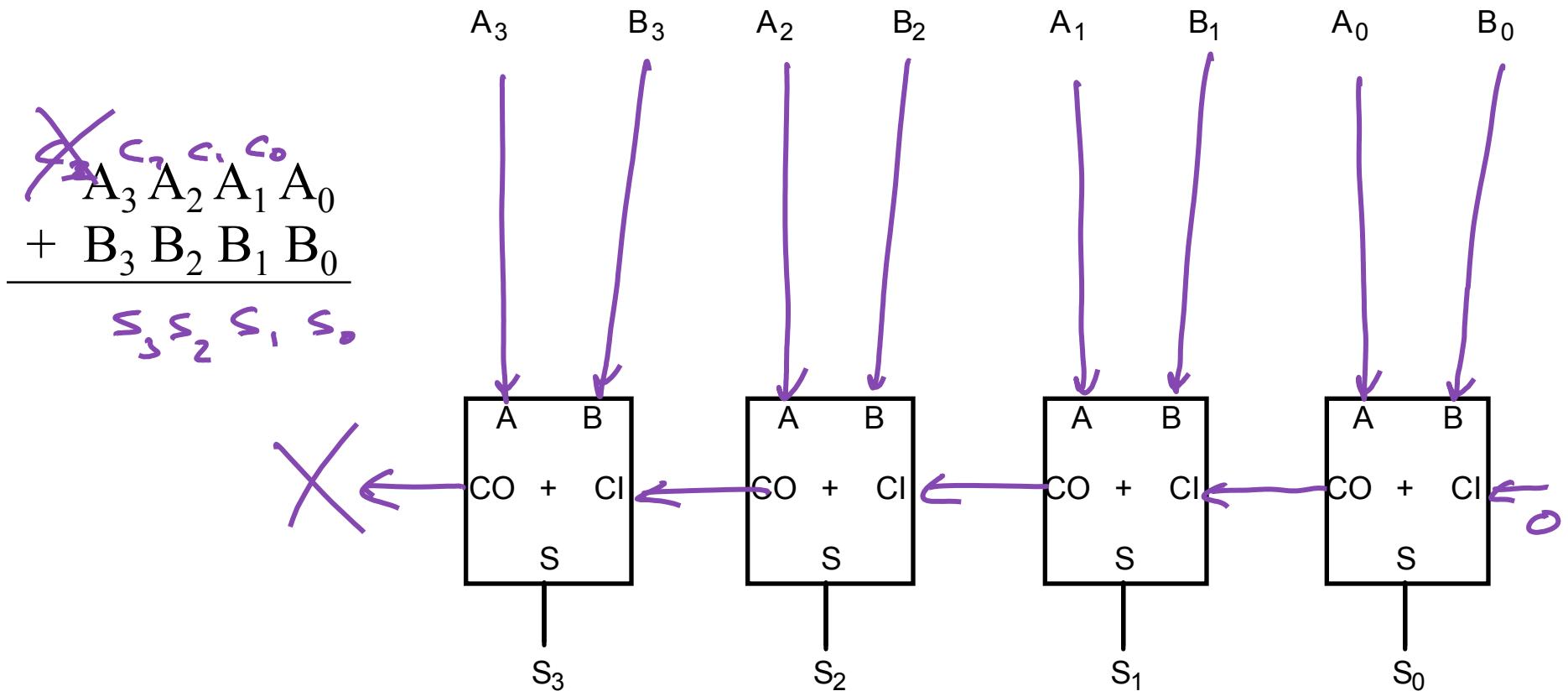

# Multi-Bit Addition in Verilog, Parameters


```
module uadd #(parameter WIDTH=8)
  (out, a, b);
  output reg [WIDTH:0] out;
  input      [WIDTH-1:0] a, b;

  always @(*) begin
    out = a + b;
  end
endmodule
```

```
module add4 #(parameter W=22)
  (out, a, b, c, d);
  output [W+1:0] out;
  input  [W-1:0] a, b, c, d;

  wire [W:0] ab, cd;

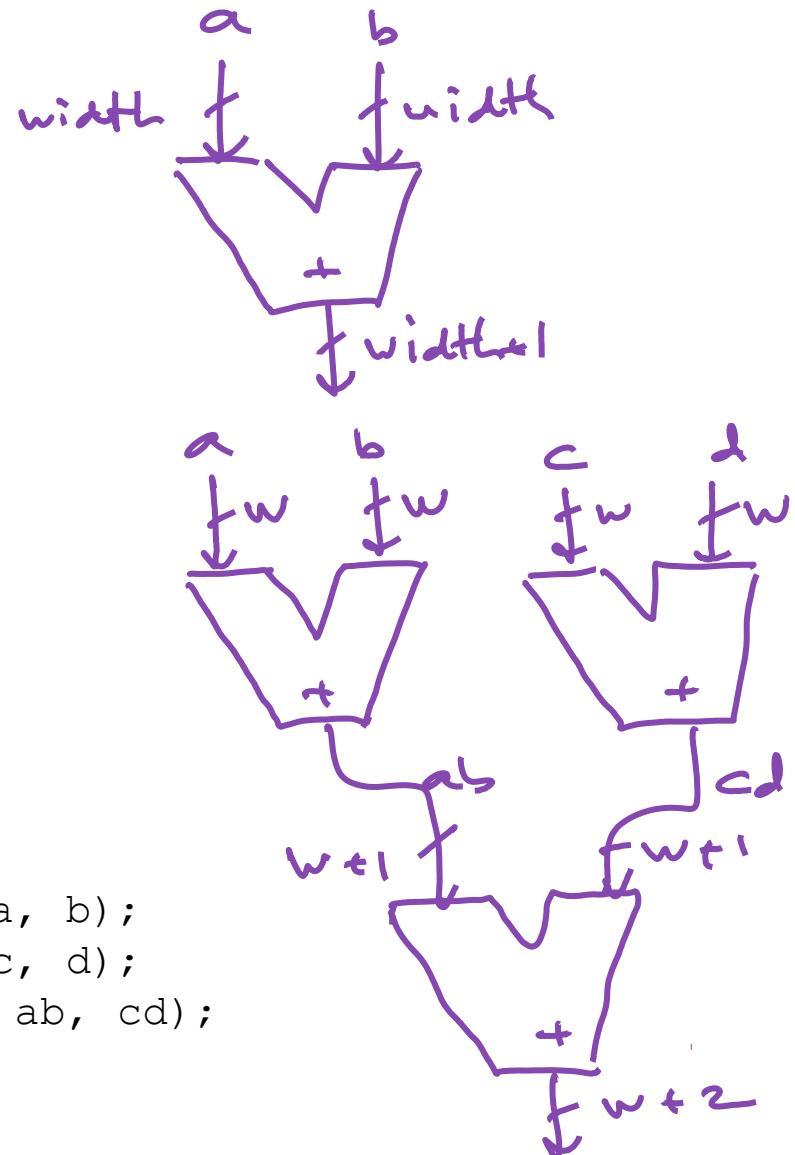  uadd #(.WIDTH(W)) u_ab (ab, a, b);
  uadd #(.WIDTH(W)) u_cd (cd, c, d);
  uadd #(.WIDTH(W+1)) u_abcd (out, ab, cd);
endmodule
```



# Negative Numbers

---


- Need an efficient way to represent negative numbers in binary
  - Both positive & negative numbers will be strings of bits
  - Use fixed-width formats (4-bit, 16-bit, etc.)
- Must provide efficient mathematical operations
  - Addition & subtraction with potentially mixed signs
  - Negation (multiply by -1)

0 → +

1 → -

1 | 0 0 0 0 0 1  
S | M<sub>4</sub>      M<sub>0</sub>  
↑                ↑  
SIGN             MAGNITUDE

# Sign/Magnitude Representation

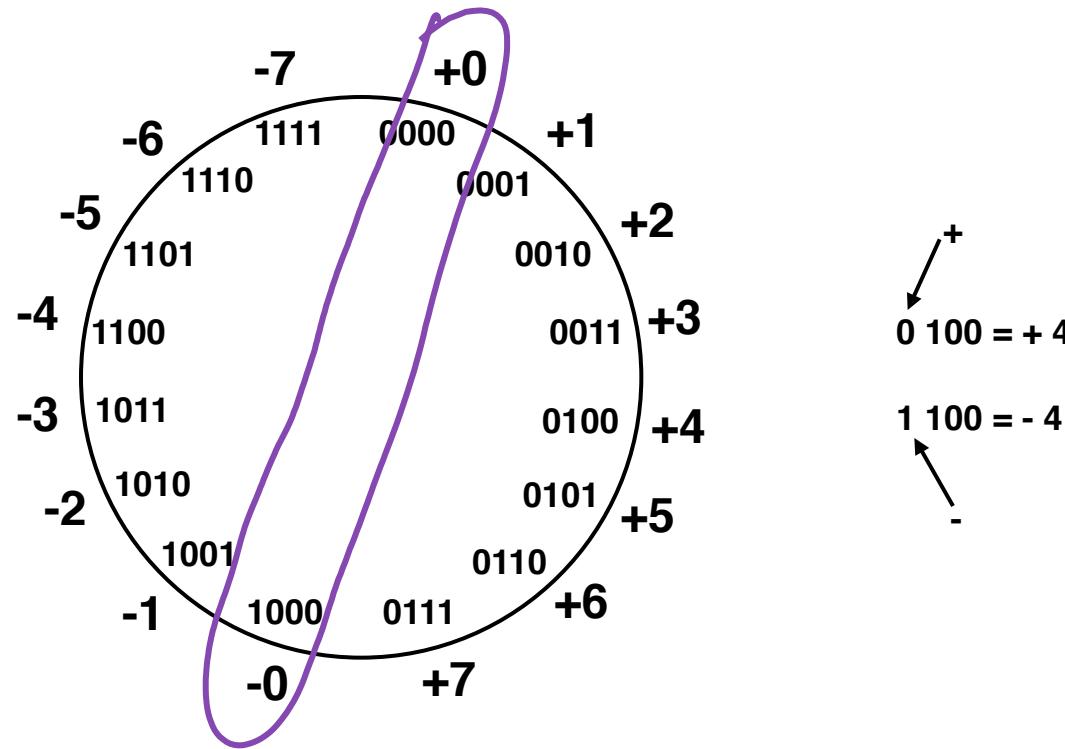

Representations for 0:

# Sign/Magnitude Addition

SIGNS ARE THE SAME: ADD MAGNITUDES, KEEP SIGN

SIGNS ARE DIFFERENT: SUBTRACT SMALLER FROM BIGGER MAG.  
KEEP SIGN OF BIGGER #

$$\begin{array}{r} 0 | 0 1 0 \text{ (+2)} \\ + 0 | 1 0 0 \text{ (+4)} \\ \hline 0 1 1 0 \quad +6 \end{array}$$

$$\begin{array}{r} 1 | 0 1 0 \text{ (-2)} \\ + 1 | 1 0 0 \text{ (-4)} \\ \hline 1 1 1 0 \quad -6 \end{array}$$

$$\begin{array}{r} 0 | 0 1 0 \text{ (+2)} \\ + 1 | 1 0 0 \text{ (-4)} \\ \hline 1 0 1 0 \quad -2 \end{array}$$

$$\begin{array}{r} 1 | 0 1 0 \text{ (-2)} \\ + 0 | 1 0 0 \text{ (+4)} \\ \hline 0 0 1 0 \quad +2 \end{array}$$

Bottom line: Basic mathematics are too complex in Sign/Magnitude

# Idea: Pick negatives so that addition works

---

- Let  $-1 = 0 - (+1)$ :

$$\begin{array}{r} 1 \ 0 \ 0 \ 0 \ 0 \ (\ 0) \\ - 0 \ 0 \ 0 \ 1 \ (\ +1) \\ \hline 1 \ 1 \ 1 \ 1 \end{array}$$

- Does addition work?


$$\begin{array}{r} 0 \ 0 \ 1 \ 0 \ (\ +2) \\ + 1 \ 1 \ 1 \ 1 \ (\ -1) \\ \hline 0 \ 0 \ 0 \ 1 \end{array}$$

- Result: Two's Complement Numbers

FOR  $0 \leq b \leq 2^n - 1$   $-b$  IS REPRESENTED BY  $2^n - b$
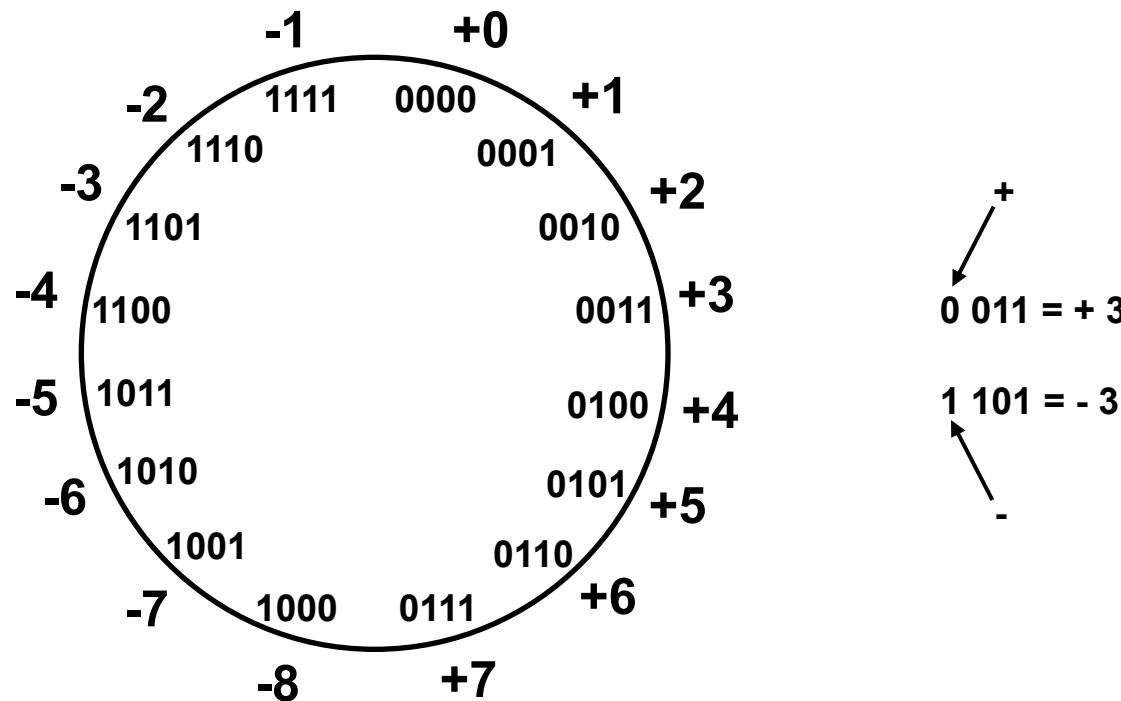
# Two's Complement

- Only one representation for 0
- One more negative number than positive number
- Fixed width format for both pos. & neg. numbers




# Negating in Two's Complement

- Flip bits & Add 1
- Negate  $(0010)_2$  (+2)

$$-2 = -0010 = 1101 + 1 = 1110$$

- Negate  $(1110)_2$  (-2)

$$-1110 = 0001 + 1 = 0010$$

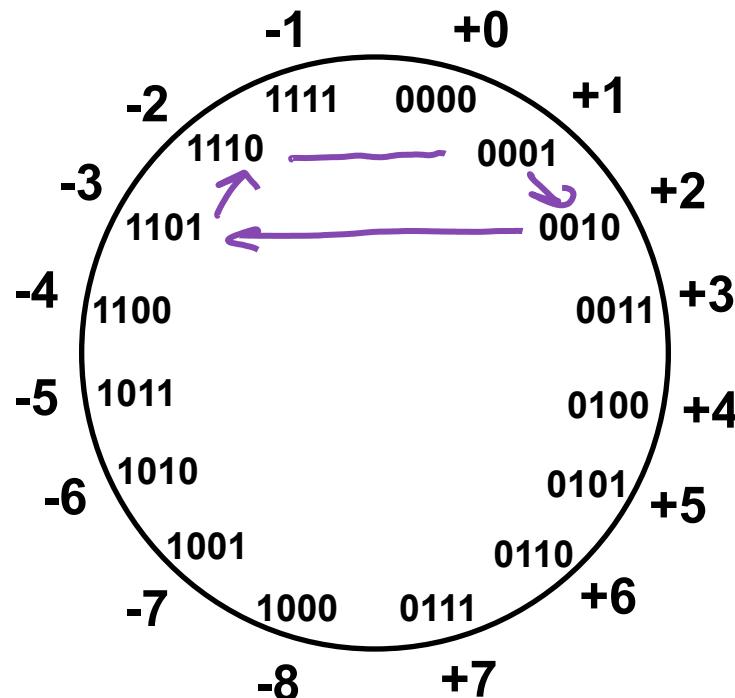

# Addition in Two's Complement

---

$$\begin{array}{r} 0 \ 0 \ 1 \ 0 \ (+2) \\ + 0 \ 1 \ 0 \ 0 \ (+4) \\ \hline 0 \ 1 \ 1 \ 0 \end{array}$$

$$\begin{array}{r} \cancel{X} \ 1 \ 1 \ 1 \ 0 \ (-2) \\ + 1, \ 1 \ 0 \ 0 \ (-4) \\ \hline 1 \ 0 \ 1 \ 0 \end{array}$$

$$\begin{aligned} &= -(-1010) = -(0101+1) \\ &= -(0110) = -6 \end{aligned}$$

$$\begin{array}{r} 0 \ 0 \ 1 \ 0 \ (+2) \\ + 1 \ 1 \ 0 \ 0 \ (-4) \\ \hline 1 \ 1 \ 1 \ 0 \end{array}$$

$$\begin{array}{r} \cancel{X} \ 1 \ 1 \ 1 \ 0 \ (-2) \\ + 0, \ 1 \ 0 \ 0 \ (+4) \\ \hline 0 \ 0 \ 1 \ 0 \end{array}$$

$$\begin{aligned} &= -(-1110) = -(0001+1) \\ &= -(0010) = -2 \end{aligned}$$

# Subtraction in Two's Complement

---

■  $A - B = A + (-B) = A + \bar{B} + 1$

■  $0010 - 0110$

$$\begin{array}{r} 0010 + (-0110) \\ \hline 2 - 6 \\ \hline 1010 \\ \hline 1100 \end{array}$$

■  $1011 - 1001$



$$\begin{bmatrix} -(0011+1) = +0100 \\ = -4 \end{bmatrix}$$

■  $1011 - 0001$
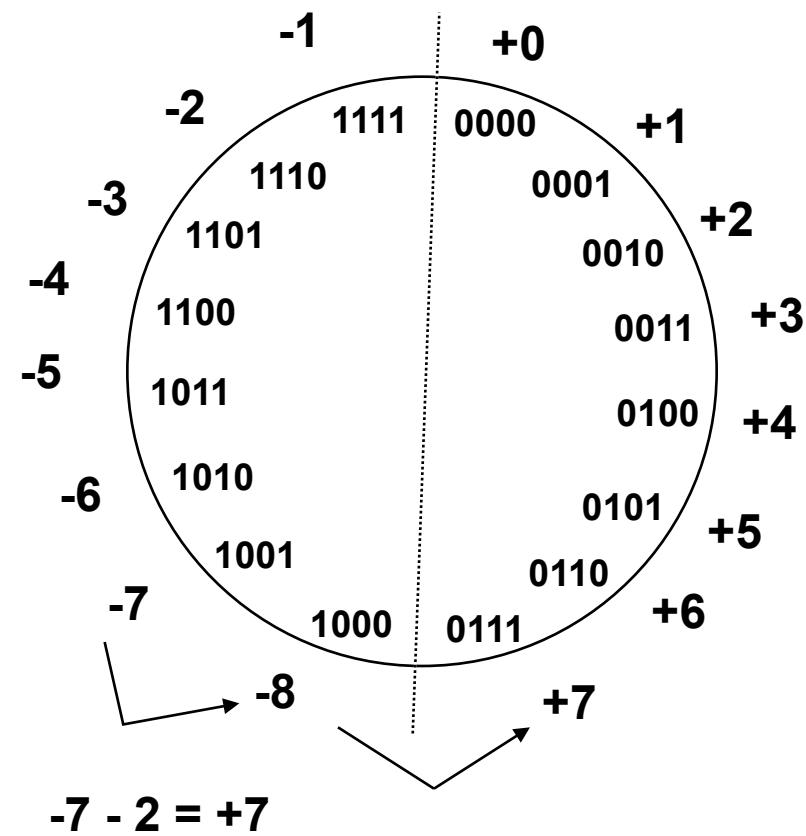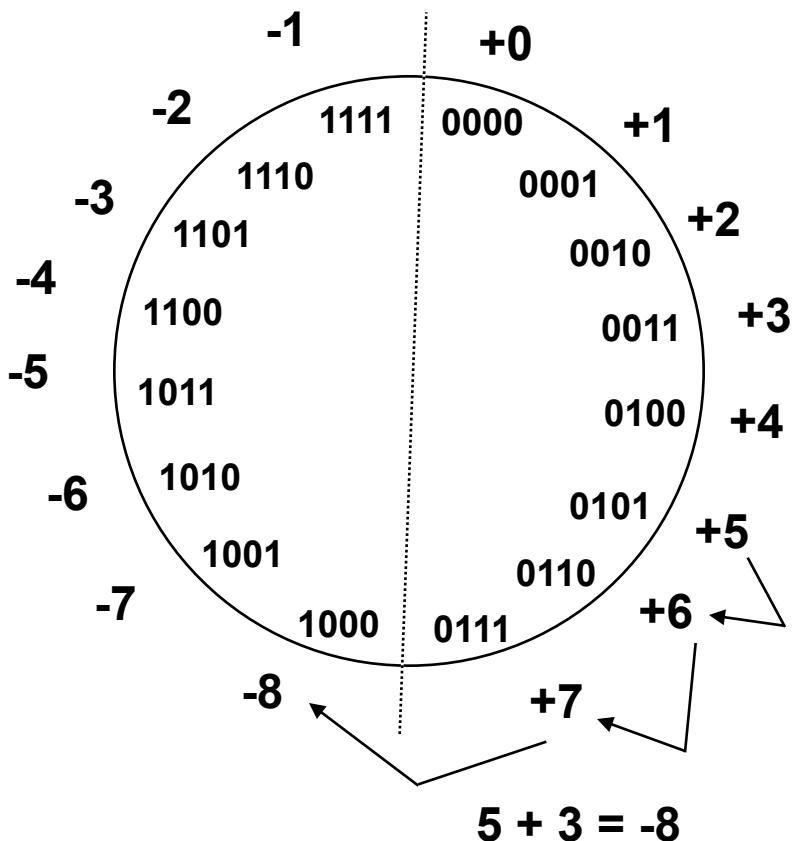
# Overflows in Two's Complement

Add two positive numbers but get a negative number

or two negative numbers but get a positive number



# Overflow Detection in Two's Complement

$$\begin{array}{r} 5 \\ -3 \\ \hline -8 \end{array} \quad \begin{array}{r} 0101 \\ -0.1.1 \\ \hline 1000 \end{array}$$

Overflow

$$\begin{array}{r} -7 \\ -2 \\ \hline 7 \end{array} \quad \begin{array}{r} 1001 \\ -1.1.0 \\ \hline 0111 \end{array}$$

Overflow

$$\begin{array}{r} 5 \\ -2 \\ \hline 7 \end{array} \quad \begin{array}{r} 0101 \\ -0.010 \\ \hline 0111 \end{array}$$


No overflow

$$\begin{array}{r} -3 \\ -5 \\ \hline -8 \end{array} \quad \begin{array}{r} 1101 \\ -1.011 \\ \hline 1000 \end{array}$$

No overflow

OVERFLOW =  $C_{in} \oplus C_{out}$  OF HIGHEST ORDER NMBR.

# Adder/Subtractor

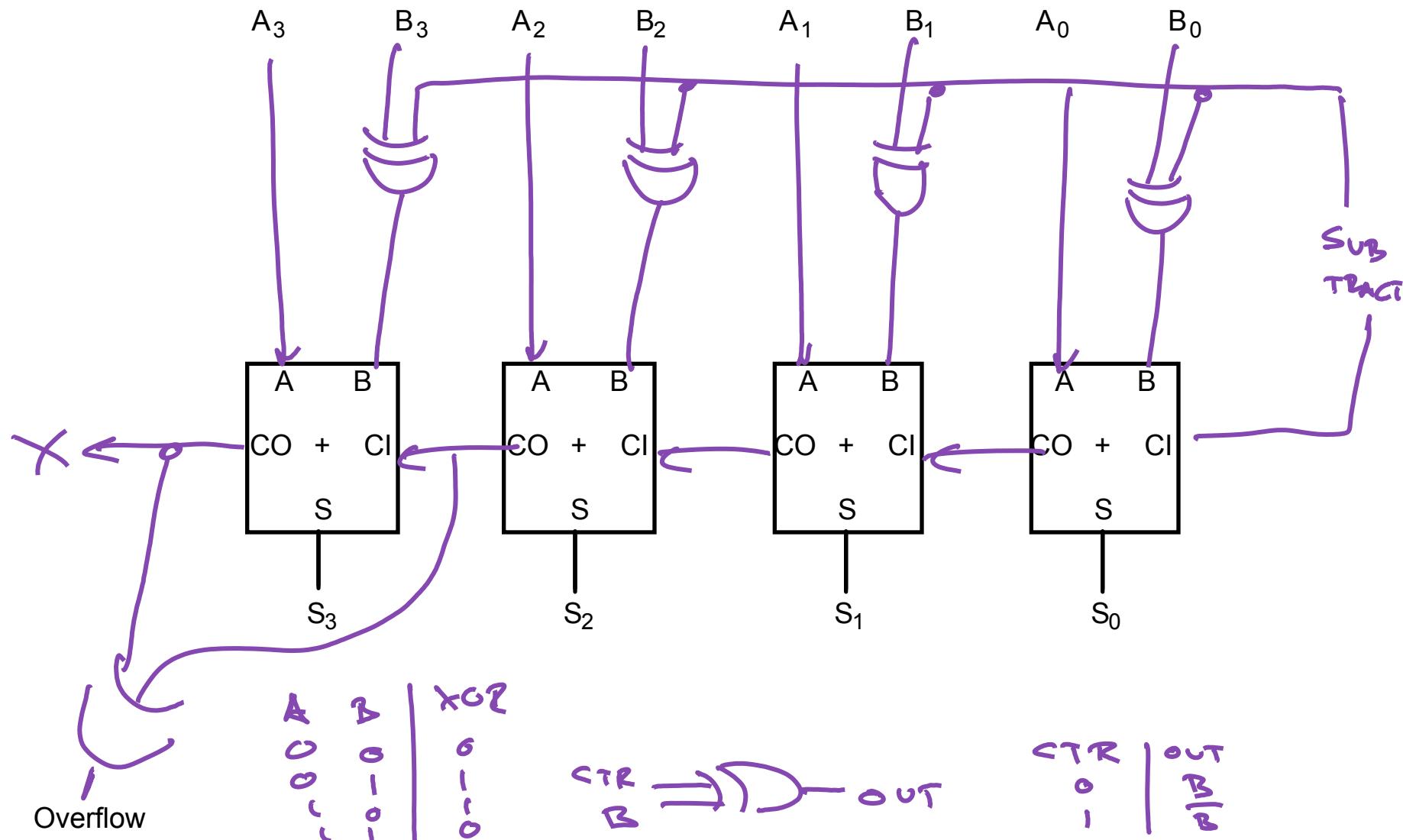

$$A - B = A + (-B) = A + \bar{B} + 1$$

# Converting Decimal to Two's Complement

---

- Convert absolute value to unsigned binary, then fixed width, then negate if necessary
- Convert  $(-9)_{10}$  to 6-bit Two's Complement
- Convert  $(9)_{10}$  to 6-bit Two's Complement

# Converting Two's Complement to Decimal

---

- If Positive, convert as normal;  
If Negative, negate then convert.
  
- Convert  $(11010)_2$  to Decimal
  
- Convert  $(01101)_2$  to Decimal

# Sign Extension

---

- To convert from N-bit to M-bit Two's Complement ( $N < M$ ), simply duplicate sign bit:
- Convert  $(0010)_2$  to 8-bit Two's Complement
- Convert  $(1011)_2$  to 8-bit Two's Complement