 


# Finite State Machines

---


- **Readings: 6-6.4.7**
- Need to implement circuits that remember history
  - Traffic Light controller, Sequence Lock, ...
- History will be held in flip flops
- Sequential Logic needs more complex design steps
  - State Diagram to describe behavior
  - State Table to specify functions (like Truth Table)
  - Implementation of combinational logic as controller



# Finite State Machine Example
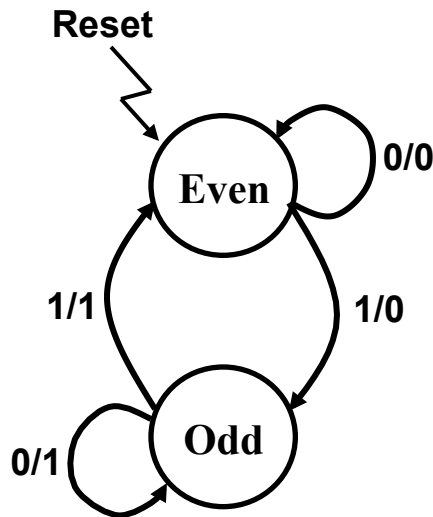
## Example: Odd Parity Checker

Assert output whenever have previously seen an odd # of 1's  
(I.e. how many have you seen NOT INCLUDING the current one)





State  
Diagram

Present State	Input	Output	Next State
0	0		
0	1		
1	0		
1	1		

Even: State = 0, Odd: State = 1
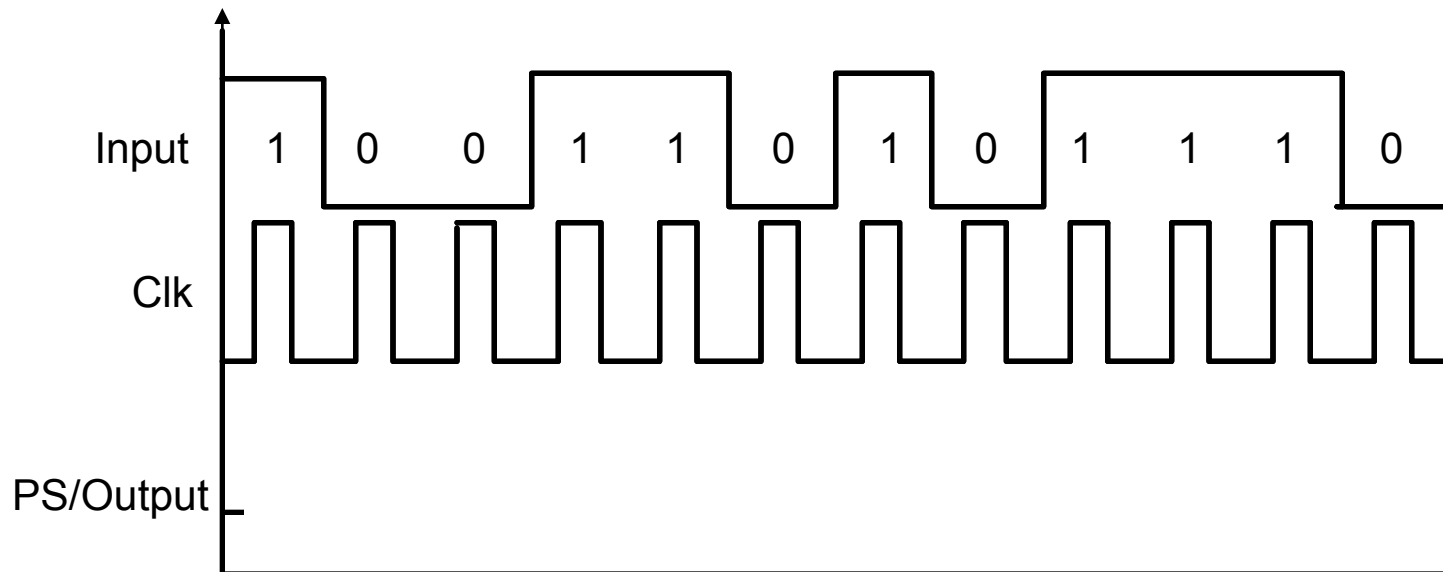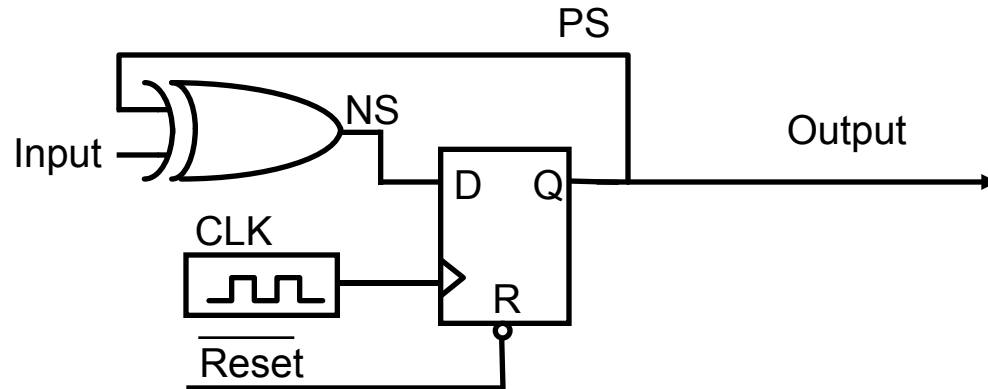
# Finite State Machine Example (cont.)


$$\text{NS} = \text{PS} \text{ xor Input}; \quad \text{OUT} = \text{PS}$$


 
# State Diagrams

---

- Graphical diagram of FSM behavior
- States represented by circles
- Transitions (actions) represented by arrows connecting states
- Labels on Transitions give  $\langle \text{triggering input pattern} \rangle / \langle \text{outputs} \rangle$ 
  - Note: We cover Mealy machines here; Moore machines put outputs on states, not transitions
- Finite State Machine: State Diagram with finite number of states



# FSM Design Process

---

- 1. Understand the problem
- 2. Draw the state diagram
- 3. Use state diagram to produce state table
- 4. Implement the combinational control logic


# Vending Machine Example

---

## ■ Vending Machine:

- Deliver package of gum after  $\geq 10$  cents deposited
- Single coin slot for dimes, nickels
- No change returned

## ■ State Diagram:

 

# Vending Machine Example (cont.)

---

- State Table:

# Vending Machine Example (cont.)

---

- Implementation:



# FSMs in Verilog - Declarations

---

```
module simple (clk, reset, w, out);  
    input      clk, reset, w;  
    output     out;  
  
    reg  [1:0] ps; // Present State  
    reg  [1:0] ns; // Next State
```

# FSMs in Verilog – Combinational Logic

---

```
parameter [1:0] A = 2'b00, B = 2'b01, C = 2'b10;

// Next State Logic
always @(*) begin
    case (ps)
        A: if (w)   ns = B;
           else    ns = A;
        B: if (w)   ns = C;
           else    ns = A;
        C: if (w)   ns = C;
           else    ns = A;
        default:   ns = 2'bxx;
    endcase
end

// Output Logic - could also be "always",
// or part of next-state logic.
assign out = (ps == C);
```

# FSMs in Verilog – DFFs

---

```
// Sequential Logic (DFFs)
always @(posedge clk)
    if (reset)
        ps <= A;
    else
        ps <= ns;

endmodule
```

# FSM Testbench

---

```
module simple_testbench();
    reg        clk, reset, w;
    wire       out;

    simple dut (.clk, .reset, .w, .out);

    // Set up the clock.
    parameter CLOCK_PERIOD=100;

    initial clk=1;



    always begin
        #(CLOCK_PERIOD/2);
        clk = ~clk;
    end
end
```

# FSM Testbench (cont.)

---

```
// Design inputs. Each line is a clock cycle.
// ONLY USE THIS FORM for testbenches!!!
initial begin
    @ (posedge clk);
    reset <= 1; @ (posedge clk);
    reset <= 0; w <= 0; @ (posedge clk);
    @ (posedge clk);
    @ (posedge clk);
    @ (posedge clk);
    w <= 1; @ (posedge clk);
    w <= 0; @ (posedge clk);
    w <= 1; @ (posedge clk);
    @ (posedge clk);
    @ (posedge clk);
    @ (posedge clk);
    w <= 0; @ (posedge clk);
    @ (posedge clk);
    $stop; // End the simulation.
end
endmodule
```

# Testbench Waveforms

  

# String Recognizer Example

---

- Recognize the string: 101

- Input: 1 0 0 1 0 1 0 1 1 0 0 1 0

- Output:

- State Machine:

# String Recognizer Example (cont.)

---

- State Table:



= vs. <=

---

- = (“Blocking”) assign immediately
- <= (“Non-Blocking”) first eval all righthand sides, then do all assignments simultaneously.

```
module swap1();
...
reg [3:0] val0, val1;

always @(posedge clk) begin
    if (swap) begin
        val0=val1;
        val1=val0;
    end
    out=val1;
end
endmodule
```

```
module swap2();
...
reg [3:0] val0, val1;

always @(posedge clk) begin
    if (swap) begin
        val0<=val1;
        val1<=val0;
    end
    out<=val1;
end
endmodule
```

# = vs. <= in practice

---

- = in combinational logic: always @\*
- <= in sequential, ps<=ns: always @(posedge clk)
- NEVER mix in one always block!
- Each variable written in only one always block

```
// Output logic
always @(*) begin
    out = (ps == A);

// Next State Logic
always @(*) begin
    case (ps)
        A: if (w)    ns = B;
           else    ns = A;
        B: if (w)    ns = C;
           else    ns = A;
        C: if (w)    ns = C;
           else    ns = A;
        default: ns = 2'bxx;
    endcase
end
```

```
// Sequential Logic
always @(posedge clk) begin
    if (reset)
        ps <= A;
    else
        ps <= ns;
end
```

# Subdividing FSMs

---

- Some problems best solved with multiple pieces
- Psychic Tester:
  - Machine generates pattern of 4 values (on or off)
  - If user guesses 8 patterns in a row, they're psychic
- States?

## Subdividing FSMs (cont.)

---

- Pieces?