

Number Systems

- Readings: 3-3.3.3, 3.3.5
- Problem: Implement simple pocket calculator
- Need: Display, adders & subtractors, inputs
 - Display: Seven segment displays
 - Inputs: Switches
- Missing: Way to implement numbers in binary

- Approach: From decimal to binary numbers
(and back)

Arithmetic Operations

Decimal:

$$\begin{array}{r} 5\ 7\ 8\ 9\ 2 \\ +\ 7\ 8\ 9\ 5\ 6 \\ \hline \end{array}$$

Binary:

$$\begin{array}{r} 1\ 0\ 1\ 0\ 1\ 1\ 1 \\ +\ 0\ 1\ 0\ 0\ 1\ 0\ 1 \\ \hline \end{array}$$

Decimal:

$$\begin{array}{r} 5\ 7\ 8\ 9\ 2 \\ -\ 3\ 2\ 9\ 4\ 6 \\ \hline \end{array}$$

Binary:

$$\begin{array}{r} 1\ 0\ 1\ 0\ 0\ 1\ 1\ 0 \\ -\ 0\ 0\ 1\ 1\ 0\ 1\ 1\ 1 \\ \hline \end{array}$$

Arithmetic Operations (cont.)

Decimal:


$$\begin{array}{r} 201 \\ * 214 \\ \hline \end{array}$$

Binary:


$$\begin{array}{r} 1001 \\ * 1011 \\ \hline \end{array}$$

Half Adder


A_i	B_i	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

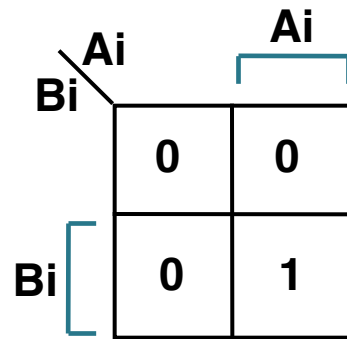

$$\text{Carry} = A_i B_i$$

 
 
$$\begin{aligned} \text{Sum} &= \bar{A}_i B_i + A_i \bar{B}_i \\ &= A_i \oplus B_i \end{aligned}$$



Half-adder Schematic

Full Adder

A	B	CI	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder Implementation

Multi-Bit Addition

A₃

B₃

A₂

B₂





A₁

B₁

A₀

B₀
    
$$\begin{array}{r} A_3 A_2 A_1 A_0 \\ + B_3 B_2 B_1 B_0 \\ \hline \end{array}$$



Multi-Bit Addition in Verilog, Parameters

```
module uadd #(parameter WIDTH=8)
  (out, a, b);
  output reg [WIDTH:0] out;
  input      [WIDTH-1:0] a, b;

  always @(*) begin
    out = a + b;
  end
endmodule
```


```
module add4 #(parameter W=22)
  (out, a, b, c, d);
  output [W+1:0] out;
  input  [W-1:0] a, b, c, d;
```

```
endmodule
```


Negative Numbers

- Need an efficient way to represent negative numbers in binary
 - Both positive & negative numbers will be strings of bits
 - Use fixed-width formats (4-bit, 16-bit, etc.)
- Must provide efficient mathematical operations
 - Addition & subtraction with potentially mixed signs
 - Negation (multiply by -1)

Sign/Magnitude Representation

 

High order bit is sign: 0 = positive (or zero), 1 = negative

Three low order bits is the magnitude: 0 (000) thru 7 (111)

Number range for n bits = $\pm 2^{n-1} - 1$

Representations for 0:

Sign/Magnitude Addition

$$\begin{array}{r} 0\ 0\ 1\ 0\ (+2) \\ +\ 0\ 1\ 0\ 0\ (+4) \\ \hline \end{array}$$

$$\begin{array}{r} 1\ 0\ 1\ 0\ (-2) \\ +\ 1\ 1\ 0\ 0\ (-4) \\ \hline \end{array}$$

$$\begin{array}{r} 0\ 0\ 1\ 0\ (+2) \\ +\ 1\ 1\ 0\ 0\ (-4) \\ \hline \end{array}$$

$$\begin{array}{r} 1\ 0\ 1\ 0\ (-2) \\ +\ 0\ 1\ 0\ 0\ (+4) \\ \hline \end{array}$$

Bottom line: Basic mathematics are too complex in Sign/Magnitude

Idea: Pick negatives so that addition works

- Let $-1 = 0 - (+1)$:

$$\begin{array}{r} 0\ 0\ 0\ 0\ (0) \\ -\ 0\ 0\ 0\ 1\ (+1) \\ \hline \end{array}$$


- Does addition work?

$$\begin{array}{r} 0\ 0\ 1\ 0\ (+2) \\ +\ 1\ 1\ 1\ 1\ (-1) \\ \hline \end{array}$$

- Result: Two's Complement Numbers

Two's Complement

 
- Only one representation for 0
- One more negative number than positive number
- Fixed width format for both pos. & neg. numbers



Negating in Two's Complement

- Flip bits & Add 1
- Negate $(0010)_2$ (+2)

- Negate $(1110)_2$ (-2)

 

Addition in Two's Complement

$$\begin{array}{r} 0010 (+2) \\ + 0100 (+4) \\ \hline \end{array}$$

$$\begin{array}{r} 1110 (-2) \\ + 1100 (-4) \\ \hline \end{array}$$

$$\begin{array}{r} 0010 (+2) \\ + 1100 (-4) \\ \hline \end{array}$$

$$\begin{array}{r} 1110 (-2) \\ + 0100 (+4) \\ \hline \end{array}$$

Subtraction in Two's Complement

■ $A - B = A + (-B) = A + \bar{B} + 1$



■ $0010 - 0110$

■ $1011 - 1001$

■ $1011 - 0001$

Overflows in Two's Complement

  Add two positive numbers but get a negative number
or two negative numbers but get a positive number



Overflow Detection in Two's Complement

5 0 1 0 1
3 0 0 1 1

-8

Overflow

-7 1 0 0 1
-2 1 1 1 0

7

Overflow

5 0 1 0 1
2 0 0 1 0

7

No overflow


-3 1 1 0 1
-5 1 0 1 1

-8

No overflow

Adder/Subtractor

A₃ B₃ A₂ B₂ A₁ B₁ A₀ B₀

 

Overflow

$$\mathbf{A - B = A + (-B) = A + \overline{B} + 1}$$

Multi-Bit Addition in Verilog, Parameters

```
module uadd #(parameter WIDTH=8)
  (out, a, b);
  output reg [WIDTH:0] out;
  input      [WIDTH-1:0] a, b;

  always @(*) begin
    out = a + b;
  end
endmodule

module add4 #(parameter W=22)
  (out, a, b, c, d);
  output [W+1:0] out;
  input  [W-1:0] a, b, c, d;

  wire [W:0] ab, cd;

  uadd #(.WIDTH(W))    u_ab    (ab, a, b);
  uadd #(.WIDTH(W))    u_cd    (cd, c, d);
  uadd #(.WIDTH(W+1)) u_abcd  (out, ab, cd);
endmodule
```

Converting Decimal to Two's Complement

- Convert absolute value to unsigned binary, then fixed width, then negate if necessary
- Convert $(-9)_{10}$ to 6-bit Two's Complement
- Convert $(9)_{10}$ to 6-bit Two's Complement

Converting Two's Complement to Decimal


- If Positive, convert as normal;
If Negative, negate then convert.
- Convert $(11010)_2$ to Decimal
- Convert $(01101)_2$ to Decimal

Sign Extension

- To convert from N-bit to M-bit Two's Complement ($N < M$), simply duplicate sign bit:
- Convert $(0010)_2$ to 8-bit Two's Complement
- Convert $(1011)_2$ to 8-bit Two's Complement

Solving Complex Problems

 - Many problems too complex to build as one system
 - Replace with communicating sub-circuits



- Design process:
 - Understand the problem
 - Break problem into subsystems, identifying connections
 - Design individual subsystems.

Complex Problem Example

- Design a digital clock, which can
 - Display the seconds, minutes and hours
 - Have three inputs
 - Increment hour
 - Increment minute
 - Reset seconds

Complex Problem Example (cont.)

Complex Problem Example (cont.)

Complex Problem Example (cont.)

Complex Problem Example

- Break into pieces:
 - Display, counter
 - Displayer becomes 6x 7-segment displays
 - Counter becomes three counters
 - Minutes, hours, seconds.
 - Need reset on seconds, override on increment on hours, minutes.
 - Break counters into digits, except hours.
 - Communicate increment to higher