

 
 


Review Problem

 - If all gates have a delay of 1ns, how long does a 4-bit adder take to compute?



=

 


7s

Basic Circuit Elements

- Readings: 4-4.1.1, 4.2, 4.3-4.3.2
- Standard TTL Small-Scale Integration:
 - 1 chip = 2-8 gates
 - Requires numerous chips to build interesting circuits
- Alternative: Complex chips for standard functions
 - Single chip that performs very complex computations
- Multiplexer/Decoder/Encoder: Standard routing elements for interconnections
- FPGAs: Programmable for arbitrary functions


Design Example: Basic Telephone System

- Put together a simple telephone system

 

Basic Telephone System (cont.)

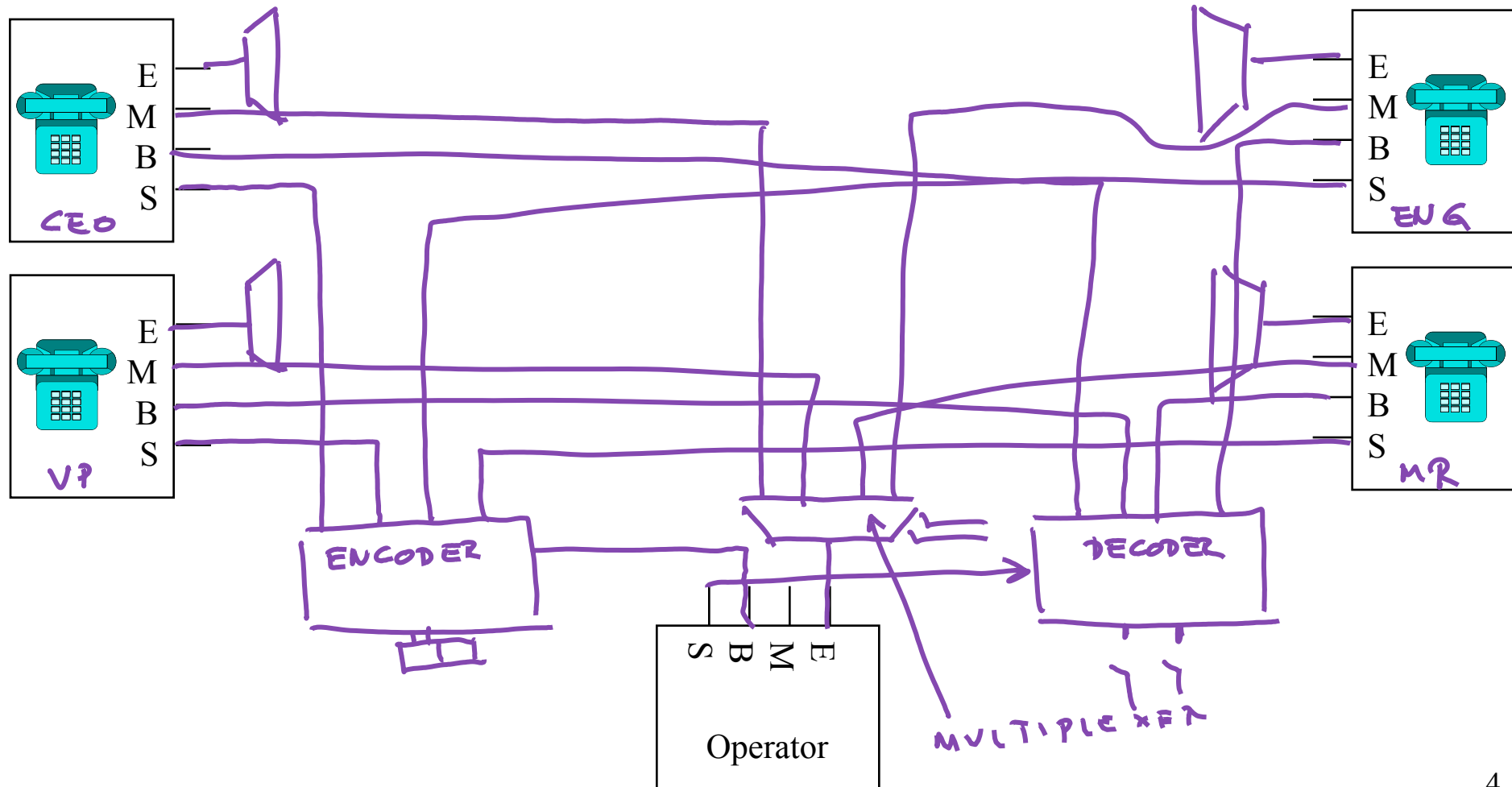- Multiple subscribers, one operator.
- Operator controls all connections




Standard Circuit Elements

- Develop implementations of important “Building Blocks”
 - Used in Networks, Computers, Stereos, etc.
- Multiplexer: Combine N sources onto 1 wire
- Encoder: Determine which input is active
- Decoder: Convert binary to one-of- N wires


Decoders

 - Used to select one of 2^N outputs based on N input bits
- Input: N bits; output: 2^N outputs -- only *one* is active
- A decoder that has n inputs and m outputs is referred to as an $n \times m$, $N:M$, or n -to- m decoder
- Example: 3-to-8 decoder



Decoder Implementation

S1	S0	D3	D2	D1	D0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

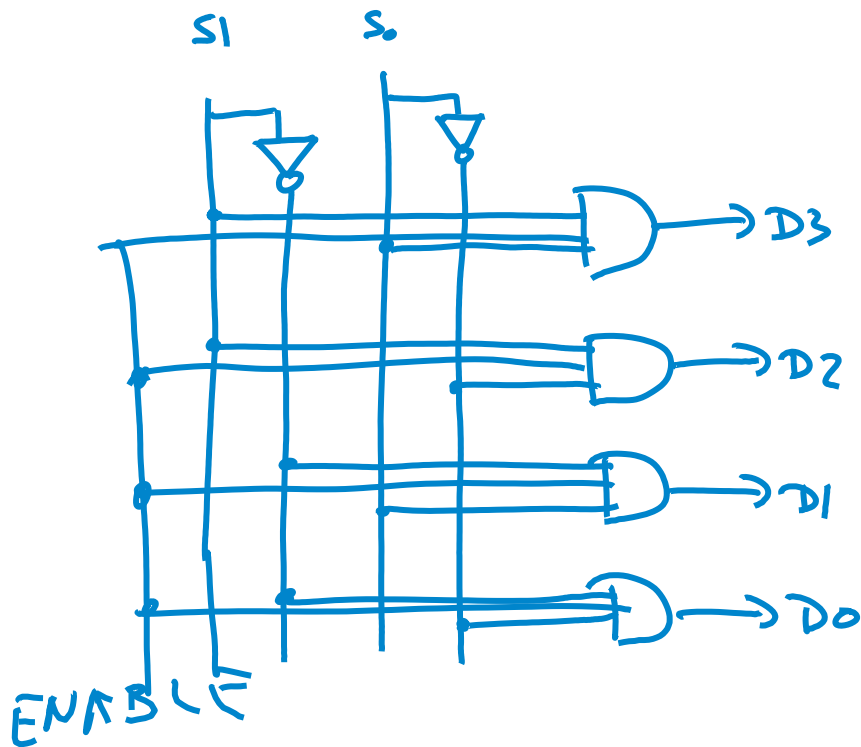

Enabled Decoder Implementation

❖ Active High enable

En	S1	S0	D3	D2	D1	D0
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

SEE
PREVIOUS
SLIDE

Enabled Decoders in Verilog

```
module enDecoder2_4 (out, in, enable);  
    output reg [3:0] out;  
    input      [1:0] in;  
    input      enable;
```

```
    always @(*) begin
```

```
        if (enable)
```

```
            case (in)
```

```
                2'b00: out = 4'b0001;
```

```
                2'b01: out = 4'b0010;
```

```
                :
```

```
            endcase
```

```
        else
```

```
            out = 4'b0000;
```

```
    endmodule
```

Encoders

- Performs the inverse operation of decoders
- Input: 2^N or less lines -- only 1 is asserted at any given time
- Output: N output lines
- Function: the output is the binary representation of the ID of the input line that is asserted


Encoder Implementation

❖ 4:2 Encoder

D3	D2	D1	D0	A1	A0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

$$A1 = D2 + D3$$

$$A0 = D1 + D3$$

 

1) WHEN NO ONE CALLS \rightarrow CODE 00

2) D2 AND D1 CALL \rightarrow CODE 11 (D3)


Priority Encoder

- Use priorities to resolve the problem of 2 or more input lines active at a time.
- One scheme: Highest ID active wins
- Also add an output to identify when at least 1 input active

D3	D2	D1	D0	A1	A0	Valid
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

Multiplexer

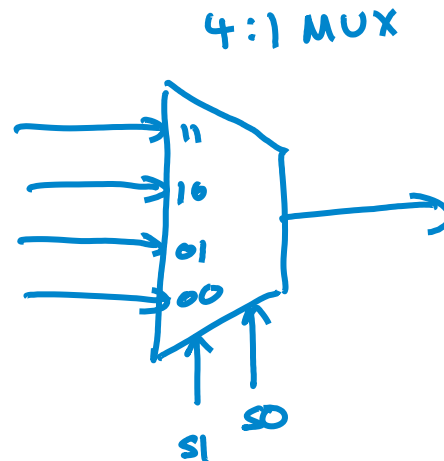- An element that selects data from one of many input lines and directs it to a single output line
- Input: 2^N input lines and N selection lines
- Output: the data from *one* selected input line
- Multiplexer often abbreviated as MUX



Multiplexer Implementation

■ 4:1 MUX


S1	S0	F
0	0	D0
0	1	D1
1	0	D2
1	1	D3

$$F = \overline{S1} \overline{S0} D0 + \overline{S1} S0 D1 + S1 \overline{S0} D2 + S1 S0 D3$$

Multiplexers in General Logic

- Implement $F = \overline{X}YZ + Y\overline{Z}$ with a 8:1 MUX

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 

Multiplexers in General Logic (cont.)

- Implement $F = \overline{X}YZ + Y\overline{Z}$ with a 4:1 MUX

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

