

Review Problem 4

- Simplify the following Boolean Equation

$$AB + AC + \overline{A}B$$

$$= AB + \overline{A}B + AC \quad (\text{COMM.})$$

$$= (A + \overline{A})B + AC \quad (\text{DIST.})$$

$$= B + AC \quad (\text{UNITY})$$

Review Problem 5



- Simplify the following Boolean Equation, starting with DeMorgan's Law

$$\overline{F} = \overline{A\overline{B}} + AC$$

$$\begin{aligned} F &= \overline{\overline{A\overline{B}} + AC} \\ &= \overline{(\overline{A\overline{B}})} \overline{(AC)} \\ &= (\overline{\overline{A}} + \overline{\overline{B}})(\overline{A} + \overline{C}) \\ &= \overline{\overline{A}} + \overline{\overline{B}} + \overline{A}\overline{C} + \overline{B}\overline{C} \\ &= \overline{\overline{A}} (1 + \overline{C} + \overline{B}) + \overline{B}\overline{C} \\ &= \overline{\overline{A}} + \overline{B}\overline{C} \end{aligned}$$



Circuit Timing Behavior

  - Simple model: gates react after fixed delay




Hazards/Glitches

 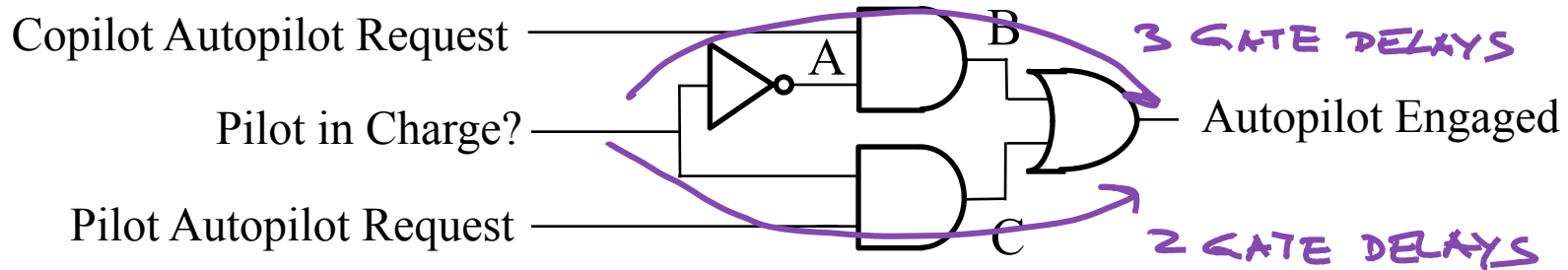- Circuit can temporarily go to incorrect states



Field Programmable Gate Arrays (FPGAs)

 

Logic cells imbedded in a general routing structure



Logic cells usually contain:

- **6-input Boolean function calculator**
- **Flip-flop (1-bit memory)**

All features electronically (re)programmable

Using an FPGA

```
// Verilog code for 2-input multiplexer
module AOI (F, A, B, C, D);
  output F;
  input A, B, C, D;
  assign F = ~(A & B) | (C & D);
endmodule

module MUX2 (V, SEL, I, J); //
  2:1 multiplexer
  output V;
  input SEL, I, J;
  wire SELB, VB;

  not G1 (SELB, SEL);
  AOI G2 (VB, I, SEL, SELB, J);
  not G3 (V, VB);
endmodule
```

Verilog




FPGA
CAD
Tools




```
00101010001010010
10010010010011000
10101000101011000
10101001010010101
00010110001001010
10101001111001001
01000010101001010
10010010000101010
10100101010010100
01010110101001010
01010010100101001
```

Bitstream

 


Simulation

 

Verilog

- Programming language for describing hardware
 - Simulate behavior before (wasting time) implementing
 - Find bugs early
 - Enable tools to automatically create implementation
- Similar to C/C++/Java
 - VHDL similar to ADA
- Modern version is “System Verilog”
 - Superset of previous; cleaner and more efficient

Structural Verilog

 

// Verilog code for AND-OR-INVERT gate

FUNCTION

```
module AOI (F, A, B, C, D);  
    output F;  
    input A, B, C, D;
```


CONTINUOUS ASSIGNMENT: F CHANGES WHEN INPUTS CHANGE

```
    assign F = ~((A & B) | (C & D));  
endmodule
```

NOT *AND* *OR*

```
// end of Verilog code
```


Verilog Wires/Variables

 


// Verilog code for AND-OR-INVERT gate

```
module AOI (F, A, B, C, D);  
    output F;  
    input A, B, C, D;  
    wire AB, CD, O; // necessary  
  
    assign AB = A & B;  
    assign CD = C & D;  
    assign O = AB | CD;  
    assign F = ~O;  
endmodule
```

LOCAL
VARIABLE
IN MODULE;
ACTUAL WIRE

Verilog Gate Level

 

// Verilog code for AND-OR-INVERT gate

```
module AOI (F, A, B, C, D);  
    output F;  
    input A, B, C, D;  
    wire AB, CD, O; // necessary
```

```
    and a1(AB, A, B);
```

```
    and a2(CD, C, D);
```

```
    or o1(O, AB, CD);
```

```
    not n1(F, O);
```

```
endmodule
```

OTHER KEYWORDS:


NAND, NOR, XOR, XNOR, BUF

Verilog Hierarchy

```
// Verilog code for 2-input multiplexer
```

```
module AOI (F, A, B, C, D);  
    output F;  
    input A, B, C, D;  
  
    assign F = ~((A & B) | (C & D));  
endmodule
```

2-input Mux

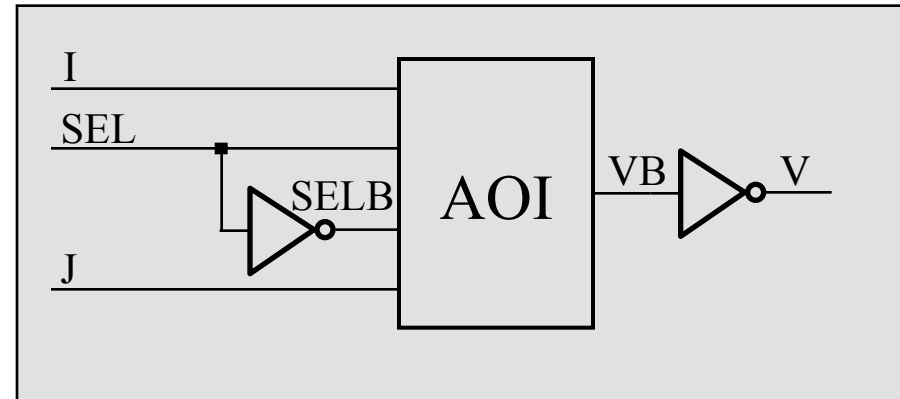


```
module MUX2 (V, SEL, I, J);    // 2:1 multiplexer  
    output V;  
    input SEL, I, J;  
    wire SELB, VB;  
  
    not G1 (SELB, SEL);  
    AOI G2 (.F(VB), .A(I), .B(SEL), .C(SELB), .D(J));  
    not G3 (V, VB);  
endmodule
```

G2(VB, I, SEL, SELB, J)

*ORDER DOESN'T
MATTER IN THIS
NOTATION*

Verilog Testbenches

 reg: SIMULATION REGISTER - KEEPS TRACK OF A SIGNAL VALUE (USE "reg" IN "INITIAL" AND "ALWAYS" BLOCK, ELSE WIRE)



```

module MUX2TEST; // No ports!
  reg SEL, I, J; // Remembers value -

```

```

reg
  wire V;

```

TIME	SEL	I	J
0	100	0	
10	110	1	
20	010	0	
30	011	1	

```

  initial // Stimulus

```

```

  begin

```

```

    SEL = 1; I = 0; J = 0;

```

```

    #10 I = 1;

```

```

    #10 SEL = 0;

```

```

    #10 J = 1; .V(V)

```

```

  end

```

```

  MUX2 M (.V, .SEL, .I, .J);

```

```

  initial // Response

```


```

    $monitor($time, , SEL, I, J, , V);


```

Debugging Complex Circuits

 - Complex circuits require careful debugging
 - Rip up and retry?
- Ex. Debug a 9-input odd parity circuit
 - True if an odd number of inputs are true



Debugging Complex Circuits (cont.)

 

DON'T


Debugging Approach

- Test all behaviors.
 - All combinations of inputs for small circuits, subcircuits.
- Identify any incorrect behaviors.
- Examine inputs and outputs to find earliest place where value is wrong.
 - Typically, trace backwards from bad outputs, forward from inputs.
 - Look at values at intermediate points in circuit.

■ DO NOT RIP UP, DEBUG!

Combinational vs. Sequential Logic

❖ Readings: 5-5.4.4

 

Network implemented from logic gates. The presence of feedback distinguishes between **sequential** and **combinational** networks.

Combinational logic

no feedback among inputs and outputs
outputs are a pure function of the inputs
e.g., seat belt light:

(Dbelt, Pbelt, Passenger) mapped into (Light)

