

# Optimization via K-Maps to 2-level forms

---

- Readings: 2.11-2.12.2, 2.14
- Sum of Products form: the OR of several AND gates, inversions over only inputs
  - $F = \bar{X} + Y\bar{Z} + XYZ$
- Circuit diagram & inversions:

# On Sets and Off Sets

---

X	Y	Z	H
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

❖ On Set is the set of input patterns where the function is TRUE

❖ Off Set is the set of input patterns where the function is FALSE

# Two-Level Simplification

**Key Tool: The Uniting Theorem —  $A(\bar{B} + B) = A$**

A	B	F
0	0	0
0	1	0
1	0	1
1	1	1

$$F = A\bar{B} + AB = A(\bar{B} + B) = A$$

**B's values change within the on-set rows**

***B is eliminated, A remains***

**A's values don't change within the on-set rows**

A	B	G
0	0	1
0	1	0
1	0	1
1	1	0

$$G = \bar{A}\bar{B} + A\bar{B} = (\bar{A} + A)\bar{B} = \bar{B}$$

**B's values stay the same within the on-set rows**

***A is eliminated, B remains***

**A's values change within the on-set rows**

**Essence of Simplification:**

**find two element subsets of the ON-set where only one variable changes its value. This single varying variable *can be eliminated!***


# Karnaugh Maps

## *Karnaugh Map Method*



**K-map is an alternative method of representing the truth table that helps visualize adjacencies in up to 4 dimensions**

**Beyond that, computer-based methods are needed**

**2-variable  
K-map**

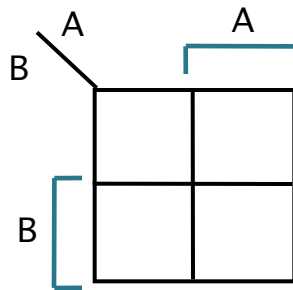


**3-variable  
K-map**

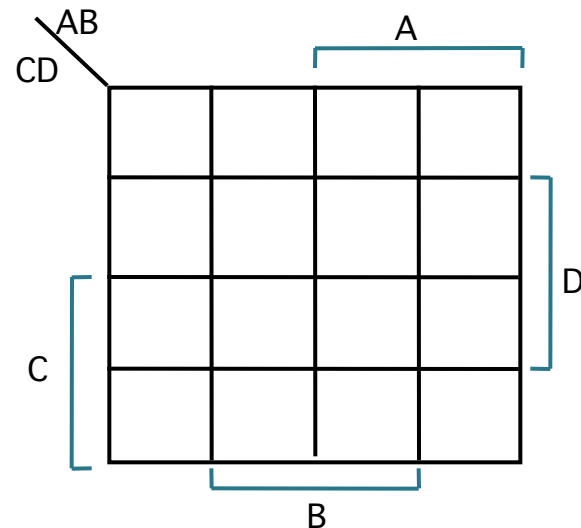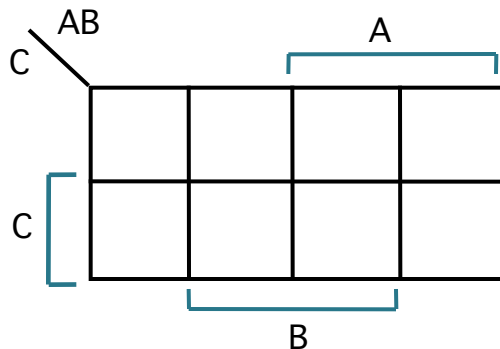


**4-variable  
K-map**

# Truth Tables to K-Maps


AB	F
0 0	0
0 1	0
1 0	1
1 1	0

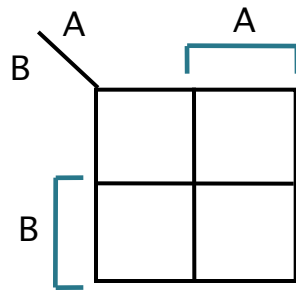

ABC	G
0 0 0	0
0 0 1	1
0 1 0	1
0 1 1	1
1 0 0	1
1 0 1	0
1 1 0	0
1 1 1	0

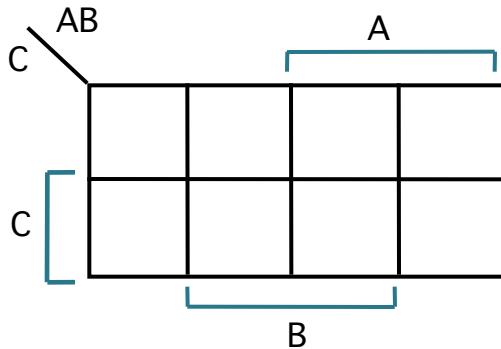

A	B	C	D	H
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

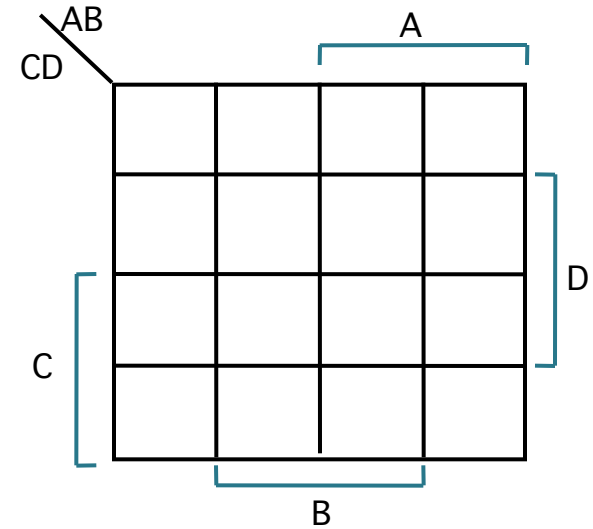

# K-Map Simplification

## K-Map Method Examples

A		A
B	0	1
	0	1

**F =**

A		A
B	1	1
	0	0

**G =**

A B		A		
Cin	0	0	1	0
	0	1	1	1
		B		

**Cout =**

AB		A		
C	0	0	1	1
	0	0	1	1
		B		

**F(A,B,C) =**

# K-Map Simplification (cont.)

## More K-Map Method Examples, 3 Variables

AB C		A			
		0	1	1	0
C	0	1	0	0	1
	1	0	0	1	1
		B			

$$F(A,B,C) = \bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + A \bar{B} C + A B C$$

F =

In the K-map, adjacency wraps from left to right and from top to bottom

AB C		A			
		0	1	1	0
C	0	1	0	0	1
	1	0	1	1	0
		B			

$\bar{F}$  simply replace 1's with 0's and vice versa


$$\bar{F}(A,B,C) = \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} C + A B \bar{C}$$

$\bar{F} =$

# 4-Variable K-Map

---

## *K-map Method Examples: 4 variables*

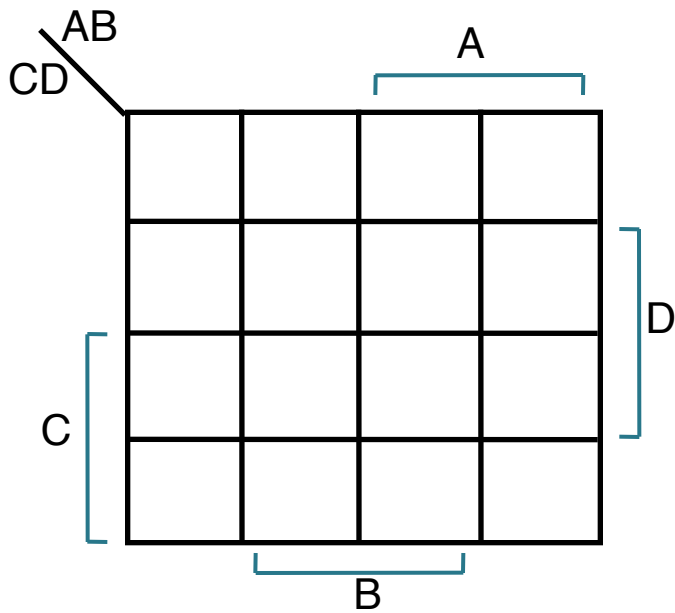

$$F = \overline{A}D + BD + \overline{B}C + \overline{A}B\overline{D}$$




# K-Map Example

---


$$F = (A \text{ xor } C) * D + A\bar{C}\bar{D} + \bar{A}BC\bar{D}$$

# K-Map Example with Multiple Solutions

---

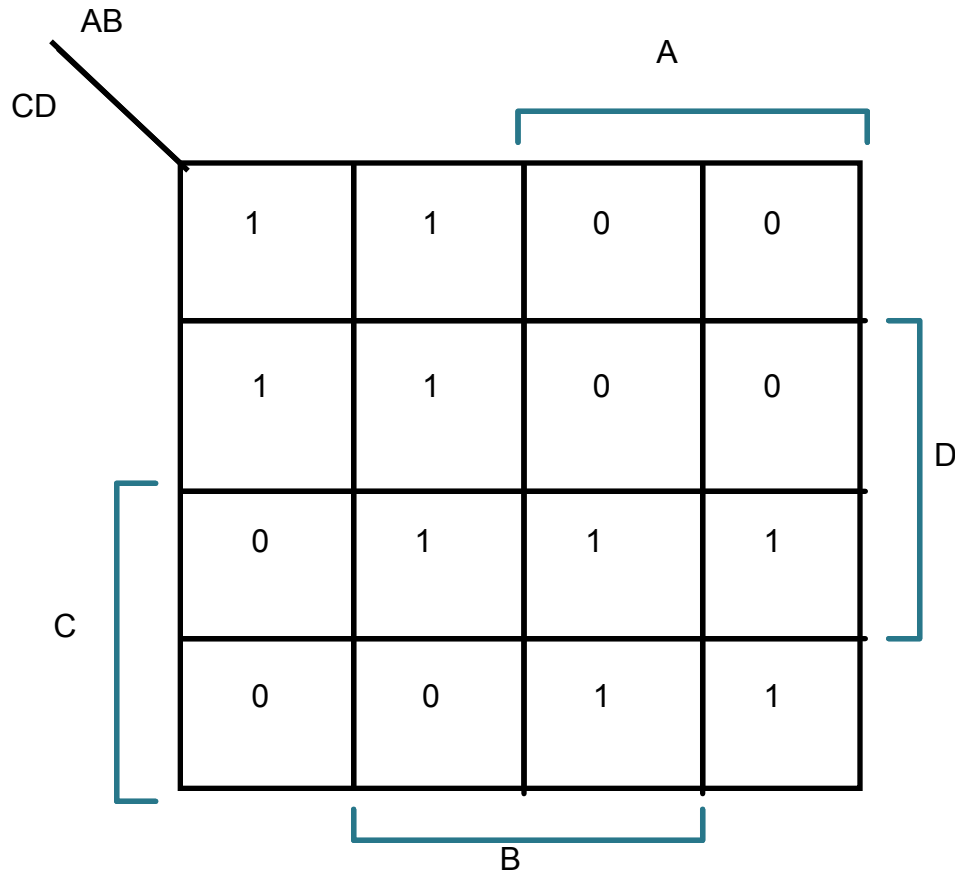

# Design Example: 2-bit Adder

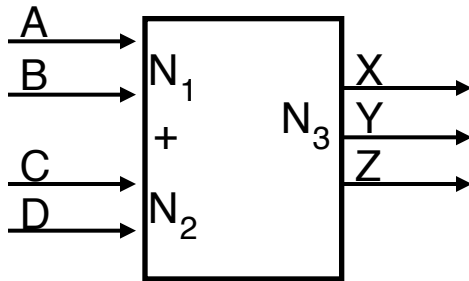

A	B	C	D	X	Y	Z
0	0	0	0	0	0	0
		0	1	0	0	1
		1	0	0	1	0
		1	1	0	1	1
0	1	0	0	0	0	1
		0	1	0	1	0
		1	0	0	1	1
		1	1	1	0	0
1	0	0	0	0	1	0
		0	1	0	1	1
		1	0	1	0	0
		1	1	1	0	1
1	1	0	0	0	1	1
		0	1	1	0	0
		1	0	1	0	1
		1	1	1	1	0

**Block Diagram  
and  
Truth Table**

# Design Example (cont.)

	AB		A		
CD					
	0	0	0	0	
	0	0	1	0	D
C	0	1	1	1	
	0	0	1	1	
			B		

K-map for X

	AB		A		
CD					
	0	0	1	1	
	0	1	0	1	D
C	1	0	1	0	
	1	1	0	0	
			B		

K-map for Y

	AB		A		
CD					
	0	1	1	0	
	1	0	0	1	D
C	1	0	0	1	
	0	1	1	0	
			B		

K-map for Z

**X =**

**Z =**

**Y =**

# Don't Cares

Don't Cares can be treated as 1's or 0's if it is advantageous to do so

	AB		A		
CD					
	0	0	X	0	
	1	1	X	1	D
	1	1	0	0	
C	0	X	0	0	
	B				

If all X=0, then

F =

	AB		A		
CD					
	0	0	X	0	
	1	1	X	1	D
	1	1	0	0	
C	0	X	0	0	
	B				

If all X=1, then

F =

	AB		A		
CD					
	0	0	X	0	
	1	1	X	1	D
	1	1	0	0	
C	0	X	0	0	
	B				

Using Don't Cares, then

F =



# Design Example: Rock-Paper-Scissors

---

- ❖ Rock (00), Paper (01), Scissors (10) for two players.
- ❖ Output: Winner = Winner's ID (0/1)  
Tie = 1 if Tie, 0 if not

# Rock, Paper, Scissors (cont.)


---

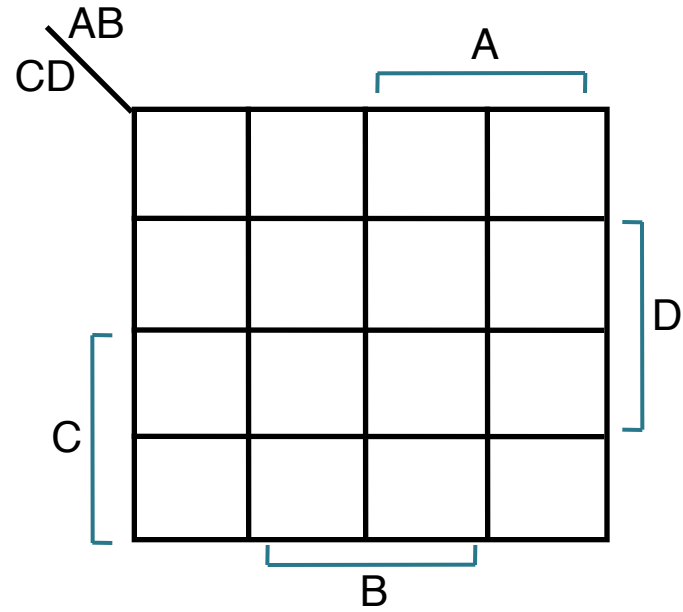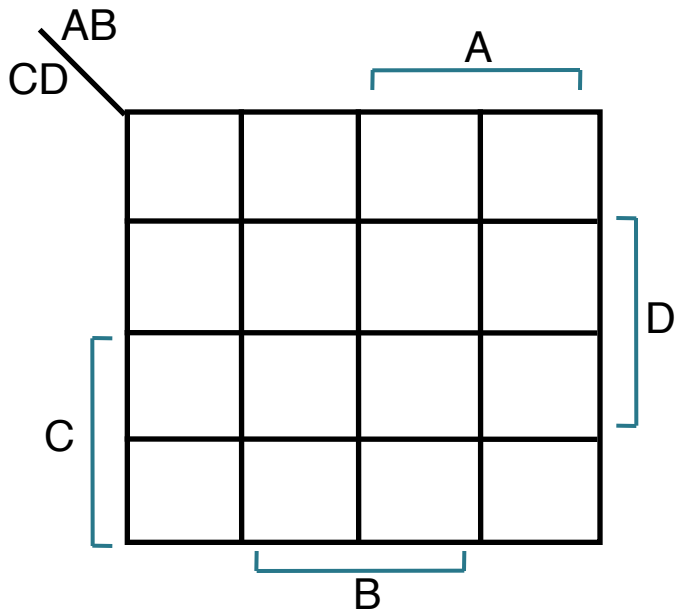

# Case Study: Seven Segment Display

---


## ■ Chip to drive digital display

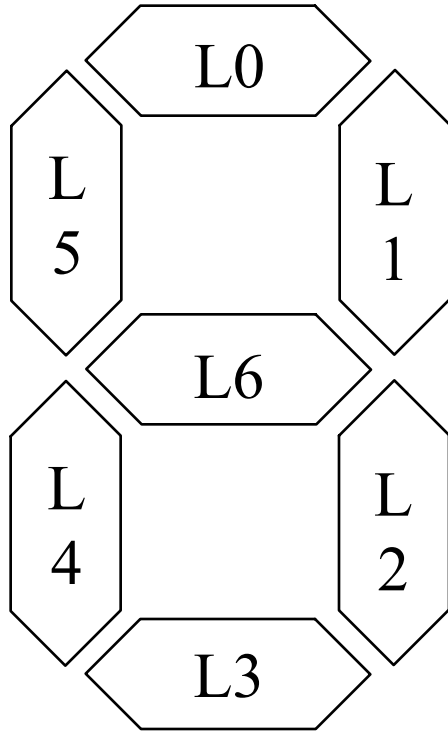


B3	B2	B1	B0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0



# Case Study (cont.)

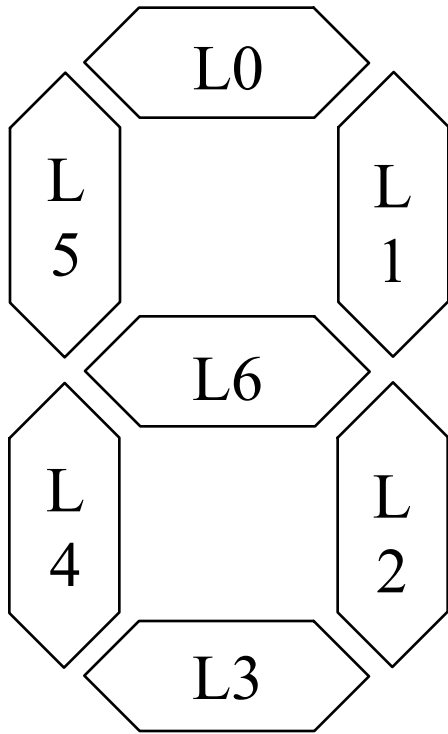

B3	B2	B1	B0	Val	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	0	1	1	0	0	0	0
0	0	1	0	2	1	1	0	1	1	0	1
0	0	1	1	3	1	1	1	1	0	0	1
0	1	0	0	4	0	1	1	0	0	1	1
0	1	0	1	5	1	0	1	1	0	1	1
0	1	1	0	6	1	0	1	1	1	1	1
0	1	1	1	7	1	1	1	0	0	0	0
1	0	0	0	8	1	1	1	1	1	1	1
1	0	0	1	9	1	1	1	1	0	1	1

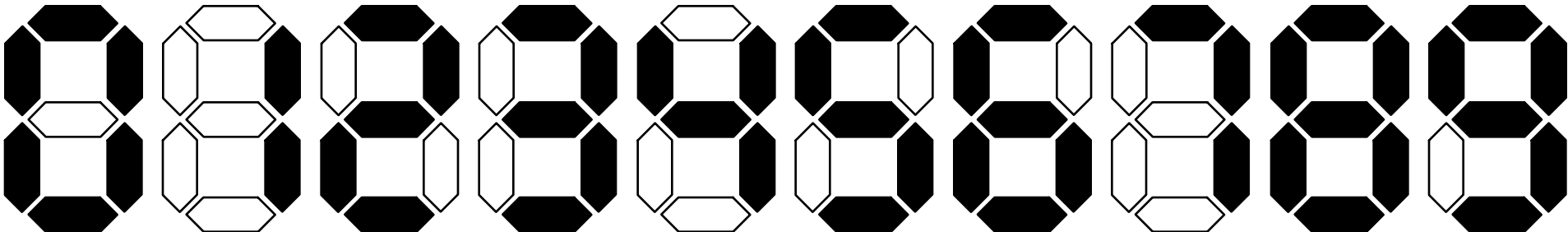

# Case Study (cont.)

---

## ■ Implement L5:

B3	B2	B1	B0	L5
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1

# 7-seg display in Verilog

---

## ■ Verilog RTL: just describe what you want

```
module seg7 (bcd, leds);
  input      [3:0] bcd;
  output reg [6:0] leds;

  always @(*)
    case (bcd)
      // 3210          6543210
      4'b0000: leds = 7'b0111111;
      4'b0001: leds = 7'b0000110;
      4'b0010: leds = 7'b1011011;
      4'b0011: leds = 7'b1001111;
      4'b0100: leds = 7'b1100110;
      4'b0101: leds = 7'b1101101;
      4'b0110: leds = 7'b1111101;
      4'b0111: leds = 7'b0000111;
      4'b1000: leds = 7'b1111111;
      4'b1001: leds = 7'b1101111;
      default: leds = 7'bX;
    endcase
endmodule
```

# Review: Circuit Implementation Techniques

---

- Truth Tables - Case-by-case circuit description
- Boolean Algebra - Math form for optimization
- K-Maps - Simplification technique
- Circuit Diagrams - TTL Implementations
- Verilog – Simulation & Mapping to FPGAs