

# Intro to Digital Design

## SystemVerilog Basics

**Instructor:** Chris Thachuk

**Teaching Assistants:**

Eujean Lee

Nandini Talukdar

Stephanie Osorio-Tristan


Wen Li

# Relevant Course Information

- ❖ Lab demo slots will be assigned on Canvas (*tomorrow*)
- ❖ Lab 1 & 2 – Basic Logic and Verilog (*due 10/16 @ 2:30pm*)
  - Digit(s) recognizer using switches and LED
  - For full credit, find minimal logic
  - Check the lab report requirements closely
- ❖ If you haven't done so yet, pick up a white lab kit + Okiocam ASAP from CSE 003 when TAs are present (labs + office hours)
- ❖ New sections Fridays @ 3 pm on Zoom
  - Materials and recording available afterward
 
# Practice Question:

- ❖ Write out the Boolean Algebra expression for Q for the following circuit. No simplification necessary.



## Practice Question:

- ❖ Implement the Boolean expression  $B(A + C)$  with the fewest number of a single universal gate. What does your solution look like?

# Lecture Outline

- ❖ **Thinking About Hardware**
- ❖ Verilog Basics
- ❖ Waveform Diagrams
- ❖ Debugging in Verilog

# Verilog



- ❖ Programming language for *describing hardware*
  - Simulate behavior before (wasting time) implementing
  - Find bugs early
  - Enable tools to automatically create implementation
- ❖ *Syntax* is similar to C/C++/Java, but behavior is very different
  - VHDL (the other major HDL) is more similar to ADA
- ❖ Modern version is **SystemVerilog**
  - Superset of previous; cleaner and more efficient

# Verilog: Hardware Descriptive Language

❖ Although it looks like code:

```
module myModule (F, A, B, C);  
  output logic F;  
  input logic A, B, C;  
  logic AN, AB, AC;  
  
  nand gate1(AB, AN, B);  
  nand gate2(AC, A, C);  
  nand gate3( F, AB, AC);  
  not not1(AN, A);  
endmodule
```

❖ Keep the hardware in mind:

  

# Verilog Primitives

- ❖ **Nets** (*wire*): transmit value of connected source
  - Problematic if connected to two different voltage sources
  - Can connect to many places (always possible to “split” wire)
- ❖ **Variables** (*reg*): variable voltage sources
  - Can “drive” by assigning arbitrary values at any given time
  - SystemVerilog: variable *logic* can be used as a net, too
- ❖ **Logic Values**
  - **0** = zero, low, FALSE
  - **1** = one, high, TRUE
  - **X** = unknown, uninitialized, contention (conflict)
  - **Z** = floating (disconnected), high impedance



# Verilog Primitives

## ❖ Gates:

Gate	Verilog Syntax
NOT a	$\sim a$
a AND b	$a \& b$
a OR b	$a   b$
a NAND b	$\sim(a \& b)$
a NOR b	$\sim(a   b)$
a XOR b	$a \wedge b$
a XNOR b	$\sim(a \wedge b)$

## ❖ Modules: “classes” in Verilog that define *blocks*

- **Input:** Signals passed from outside to inside of block
- **Output:** Signals passed from inside to outside of block


# Verilog Execution

- ❖ Physical wires transmit voltages (electrons) near-instantaneously
  - Wires by themselves have no notion of sequential execution
- ❖ Gates and modules are constantly performing computations
  - Can be hard to keep track of!
- ❖ In pure hardware, there is no notion of initialization
  - A wire that is not driven by a voltage will naturally pick up a voltage from the environment


# Lecture Outline

- ❖ Thinking About Hardware
- ❖ **Verilog Basics**
- ❖ Waveform Diagrams
- ❖ Debugging in Verilog


# Using an FPGA

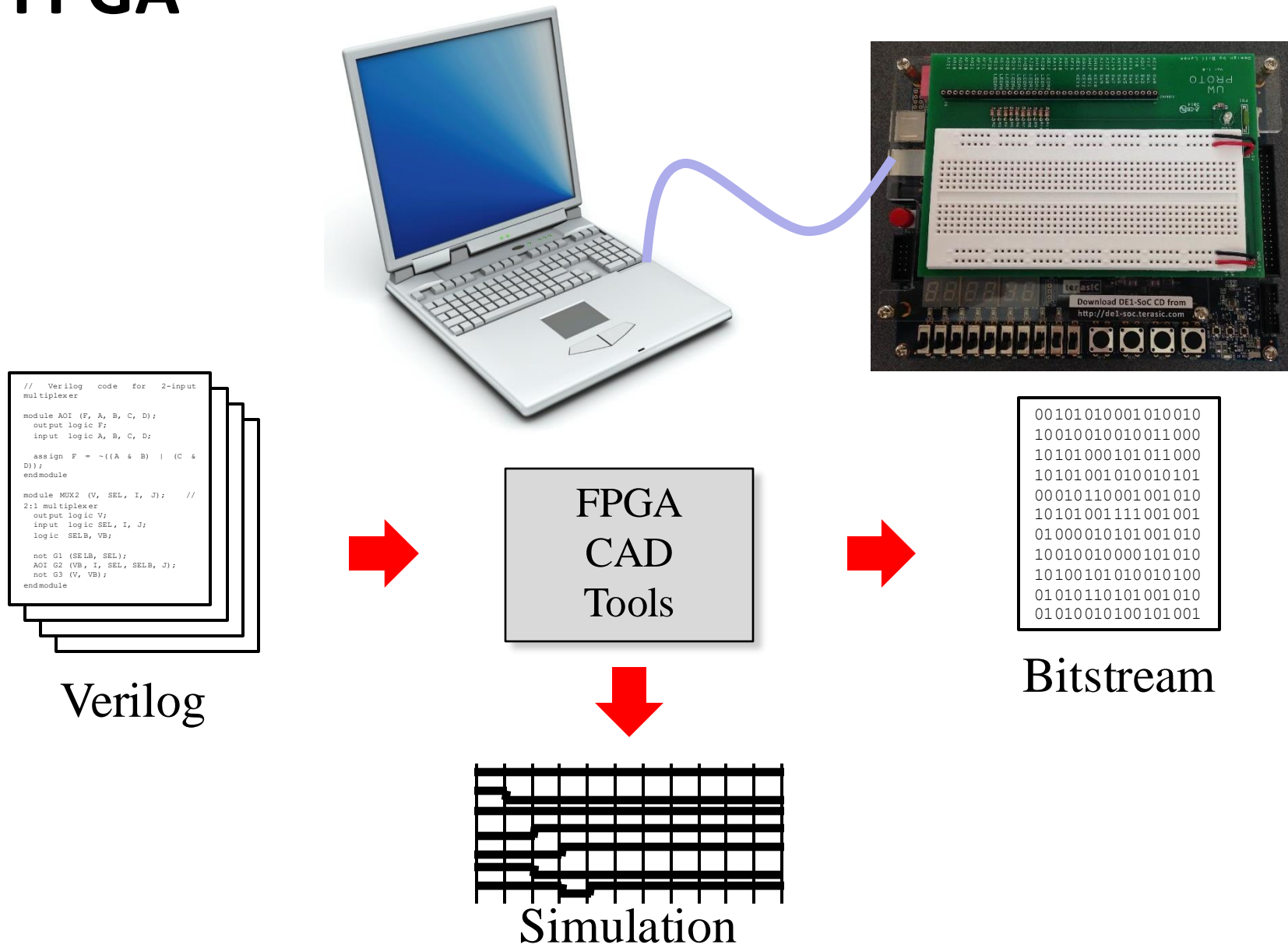

# Structural Verilog

 

Block Diagram:

 


```
// SystemVerilog code for AND-OR-INVERT circuit
```

```
module AOI (F, A, B, C, D);  
    output logic F;  
    input  logic A, B, C, D;  
  
    assign F = ~((A & B) | (C & D));  
endmodule
```

```
// end of SystemVerilog code
```


# Verilog Wires

 

```
// SystemVerilog code for AND-OR-INVERT circuit
```

```
module AOI (F, A, B, C, D);  
    output logic F;  
    input  logic A, B, C, D;  
    logic  AB, CD, O; // now necessary  
  
    assign AB = A & B;  
    assign CD = C & D;  
    assign O = AB | CD;  
    assign F = ~O;  
endmodule
```

# Verilog Gate Level

 

```
// SystemVerilog code for AND-OR-INVERT circuit
```

```
module AOI (F, A, B, C, D);
```

```
    output logic F;
```

```
    input  logic A, B, C, D;
```

```
    logic  AB, CD, O; // now necessary
```

```
    and a1(AB, A, B);
```

```
    and a2(CD, C, D);
```

```
    or  o1(O, AB, CD);
```

```
    not n1(F, O);
```

```
endmodule
```

} was:

```
assign AB = A & B;
assign CD = C & D;
assign O  = AB | CD;
assign F  = ~O;
```


# Verilog Hierarchy

```
// SystemVerilog code for AND-OR-INVERT circuit
module AOI (F, A, B, C, D);
    output logic F;
    input  logic A, B, C, D;

    assign F = ~((A & B) | (C & D));
endmodule
```

```
// 2:1 multiplexer built on top of AOI module
module MUX2 (V, SEL, I, J);
    output logic V;
    input  logic SEL, I, J;
    logic  SELN, VN;

     not G1 (SELN, SEL);
    AOI G2 (.F(VN), .A(I), .B(SEL), .C(SELN),
    .D(J));
    not G3 (V, VN);
endmodule
```






# Technology Break

# Lecture Outline

- ❖ Thinking About Hardware
- ❖ Verilog Basics
- ❖ **Waveform Diagrams**
- ❖ Debugging in Verilog

 
# Signals and Waveforms

- ❖ **Signals** transmitted over wires continuously
  - Transmission is effectively instantaneous  
(a wire can only contain one value at any given time)
  - In digital system, a wire holds either a 0 (low voltage) or 1 (high voltage)





Stack multiple signals in  
same *waveform diagram*  
vertically (syncing times)

# Signal Grouping

 

  
# Circuit Timing Behavior

- ❖ Simple Model: Gates “react” after fixed delay
  - Example: Assume delay of all gates is 1 ns (= 3 ticks)





# Verilog Buses

 

```
// SystemVerilog code for AND-OR-INVERT circuit
```

```
module AOI (F, A, B, C, D);  
  output logic F;  
  input  logic A, B, C, D;  
  logic  [2:0] w; // necessary  
  
  assign w[0] = A & B;  
  assign w[1] = C & D;  
  assign w[2] = w[0] | w[1];  
  assign F = ~w[2];  
endmodule
```

Just for illustration –  
this is bad coding style!

# Verilog Signal Manipulation

- ❖ Bus definition: `[n-1:0]` is an n-bit bus
  - Good practice to follow bit numbering notation
  - Access individual bit/wire using “array” syntax (*e.g.*, `bus[1]`)
  - Can access sub-bus using similar notation (*e.g.*, `bus[4:2]`)
- ❖ Multi-bit constants: `n'b#...#`
  - n is width, b is radix specifier (b for binary), #s are digits of number
  - *e.g.*, `4'd12`, `4'b1100`, `4'hC`
- ❖ Concatenation: `{sig, ..., sig}`
  - Ordering matters; result will have combined widths of all signals
- ❖ Replication operator: `{n{m}}`
  - repeats value m, n times



# Practice Question

```
logic [4:0] apple;  
logic [3:0] pear;  
logic [9:0] orange;  
assign apple = 5'd20;  
assign pear = {1'b0, apple[2:1], apple[4]};
```

- ❖ What's the value of pear?
- ❖ If we want orange to be the *sign-extended* version of apple, what is the appropriate Verilog statement?

```
assign orange =
```


# Lecture Outline

- ❖ Thinking About Hardware
- ❖ Verilog Basics
- ❖ Waveform Diagrams
- ❖ **Debugging in Verilog**

# Test Benches

- ❖ *Needed for simulation only!*
  - Software constraint to mimic hardware
- ❖ ModelSim runs entirely on your computer
  - Tries to simulate your FPGA environment without actually using hardware – no physical signals available
  - Must create fake inputs for FPGA's physical connections
    - *e.g.*, LEDR, HEX, KEY, SW, CLOCK\_50
  - Unnecessary when code is loaded onto FPGA
- ❖ Need to define both input signal combinations as well as their *timing*

# Verilog Test Benches

 

```
module MUX2_tb ();
  logic SEL, I, J; // simulated inputs
  logic V;        // net for reading output

  // instance of module we want to test ("device under test")
  MUX2 dut (.V(V), .SEL(SEL), .I(I), .J(J));

  initial // build stimulus (test vectors)
  begin // start of "block" of code
    {SEL, I, J} = 3'b100; #10; // t=0: S=1, I=0, J=0 -> V=0
    I = 1; #10; // t=10: S=1, I=1, J=0 -> V=1
    SEL = 0; #10; // t=20: S=0, I=1, J=0 -> V=0
    J = 1; #10; // t=30: S=0, I=1, J=1 -> V=1
  end // end of "block" of code

endmodule // MUX2_tb
```

# Better Verilog Test Bench

```
module MUX2_tb ();
  logic SEL, I, J; // simulated inputs
  logic V;        // net for reading output

  // instance of module we want to test ("device under
  test")
  MUX2 dut (.V(V), .SEL(SEL), .I(I), .J(J));

  int i;
  initial // build stimulus (test vectors)
  begin // start of "block" of code
    for(i = 0; i < 8; i = i + 1) begin
      {SEL, I, J} = i; #10;
    end
  end // end of "block" of code
endmodule // MUX2_tb
```

# Debugging Circuits

- ❖ Complex circuits require careful debugging
  - Test as you go; don't wait until the end (system test)
  - *Every* module should have a test bench (unit test)
- 1) Test all behaviors
  - All combinations of inputs for small circuits, subcircuits
- 2) Identify any incorrect behaviors
- 3) Examine inputs & outputs to find earliest place where value is wrong
  - Typically trace backwards from bad outputs, forwards from inputs
  - Look at values at intermediate points in circuit

# Hardware Debugging

- ❖ Simulation (ModelSim) is used to debug logic *design* and should be done thoroughly before touching FPGA
  - Unfortunately, ModelSim is not a perfect simulator
- ❖ If interfacing with other circuitry (*e.g.*, breadboard), will also need to debug circuitry layout there
  - Similar process, but with power sources (inputs) and voltmeters (probe the wires)
  - Often just a poor electrical connection somewhere
- ❖ Sometimes things simply fail
  - All electrical components fail eventually, whether you caused it to or not

# Summary

- ❖ SystemVerilog is a hardware description language (HDL) used to program your FPGA
  - Programmatic syntax used to describe the connections between gates and registers
- ❖ Waveform diagrams used to track intermediate signals as information propagates through CL
- ❖ Hardware debugging is a critical skill
  - Similar to debugging software, but using different tools