

Intro to Digital Design

Karnaugh Maps

Instructor: Chris Thachuk

Teaching Assistants:

Eujean Lee

Stephanie Osorio-Tristan


Nandini Talukdar

Wen Li

Question:

- Let the CL delays be 1 tick (NOT) and 3 ticks (AND, OR). How many ticks is the signal X high?

14 ticks

 

Relevant Course Information

- ❖ Lab 1 & 2 Demos due during your assigned demo slots
 - Don't forget to submit your lab materials *before* Wednesday at 2:30 pm, regardless of your demo time
- ❖ Lab 3 – Logic simplification in Verilog
 - Get practice with K-maps
 - Full credit for minimal logic
- ❖ Quiz #1 – 10/29 during lecture time

Lecture Outline

- ❖ **Karnaugh Maps (K-maps)**
- ❖ Design Examples

On and Off Sets

- ❖ *On Set* is the set of input patterns where the function is TRUE
 - Here on set = $\{\bar{A}\bar{B}C, \bar{A}BC, A\bar{B}\bar{C}, A\bar{B}C\}$
- ❖ *Off Set* is the set of input patterns where the function is FALSE
 - Here off set = $\{\bar{A}\bar{B}\bar{C}, \bar{A}B\bar{C}, AB\bar{C}, ABC\}$
- ❖ **Recall:** Use the On Set for *Sum of Products* (SoP) and the Off Set for *Product of Sums* (PoS)
 - Considered **two-level** Boolean expressions

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Two-Level Simplification

- ❖ Using Sum of Products, “neighboring” input combinations simplify
 - “Neighboring”: inputs that differ by a single signal
 - The Uniting Theorem: $A(\overline{B}^{\textcolor{red}{1}} + B) = A$
 - e.g., $AB + \overline{A}B = B$, $\overline{A}BC + \overline{A}B\overline{C} = \overline{A}B$
- ❖ **Goal:** Find neighboring subsets of the On Set to eliminate variables and simplify the expression
- ❖ **Idea:** Let’s write out our Truth Table such that the neighbors become apparent!
 - Need a Karnaugh map for *EACH* output

Karnaugh Maps

- ❖ A **K-map** is a method of representing a truth table that helps visualize adjacencies in ≤ 4 dimensions
 - For more dimensions, computer-based methods are needed

1) Split inputs into 2 *evenly-sized* groups

- One group will have an extra if an odd # of inputs

2) Write out all combinations of each group on each axis Group of n inputs
 $\rightarrow 2^n$ combinations

- Successive combinations change only 1 input (Gray code)

2 Inputs:

group 1

group 2

	B	0	1
A	0		
1			

3 Inputs:

group 1

group 2

AB

C

00	01	11	10
0			
1			


Karnaugh Maps

- Also see visualization with brackets for “asserted” simplifications:

4 Inputs:

		AB	00	01	11	10
		CD	00	01	11	10
AB	CD	00	$\bar{A}\bar{B}\bar{C}\bar{D}$			
		01		$A\bar{B}\bar{C}D$		
		11				
		10				

 each cell corresponds to a different input combination



K-map Example: Majority Circuit

- ❖ Filling in a Karnaugh map:

A B C			F	#	AB	C	00	01	11	10
0	0	0	0	0	6					
0	0	1	0	0	1	0	0	2	6	4
0	1	0	0	0	2	1	1	1	1	1
0	1	1	1	1	3	1	1	1	1	5
1	0	0	0	0	4					
1	0	1	1	1	5					
1	1	0	0	1	6					
1	1	1	1	1	7					

- ❖ Each row of truth table corresponds to ONE cell of Karnaugh map
- ❖ Note the jump when you go from input 011 to 100
(most mistakes made here)

K-map Example: Majority Circuit

- ❖ Filling in alternate Karnaugh map:

			F	#	BC			
A	B	C			00	01	11	10
0	0	0	0	0	0	0	1	2
0	0	1	0	1	0	0	1	2
0	1	0	0	2	0	0	0	1
0	1	1	1	3	0	0	1	2
1	0	0	0	4	0	0	0	0
1	0	1	1	5	1	1	1	1
1	1	0	1	6	1	1	1	1
1	1	1	1	7	1	1	1	1

- ❖ Each row of truth table corresponds to ONE cell of Karnaugh map
- ❖ Note the jump when you go from input 001 to 010 and 101 to 110
(most mistakes made here)

K-map Simplification


- ❖ Group neighboring 1's so all are accounted for:

- Each group of neighbors becomes a product term in the output

- ❖ $F = BC + AB + AC$


- ❖ Larger groups become smaller terms

 - The single 1 in top row $\rightarrow AB\bar{C}$
 - Vertical group of two 1's $\rightarrow AB$
 - If entire lower row was 1's $\rightarrow C$



General K-map Rules

 
- ❖ Only group in powers of 2
 - Grouping should be of size $2^i \times 2^j$
 - Applies for both directions
- ❖ Wraps around in all directions
 - “Corners” case is extreme example
- ❖ Always choose largest groupings possible
 - Avoid single cells whenever possible
- ❖ $F = BD + \overline{BD} \left(+ ACD \right) \left(+ A\bar{B}C \right)$



 - 1) NOT a valid group
- 2) IS a valid group
- 3) IS a valid group
- 4) “Corners” case
- 5) 1 of 2 good choices here

K-Map Example

$$\diamond F = \cancel{\bar{A}D} + \cancel{BD} + \cancel{\bar{B}C} + \cancel{A\bar{B}D}$$
$$F = D + \bar{B}C$$




Lecture Outline

- ❖ Karnaugh Maps (K-maps)
- ❖ Design Examples

Design Example: 2-bit Adder

- ❖ Block Diagram and Truth Table:

 




				MSB	LSB	
A	B	C	D	X	Y	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1

0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0

1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1

1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Design Example: 2-bit Adder

   

$$X = \underset{1}{AC} + \underset{2}{ABD} + \underset{3}{BCD}$$

$$Y = \underset{1}{\overline{A}\overline{B}\overline{C}D} + \underset{2}{ABCD} + \underset{3}{A\overline{C}\overline{D}} + \underset{4}{\overline{A}\overline{B}\overline{C}} + \underset{5}{\overline{A}\overline{B}C} + \underset{6}{\overline{A}C\overline{D}}$$

$$Z = \underset{1}{\overline{B}D} + \underset{2}{B\overline{D}} = B \oplus D$$

Technology Break

Don't Cares

- ❖ Use symbol 'X' to mean it can be either a 0 or 1
 - Make choice to simplify final expression

AB		A	
CD			
		0	1
C	D	0	1
0	0	0	X
1	1	1	X
1	1	0	0
0	X	0	0

Let all X = 0:

$$F = \bar{A}D + \bar{B}\bar{C}D$$

AB		A	
CD			
		0	1
C	D	0	1
0	0	0	X
1	1	X	1
1	1	0	0
0	X	0	0

Let all X = 1:

$$F = \bar{A}D + \bar{C}D + AB\bar{C} + \bar{A}BC$$

AB		A	
CD			
		0	1
C	D	0	1
0	0	0	X
1	1	X	1
1	1	0	0
0	X	0	0


Choose wisely:

$$F = \bar{A}D + \bar{C}D$$

Design Example: Rock-Paper-Scissors

should never see 11 input, so outputs are don't cares!

 
- ❖ Rock (00), Paper (01), Scissors (10)
for two players P0 and P1
- ❖ **Output:** Win = Winner's ID (0/1)
Tie = 1 if Tie, 0 else



		P1		P0		Win	Tie
		A	B	C	D		
Rock	0	0	0	R	0	X	1
	0	0	0	P	1	O	0
	0	0	1	S	0	I	0
	0	0	1	?	1	X	X
Paper	0	1	0	R	0	I	0
	0	1	0	P	1	X	1
	0	1	1	S	0	O	0
	0	1	1	?	1	X	X
Scissors	1	0	0	R	0	O	0
	1	0	0	P	1	I	0
	1	0	1	S	0	X	1
	1	0	1	?	1	X	X
??	1	1	0	0	0	X	X
	1	1	0	1	1	X	X
	1	1	1	0	0	X	X
	1	1	1	1	1	X	X

Case Study: Seven-Segment Display


- ❖ Chip to drive digital display

 


"binary-coded decimal" (BCD)

B3	B2	B1	B0	#
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6

Case Study: Seven-Segment Display

 


B3	B2	B1	B0	Val	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	0	1	1	0	0	0	0
0	0	1	0	2	1	1	0	1	1	0	1
0	0	1	1	3	1	1	1	1	0	0	1
0	1	0	0	4	0	1	1	0	0	1	1
0	1	0	1	5	1	0	1	1	0	1	1
0	1	1	0	6	1	0	1	1	1	1	1
0	1	1	1	7	1	1	1	0	0	0	0
1	0	0	0	8	1	1	1	1	1	1	1
1	0	0	1	9	1	1	1	1	0	1	1

 

Case Study: Seven-Segment Display

❖ Implement L5:

B3	B2	B1	B0	L5	Cell
0	0	0	0	1	6
0	0	0	1	0	1
0	0	1	0	0	2
0	0	1	1	0	3
0	1	0	0	1	4
0	1	0	1	1	5
0	1	1	0	1	6
0	1	1	1	0	7
1	0	0	0	1	8
1	0	0	1	1	9
					⋮

 

$$L5 = \bar{B}_3 \bar{B}_0 + B_2 \bar{B}_1 + B_2 \bar{B}_0 + B_3$$


7-Seg Display in Verilog

```
module seg7 (bcd, leds);
    input logic [3:0] bcd;
    output logic [6:0] leds;
    this is new
    always_comb
        case (bcd)
            // 3210
            4'b0000: leds = 7'b0111111;
            4'b0001: leds = 7'b00000110;
            4'b0010: leds = 7'b1011011;
            4'b0011: leds = 7'b1001111;
            4'b0100: leds = 7'b1100110;
            4'b0101: leds = 7'b1101101;
            4'b0110: leds = 7'b1111101;
            4'b0111: leds = 7'b00000111;
            4'b1000: leds = 7'b1111111;
            4'b1001: leds = 7'b1101111;
            default: leds = 7'bx;
        endcase
    endmodule
```

bit positions within bus

binary constants

don't care's

 

no fall-through
(no breaks necessary)
because it is
describing hardware!

Procedural Blocks


- ❖ **assign**: continuous assignment
 - Used with wires
 - e.g., `assign F = ~((A & B) | (C & D));`
- ❖ **initial**: executes once at time zero
 - Set initial values (**generally simulation only!!!**)
 - Define testbench waveforms (and monitor)
 - e.g., `initial`
 `for(i = 0; i < 8; i = i+1) begin`
 `{SEL, I, J} = i; #10;`
 `end`

Procedural Blocks

- ❖ **always**: loop to execute over and over again
 - Block gets triggered by a sensitivity list
 - Any object that is assigned a value in an **always** statement must be declared as a variable (**reg/logic**).
 - Examples:
 - **always** @ (a or b or c) \leftrightarrow **always** @ (a, b, c)
 - **always** @ (*) implicitly contains all read signals within the block
- ❖ **always_comb**: special SystemVerilog for CL
 - Similar to **always** @(*), but generally more robust
 - *Only for use with combinational logic!!!*

Verilog: Extend 7-Seg to Hex

 - ❖ Show “A” on 0b1010 (ten) to “F” on 0b1111 (fifteen)



```
module seg7 (bcd, leds);
    input logic [3:0] bcd;
    output logic [6:0] leds;

    always_comb
        case (bcd)
            // 3210      6543210
            4'b0000: leds = 7'b0111111;
            4'b0001: leds = 7'b00000110;
            4'b0010: leds = 7'b1011011;
            4'b0011: leds = 7'b1001111;
            4'b0100: leds = 7'b1100110;
            4'b0101: leds = 7'b1101101;
            4'b0110: leds = 7'b1111101;
            4'b0111: leds = 7'b00000111;
            4'b1000: leds = 7'b1111111;
            4'b1001: leds = 7'b1101111;
            default: leds = 7'bx;
        endcase
endmodule
```

Circuit Implementation Techniques

- ❖ **Truth Tables** – “Black box” circuit description
- ❖ **Boolean Algebra** – Math form for optimization
 - **K-Maps** – Alternate simplification technique
- ❖ **Circuit Diagrams** – TTL Implementations
- ❖ **Verilog** – Simulation & mapping to FPGAs