

# Intro to Digital Design

## Project Tips, Memory

**Instructor:** Chris Thachuk

**Teaching Assistants:**

Eujean Lee

Stephanie Osorio-Tristan

Nandini Talukdar

Wen Li

# Relevant Course Information

## ❖ Lab 8 – Project

- 2 weeks to work on it – don't wait to start!
  - Reports due Friday, Dec 6 @ 11:59 pm
  - Lab 8 check-in due next week during demo slot, or by Monday O/Hs due to holiday
  - Demos can be scheduled outside of the lab hours by making a *private* post on Ed Discussion
- 8 suggested projects, or get your own approved
  - **Most use LED breakout board – included in your lab kit**
  - Not all are worth the same number of points (“full credit” is 150)
  - Think carefully about what you want to tackle  
(*e.g.*, complex FSM, LED board, multiple “clock speeds”)
- Bonus points for adding cool features and early finish
  - Up to 20 points for extra features; up to 10 points for early finish

# Practice

❖ Implement a **counter** that goes through the state sequence


**000** → **001** → **011** → **010** → **110** → **111** → **101** → **100** → 000 → ...

■ Include an Enable signal to count and a Reset signal (to 000)

P <sub>2</sub>	P <sub>1</sub>	P <sub>0</sub>	N <sub>2</sub>	N <sub>1</sub>	N <sub>0</sub>
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	1

- $N_2 = P_2 \bar{P}_0 + P_1 \bar{P}_0$
- $N_1 = \bar{P}_2 P_0 + P_1 \bar{P}_0$
- $N_0 = \bar{P}_2 \bar{P}_1 + P_2 P_1$

R	E	D
0	0	0
0	1	0
1	0	0
1	1	0

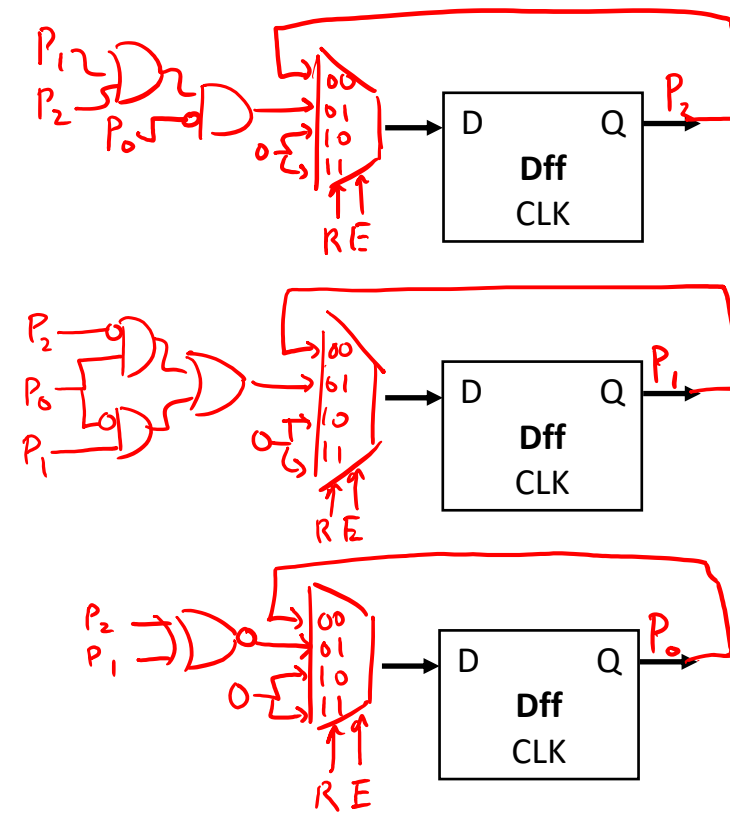

# Outline

- ❖ **Project Tips**
  - “Multiple clocks”
  - **Verilog generate**
  - **SystemVerilog Arrays**
- ❖ **Computer Components**
  - Memory/RAM

# Comparator (Multibit)

## ❖ Equality ( $A == B$ )

- XNOR corresponding bits of A and B, then AND together
- NOR all bits of  $A-B$


a	b	xnor	nor
0	0	1	1
0	1	0	0
1	0	0	0
1	1	1	0

## ❖ Comparator ( $A < B$ , $A == B$ , $A > B$ )

- $A < B$ : MSB of  $A-B$
  - $A == B$ : NOR of all bits of  $A-B$
  - $A > B$ : NOT of MSB of  $A-B$
- computed just once!*
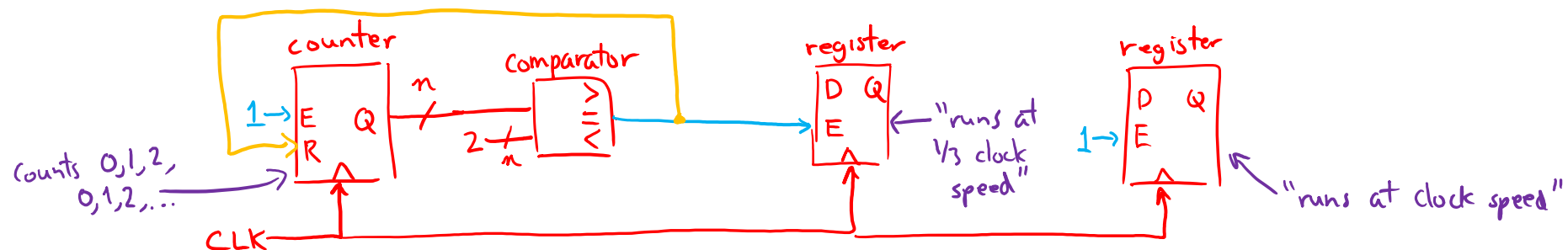
# “Multiple Clocks” Via Counters

- ❖ The `clock_divider` module is a 32-bit up counter
  - All output bits update at same time ( $t_{C2Q}$ )
  - Output bits get us powers of 2 differences in speed
- ❖ Still want to use *single* clock for all state elements
  - We will instead control actions using the Enable signal
- ❖ Use comparator on a counter as Enable signal
  - May need to feedback into Reset signal on counter



# Advanced Verilog: generate

- ❖ Condense your code using loops and conditionals
  - Often used with assign and module instantiation

testbenches:

integer i;

```
for(i=0; i<8; i=i+1) {
  // set input signals
}
```

- ❖ Details:

- Loop variables must be declared as genvar outside of generate statement
- Block statements (for/if) *must* have begin and end and be labeled

```
genvar <loop_var>;

generate
  for (<init>; <cond>; <update>) begin : <label>
    // do something with loop_var
  end
endgenerate
```

*Handwritten annotations:*

- i* above `<loop_var>`
- i=0*, *i<N*, *i=i+1* above the for loop parameters
- adders* above `<label>`, which is circled in red
- FullAdd fA (* above the body of the for loop
- we i here* with an arrow pointing to the `<loop_var>` parameter

# Add/Sub in Verilog (parameterized)


## ❖ Variable-width add/sub (with overflow, carry)

```
module addN #(parameter N=32) (OF, CF, S, sub, A, B);
  output logic          OF, CF;
  output logic [N-1:0] S;
  input  logic          sub;
  input  logic [N-1:0] A, B;
  logic  [N-1:0] D;      // possibly flipped B
  logic          C2;     // second-to-last carry-out

  always_comb begin
    D = B ^ {N{sub}}; // replication operator
    {C2, S[N-2:0]} = A[N-2:0] + D[N-2:0] + sub;
    {CF, S[N-1]} = A[N-1] + D[N-1] + C2;
    OF = CF ^ C2;
  end
endmodule // addN
```



# Add/Sub in Verilog (generate)

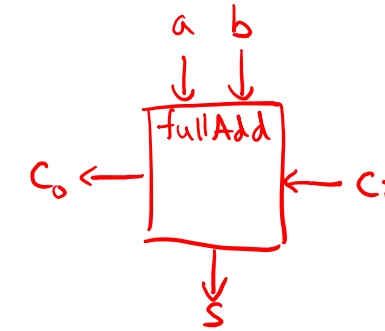

- ❖ Generate produces N fulladd modules

```

module addNgen #(parameter N=32) (OF, CF, S, sub, A, B);
  output logic OF, CF;           // overflow and carry flags
  output logic [N-1:0] S;       // sum output bus
  input logic sub;              // subtract signal
  input logic [N-1:0] A, B;     // input busses
  logic [N:0] C;               // carry signals between
  modules
  genvar i;
  generate
    for (i=0; i < N; i=i+1) begin : adders
      fulladd FA (.cout(C[i+1]), .s(S[i]), .cin(C[i]), .a(A[i]), .b(B[i]));
    end
  endgenerate

```

- ❖ Reminder: `module fulladd (cout, s, cin, a, b);`

# SystemVerilog Arrays


- ❖ A *bus* is known as a *vector* or **packed array**
  - e.g., `logic [31:0] divided_clocks;`
  - Can only be made of single bit datatypes
- ❖ “Regular” array syntax is known as an **unpacked array**
  - e.g., `logic an_unpacked_array[4:0];`
  - Can be made of any datatype
- ❖ **Multidimensional arrays** can be combinations of packed and unpacked dimensions
  - e.g., `logic [3:0] two_D_array[4:0];`
  - Accessed left to right, starting with unpacked dimensions

# Outline

- ❖ Project Tips
  - “Multiple clocks”
  - Verilog generate
  - SystemVerilog Arrays
- ❖ **Computer Components**
  - **Memory/RAM**
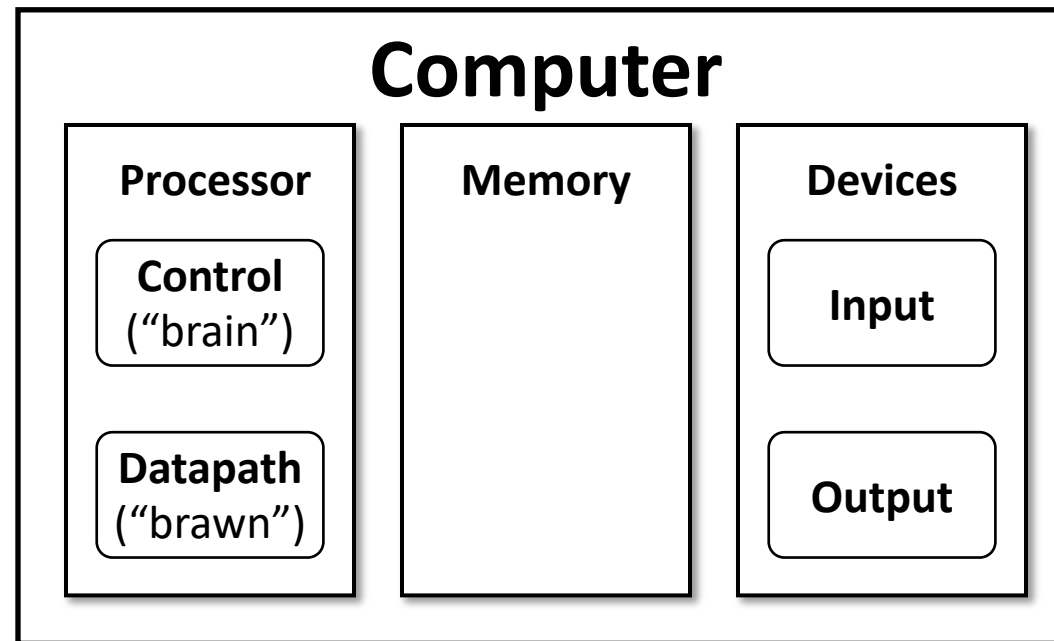
# Five Components of a Computer

- ❖ Components a computer needs to work:
  - Control
  - Datapath
  - Memory
  - Input
  - Output



# Executing an Instruction

Example: `addq (%rdi), %rax`

❖ Depends on ISA, but generally:

- Instruction Fetch ← get instruction from Memory (Code) (0x 48 03 07)
- Instruction Decode ← what is this instruction telling us to do?
- Data Fetch → register values  
→ memory
- Computation → address computation  
→ instruction operation
- Store Result → into register or memory




❖ Basic Datapath Components (idealized)

- Register File } Next lecture
- Memory Management Unit } Today
- Arithmetic Logic Unit (ALU) } Previous two lectures
- Routing Elements }

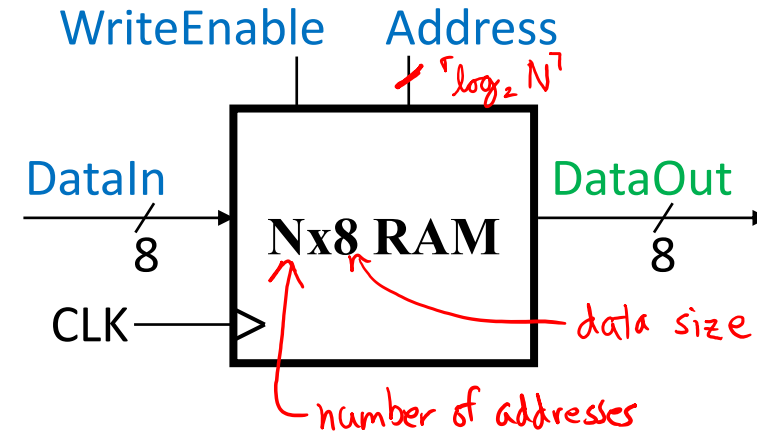
# Storage Element: Idealized Memory

- ❖ Memory (idealized)
  - One input bus: **DataIn**
  - One output bus: **DataOut**
  - In reality, often combined
- ❖ Memory access:
  - Read: Data at **Address** placed on **DataOut**
  - Write: If **WriteEnable** = 1, **DataIn** written to **Address**
- ❖ For N addresses, need **Address** input to be  $(\log_2 N)$ -bits wide
- ❖ Clock (**CLK**) is a factor ONLY during write operation



# 8x4 RAM

WriteEnable

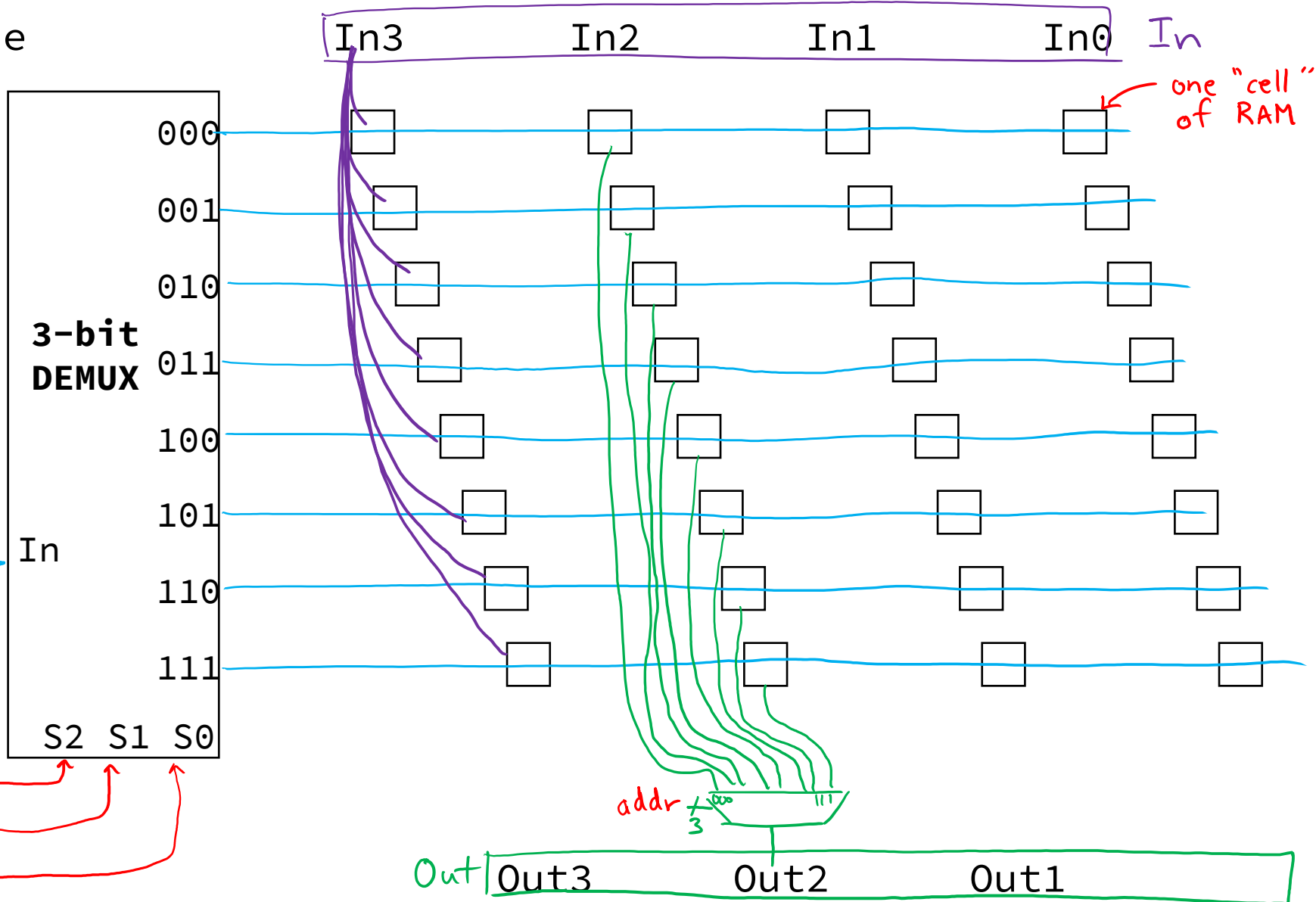


# RAM Cell

## ❖ Requirements:

- Store one bit of data
- Change data based on input when row is selected
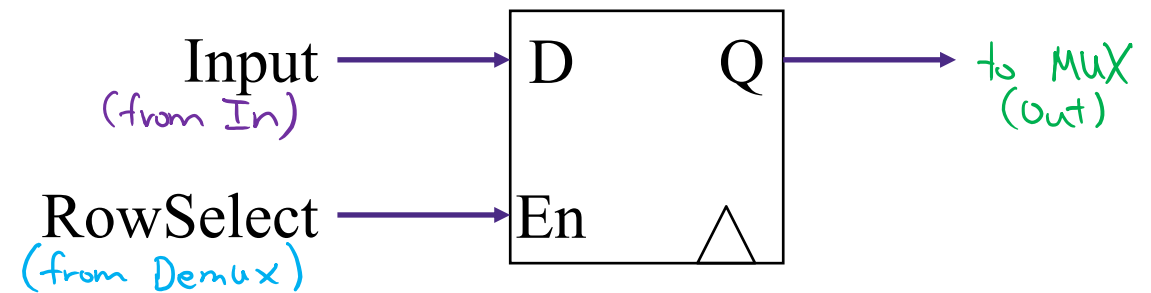
## ❖ Just a controlled register!

- No need to Reset
- Use RowSelect as Enable





# Verilog Memories

```
module memory16x8 (data_out, data_in, addr, write, clk);  
  
    output logic [7:0] data_out;  
    input  logic [7:0] data_in;  
    input  logic [3:0] addr;  
    input  logic      write, clk;  
  
    logic      [7:0] mem [15:0]; // array of vectors  
    assign data_out = mem[addr];  
  
    always @(posedge clk)  
        if (write)  
            mem[addr] <= data_in;  
  
endmodule // memory16x8
```

*both sides* (with arrows pointing to [7:0] and [15:0])  
*first index accesses this dimension* (with arrow pointing to [15:0])