

Intro to Digital Design

SystemVerilog Basics

Instructor: Justin Hsia

Teaching Assistants:

Emilio Alcantara

Eujean Lee

Naoto Uemura

Pedro Amarante


Wen Li

Relevant Course Information

- ❖ Lab demo slots have been assigned on Canvas
- ❖ Lab 1 & 2 – Basic Logic and Verilog
 - Digit(s) recognizer using switches and LED
 - For full credit, find minimal logic
 - Check the lab report requirements closely
- ❖ If you haven't done so yet, pick up a white lab kit + Okiocam ASAP from CSE 003 when TAs are present (labs + office hours)
- ❖ New sections Fridays @ 1:30 pm on Zoom
 - Materials and recording available afterward


Practice Question:

 - ❖ Write out the Boolean Algebra expression for Q for the following circuit. No simplification necessary.






Practice Question:

DeMorgan's:

 

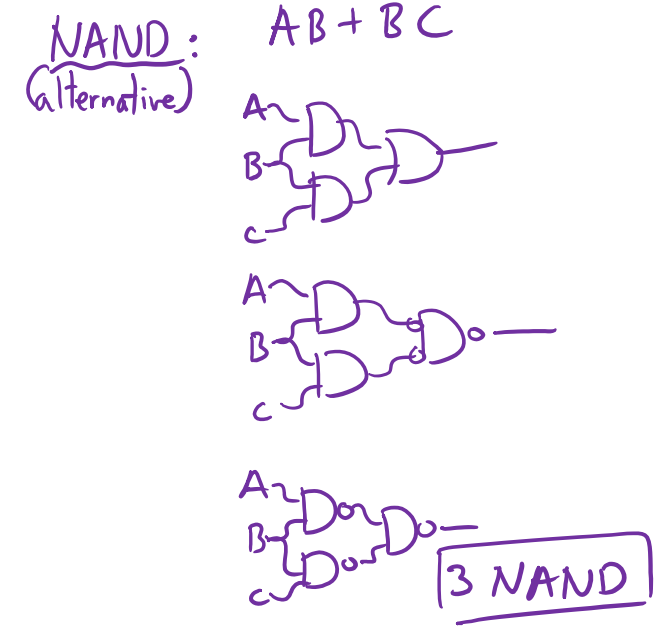 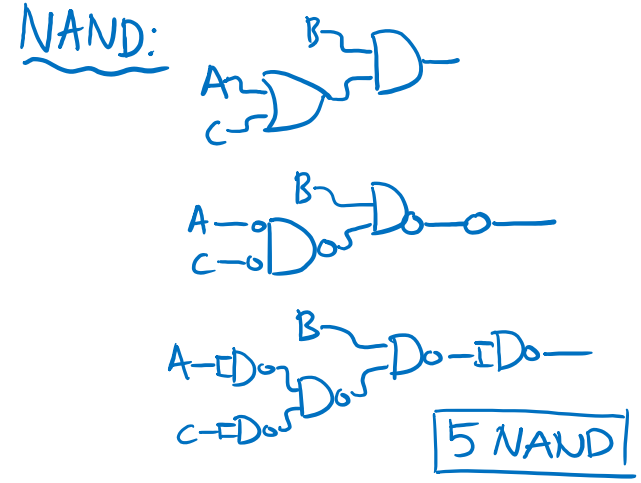- ❖ Implement the Boolean expression $B(A + C)$ with the fewest number of a single universal gate. What does your solution look like?
(NOR/NAND)



Lecture Outline

- ❖ **Thinking About Hardware**
- ❖ Verilog Basics
- ❖ Waveform Diagrams
- ❖ Debugging in Verilog

Verilog

- ❖ Programming language for *describing hardware*
 - Simulate behavior before (wasting time) implementing
 - Find bugs early
 - Enable tools to automatically create implementation
- ❖ *Syntax* is similar to C/C++/Java, but behavior is very different
 - VHDL (the other major HDL) is more similar to ADA
- ❖ Modern version is **SystemVerilog**
 - Superset of previous; cleaner and more efficient



Verilog: Hardware Descriptive Language

- ❖ Although it looks like code:

```
module myModule (F, A, B, C);  
  output logic F;  
  input  logic A, B, C;  
  logic AN, AB, AC;  
  
  nand gate1(AB, AN, B);  
  nand gate2(AC, A, C);  
  nand gate3( F, AB, AC);  
  not  not1(AN, A);  
endmodule
```

←
equivalent
→

- ❖ Keep the hardware in mind:

  

Verilog Primitives

- ❖ **Nets** (*wire*): transmit value of connected source
 - Problematic if connected to two different voltage sources
 - Can connect to many places (always possible to “split” wire)
- ❖ **Variables** (*reg*): variable voltage sources
 - Can “drive” by assigning arbitrary values at any given time
 - SystemVerilog: variable **logic** can be used as a net, too
 - ★ we will primarily use this
- ❖ **Logic Values**
 - **0** = zero, low, FALSE
 - **1** = one, high, TRUE
 - **X** = unknown, uninitialized, contention (conflict)
 - **Z** = floating (disconnected), high impedance


Verilog Primitives

❖ Gates:

Gate	Verilog Syntax
NOT a	$\sim a$
a AND b	$a \& b$
a OR b	$a b$
a NAND b	$\sim(a \& b)$
a NOR b	$\sim(a b)$
a XOR b	$a \wedge b$
a XNOR b	$\sim(a \wedge b)$

❖ Modules: “classes” in Verilog that define blocks

 - **Input:** Signals passed from outside to inside of block
- **Output:** Signals passed from inside to outside of block




Verilog Execution

- ❖ Physical wires transmit voltages (electrons) near-instantaneously
 - Wires by themselves have no notion of sequential execution
- ❖ Gates and modules are constantly performing computations
 - Can be hard to keep track of!
- ❖ In pure hardware, there is no notion of initialization
 - A wire that is not driven by a voltage will naturally pick up a voltage from the environment


Lecture Outline

- ❖ Thinking About Hardware
- ❖ **Verilog Basics**
- ❖ Waveform Diagrams
- ❖ Debugging in Verilog

Using an FPGA

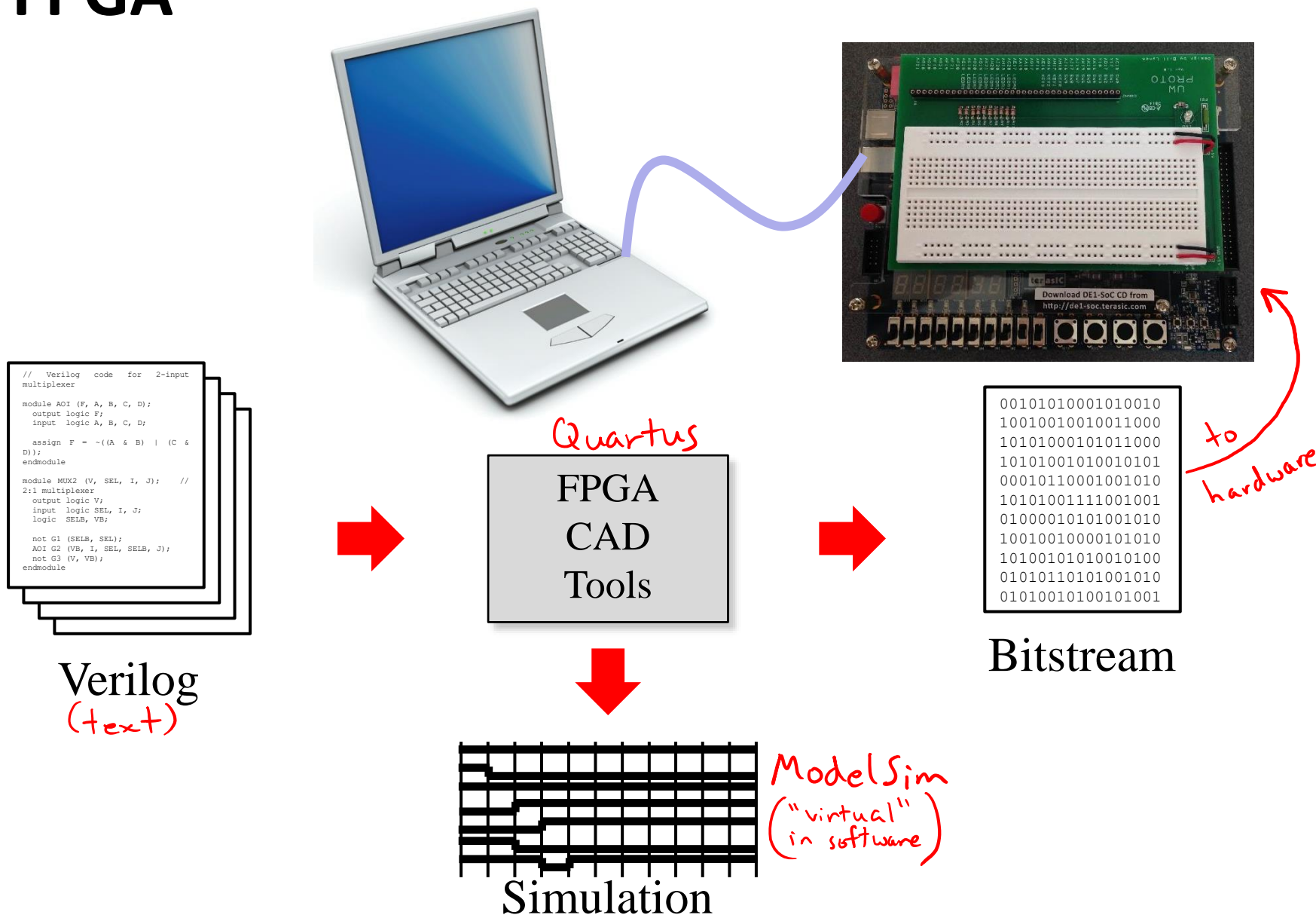

Structural Verilog

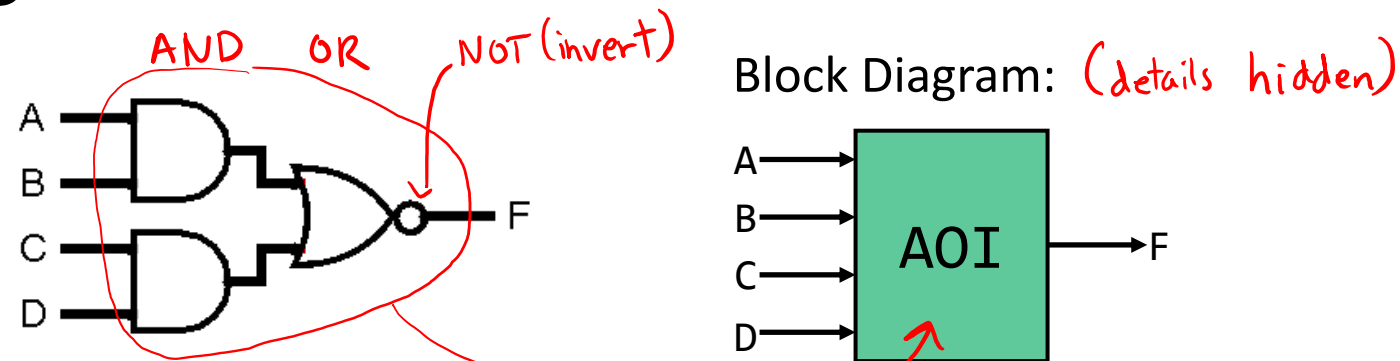

```

// SystemVerilog code for AND-OR-INVERT circuit
module AOI (F, A, B, C, D);
    output logic F;
    input logic A, B, C, D;


    assign F = ~((A & B) | (C & D));
endmodule

// end of SystemVerilog code
    
```

Handwritten annotations in red:

- `module AOI`: module name
- `(F, A, B, C, D)`: ports (connections to block)
- `output logic F`: port type
- `input logic A, B, C, D`: port type
- `~`: NOT
- `&`: AND
- `|`: OR

Verilog Wires

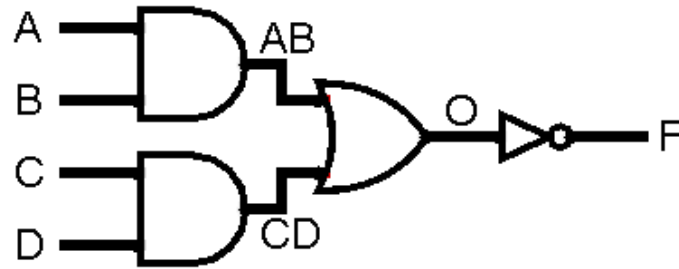

```
// SystemVerilog code for AND-OR-INVERT circuit
```

```
module AOI (F, A, B, C, D);
```

```
    output logic F;
```

```
    input  logic A, B, C, D;
```

```
    logic  AB, CD, O; // now necessary
```

```
    assign AB = A & B;
```

```
    assign CD = C & D;
```


```
    assign O = AB | CD;
```

```
    assign F = ~O;
```

```
endmodule
```

*identical in hardware,
just more explicit in Verilog code*

Verilog Gate Level

 

// SystemVerilog code for AND-OR-INVERT circuit

```
module AOI (F, A, B, C, D);
```

```
  output logic F;
```

```
  input  logic A, B, C, D;
```

```
  logic  AB, CD, O; // now necessary
```

module type

```
  and a1(AB, A, B);
```

```
  and a2(CD, C, D);
```

```
  or  o1(O, AB, CD);
```

```
  not n1(F, O);
```

```
endmodule
```

instance name

port connections

was:

```
assign AB = A & B;
```

```
assign CD = C & D;
```


```
assign O = AB | CD;
```

```
assign F = ~O;
```

Verilog Hierarchy

```
// SystemVerilog code for AND-OR-INVERT circuit
module AOI (F, A, B, C, D);
    output logic F;
    input logic A, B, C, D;

    assign F = ~((A & B)|(C & D));
endmodule
```

 

if SEL==0, V=J
if SEL==1, V=I

user-defined

```
// 2:1 multiplexer built on top of AOI module
module MUX2 (V, SEL, I, J);
    output logic V;
    input logic SEL, I, J;
    logic SELN, VN;

    not G1 (SELN, SEL);
    AOI G2 (.F(VN), .A(I), .B(SEL), .C(SELN), .D(J));
    not G3 (V, VN);
endmodule
```

primitive (built-in)

explicit connection to port


Technology Break

Lecture Outline


- ❖ Thinking About Hardware
- ❖ Verilog Basics
- ❖ **Waveform Diagrams**
- ❖ Debugging in Verilog

Signals and Waveforms

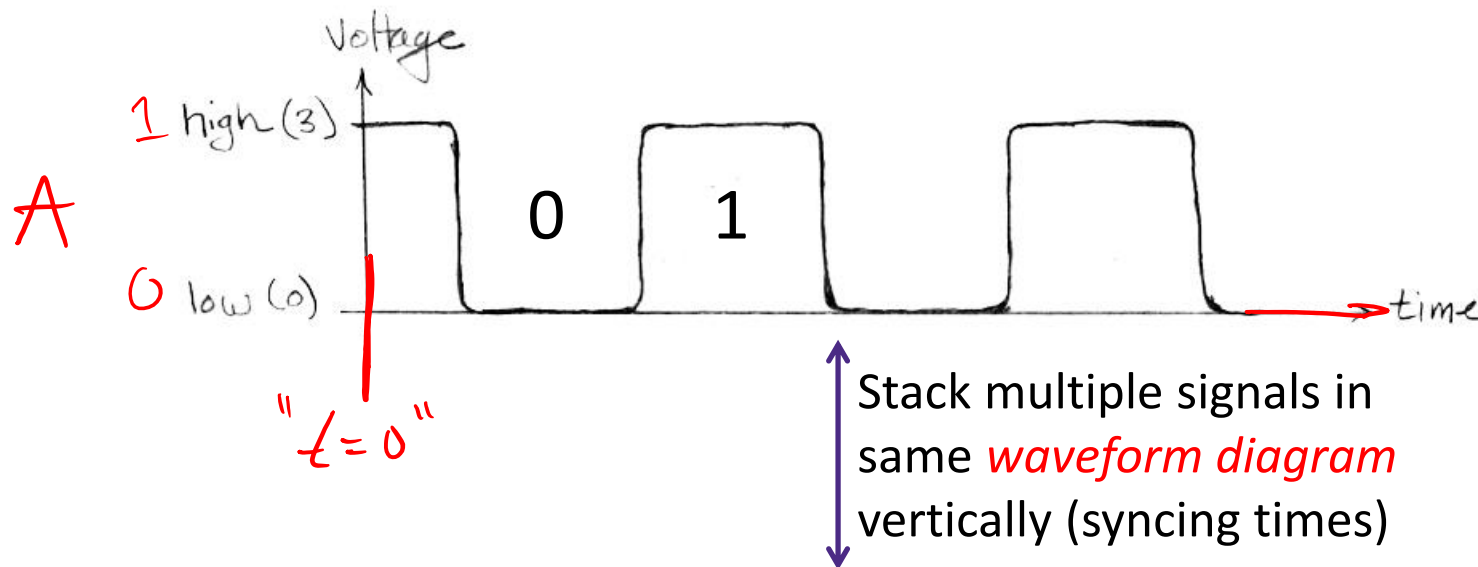- ❖ **Signals** transmitted over wires continuously
 - Transmission is effectively instantaneous
(a wire can only contain one value at any given time)
 - In digital system, a wire holds either a 0 (low voltage) or 1 (high voltage)




Signal Grouping

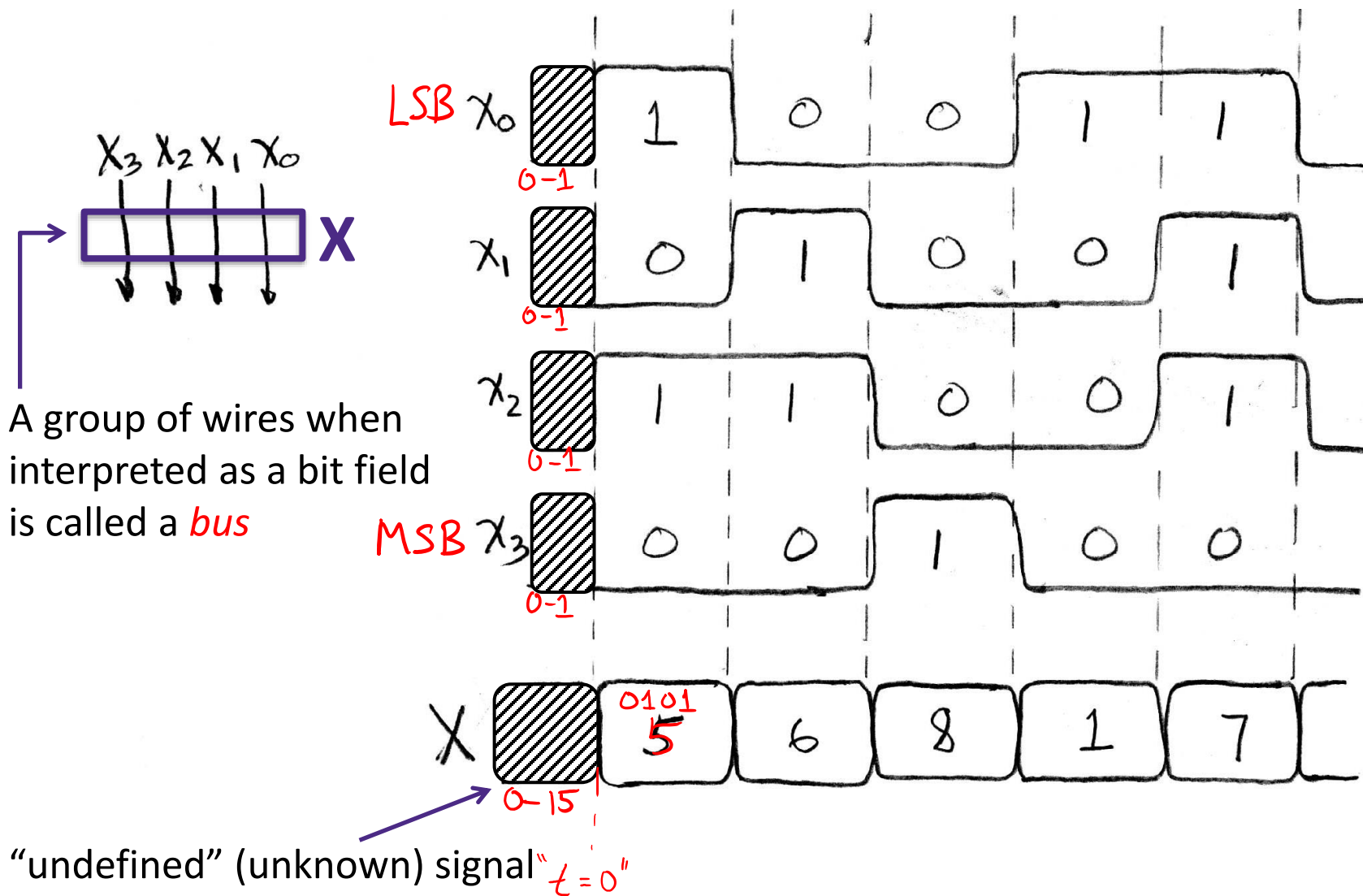

Circuit Timing Behavior


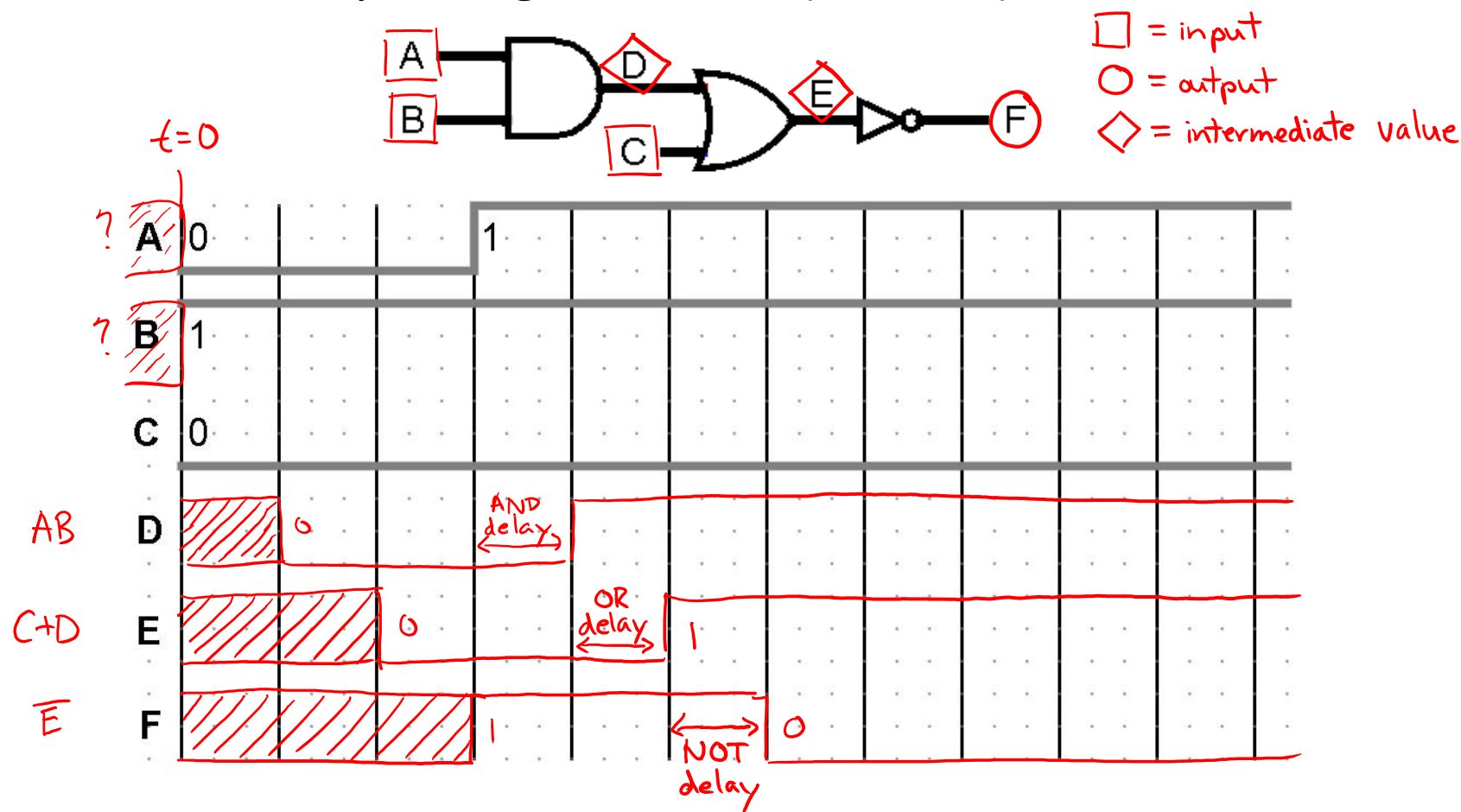
- ❖ Simple Model: Gates “react” after fixed delay
 - Example: Assume delay of all gates is 1 ns (= 3 ticks)




Circuit Timing: Hazards/Glitches

❖ Circuits can temporarily go to incorrect states!

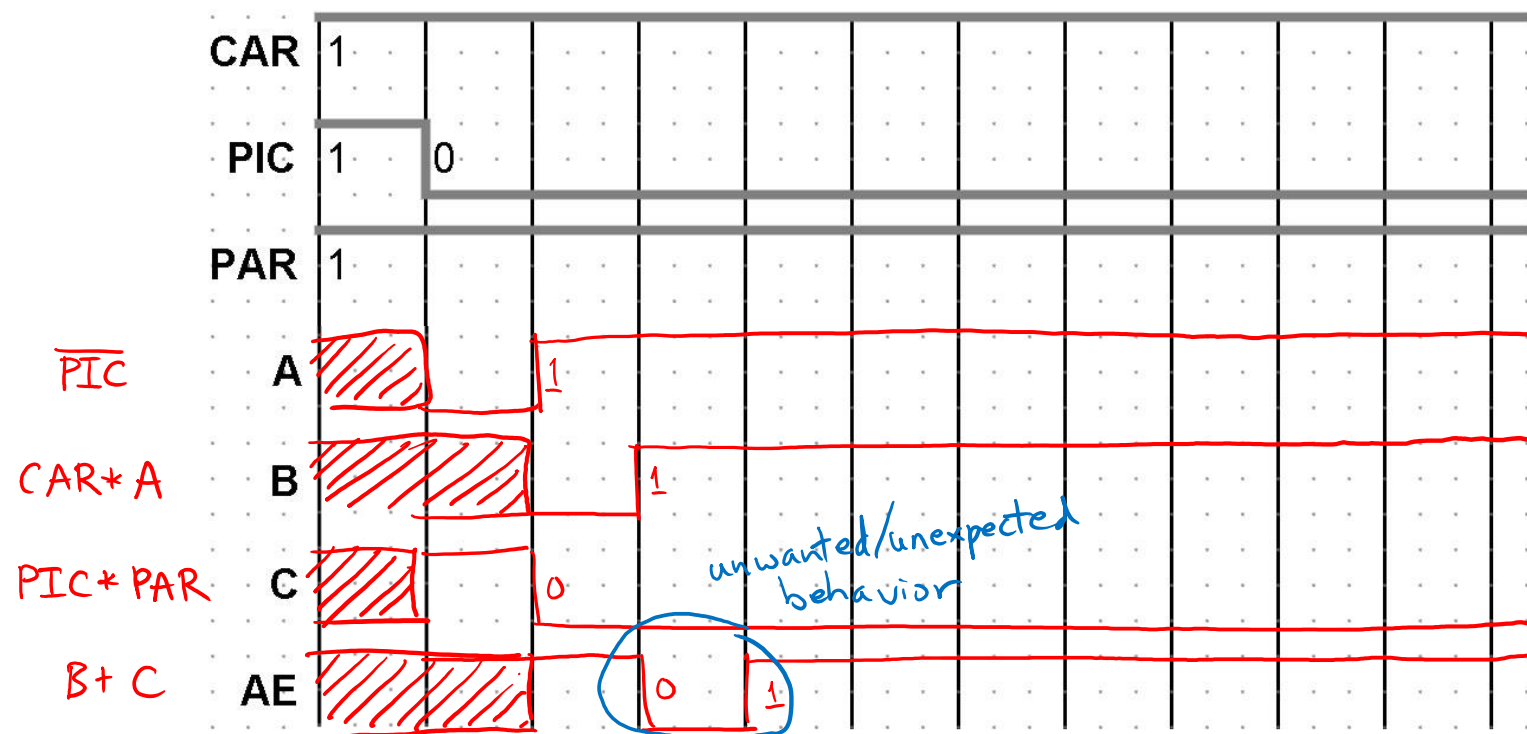 - Assume 1 ns delay (3 ticks) for all gates



Verilog Buses

 

// SystemVerilog code for AND-OR-INVERT circuit

```

module AOI (F, A, B, C, D);
  output logic F;
  input  logic A, B, C, D;
  logic [2:0] w; // necessary
  declare bus width ↑
  assign w[0] = A & B;
  assign w[1] = C & D;
  assign w[2] = w[0] | w[1];
  assign F = ~w[2];
endmodule


```

Just for illustration –
this is bad coding style!

↑ individual wire of bus

Verilog Signal Manipulation

- ❖ Bus definition: $[n-1:0]$ is an n-bit bus
 - Good practice to follow bit numbering notation
 - Access individual bit/wire using “array” syntax (e.g., `bus[1]`)
 - Can access sub-bus using similar notation (e.g., `bus[4:2]`)
- ❖ Multi-bit constants: $n' b\#\dots\#$
 - n is width, b is radix specifier (b for binary), #s are digits of number
 - e.g., ^{decimal}`4'd12`, ^{binary}`4'b1100`, ^{hex}`4'hC` ← these are all equivalent
- ❖ Concatenation: $\{sig, \dots, sig\}$
 - Ordering matters; result will have combined widths of all signals
- ❖ Replication operator: $\{n\{m\}\}$
 - repeats value m, n times

 

Practice Question

```

logic [4:0] apple;
logic [3:0] pear;
logic [9:0] orange;
assign apple = 5'd20;
assign pear = {1'b0, apple[2:1], apple[4]};

```

^{width 5}
^{width 4}
^{width 10}

index: 4 3 2 1 0
 $\rightarrow 5'b \underline{1}0\underline{1}00$
 $\{0, 10, 1\}$

- ❖ What's the value of pear?

$4'b 0101 = \boxed{5}$ (across 4 wires)

- ❖ If we want orange to be the *sign-extended* version of apple, what is the appropriate Verilog statement?

$\boxed{\text{assign orange} = \{5\{apple[4]\}, apple\};}$

MSB
 $\begin{array}{l} \boxed{0000} \xrightarrow{\text{sign extension}} 0000\ 0000 \\ \boxed{1000} \xrightarrow{\text{from 4 to 8 bits}} 1111\ 1000 \end{array}$

Lecture Outline

- ❖ Thinking About Hardware
- ❖ Verilog Basics
- ❖ Waveform Diagrams
- ❖ **Debugging in Verilog**

Test Benches

❖ *Needed for simulation only!*

- Software constraint to mimic hardware


❖ ModelSim runs entirely on your computer

- Tries to simulate your FPGA environment without actually using hardware – no physical signals available
- Must create fake inputs for FPGA's physical connections
 - *e.g.*, LEDR, HEX, KEY, SW, CLOCK_50

★ Unnecessary when code is loaded onto FPGA

★ Need to define both input signal combinations as well as their timing

Verilog Test Benches (simulation only!)

 

defines simulation environment & timing

self-contained environment so no parts

variables for inputs

read output

```

module MUX2_tb ();
  logic SEL, I, J; // simulated inputs
  logic V;        // net for reading output

  // instance of module we want to test ("device under test")
  MUX2 dut (.V(V), .SEL(SEL), .I(I), .J(J));

  initial // build stimulus (test vectors)
  {
    begin // start of "block" of code
      {SEL, I, J} = 3'b100; #10; // t=0: S=1, I=0, J=0 -> V=0
      I = 1; #10; // t=10: S=1, I=1, J=0 -> V=1
      SEL = 0; #10; // t=20: S=0, I=1, J=0 -> V=0
      J = 1; #10; // t=30: S=0, I=1, J=1 -> V=1
    }
  } end // end of "block" of code

endmodule // MUX2_tb
    
```

time delay

Better Verilog Test Bench

```



module MUX2_tb ();
  logic SEL, I, J; // simulated inputs
  logic V;        // net for reading output

  // instance of module we want to test ("device under test")
  MUX2 dut (.V(V), .SEL(SEL), .I(I), .J(J));


  int i;
  initial // build stimulus (test vectors)
  begin // start of "block" of code
    for(i = 0; i < 8; i = i + 1) begin
      {SEL, I, J} = i; #10; ← runs through SEL, I, J with delay between each one
    end
  end // end of "block" of code
endmodule // MUX2_tb

```

Debugging Example (Demo)

  

- ❖ Check MUX2_tb waveforms:

 

- ❖ Identify buggy component(s) and dive deeper as necessary until bug is found
 - Demo: check NOT gates then check AND, OR gates

Debugging Circuits

- ❖ Complex circuits require careful debugging
 - Test as you go; don't wait until the end (system test)
 - *Every* module should have a test bench (unit test)
- 1) Test all behaviors
 - All combinations of inputs for small circuits, subcircuits
- 2) Identify any incorrect behaviors
- 3) Examine inputs & outputs to find earliest place where value is wrong
 - Typically trace backwards from bad outputs, forwards from inputs
 - Look at values at intermediate points in circuit

Hardware Debugging

- ❖ Simulation (ModelSim) is used to debug logic *design* and should be done thoroughly before touching FPGA
 - Unfortunately, ModelSim is not a perfect simulator
- ❖ If interfacing with other circuitry (*e.g.*, breadboard), will also need to debug circuitry layout there
 - Similar process, but with power sources (inputs) and voltmeters (probe the wires)
 - Often just a poor electrical connection somewhere
- ❖ Sometimes things simply fail
 - All electrical components fail eventually, whether you caused it to or not

Summary

- ❖ SystemVerilog is a hardware description language (HDL) used to program your FPGA
 - Programmatic syntax used to describe the connections between gates and registers
- ❖ Waveform diagrams used to track intermediate signals as information propagates through CL
- ❖ Hardware debugging is a critical skill
 - Similar to debugging software, but using different tools