 

Section 4

— Sequential Logic —

Administrivia

- **Lab 4:** Report due next Wednesday (4/24) @ 2:30 pm, demo by last OH on Friday (4/26), but expected during your assigned slot.
- **Lab 5:** Report due 5/1, demo by last OH on 5/3.
 - ⚠ This lab is a LOT harder than previous labs ⚠
- **Quiz 1:** Tuesday (4/23) at end of Lecture.
 - Very formulaic: gates, DeMorgan's, K-map, waveforms, test benches
 - Study from past quizzes on course website!




Parameters

New SystemVerilog Commands

- `parameter` – create a symbolic constant for a value that can be referenced in scope.
 - Like `#define` in C/C++.
 - Useful for things like timing constants, state names, module widths.

New SystemVerilog Commands

- **parameter** – create a symbolic constant for a value that can be referenced in scope.
 - Like `#define` in C/C++.
 - Useful for things like timing constants, state names, module widths.
- Parameterized modules:
 - Definition: `module <name> #(<param list>) (<port list>);`
 - `<param list>` is comma-separated and can include default values (e.g., `#(M, N=4)`).
 - Instantiation: `<name> #(<params>) <inst_name> (<ports>);`
 - Notice that parameter definitions are to the *left* of the instance name!
 - Generates different *versions* of the same module definition (like templates in C++).

Exercise 1

- (1) Parameterize the comparator module for bit-width **N**:
 - Hint: you will need to use a reduction operator (e.g., `~&A`), which will reduce all the bits of a vector into a single value using the specified Boolean operator.

```
// Implements an N-bit comparator circuit  
module comparator (A, B, is_lt, is_eq, is_gt);
```

- (2) Parameterize the guessing_game module for bit-width **N** and secret number **S**:

```
// Game to check user's N-bit input guess against a secret #  
module guessing_game (LEDR, KEY, SW);
```

Exercise 1 (Solution)

- Changes underlined and shown in red:

```
module comparator #(N = 3)
    (input logic [N-1:0] A, B,
      output logic is_lt, is_gt, is_eq);

    // subtraction result (intermediate)
    logic [N-1:0] sub;
    assign sub = A - B;

    assign is_eq = ~|sub;
    assign is_lt = sub[N-1];
    assign is_gt = ~is_eq & ~is_lt;

endmodule // comparator
```

Exercise 1 (Solution)

- Changes underlined and shown in red:

```
module guessing_game  #(N=3, S=3'd1)
    (output logic [9:0] LEDR,
     input logic [3:0] KEY, input logic [9:0] SW);

    logic is_lt, is_eq, is_gt;

    comparator  #(.N(N)) number_comparator (
        .A(SW[N-1:0]), .B(S), .is_lt, .is_eq, .is_gt
    );

    ... // LEDR assignments (unchanged)

endmodule // guessing_game
```


Sequential Logic


New SystemVerilog Commands

- `always_ff` – higher-level description of behavior that includes sequential logic.
 - Requires an explicit sensitivity/trigger list (e.g., `@(posedge clk)`) that dictates when the code block will take effect.
- Non-blocking statements (`<=`) should be used with `always_ff`, blocking statements (`=`) should be used with `assign` and `always_comb`.

Flip-Flops and Registers (Review)


- A **flip-flop** samples `d` on triggers and transfers its value to `q`.
 
```
module basic_D_FF (output logic q, input logic d, clk);  
    always_ff @(posedge clk)  
        q <= d;  
endmodule // basic_D_FF
```



- A **register** is a collection of `N` flip-flops together.
 
```
module basic_reg #(N) (output logic [N-1:0] Q,  
                       input logic [N-1:0] D,  
                       input logic clk);  
    always_ff @(posedge clk)  
        Q <= D;  
endmodule // basic_reg
```



Reset Functionality (Review)

- A sequential element often has a **reset** signal that will drive its output to a *known value*.
 - Useful in hardware to substitute for “initialization.”
 - Two options, **synchronous** (left) or **asynchronous** (right):

```
module D_FF1 (output logic q,  
  input logic d, reset, clk);  
  always_ff @(posedge clk)  
    if (reset)  
      q <= 0;  
  else  
    q <= d;  
endmodule // D_FF1
```

```
module D_FF2 (output logic q,  
  input logic d, reset, clk);  
  always_ff @(posedge clk or posedge reset)  
    if (reset)  
      q <= 0;  
  else  
    q <= d;  
endmodule // D_FF2
```


Clock in Hardware

- We will use the DE1-SoC's built-in 50 MHz clock called `CLOCK_50`.
 - Accessed by adding `CLOCK_50` as an `input logic` to your top-level module.
- Because 50 MHz (*i.e.*, clock period = 20 ns) may be too fast for humans, can use provided `clock_divider` module to slow things down.
 - Recommendation: assign extra signal `clk` to `divided_clocks[#]`.
 - Make sure to comment out `clock_divider` for simulation!

```
logic [31:0] divided_clocks;
logic clk;
clock_divider cdiv (.clock(CLOCK_50), .divided_clocks);
assign clk = divided_clocks[23]; // replace with = CLOCK_50 for simulation
// Instantiating a module that is using clock 23
<module_name> <instance_name> (.clk, .reset, ... );
```

 Exercise 2

- Write a module called **string_lights** that implements the system shown below (a string of 10 flip-flops/1-bit registers tied to the LEDRs) for the DE1-SoC.
 - Use `SW[9]` as the reset, `SW[0]` as `In`, and `~KEY[0]` as `clk`.
 - Since we are using a `KEY` for the clock, no need for `clock_divider`.
 - Hint: flip-flops can be module instances or inferred from an `always_ff` block.



Exercise 2 (Solution)

- **Version 1:** module instances
 - Connections made via ports.

```
module string_lights (output logic [9:0] LEDR,  
                    input  logic [3:0] KEY,  
                    input  logic [9:0] SW);  
  
    logic clk, reset, in;  
    assign clk    = ~KEY[0];  
    assign reset  = SW[9];  
    assign in     = SW[0];  
  
    D_FF1 ff9 (.q(LED[9]), .d(in),      .reset, .clk);  
    D_FF1 ff8 (.q(LED[8]), .d(LED[9]), .reset, .clk);  
    ...  
    D_FF1 ff1 (.q(LED[1]), .d(LED[2]), .reset, .clk);  
    D_FF1 ff0 (.q(LED[0]), .d(LED[1]), .reset, .clk);  
  
endmodule // string_lights
```

Exercise 2 (Solution)

- **Version 2: always_ff**
 - Connections made via non-blocking assignments.

```
module string_lights (output logic [9:0] LEDR,  
                    input  logic [3:0] KEY,  
                    input  logic [9:0] SW);  
  
    logic clk, reset, in;  
    assign clk    = ~KEY[0];  
    assign reset  = SW[9];  
    assign in     = SW[0];  
  
    always_ff @(posedge clk)  
        if (reset)  
            LEDR <= 10'd0;  
        else  
            LEDR <= {in, LEDR[9:1]};  
  
endmodule // string_lights
```


Exercise 2 Demo (If Time)

- Compile and run `string_lights` on a DE1-SoC.
 - Normally, you should ALWAYS run simulations first.

Sequential Logic Test Benches

Clock Generation (Review)

- In simulation, need to create a clock signal yourself (steady square wave).
 - Just pick your favorite form and copy-and-paste into your future test benches.
 - Exact period doesn't really matter since it's all arbitrary time units.

Explicit Edges:

```
parameter T = 100; // period
initial
  clk = 0;
always begin
  #(T/2) clk <= 1;
  #(T/2) clk <= 0;
end
```

Toggle:

```
parameter T = 100; // period
initial
  clk = 0;
always
  #(T/2) clk <= ~clk;
```

Edge-Sensitive Delays


- Delays until specified transition on signal: `@(<pos/negedge> signal);`
 - Allows us to wait for the next clock trigger in our simulation since that's when sequential elements will update.
- Example test bench block:

```
initial begin
  d <= 1'b1; reset <= 1'b1; @(posedge clk); // reset
      reset <= 1'b0; @(posedge clk); // store 1
      @(posedge clk); // hold 1
  d <= 1'b0;      @(posedge clk); // store 0
      @(posedge clk); // hold 0

  $stop();
end
```

Sequential Test Bench Notes

- Need to manually track the expected state for sequential elements.
- Always define ALL of your inputs at $t=0$, even if you're resetting, to eliminate unnecessary red lines in simulation.
- Whitespace in `initial` block doesn't matter but we recommend being consistent (*i.e.*, line up your delays on right or left side of each line).
- All logic delays set to 0 in our ModelSim setup, so be careful with interpreting signal changes.

 

- Include an extra delay at the end to see the effects of your last input changes.

Exercise 3

- Create a test bench for `string_lights` and simulate it in ModelSim.
 - Do we need this test bench to be *thorough*? What would be enough to convince you that it is working properly?
 - What do you think the best combination of signals (and radices) are to use for the reader of your simulation?
 - *e.g.*, do you want to show the top-level `SW[9]` signal or an internal `reset` signal?

Exercise 3 (Solution)

- Create Module , create ports, instantiate dut

```
module string_lights_tb ();  
    logic [9:0] LEDR;  
    logic [3:0] KEY;  
    logic [9:0] SW;  
  
    string_lights dut (.*);  
  
endmodule // string_lights_tb
```

Exercise 3 (Solution)

- Setup clock – since KEY[0] is *active-low*, need to start with 1 instead of 0.

```
module string_lights_tb ();
    ... // signal declarations and dut instantiation

    parameter T = 100;
    initial
        KEY[0] = 1'b1;
    always begin
        #(T/2) KEY[0] <= 1'b0;
        #(T/2) KEY[0] <= 1'b1;
    end

endmodule // string_lights_tb
```


Exercise 3 (Solution)

- Define `initial` block and add `$stop` system task.
 - Make sure to initialize all inputs at `t = 0`!

```
module string_lights_tb ();
    ... // signal declarations and dut instantiation
    ... // clock generation

    initial begin
        SW[0] <= 1'b0; SW[9] <= 1'b1; @(negedge KEY[0]); // reset

        $stop;
    end

endmodule // string_lights_tb
```

Exercise 3 (Solution)

- We can now start simulating some possible behaviors of our design!
 - e.g., let's try the input sequence 0, 1, 0, 0, 1, 1, 0, 0, 0, 1, 1, 1



```
module string_lights_tb ();
    ... // signal declarations and dut instantiation
    ... // clock generation

    initial begin
        SW[0] <= 1'b0; SW[9] <= 1'b1; @(negedge KEY[0]); // reset
        SW[0] <= 1'b0; SW[9] <= 1'b0; @(negedge KEY[0]); // 0
        SW[0] <= 1'b1;          @(negedge KEY[0]); // 1
        ... // finish desired pattern
                                   @(negedge KEY[0]); // final delay

        $stop;
    end
endmodule // string_lights_tb
```

  Exercise 3 (Solution)

- Simulation results verify (1) reset works, (2) inputs travel across entire string, and (3) a variety of combinations of inputs.
 - Using internal signal names for readability.



Exercise 3 (Solution)

- Simulation results verify (1) reset works, (2) inputs travel across entire string, and (3) a variety of combinations of inputs.
 - Using internal signal names for readability.
- Many other behaviors are possible and should be tested!
 - The idea here is not necessarily to test out all possibilities like in combinational logic but enough relevant scenarios to give you confidence that it is working properly.