
Section 7

Common Issues When
Connecting Modules

Administrivia

- **Lab 7:** Report due next Wednesday (5/15) @ 2:30 pm, demo by last OH on Friday (5/17), but expected during your assigned slot.
 - Tunable cyber player opponent (counter, LFSR, adder).
- **Lab 8:** Final project is coming up!
 - Choose from 8 possible projects or suggest your own.
 - Range of difficulties (and point values).
 - Extra credit opportunities for early finish and bonus features!



General Debugging Tips



SystemVerilog Debugging

- Many things are similar to software debugging!
 - Have compiler messages and program output to work with.
 - Identify the behavior(s) that differ from what you expect and work backwards from there.
 - Need to understand data representation and manipulation.

SystemVerilog Debugging

- Many things are similar to software debugging!
 - Have compiler messages and program output to work with.
 - Identify the behavior(s) that differ from what you expect and work backwards from there.
 - Need to understand data representation and manipulation.
- However, many things are different in hardware!
 - Parallel (instead of sequential) execution makes interpreting programs more difficult.
 - We often rely on simulation waveforms instead of terminal output.
 - Timing is always a factor/consideration (e.g., timing delays, sensitivity lists, blocking vs. non-blocking assignments).
 - Can make mistakes between simulation and bit file (e.g., `clock_divider`).




General Debugging Tips

- The best debugging advice is to not have to debug at all!
 - **Focus on the design** (*i.e.*, block diagrams, state diagrams) to avoid impractical designs and major logical flaws.

General Debugging Tips

- The best debugging advice is to not have to debug at all!
 - **Focus on the design** (*i.e.*, block diagrams, state diagrams) to avoid impractical designs and major logical flaws.
- Staring at code until you think you spot a bug is generally not an effective way to debug.
 - Of course it looks logically correct to you – you wrote it!
 - SystemVerilog is a really tricky language – we've only scratched the surface and the code often obfuscates the synthesized hardware.
- Instead, lean on the available tools, which are intended to help you.
 - We'll cover some tips in the following slides.

Quartus Debugging Tips

- The built-in syntax highlighting can help find typos in keywords (black vs. blue text) and what is currently commented out (green vs. not green).
- Double-clicking a word will highlight *all instances* of that word in your code, making for easier visual scanning and spotting of typos.
- Pay attention to compiler output messages, *which usually point out the problematic line of code!*
 - Can filter by (1) Errors , (2) Critical Warnings , and (3) Warnings .
 - Some common messages and their suggested fixes can be found in our [SystemVerilog Warnings & Errors Doc.](#)
 - Double-click a warning or error message to have it automatically take you to the appropriate point in the code.

ModelSim Debugging Tips

- ModelSim has its own compiler so pay attention to output messages here as well.
- Add internal signals from any instantiated module to your simulation!
 - For a buggy signal, add *all* signals involved in the computation of that signal.
- Make sure you're using the appropriate radix (e.g., binary vs. decimal vs. unsigned) for that signal's particular use case.
- **Red lines** have multiple causes; it's important to identify which is the case so you can narrow down your fix.
 - Undefined signal (e.g., no initialization), net contention (e.g., multiple drivers), explicit don't care in code (e.g., `default: leds = 7'bX;`).

Debugging Time!

Exercise 1 – Interpreting Messages

- Given the following modules and error messages, identify & fix the bug.

```
2 module ex1 (output logic dout, input logic [2:0] upc);
3   assign dout = upc[1] & upc[0] ^ upc[2];
4 endmodule // ex1
```

```
2 module DE1_SoC (input logic [9:0] SW, output logic [9:0] LEDR);
3   ex1 e1 (.dout(LEDR[0]), .upc(SW[1:0]));
4 endmodule // DE1_SoC
```

```
▲ 122411 hierarchies have connectivity warnings - see the Connectivity Checks report folder
● 144001Generated suppressed messages file c:/369/sec7/output_files/DE1_SoC.map.smsg
> ● 16010Generating hard_block partition "hard_block:auto_generated_inst"
> ● 21057Implemented 20 device resources after synthesis - the final resource count might be different
> ● Quartus Prime Analysis & Synthesis was successful. 0 errors, 1 warning
```

Port Connectivity Checks: "ex1:e1"

🔍 <<Filter>>

	Port	Type	Severity	Details
1	upc	Input	Warning	Input port expression (2 bits) is smaller than the input port (3 bits) it drives. Extra input bit(s) "upc[2..2]" will be connected to GND.

Exercise 1 (Solution)

- Given the following modules and error messages, identify & fix the bug.

```
2 module ex1 (output logic dout, input logic [2:0] upc);
3   assign dout = upc[1] & upc[0] ^ upc[2];
4 endmodule // ex1
```

```
2 module DE1_SoC (input logic [9:0] SW, output logic [9:0] LEDR);
3   ex1 e1 (.dout(LED[0]), .upc(SW[2:0])); ← changed to [2:0]
4 endmodule // DE1_SoC
```

```
▲ 122411 hierarchies have connectivity warnings - see the Connectivity Checks report folder
● 144001Generated suppressed messages file c:/369/sec7/output_files/DE1_SoC.map.smsg
> ● 16010Generating hard_block partition "hard_block:auto_generated_inst"
> ● 21057Implemented 20 device resources after synthesis - the final resource count might be different
> ● Quartus Prime Analysis & Synthesis was successful. 0 errors, 1 warning
```

Port Connectivity Checks: "ex1:e1"

🔍 <<Filter>>

	Port	Type	Severity	Details
1	upc	Input	Warning	Input port expression (2 bits) is smaller than the input port (3 bits) it drives. <u>Extra input bit(s) "upc[2..2]" will be connected to GND.</u>

Exercise 2 – Port Connection Analysis

- Given the modules to the right, analyze the ports instantiations in ex2 *independently*.
 - Is there an issue?
 - If so, what is it? Do you think it will produce a warning or an error?

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6   ports option1 (.a, .c);  
7   ports option2 (.a, .b(e), .c);  
8   ports option3 (.*);  
9   ports option4 (.a, .b(e), .c, .d);  
10  ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```

Exercise 2-1 (Solution)

- option1:

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6     ports option1 (.a, .c);  
7     ports option2 (.a, .b(e), .c);  
8     ports option3 (.*);  
9     ports option4 (.a, .b(e), .c, .d);  
10    ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```

Exercise 2-1 (Solution)

- option1:
 - Only 2 ports connected to 3-port module.
 - Compiler warning:

 Warning (12241): 1 hierarchies have connectivity warnings - see the Connectivity Checks report folder

 Info: Quartus Prime Analysis & Synthesis was successful. 0 errors, 2 warnings

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6   ports option1 (.a, .c);  
7   ports option2 (.a, .b(e), .c);  
8   ports option3 (.*);  
9   ports option4 (.a, .b(e), .c, .d);  
10  ports option5 (.a, .b(e), .c(d)).
```

Port Connectivity Checks: "ports:option1"

<<Filter>>

	Port	Type	Severity	Details
1	b	Input	Warning	Declared by entity but not connected by instance. If a default value exists, it will be used. Otherwise, the port will be connected to GND.

Exercise 2-2 (Solution)

- option2:

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6   ports option1 (.a, .c);  
7   ports option2 (.a, .b(e), .c);  
8   ports option3 (.*);  
9   ports option4 (.a, .b(e), .c, .d);  
10  ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```


Exercise 2-2 (Solution)

- option2:
 - No issues!
 - Though this is confusing port naming and is not recommended.



```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6   ports option1 (.a, .c);  
7   ports option2 (.a, .b(e), .c);  
8   ports option3 (.*);  
9   ports option4 (.a, .b(e), .c, .d);  
10  ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```

Exercise 2-3 (Solution)

- option3:

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6   ports option1 (.a, .c);  
7   ports option2 (.a, .b(e), .c);  
8   ports option3 (.*);  
9   ports option4 (.a, .b(e), .c, .d);  
10  ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```

Exercise 2-3 (Solution)

- option3:
 - Implicit port connections fails for b because the types don't match.
 - Compiler errors:

❑ Error (10897): SystemVerilog error at ex2.sv(8): can't implicitly connect port "b" on instance "option3" of module "ports" - matching object in present scope does not have an equivalent data type

❑ Error (10784): HDL error at ports.sv(3): see declaration for object "b"

❑ Error (10784): HDL error at ex2.sv(2): see declaration for object "b"

❑ Error (12153): Can't elaborate top-level user hierarchy

❑ Error: Quartus Prime Analysis & Synthesis was unsuccessful. 4 errors, 0 warnings

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6   ports option1 (.a, .c);  
7   ports option2 (.a, .b(e), .c);  
8   ports option3 (.*);  
9   ports option4 (.a, .b(e), .c, .d);  
10  ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```

Exercise 2-4 (Solution)

- option4:

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6   ports option1 (.a, .c);  
7   ports option2 (.a, .b(e), .c);  
8   ports option3 (. *);  
9   ports option4 (.a, .b(e), .c, .d);  
10  ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```

Exercise 2-4 (Solution)

- option4:
 - There is no d port for ports (only 3 ports, too).
 - Compiler errors:

□ Error (10284): Verilog HDL Module Instantiation error at ex2.sv(9): port "d" is not declared by module "ports"

□ Error: Quartus Prime Analysis & Synthesis was unsuccessful. 1 error, 0 warnings

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6   ports option1 (.a, .c);  
7   ports option2 (.a, .b(e), .c);  
8   ports option3 (.*);  
9   ports option4 (.a, .b(e), .c, .d);  
10  ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```

Exercise 2-5 (Solution)

- option5:

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6   ports option1 (.a, .c);  
7   ports option2 (.a, .b(e), .c);  
8   ports option3 (.*);  
9   ports option4 (.a, .b(e), .c, .d);  
10  ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```

Exercise 2-5 (Solution)

- option5:
 - Multiple drivers: c is an output port for ports but connected to an input port.
 - Compiler errors:

- Error (10031): Net "d" at ex2.sv(10) is already driven by input port "d", and cannot be driven by another signal
- Error (10032): "d" was declared at ex2.sv(2)
- Error (12153): Can't elaborate top-level user hierarchy
- Error: Quartus Prime Analysis & Synthesis was unsuccessful. 3 errors, 0 warnings

```
2 module ports (input logic a,  
3               input logic [1:0] b,  
4               output logic c);  
5 endmodule // ports
```

```
2 module ex2 (input logic a, b, d,  
3             input logic [1:0] e,  
4             output logic c);  
5  
6     ports option1 (.a, .c);  
7     ports option2 (.a, .b(e), .c);  
8     ports option3 (.*);  
9     ports option4 (.a, .b(e), .c, .d);  
10    ports option5 (.a, .b(e), .c(d));  
11  
12 endmodule // ex2
```

Contention on a Net

- A situation where two or more drivers (sources of signals) are trying to drive a net to different values at the same time is known as **contention**.
 - This will show up as an **X** value in simulation, and could result in damage to the drivers in a physical device!

Contention on a Net

- A situation where two or more drivers (sources of signals) are trying to drive a net to different values at the same time is known as **contention**.
 - This will show up as an **X** value in simulation, and could result in damage to the drivers in a physical device!
- Example:

```
module DE1_SoC (input logic [9:0] SW, output logic [6:0] HEX0, HEX1);  
  
    seg7 display(.leds(HEX0), .bcd({SW[3], SW[2], SW[1], SW[0]}));  
  
    // Default values, turns off the HEX displays  
    assign HEX0 = 7'b1111111;  
    assign HEX1 = 7'b1111111;  
  
endmodule // DE1_SoC
```

Contention on a Net Example Analysis

multiply driven!

```
module DE1_SoC (input logic [9:0] SW, output logic [6:0] HEX0, HEX1);  
    seg7 display(.leds(HEX0), .bcd({SW[3], SW[2], SW[1], SW[0]}));  
  
    // Default values, turns off the HEX displays  
assign HEX0 = 7'b1111111;  
    assign HEX1 = 7'b1111111;  
  
endmodule // DE1_SoC
```

remove the unnecessary assignment here

- ❑ Error (12014): Net "HEX0[6]", which fans out to "HEX0[6]", cannot be assigned more than one value
- ❑ Error (12014): Net "HEX0[5]", which fans out to "HEX0[5]", cannot be assigned more than one value
- ❑ Error (12014): Net "HEX0[4]", which fans out to "HEX0[4]", cannot be assigned more than one value
- ❑ Error (12014): Net "HEX0[3]", which fans out to "HEX0[3]", cannot be assigned more than one value
- ❑ Error (12014): Net "HEX0[2]", which fans out to "HEX0[2]", cannot be assigned more than one value
- ❑ Error (12014): Net "HEX0[1]", which fans out to "HEX0[1]", cannot be assigned more than one value
- ❑ Error (12014): Net "HEX0[0]", which fans out to "HEX0[0]", cannot be assigned more than one value
- Error (12015): Net is fed by "VCC"
- Error (12015): Net is fed by "seg7:display|leds[0]" ← these are expanded messages
- ❑ Error: Quartus Prime Analysis & Synthesis was unsuccessful. 21 errors, 0 warnings

Example 1

Identify the bug in the following code:

```
module parent (  
    input logic Clk, in,  
    output logic out  
);  
  
    child c (.Clk, .in, .out);  
  
endmodule // parent
```

❑ Error: Port "Clk" does not exist in macrofunction "f"

```
module child (  
    input logic clk, in,  
    output logic out  
);  
  
    logic ps, ns;  
  
    always_comb  
        case (ps)  
            1'b0: ns = (in ? 1'b1 : 1'b0);  
            1'b1: ns = (in ? 1'b0 : 1'b1);  
            default: ns = ps;  
        endcase  
  
    assign out = ns;  
  
    always_ff @(posedge clk)  
        ps <= ns;  
  
endmodule // child
```

*Note that reset is omitted for simplicity

Example 1

Clk ≠ clk!

Make sure port connections are sound
(esp. c vs. C is hard to tell on Quartus)

```
module parent (  
    input logic clk, in,  
    output logic out  
);  
  
    // alternatively, .clk(Clk)  
    child c (.clk, .in, .out);  
  
endmodule // parent
```

```
module child (  
    input logic clk, in,  
    output logic out  
);  
  
    logic ps, ns;  
  
    always_comb  
        case (ps)  
            1'b0: ns = (in ? 1'b1 : 1'b0);  
            1'b1: ns = (in ? 1'b0 : 1'b1);  
            default: ns = ps;  
        endcase  
  
    assign out = ns;  
  
    always_ff @(posedge clk)  
        ps <= ns;  
  
endmodule // child
```


*Note that reset is omitted for simplicity

Example 2

Identify the bug in the following code:

```
module DE1_SoC (  
    input logic CLOCK_50,  
    output logic [6:0] HEX0, ...  
    ...  
    output logic [9:0] SW  
);  
  
    // instantiate an fsm that lights LEDR[0] on  
    // when KEY[0] is pressed for two frames in a row  
    fsm f (.clk(CLOCK_50), .in(KEY[0]) .out(LEDR[0]));  
  
endmodule // DE1_SoC
```

Buggy Simulation:

 


Example 2

KEYs are **Active-Low!**

Make sure to account for hardware realities.

```
module DE1_SoC (  
    input logic CLOCK_50,  
    output logic [6:0] HEX0, ...  
    ...  
    output logic [9:0] SW  
);  
  
    // instantiate an fsm that lights LEDR[0] on  
    // when KEY[0] is pressed for two frames in a row  
    fsm f (.clk(CLOCK_50), .in(~KEY[0]) .out(LEDR[0]));  
  
endmodule // DE1_SoC
```

Correct Simulation:

 

Timing Issues

Example 3 - Different Clocks Issue

- A situation where not all module instances are using the same clock.
- For example, say we have this register A that captures and outputs a 4-bit input signal:

```
module A(  
    input logic clk,  
    input logic reset,  
    input logic [3:0] in,  
    output logic [3:0] out);  
  
    always_ff @(posedge clk)  
        if (reset)  
            out <= 0;  
        else  
            out <= in;  
endmodule // moduleA
```


Example 3 - Different Clocks Issue

In the top-level module, we instantiate module A twice.

```
module top_module(  
    input logic CLOCK_50,  
    input logic reset,  
    input logic [3:0] in,  
    output logic [3:0] out1, out2  
);  
  
    // clock divider  
    logic [31:0] clock;  
    clock_divider cdiv (.clock(clk), .divided_clocks(clock));  
  
    A a1(.clk(CLOCK_50), .reset, .in, .out(out1));  
    A a2(.clk(clock[1]), .reset, .in, .out(out2));  
  
endmodule // top_module
```

```
module A(  
    input logic clk,  
    input logic reset,  
    input logic [3:0] in,  
    output logic [3:0] out);  
  
    always_ff @(posedge clk)  
        if (reset)  
            out <= 0;  
        else  
            out <= in;  
endmodule // moduleA
```

Example 3 - Different Clocks Issue

- Instance a1 with the clock_50
- Instance a2 with the divided clock

```
module top_module(  
    input logic CLOCK_50,  
    input logic reset,  
    input logic [3:0] in,  
    output logic [3:0] out1, out2  
);  
  
    // clock divider  
    logic [31:0] clock;  
    clock_divider cdiv (.clock(clk), .divided_clocks(clock));  
  
    // a1 is using a 50Mhz clock  
    // a2 is using a slower clock with 12.5 MHz  
    A a1(.clk(CLOCK_50), .reset, .in, .out(out1));  
    A a2(.clk(clock[1]), .reset, .in, .out(out2));  
  
endmodule // top_module
```

```
module A(  
    input logic clk,  
    input logic reset,  
    input logic [3:0] in,  
    output logic [3:0] out);  
  
    always_ff @(posedge clk)  
        if (reset)  
            out <= 0;  
        else  
            out <= in;  
endmodule // moduleA
```

Example 3 - Different Clocks Issue


- This will cause a **desynchronization** in our system!
- Easy to miss when going between hardware ↔ sim.

```
module top_module(  
    input logic CLOCK_50,  
    input logic reset,  
    input logic [3:0] in,  
    output logic [3:0] out1, out2  
);  
  
    // clock divider  
    logic [31:0] clock;  
    clock_divider cdiv (.clock(clk), .divided_clocks(clock));  
  
    // a1 is using a 50Mhz clock  
    // a2 is using a slower clock with 12.5 MHz  
    A a1(.clk(CLOCK_50), .reset, .in, .out(out1));  
    A a2(.clk(clock[1]), .reset, .in, .out(out2));  
  
endmodule // top_module
```

```
module A(  
    input logic clk,  
    input logic reset,  
    input logic [3:0] in,  
    output logic [3:0] out);  
  
    always_ff @(posedge clk)  
        if (reset)  
            out <= 0;  
        else  
            out <= in;  
endmodule // moduleA
```

Different Clocks Issue (Simulation)

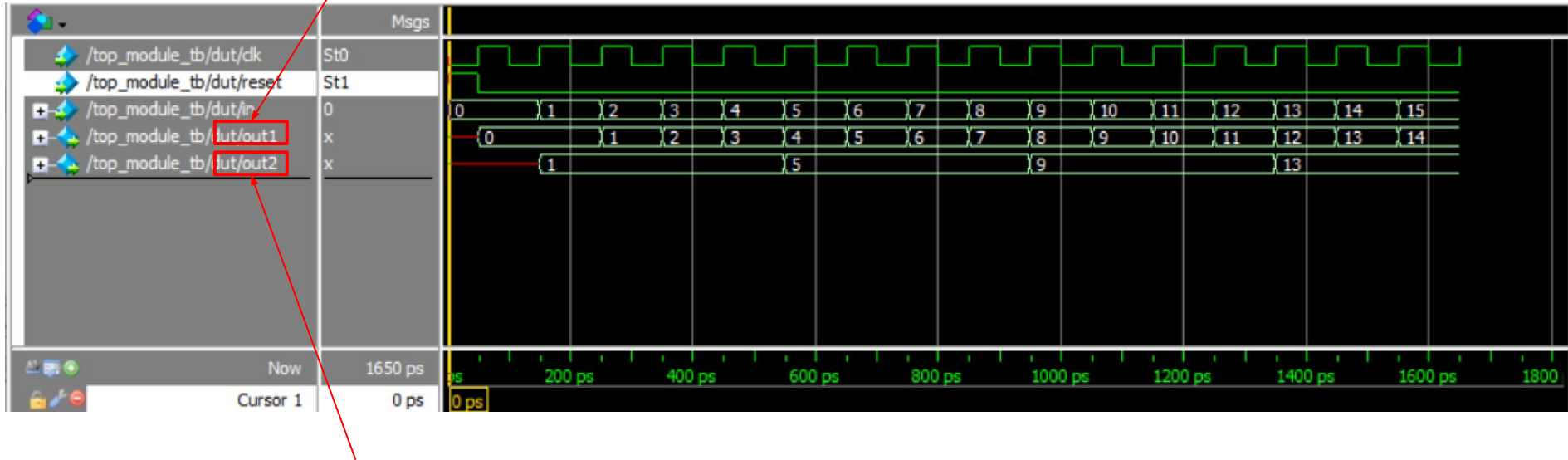
Output of the module A that does not use divided clock (50 MHz clock)



Output of the module A that does use divided clock (12.5 MHz clock)

Different Clocks Issue (Simulation)

 Let's take a closer look at the clock in each module




The clocks in module a1 and a2 have different clock frequency. Module a2 has a slower clock than a1 does, causing desynchronization issue.

Different Clocks Issue (Simulation)


Using the same clock!

```
module top_module(...);  
    ...  
    A a1(.clk(CLOCK_50), .reset, .in, .out(out1));  
    A a2(.clk(CLOCK_50), .reset, .in, .out(out2));  
endmodule // top_module
```

 



Exercise 3

- In Section 6, we worked on a design of the **psychic tester**, where the user needs to correctly guess 8 consecutive 4-bit patterns to be declared a psychic.
- Say we want to modify our design so the next signal comes directly from user_input.

 


Exercise 3

- In Section 6, we worked on a design of the **psychic tester**, where the user needs to correctly guess 8 consecutive 4-bit patterns to be declared a psychic.
- Say we want to modify our design so the next signal comes directly from user_input.

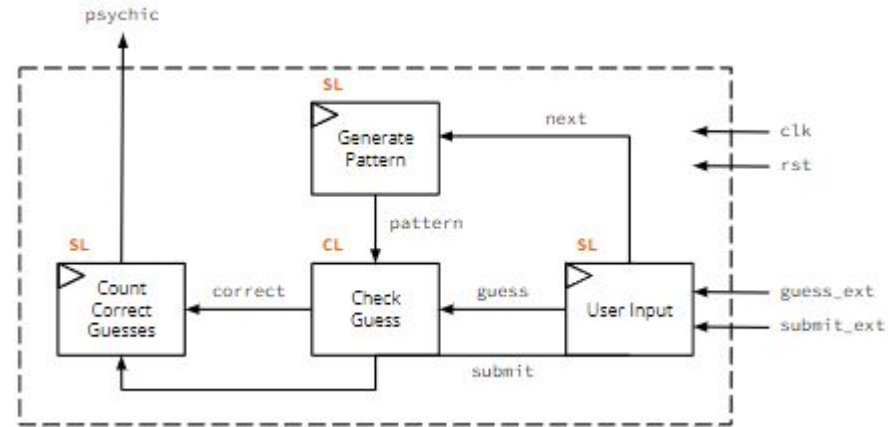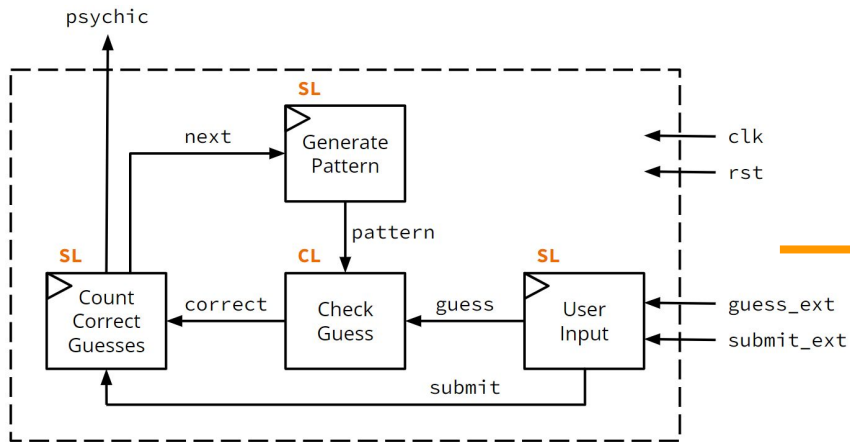

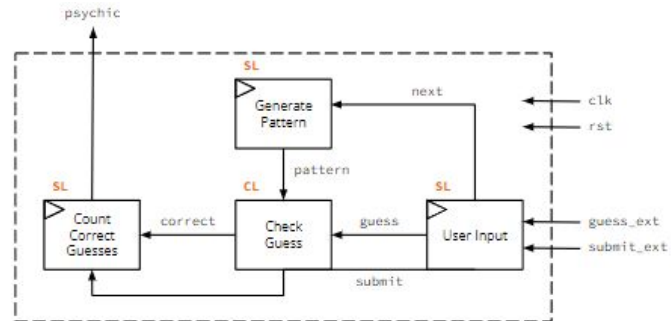Exercise 3

- Let's see how one might modify **psychic_tester**




```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);
  input logic clk, rst, submit_ext;
  input logic [3:0] guess_ext;
  output logic psychic;

  logic [3:0] pattern, guess;
  logic correct, next, submit;

  genPatt pat (.clk, .rst, .pattern, .next);
  userIn inp (.clk, .rst,
             .guess_ext, .submit_ext, .guess, .submit);
  checkGuess chk (.pattern, .guess, .correct);
  countRight cnt (.clk, .rst, .correct, .submit, .next, .psychic);
endmodule // psychic_tester
```

 Exercise 3

- Remove the next signal from countRight:




```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);
    input logic      clk, rst, submit_ext;
    input logic [3:0] guess_ext;
    output logic     psychic;

    logic [3:0] pattern, guess;
    logic correct, next, submit;

    genPatt    pat (.clk, .rst, .pattern, .next);
    userIn     inp (.clk, .rst,
                   .guess_ext, .submit_ext, .guess, .submit);
    checkGuess chk (.pattern, .guess, .correct);
    countRight cnt (.clk, .rst, .correct, .submit, .psychic);
endmodule // psychic_tester
```

Exercise 3

- Assign next to submit_ext

 

```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);
    input logic      clk, rst, submit_ext;
    input logic [3:0] guess_ext;
    output logic     psychic;


    logic [3:0] pattern, guess;
    logic correct, next, submit;
    assign next = submit_ext;
    genPatt    pat (.clk, .rst, .pattern, .next);
    userIn     inp (.clk, .rst,
                  .guess_ext, .submit_ext, .guess, .submit);
    checkGuess chk (.pattern, .guess, .correct);
    countRight cnt (.clk, .rst, .correct, .submit, .psychic);
endmodule // psychic_tester
```

Exercise 3

- Because we didn't modify how our input and outputs work and how the design should behave, we should be able to use the same testbench!
- Let's take a look at ModelSim and see if things are behaving the way we expect...

Exercise 3


- Because we didn't modify how our input and outputs work and how the design should behave, we should be able to use the same testbench!
- Let's take a look at ModelSim and see if things are behaving the way we expect...

 

Exercise 3a




- We don't get a high signal for `psychic` anymore...
- **Group brainstorm:** What could be causing this issue? What would you investigate?

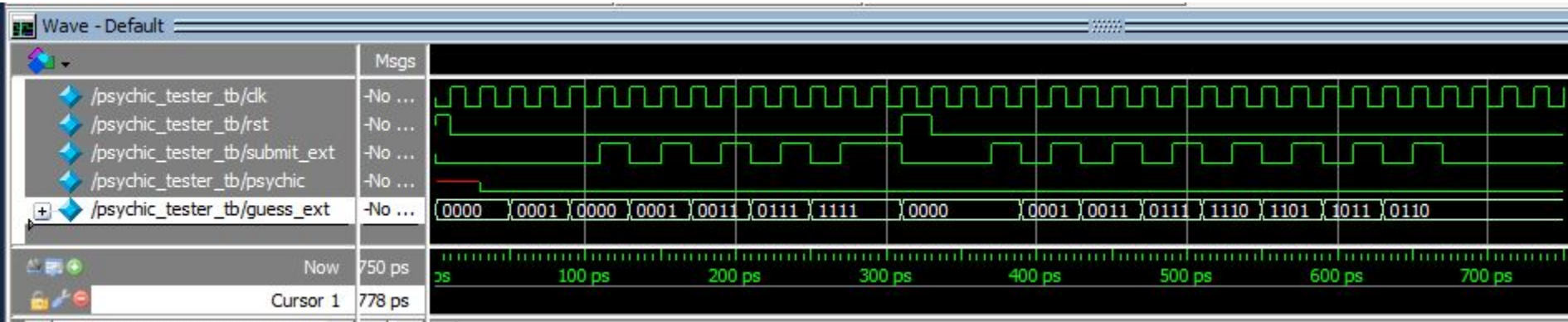


Exercise 3a

- We don't get a high signal for `psychic` anymore...
- **Group brainstorm:** What could be causing this issue? What would you investigate?
- Check intermediate signals!
 - Counter signal
 - Pattern signal
- Investigate internal signal of submodules that could have been affected by our modifications!

 

Exercise 3b


- Let's analyze our internal signals

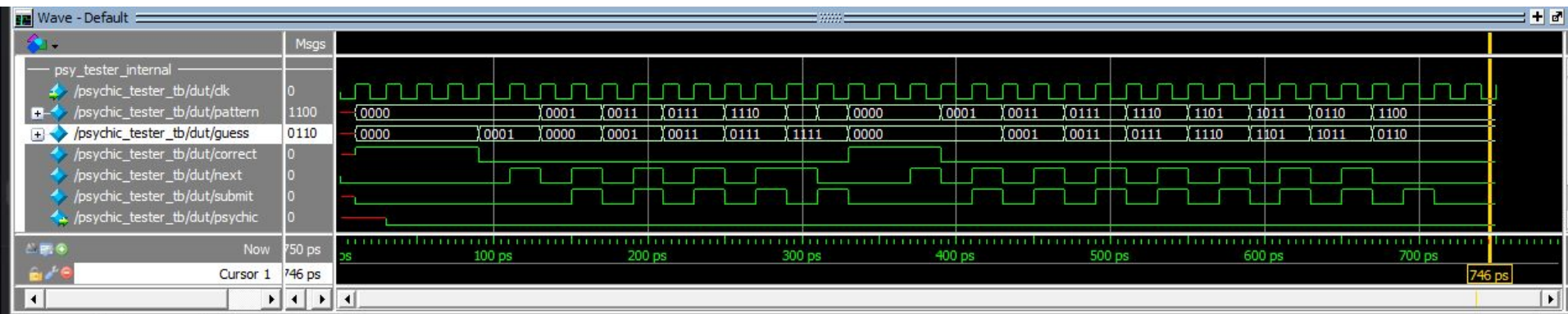

- Group Brainstorming:** What incorrect behavior do you notice?

Exercise 3b


- Let's analyze our internal signals

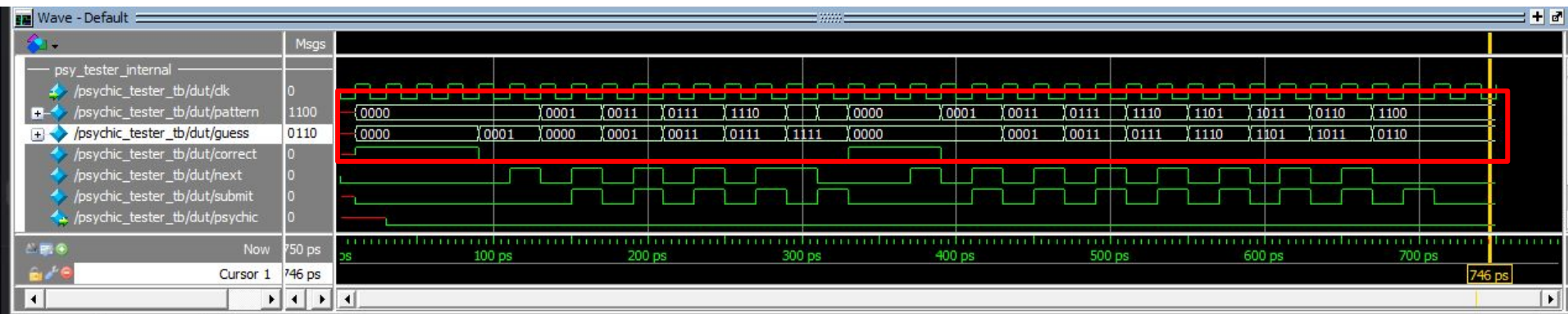

- It's clear that our pattern is not changing like we expect anymore!
- Group Brainstorming:** What other weird behaviors do you notice?

Exercise 3b


- Let's analyze our internal signals

 

- It's clear that our pattern is not changing like we expect anymore!
- Group Brainstorming:** What other weird behaviors do you notice?
- Notice how at 310 ps our pattern changes, even though the next signal should be synchronized to have a 1 clock delay!

Exercise 3b

- Let's analyze our internal signals

 

- It's clear that our pattern is not changing like we expect anymore!
- Group Brainstorming:** What other weird behaviors do you notice?
- Notice the difference between signals next and submit! One is not edge detected!

Exercise 3c

- **Group Brainstorm:** Let's go back to the code and see if we can spot the bug! What lines could be causing our timing issue?

```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);
  input logic          clk, rst, submit_ext;
  input logic [3:0]   guess_ext;
  output logic        psychic;

  logic [3:0] pattern, guess;
  logic correct, next, submit;
  assign next = submit_ext;
  genPatt     pat (.clk, .rst, .pattern, .next);
  userIn     inp (.clk, .rst,
                  .guess_ext, .submit_ext, .guess, .submit);
  checkGuess chk (.pattern, .guess, .correct);
  countRight cnt (.clk, .rst, .correct, .submit, .psychic);
endmodule // psychic_tester
```

Exercise 3c

- **Group Brainstorm:** Remember the two weird behaviors we noticed: `pattern` is not synchronized and `next` is not being edge detected.

```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);
  input logic      clk, rst, submit_ext;
  input logic [3:0] guess_ext;
  output logic     psychic;

  logic [3:0] pattern, guess;
  logic correct, next, submit;
  assign next = submit_ext;
  genPatt     pat (.clk, .rst, .pattern, .next);
  userIn      inp (.clk, .rst,
                  .guess_ext, .submit_ext, .guess, .submit);
  checkGuess  chk (.pattern, .guess, .correct);
  countRight cnt (.clk, .rst, .correct, .submit, .psychic);
endmodule // psychic_tester
```

Exercise 3c

- We incorrectly assigned next to submit_ext instead of submit!

```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);
  input logic      clk, rst, submit_ext;
  input logic [3:0] guess_ext;
  output logic     psychic;

  logic [3:0] pattern, guess;
  logic correct, next, submit;
  assign next = submit_ext;
  genPatt    pat (.clk, .rst, .pattern, .next);
  userIn     inp (.clk, .rst,
                  .guess_ext, .submit_ext, .guess, .submit);
  checkGuess chk (.pattern, .guess, .correct);
  countRight cnt (.clk, .rst, .correct, .submit, .psychic);
endmodule // psychic_tester
```

Exercise 3c

- We incorrectly assigned next to submit_ext instead of submit!
- Fixing the bug:

```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);
    input logic      clk, rst, submit_ext;
    input logic [3:0] guess_ext;
    output logic     psychic;

    logic [3:0] pattern, guess;
    logic correct, next, submit;
    assign next = submit;
    genPatt     pat (.clk, .rst, .pattern, .next);
    userIn      inp (.clk, .rst,
                    .guess_ext, .submit_ext, .guess, .submit);
    checkGuess  chk (.pattern, .guess, .correct);
    countRight cnt (.clk, .rst, .correct, .submit, .psychic);
endmodule // psychic_tester
```

That's all!
Thanks for coming!