

# Intro to Digital Design

## Karnaugh Maps

**Instructor:** Justin Hsia

**Teaching Assistants:**

Caitlyn Rawlings

Donovan Clay


Emilio Alcantara

Joy Jung

Naoto Uemura
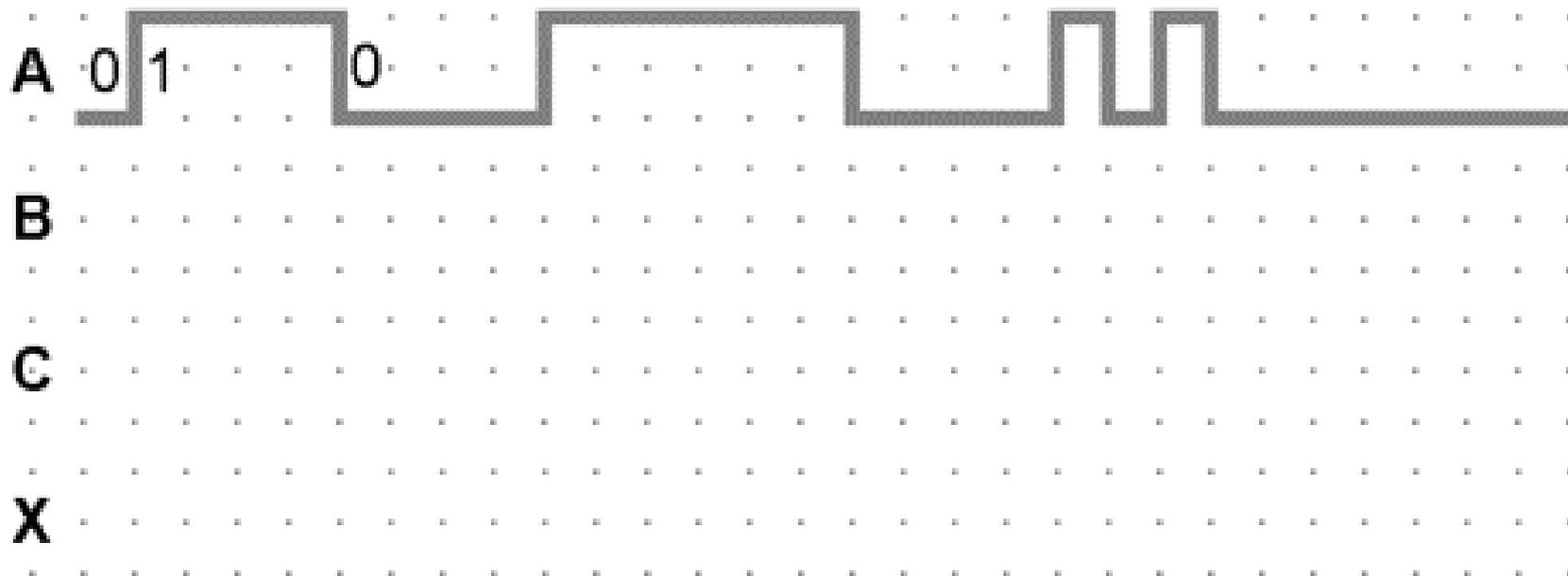
# Question:

- ❖ Let the CL delays be 1 tick (NOT) and 3 ticks (AND, OR). How many ticks is the signal X high?



# Relevant Course Information

- ❖ Lab 1 & 2 Demos due during your assigned demo slots
  - Don't forget to submit your lab materials *before* Wednesday at 2:30 pm, regardless of your demo time
- ❖ Lab 3 – Logic simplification in Verilog
  - Get practice with K-maps
  - Full credit for minimal logic

# Lecture Outline

- ❖ **Karnaugh Maps (K-maps)**
- ❖ Design Examples

# On and Off Sets

❖ *On Set* is the set of input patterns where the function is TRUE

- Here on set =  $\{\bar{A}\bar{B}C, \bar{A}BC, A\bar{B}\bar{C}, A\bar{B}C\}$

❖ *Off Set* is the set of input patterns where the function is FALSE

- Here off set =  $\{\bar{A}\bar{B}\bar{C}, \bar{A}B\bar{C}, A\bar{B}\bar{C}, ABC\}$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

❖ **Recall:** Use the On Set for *Sum of Products* (SoP) and the Off Set for *Product of Sums* (PoS)

- Considered **two-level** Boolean expressions

# Two-Level Simplification

- ❖ Using Sum of Products, “neighboring” input combinations simplify
  - “Neighboring”: inputs that differ by a single signal
  - *The Uniting Theorem*:  $A(\bar{B} + B) = A$
  - *e.g.*,  $AB + \bar{A}B = B$ ,  $\bar{A}BC + \bar{A}B\bar{C} = \bar{A}B$
- ❖ **Goal**: Find neighboring subsets of the On Set to eliminate variables and simplify the expression
- ❖ **Idea**: Let’s write out our Truth Table such that the neighbors become apparent!
  - Need a Karnaugh map for *EACH* output


# Karnaugh Maps

- ❖ A **K-map** is a method of representing a truth table that helps visualize adjacencies in  $\leq 4$  dimensions
  - For more dimensions, computer-based methods are needed
- 1) Split inputs into 2 *evenly-sized* groups
  - One group will have an extra if an odd # of inputs
- 2) Write out all combinations of each group on each axis
 


Group of  $n$  inputs  $\rightarrow 2^n$  combinations

  - **Successive combinations change only 1 input (Gray code)**

**2 Inputs:**

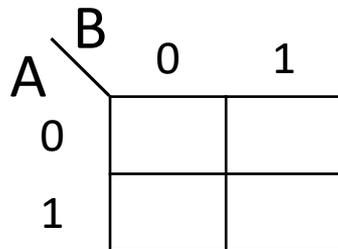

**3 Inputs:**

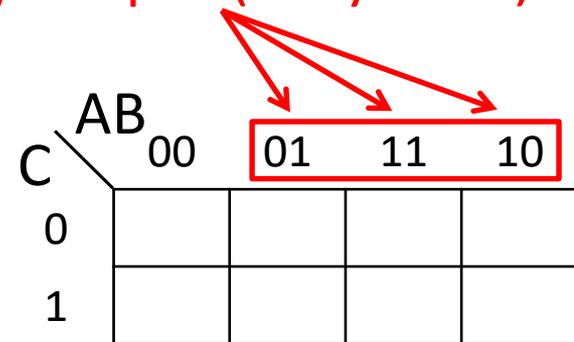


# Karnaugh Maps

- ❖ Also see visualization with brackets for “asserted” simplifications:

## 4 Inputs:

CD \ AB	00	01	11	10
00				
01				
11				
10				

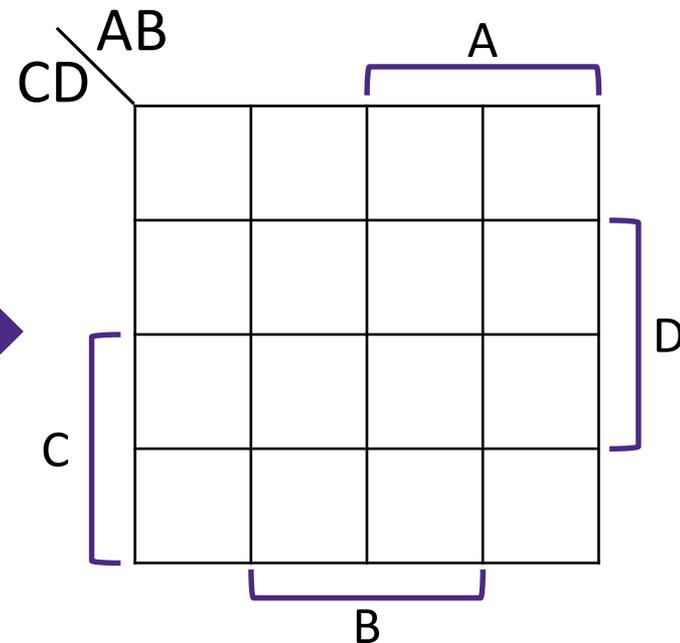

# K-map Example: Majority Circuit

- ❖ Filling in a Karnaugh map:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		AB			
		00	01	11	10
C	0				
	1				

- ❖ Each row of truth table corresponds to ONE cell of Karnaugh map
- ❖ Note the jump when you go from input 011 to 100  
(*most mistakes made here*)

# K-map Example: Majority Circuit

- ❖ Filling in alternate Karnaugh map:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		BC			
		00	01	11	10
A	0				
	1				

- ❖ Each row of truth table corresponds to ONE cell of Karnaugh map
- ❖ Note the jump when you go from input 001 to 010 and 101 to 110 (*most mistakes made here*)


# K-map Simplification

- ❖ Group neighboring 1's so all are accounted for:
  - Each group of neighbors becomes a product term in output

- ❖  $F = BC + AB + AC$

- ❖ Larger groups become smaller terms

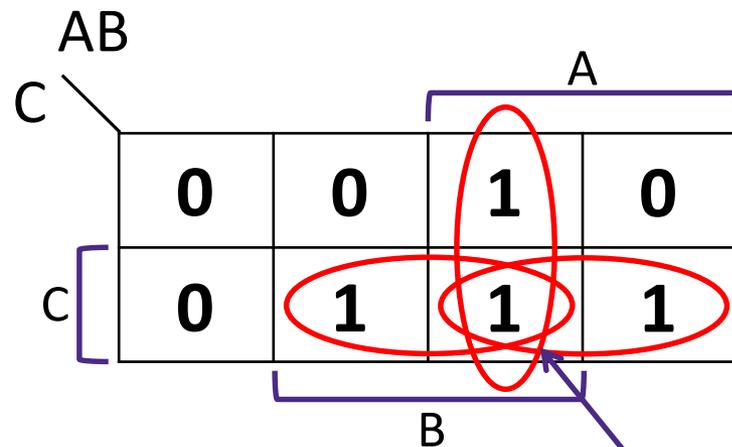- The single 1 in top row  $\rightarrow ABC\bar{C}$
- Vertical group of two 1's  $\rightarrow AB$
- If entire lower row was 1's  $\rightarrow C$



Single cell can be part of many groups

# General K-map Rules


- ❖ Only group in powers of 2
  - Grouping should be of size  $2^i \times 2^j$
  - Applies for both directions
- ❖ Wraps around in all directions
  - “Corners” case is extreme example
- ❖ Always choose largest groupings possible
  - Avoid single cells whenever possible
- ❖  $F = BD + \overline{B}\overline{D} + ACD$

		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	0	1	1	0
	11	0	1	1	1
	10	1	0	0	1

- 1) NOT a valid group
- 2) IS a valid group
- 3) IS a valid group
- 4) “Corners” case
- 5) 1 of 2 good choices here
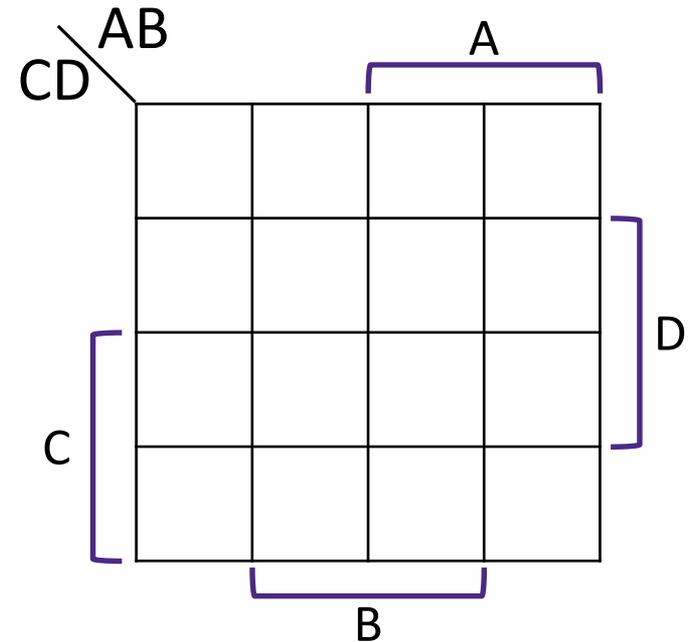
# K-Map Example

$$\diamond F = \bar{A}D + BD + \bar{B}C + A\bar{B}D$$




# Lecture Outline

- ❖ Karnaugh Maps (K-maps)
- ❖ **Design Examples**




# Design Example: 2-bit Adder

❖ Block Diagram and Truth Table:

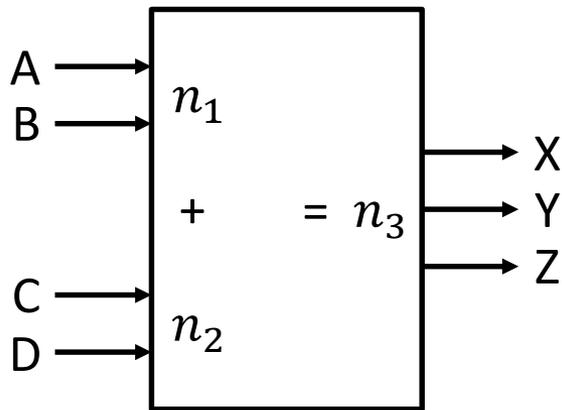

A	B	C	D	X	Y	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

# Design Example: 2-bit Adder

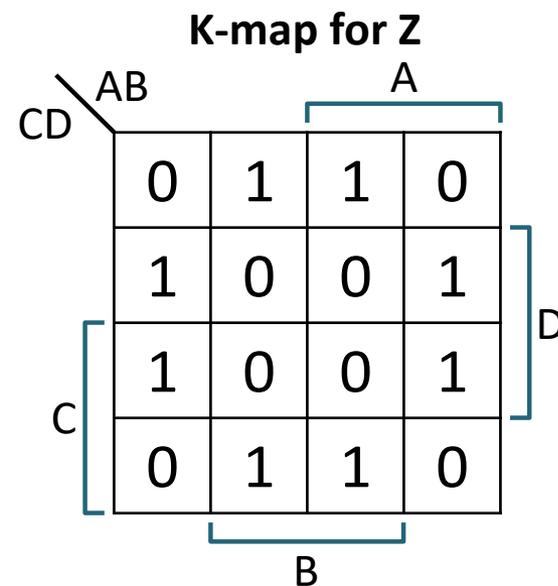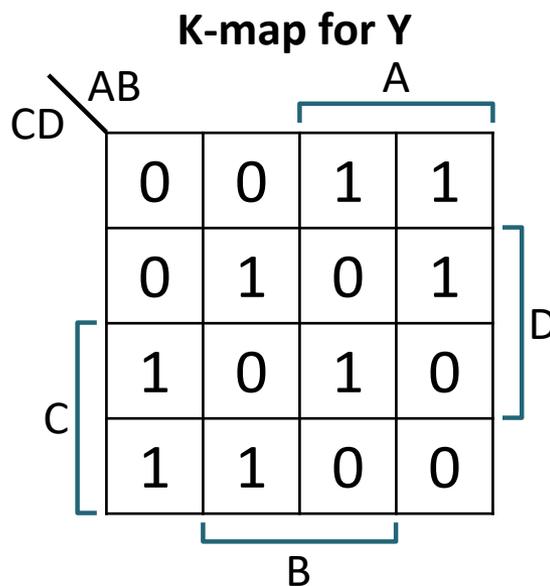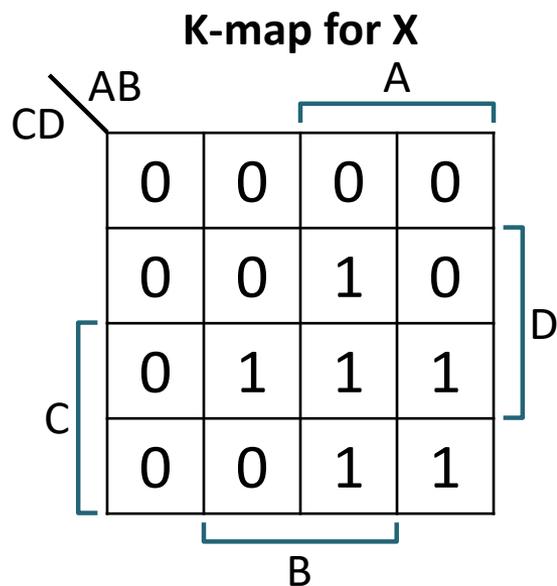

X =

Y =

Z =

# Technology Break

# Don't Cares

- ❖ Use symbol 'X' to mean it can be either a 0 or 1
  - Make choice to simplify final expression

	AB		A		
CD	0	0	X	0	
	1	1	X	1	D
	1	1	0	0	
C	0	X	0	0	
	B				

Let all X = 0:

F =

	AB		A		
CD	0	0	X	0	
	1	1	X	1	D
	1	1	0	0	
C	0	X	0	0	
	B				

Let all X = 1:

F =

	AB		A		
CD	0	0	X	0	
	1	1	X	1	D
	1	1	0	0	
C	0	X	0	0	
	B				


Choose wisely:

F =

# Design Example: Rock-Paper-Scissors


- ❖ Rock (00), Paper (01), Scissors (10) for two players P0 and P1
- ❖ **Output:** Win = Winner's ID (0/1)  
Tie = 1 if Tie, 0 else

P1		P0		Win	Tie
A	B	C	D		
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

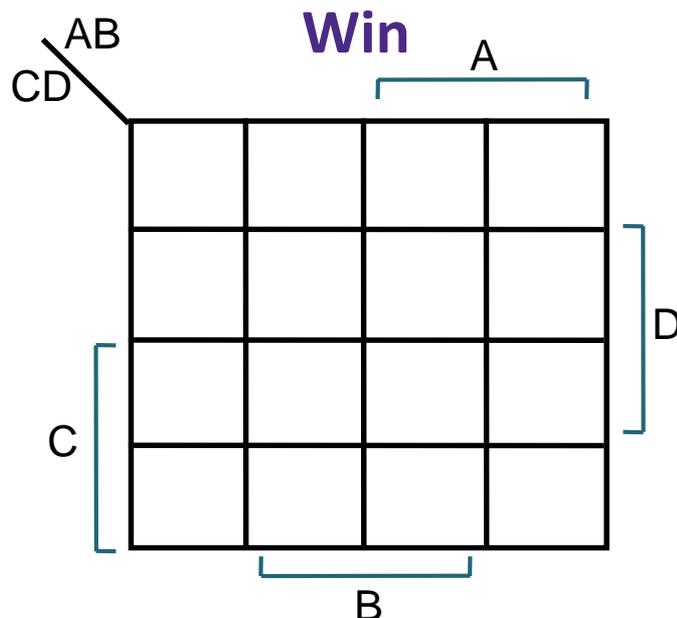


# Case Study: Seven-Segment Display

- ❖ Chip to drive digital display

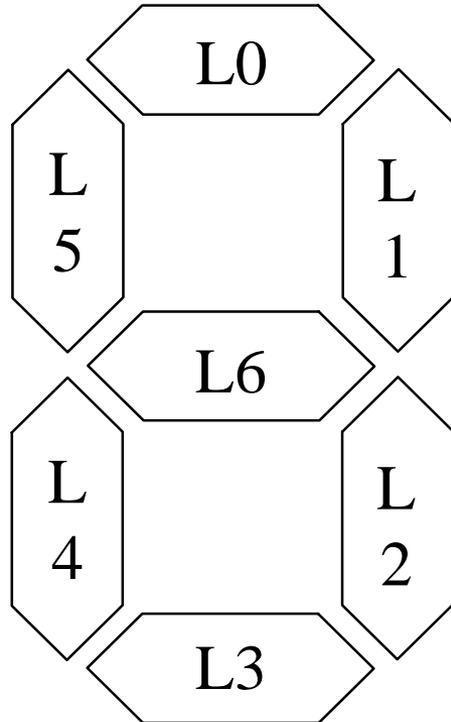


B3	B2	B1	B0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0

# Case Study: Seven-Segment Display

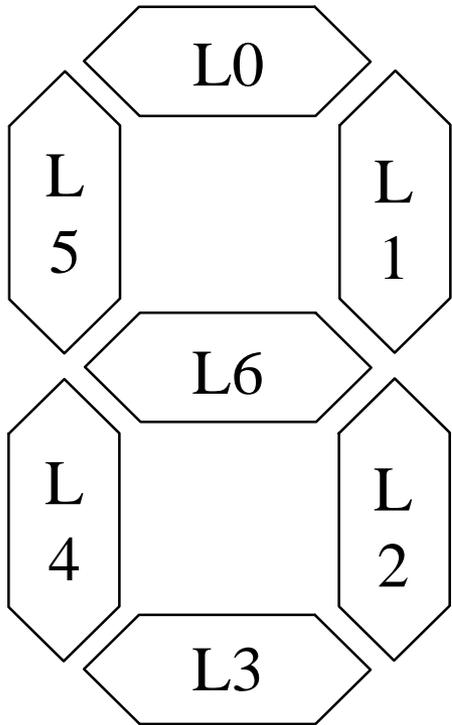


B3	B2	B1	B0	Val	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	0	1	1	0	0	0	0
0	0	1	0	2	1	1	0	1	1	0	1
0	0	1	1	3	1	1	1	1	0	0	1
0	1	0	0	4	0	1	1	0	0	1	1
0	1	0	1	5	1	0	1	1	0	1	1
0	1	1	0	6	1	0	1	1	1	1	1
0	1	1	1	7	1	1	1	0	0	0	0
1	0	0	0	8	1	1	1	1	1	1	1
1	0	0	1	9	1	1	1	1	0	1	1

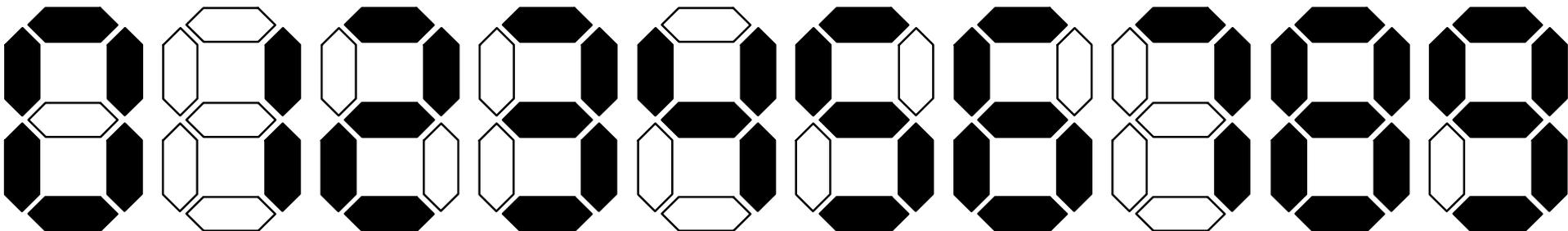

# Case Study: Seven-Segment Display

## ❖ Implement L5:

B3	B2	B1	B0	L5
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1

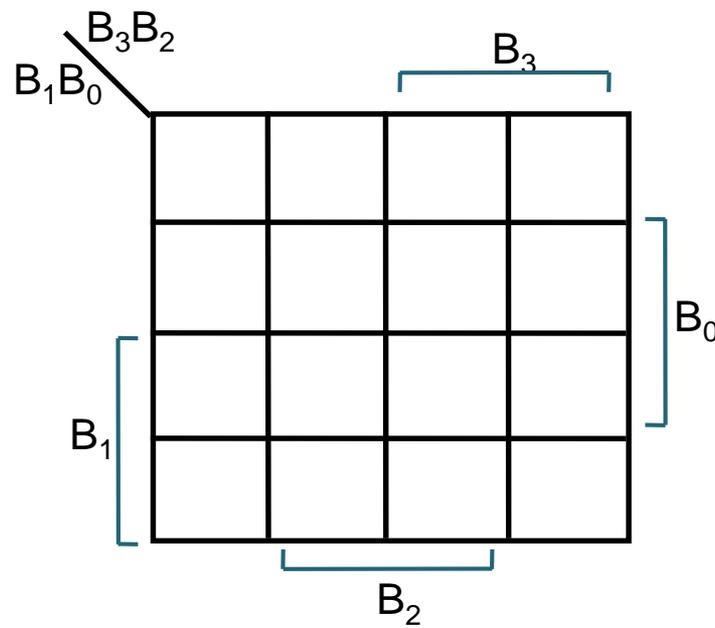

# 7-Seg Display in Verilog

```
module seg7 (bcd, leds);
  input logic [3:0] bcd;
  output logic [6:0] leds;

  always_comb
    case (bcd)
      // 3210           6543210
      4'b0000: leds = 7'b0111111;
      4'b0001: leds = 7'b0000110;
      4'b0010: leds = 7'b1011011;
      4'b0011: leds = 7'b1001111;
      4'b0100: leds = 7'b1100110;
      4'b0101: leds = 7'b1101101;
      4'b0110: leds = 7'b1111101;
      4'b0111: leds = 7'b0000111;
      4'b1000: leds = 7'b1111111;
      4'b1001: leds = 7'b1101111;
      default: leds = 7'bX;
    endcase
endmodule
```

# Procedural Blocks

- ❖ **assign**: continuous assignment
  - Used with wires
  - *e.g.*, **assign**  $F = \sim((A \ \& \ B) \ | \ (C \ \& \ D));$
- ❖ **initial**: executes once at time zero
  - Set initial values (**generally simulation only!!!**)
  - Define testbench waveforms (and monitor)
  - *e.g.*, **initial begin**


```
        for(i = 0; i < 8; i = i+1)
            {SEL, I, J} = i;    #10;
    end
```

# Procedural Blocks

- ❖ **always**: loop to execute over and over again
  - Block gets triggered by a *sensitivity list*
  - Any object that is assigned a value in an **always** statement must be declared as a variable (**reg/logic**).
  - Examples:
    - **always** @ (a or b or c) ↔ **always** @ (a, b, c)
    - **always** @ (\*) implicitly contains all read signals within the block
  
- ❖ **always\_comb**: special SystemVerilog for CL
  - Similar to **always** @(\*), but generally more robust
  - *Only for use with combinational logic!!!*
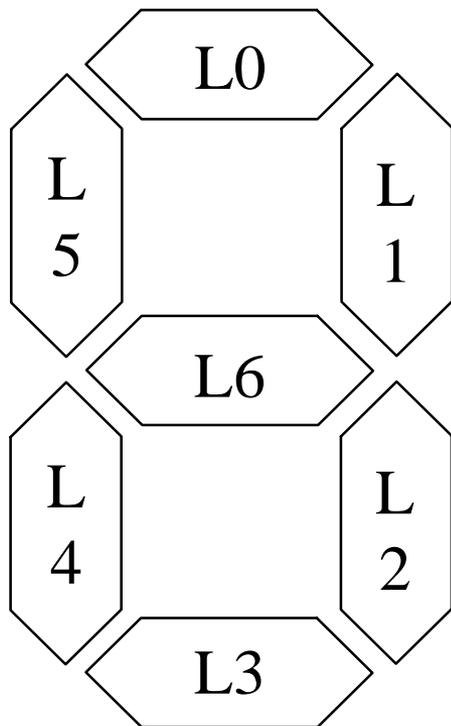
# Verilog: Extend 7-Seg to Hex

- ❖ Show “A” on 0b1010 (ten) to “F” on 0b1111 (fifteen)



```
module seg7 (bcd, leds);  
  input logic [3:0] bcd;  
  output logic [6:0] leds;  
  
  always_comb  
    case (bcd)  
      // 3210           6543210  
      4'b0000: leds = 7'b0111111;  
      4'b0001: leds = 7'b0000110;  
      4'b0010: leds = 7'b1011011;  
      4'b0011: leds = 7'b1001111;  
      4'b0100: leds = 7'b1100110;  
      4'b0101: leds = 7'b1101101;  
      4'b0110: leds = 7'b1111101;  
      4'b0111: leds = 7'b0000111;  
      4'b1000: leds = 7'b1111111;  
      4'b1001: leds = 7'b1101111;  
      default: leds = 7'bX;  
    endcase  
endmodule
```

# Circuit Implementation Techniques

- ❖ **Truth Tables** – “Black box” circuit description
- ❖ **Boolean Algebra** – Math form for optimization
  - *K-Maps* – Alternate simplification technique
- ❖ **Circuit Diagrams** – TTL Implementations
- ❖ **Verilog** – Simulation & mapping to FPGAs