

Intro to Digital Design

Karnaugh Maps

Instructor: Justin Hsia

Teaching Assistants:

Caitlyn Rawlings

Donovan Clay


Emilio Alcantara

Joy Jung

Naoto Uemura

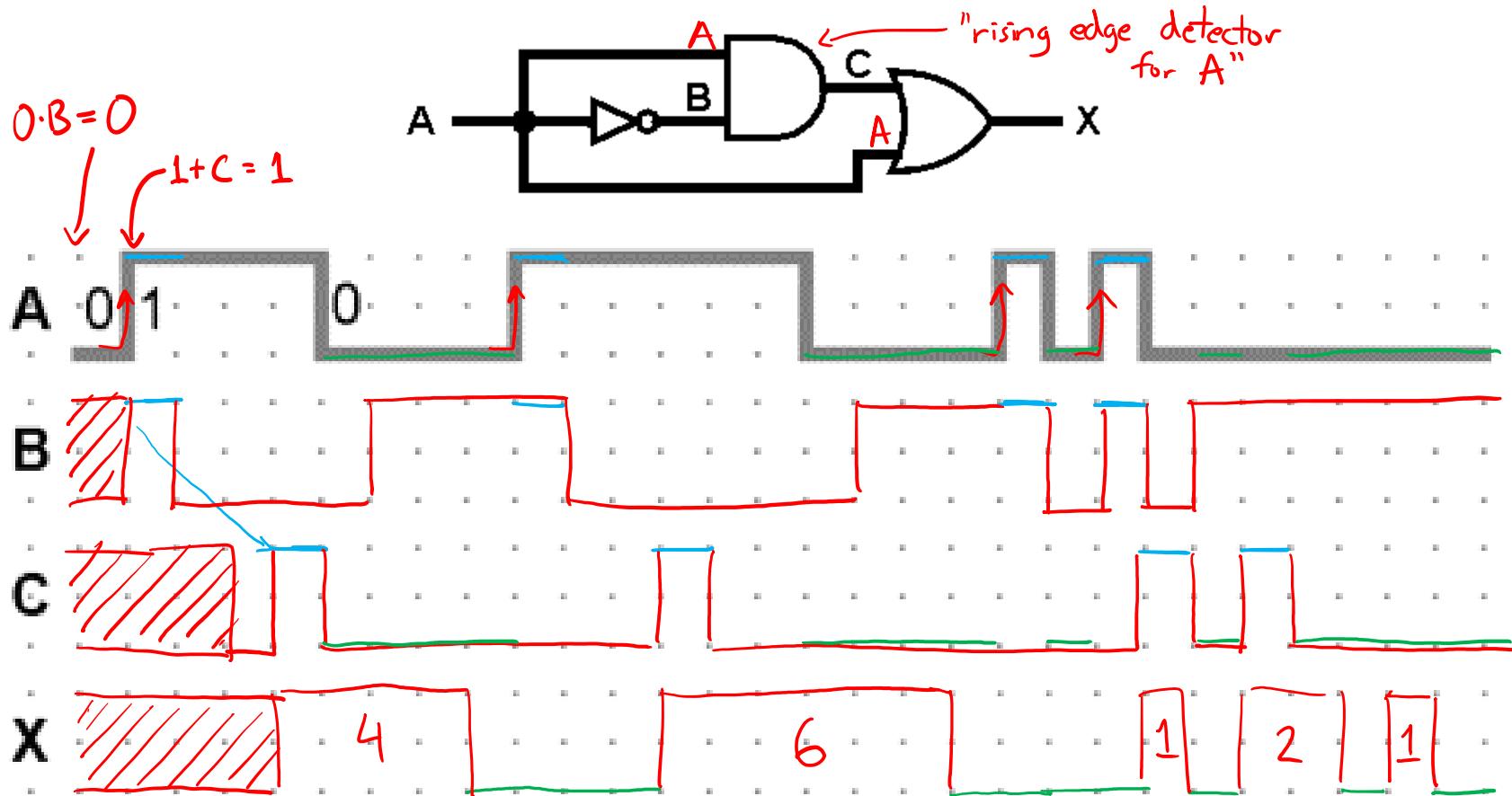Question:

- Let the CL delays be 1 tick (NOT) and 3 ticks (AND, OR). How many ticks is the signal X high? 14 ticks



Relevant Course Information

- ❖ Lab 1 & 2 Demos due during your assigned demo slots
 - Don't forget to submit your lab materials *before* Wednesday at 2:30 pm, regardless of your demo time
- ❖ Lab 3 – Logic simplification in Verilog
 - Get practice with K-maps
 - Full credit for minimal logic

Lecture Outline

- ❖ Karnaugh Maps (K-maps)
- ❖ Design Examples

On and Off Sets

- ❖ *On Set* is the set of input patterns where the function is TRUE

- Here on set = $\{\bar{A}\bar{B}C, \bar{A}BC, A\bar{B}\bar{C}, AB\bar{C}\}$

- ❖ *Off Set* is the set of input patterns where the function is FALSE

- Here off set = $\{\bar{A}\bar{B}\bar{C}, \bar{A}B\bar{C}, A\bar{B}\bar{C}, ABC\}$

- ❖ **Recall:** Use the On Set for *Sum of Products* (SoP) and the Off Set for *Product of Sums* (PoS)
 - Considered **two-level** Boolean expressions

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Two-Level Simplification

- ❖ Using Sum of Products, “neighboring” input combinations simplify
 - “Neighboring”: inputs that differ by a single signal
 - *The Uniting Theorem*: $A(\bar{B} + B) = A$
 - e.g., $AB + \bar{A}B = B$, $\bar{A}BC + \bar{A}B\bar{C} = \bar{A}B$
- ❖ **Goal:** Find neighboring subsets of the On Set to eliminate variables and simplify the expression
- ❖ **Idea:** Let’s write out our Truth Table such that the neighbors become apparent!
 - Need a Karnaugh map for *EACH* output

Karnaugh Maps


- ❖ A **K-map** is a method of representing a truth table that helps visualize adjacencies in ≤ 4 dimensions
 - For more dimensions, computer-based methods are needed

- 1) Split inputs into 2 *evenly-sized* groups
 - One group will have an extra if an odd # of inputs
- 2) Write out all combinations of each group on each axis


Group of n inputs $\rightarrow 2^n$ combinations

- Successive combinations change only 1 input (Gray code)
including wrap-around!

2 Inputs:

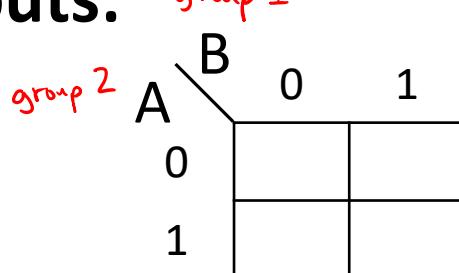

3 Inputs:

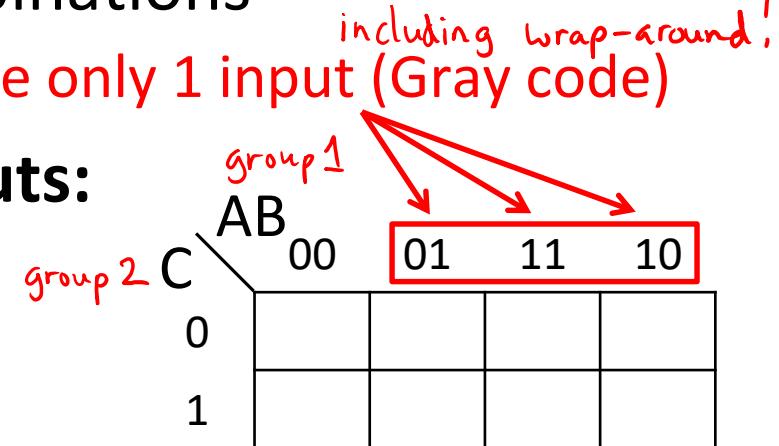


Karnaugh Maps

- Also see visualization with brackets for “asserted” simplifications:

4 Inputs:

CD \ AB	00	01	11	10
00	$\bar{A}\bar{B}\bar{C}\bar{D}$			
01			$A\bar{B}C\bar{D}$	
11				
10				

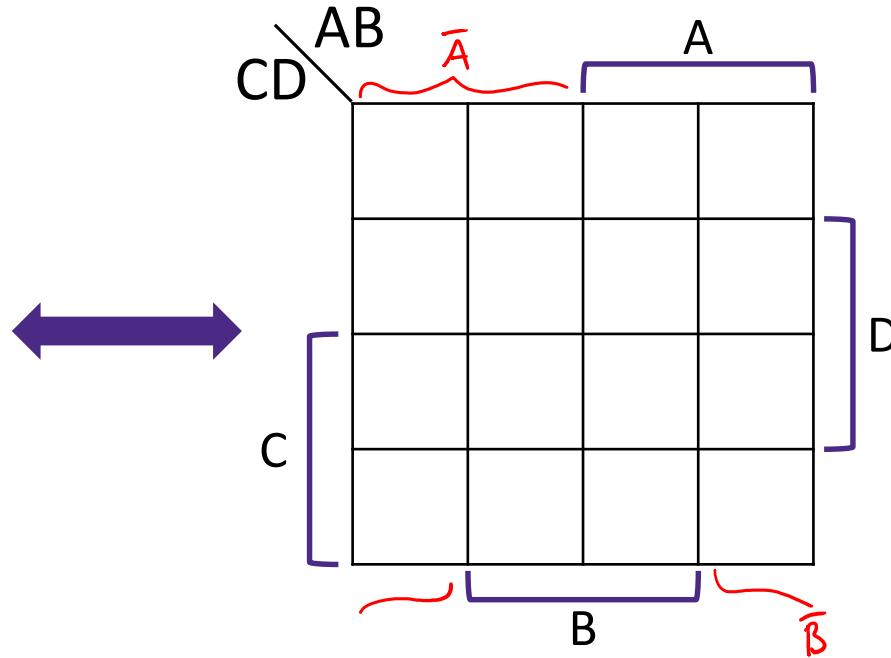each cell corresponds to a different input combination



K-map Example: Majority Circuit

- ❖ Filling in a Karnaugh map:

group 1

A	B	C	F	#	AB	00	01	11	10
0	0	0	0	6	0	0	0	1	0
0	0	1	0	1	0	0	0	1	0
0	1	0	0	2	1	0	0	1	0
0	1	1	1	3	1	0	1	1	1
1	0	0	0	4		1	1	1	1
1	0	1	1	5		1	1	1	1
1	1	0	1	6		1	1	1	1
1	1	1	1	7		1	1	1	1

- ❖ Each row of truth table corresponds to ONE cell of Karnaugh map
- ❖ Note the jump when you go from input 011 to 100
(most mistakes made here)

K-map Example: Majority Circuit

- ❖ Filling in alternate Karnaugh map:

			F	#	BC		A			
A	B	C			00	01	11	10		
0	0	0	0	0	0	1	1	2		
0	0	1	0	0	0	0	1	3		
0	1	0	0	2	0	0	0	4		
0	1	1	1	3	0	0	1	5		
1	0	0	0	4	0	0	1	6		
1	0	1	1	5	0	1	1	7		
1	1	0	1	6	1	1	1	7		
1	1	1	1	7	1	1	1	6		


- ❖ Each row of truth table corresponds to ONE cell of Karnaugh map
- ❖ Note the jump when you go from input 001 to 010 and 101 to 110 (*most mistakes made here*)

K-map Simplification

- ❖ Group neighboring 1's so all are accounted for:
 - Each group of neighbors becomes a product term in output
- ❖ $F = BC + AB + AC$


❖ Larger groups become smaller terms

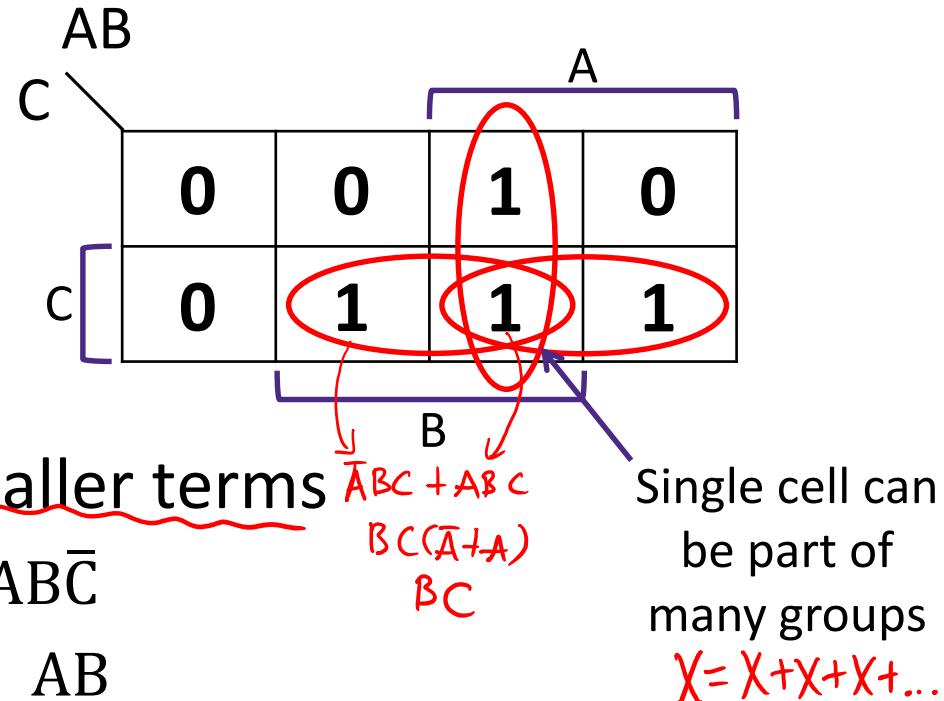- The single 1 in top row $\rightarrow AB\bar{C}$
- Vertical group of two 1's $\rightarrow AB$
- If entire lower row was 1's $\rightarrow C$



General K-map Rules

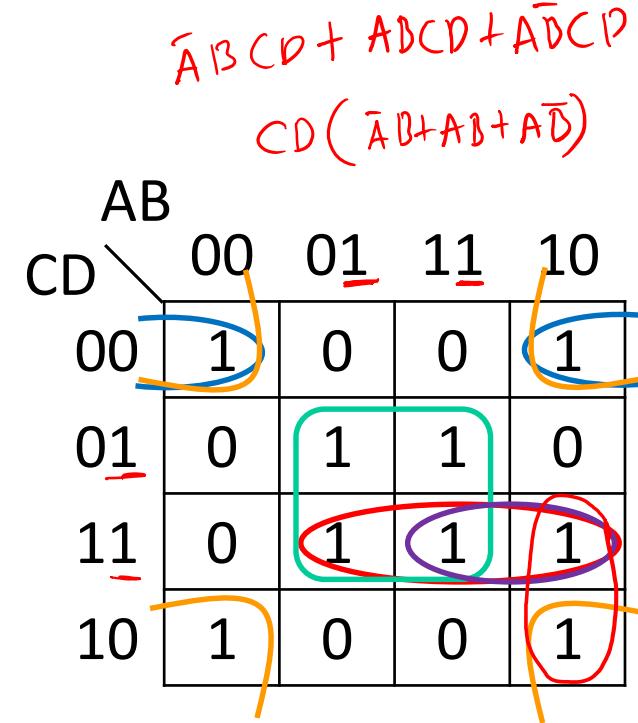- ❖ Only group in powers of 2
 - Grouping should be of size $2^i \times 2^j$
 - Applies for both directions
- ❖ Wraps around in all directions
 - “Corners” case is extreme example
- ❖ Always choose largest groupings possible
 - Avoid single cells whenever possible
- ❖ $F = BD + \overline{BD} (+ ACD)$
 $\quad\quad\quad (+ A\bar{B}C)$




- 1) NOT a valid group
- 2) IS a valid group
- 3) IS a valid group
- 4) “Corners” case
- 5) 1 of 2 good choices here

K-Map Example

$$\diamond F = \cancel{\underline{AD}} + \cancel{\underline{BD}} + \cancel{\underline{BC}} + \cancel{\underline{ABD}}$$

$$F = D + \bar{B}C$$

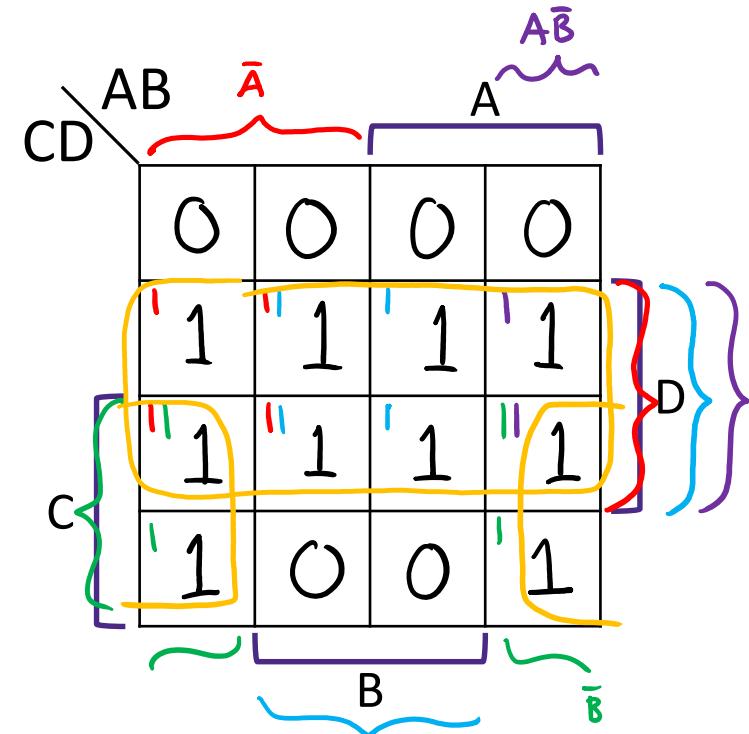


Lecture Outline

- ❖ Karnaugh Maps (K-maps)
- ❖ Design Examples




Design Example: 2-bit Adder

- ❖ Block Diagram and Truth Table:

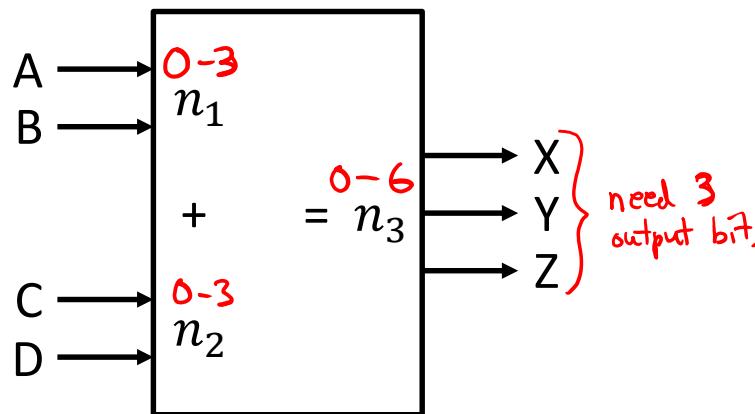

				MSB			LSB	
A	B	C	D	X	Y	Z		
0	0	0	0	0	0	0		
0	0	0	1	0	0	1		
0	0	1	0	0	1	0		
0	0	1	1	0	1	1		
				0	1	0	1	1
0	1	0	0	0	0	1		
0	1	0	1	0	1	0		
0	1	1	0	0	1	1		
0	1	1	1	1	0	0		
				1	0	0	1	0
1	0	0	0	0	1	0		
1	0	0	1	0	1	1		
1	0	1	0	1	0	0		
1	0	1	1	1	0	1		
				1	1	0	1	1
1	1	0	1	1	0	0		
1	1	1	0	1	0	1		
1	1	1	1	1	1	0		

Design Example: 2-bit Adder

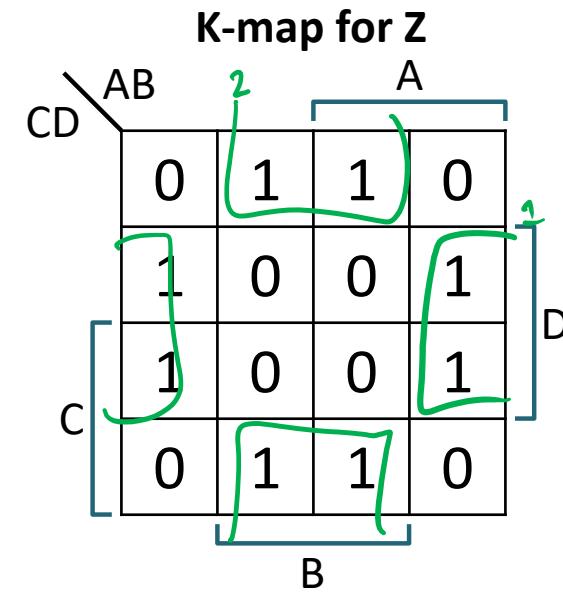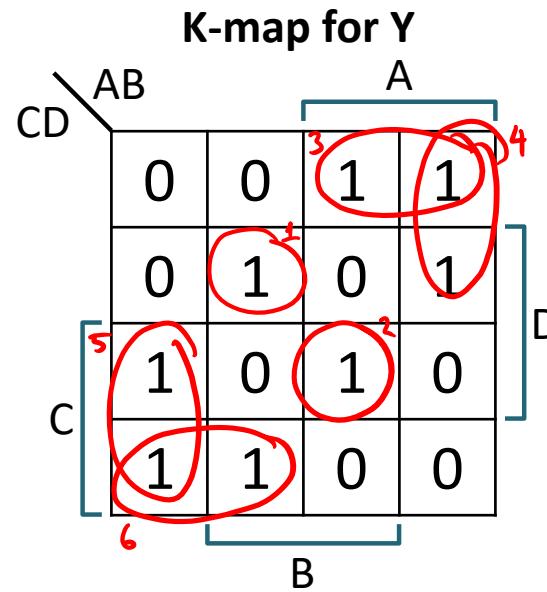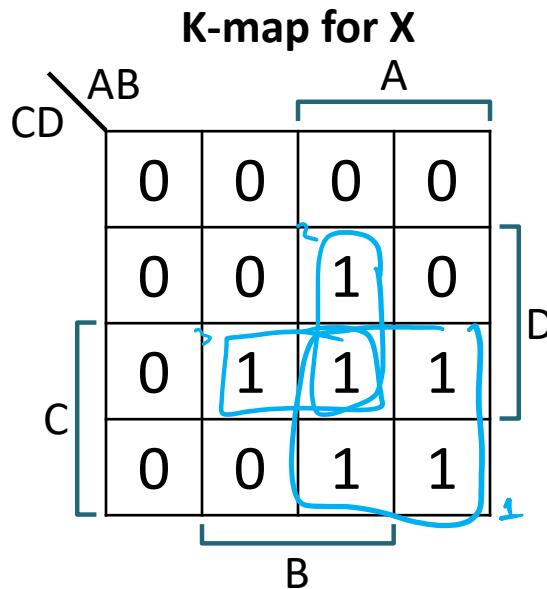

$$X = \underbrace{AC}_{1} + \underbrace{ABD}_{2} + \underbrace{BCD}_{3}$$

$$Y = \underbrace{\bar{A}B\bar{C}D}_{1} + \underbrace{ABC\bar{D}}_{2} + \underbrace{A\bar{C}\bar{D}}_{3} + \underbrace{\bar{A}\bar{B}\bar{C}}_{4} + \underbrace{\bar{A}\bar{B}C}_{5} + \underbrace{\bar{A}C\bar{D}}_{6}$$

$$Z = \underbrace{\bar{B}D}_{1} + \underbrace{B\bar{D}}_{2} = B \oplus D$$

Technology Break

Don't Cares

- ❖ Use symbol 'X' to mean it can be either a 0 or 1
 - Make choice to simplify final expression

	AB	A	
CD	0 0	X	0
C	1 1	X	1
B	1 1	0	0
	0 X 0 0		D

Let all X = 0:

$$F = \bar{A}D + \bar{B}\bar{C}D$$

	AB	A	
CD	0 0	X	0
C	1 1	X	1
B	1 1	0	0
	0 X 0 0		D

Let all X = 1:

$$F = \bar{A}D + \bar{C}D + AB\bar{C} + \bar{A}BC$$

	AB	A	
CD	0 0	X	0
C	1 1	X	1
B	1 1	0	0
	0 X 0 0		D


Choose wisely:

$$F = \bar{A}D + \bar{C}D$$

Design Example: Rock-Paper-Scissors

should never see 11 input, so outputs are don't cares!

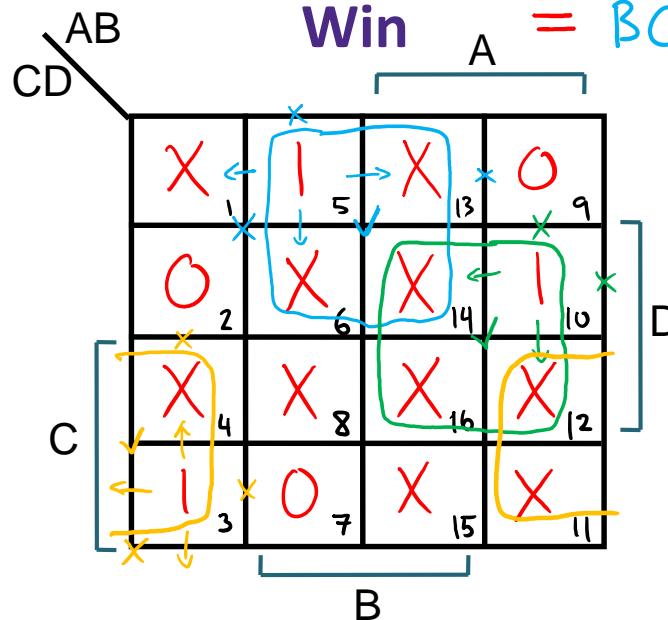
- ❖ Rock (00), Paper (01), Scissors (10)
for two players P0 and P1
- ❖ Output: Win = Winner's ID (0/1)
Tie = 1 if Tie, 0 else



	P1		P0		Win	Tie
	A	B	C	D		
Rock	0	0	0	R	0	X
	0	0	0	P	1	O
	0	0	1	S	0	I
	0	0	1	?	1	X
Paper	0	1	0	R	0	I
	0	1	0	P	1	X
	0	1	1	S	0	O
	0	1	1	?	1	X
Scissors	1	0	0	R	0	O
	1	0	0	P	1	G
	1	0	1	S	0	X
	1	0	1	?	1	X
??	1	1	0	0	0	X
	1	1	0	1	1	X
	1	1	1	0	0	X
	1	1	1	1	1	X

Case Study: Seven-Segment Display

- ❖ Chip to drive digital display

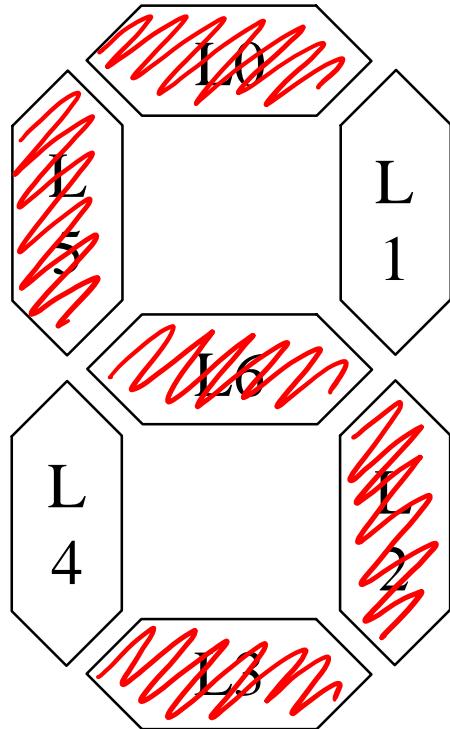


"binary-coded decimal" (BCD)


	B3	B2	B1	B0	#
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	2
3	0	0	1	1	3
4	0	1	0	0	4
5	0	1	0	1	5
6	0	1	1	0	6



Case Study: Seven-Segment Display

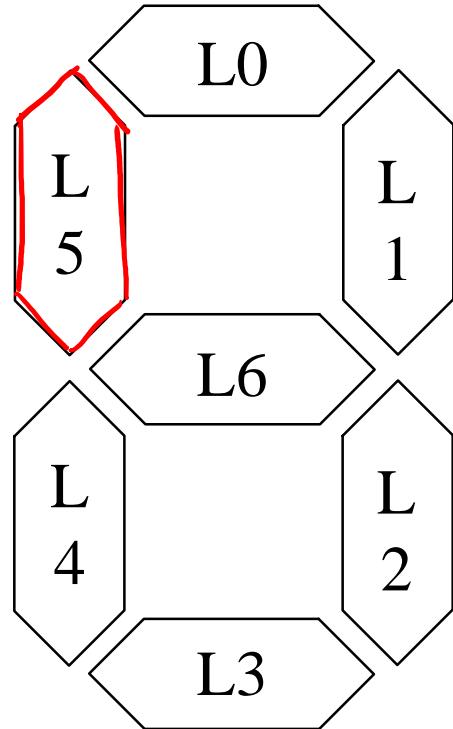


B3	B2	B1	B0	Val	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	0	1	1	0	0	0	0
0	0	1	0	2	1	1	0	1	1	0	1
0	0	1	1	3	1	1	1	1	0	0	1
0	1	0	0	4	0	1	1	0	0	1	1
0	1	0	1	5	1	0	1	1	0	1	1
0	1	1	0	6	1	0	1	1	1	1	1
0	1	1	1	7	1	1	1	0	0	0	0
1	0	0	0	8	1	1	1	1	1	1	1
1	0	0	1	9	1	1	1	1	0	1	1

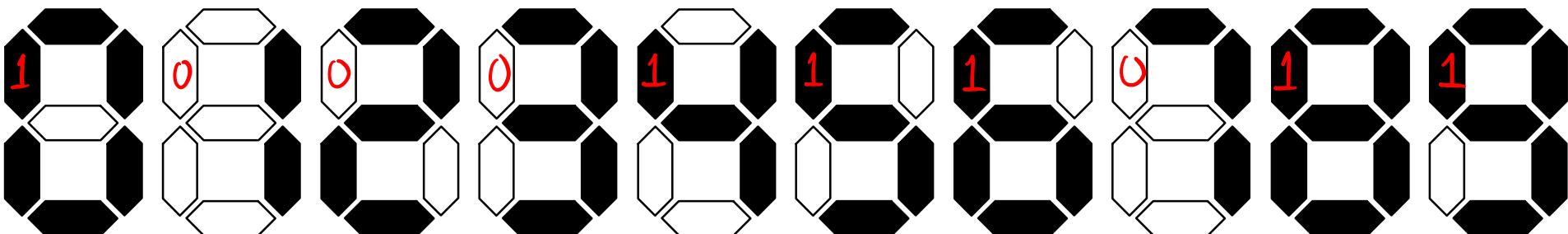

Case Study: Seven-Segment Display

❖ Implement L5:

B3	B2	B1	B0	L5	Cell
0	0	0	0	1	6
0	0	0	1	0	1
0	0	1	0	0	2
0	0	1	1	0	3
0	1	0	0	1	4
0	1	0	1	1	5
0	1	1	0	1	6
0	1	1	1	0	7
1	0	0	0	1	8
1	0	0	1	1	9
					.

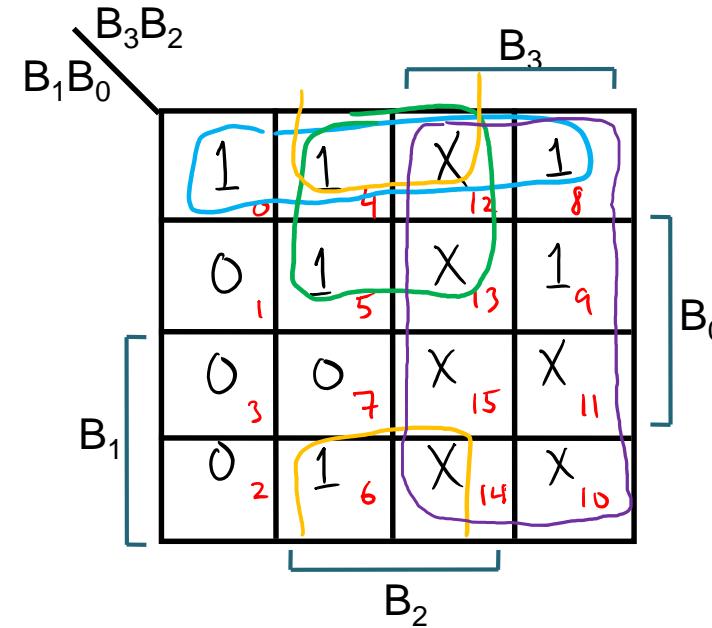

$$L5 = \bar{B}_1 \bar{B}_0 + B_2 \bar{B}_1 + B_2 \bar{B}_0 + B_3$$

7-Seg Display in Verilog

```
module seg7 (bcd, leds);  
    input logic [3:0] bcd;  
    output logic [6:0] leds;
```

this is new

always_comb

case (bcd)

// 3210

4'b0000: leds = 7'b0111111;
4'b0001: leds = 7'b0000110;
4'b0010: leds = 7'b1011011;
4'b0011: leds = 7'b1001111;
4'b0100: leds = 7'b1100110;
4'b0101: leds = 7'b1101101;
4'b0110: leds = 7'b1111101;
4'b0111: leds = 7'b0000111;
4'b1000: leds = 7'b1111111;
4'b1001: leds = 7'b1101111;
default: leds = 7'bX;

endcase

endmodule

bit positions
within bus

binary
constants

6543210

↑ don't care's

block diagram:



no fall-through
(no breaks necessary)
because it is
describing hardware!

Procedural Blocks

- ❖ **assign**: continuous assignment
 - Used with wires
 - e.g., `assign F = ~((A & B) | (C & D));`


- ❖ **initial**: executes once at time zero
 - Set initial values (**generally simulation only!!!**)
 - Define testbench waveforms (and monitor)
 - e.g.,
`initial begin`
 `for(i = 0; i < 8; i = i+1)`
 `{SEL, I, J} = i; #10;`
`end`

Procedural Blocks

- ❖ **always**: loop to execute over and over again
 - Block gets triggered by a sensitivity list
 - Any object that is assigned a value in an **always** statement must be declared as a variable (**reg/logic**).
 - Examples:
 - `always @ (a or b or c) ↔ always @ (a, b, c)`
 - `always @ (*)` implicitly contains all read signals within the block
- ❖ **always_comb**: special SystemVerilog for CL
 - Similar to **always @(*)**, but generally more robust
 - *Only for use with combinational logic!!!*

Verilog: Extend 7-Seg to Hex

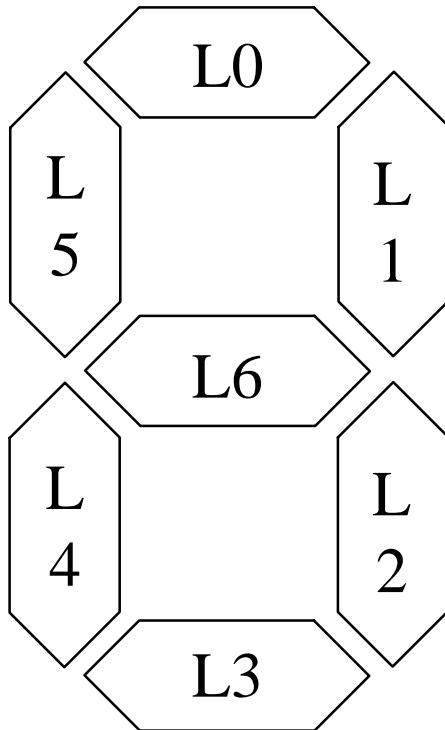- ❖ Show “A” on 0b1010 (ten) to “F” on 0b1111 (fifteen)



```
module seg7 (bcd, leds);
    input logic [3:0] bcd;
    output logic [6:0] leds;

    always_comb
        case (bcd)
            // 3210          6543210
            4'b0000: leds = 7'b0111111;
            4'b0001: leds = 7'b0000110;
            4'b0010: leds = 7'b1011011;
            4'b0011: leds = 7'b1001111;
            4'b0100: leds = 7'b1100110;
            4'b0101: leds = 7'b1101101;
            4'b0110: leds = 7'b1111101;
            4'b0111: leds = 7'b0000111;
            4'b1000: leds = 7'b1111111;
            4'b1001: leds = 7'b1101111;
            default: leds = 7'bX;
        endcase
    endmodule
```

Circuit Implementation Techniques

- ❖ **Truth Tables** – “Black box” circuit description
- ❖ **Boolean Algebra** – Math form for optimization
 - **K-Maps** – Alternate simplification technique
- ❖ **Circuit Diagrams** – TTL Implementations
- ❖ **Verilog** – Simulation & mapping to FPGAs