

# Intro to Digital Design

## Computer Components, FPGAs

**Instructor:** Justin Hsia

**Teaching Assistants:**

Caitlyn Rawlings

Donovan Clay

Emilio Alcantara

Joy Jung

Naoto Uemura

# Relevant Course Information


- ❖ Lab 8 – Project
  - Reports due Friday, March 8 @ 11:59 pm
  - Project check-ins this week during demos
  - Demos can be scheduled outside of the lab hours by making a private Ed Discussion post
- ❖ Lab kit (+ Okiocam) return when you are done
- ❖ **Quiz 3** is next week: Tuesday, May 30 @ 11:40 pm
  - 60 (+10) minutes, worth 14% of your course grade
  - Topics: Timing, Routing Elements, Computational Building Blocks, Verilog
  - Past Quiz 3 (+ solutions) on website: Course Info → Quizzes
    - **Note**: Your Quiz 3 will be a little different – focus on problem solving

# Outline


- ❖ **Computer Components (Cont.)**
  - Register File
  - Datapath teaser
  - Serial Communication
- ❖ FPGAs
- ❖ Course Wrap-up
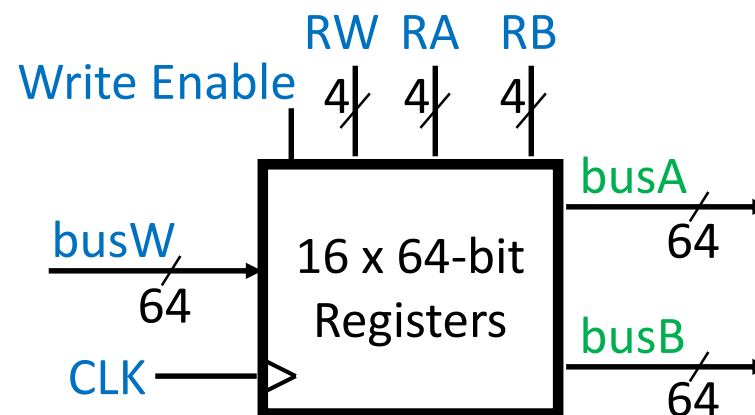
# Storage Element: Register File

- ❖ Contains all programmer-accessible registers
  - Output buses **busA** and **busB**
  - Input bus **busW**
- ❖ Register selection
  - Place data of registers **RA/RB** (numbers) onto **busA/busB**
  - Store data on **busW** into register **RW** (number) when **Write Enable** is 1




# Simple Register File (4 Registers)

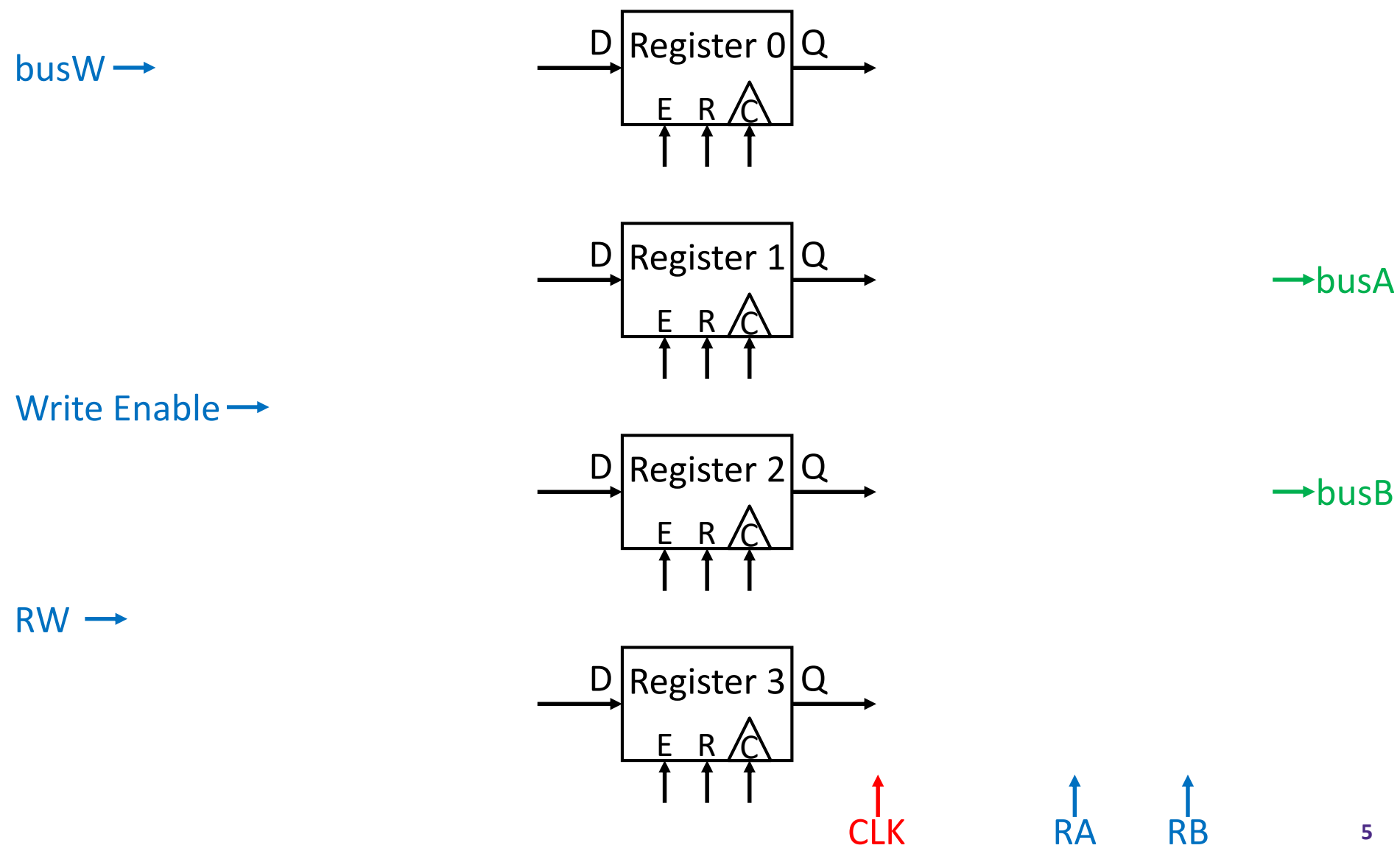

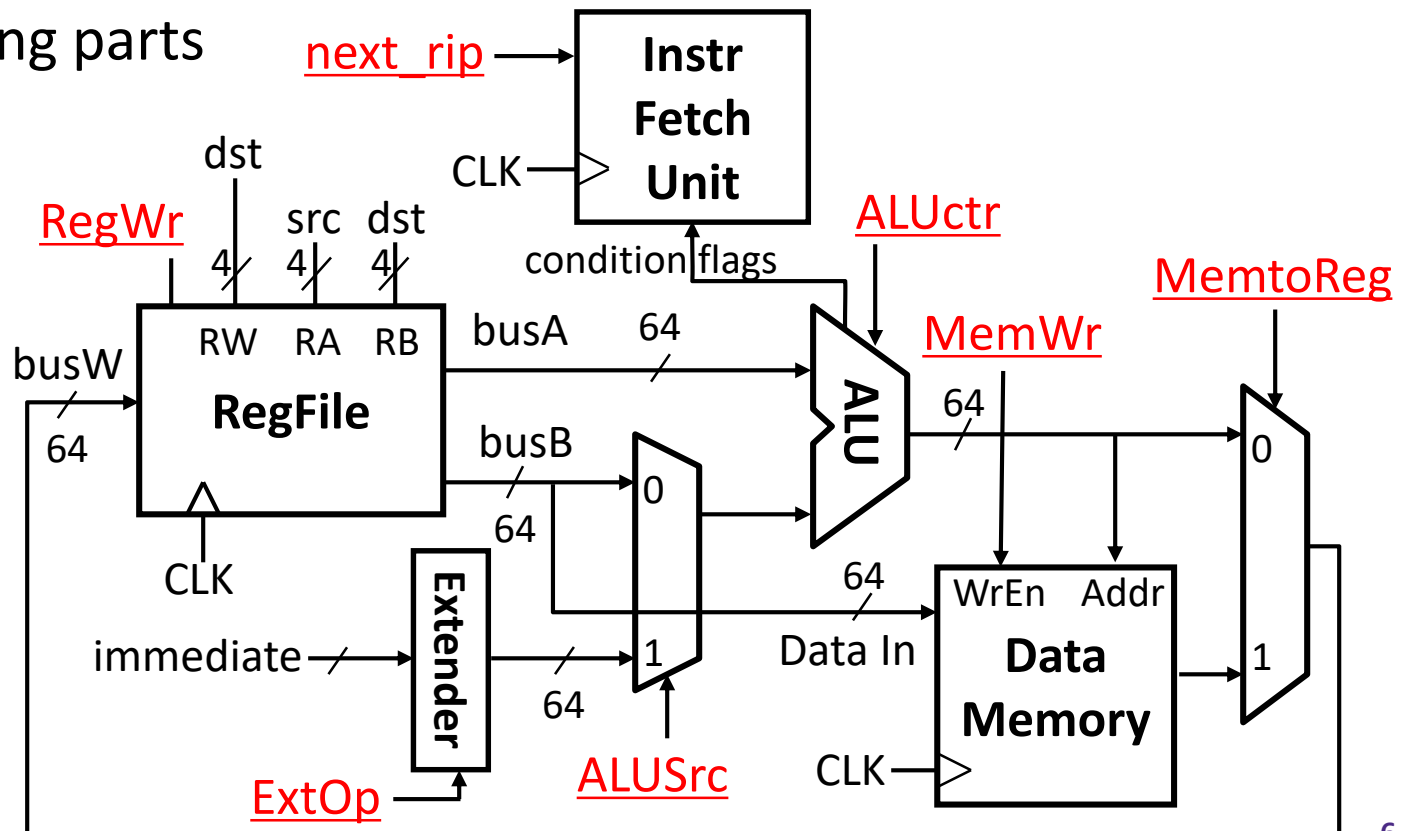
# Datapath Teaser

- ❖ Instructions of the form: `operation src, dst`
  - Signals in **red** are set by Control based on `operation`
  - This is inaccurate/incomplete but gives you a vague idea of connecting parts


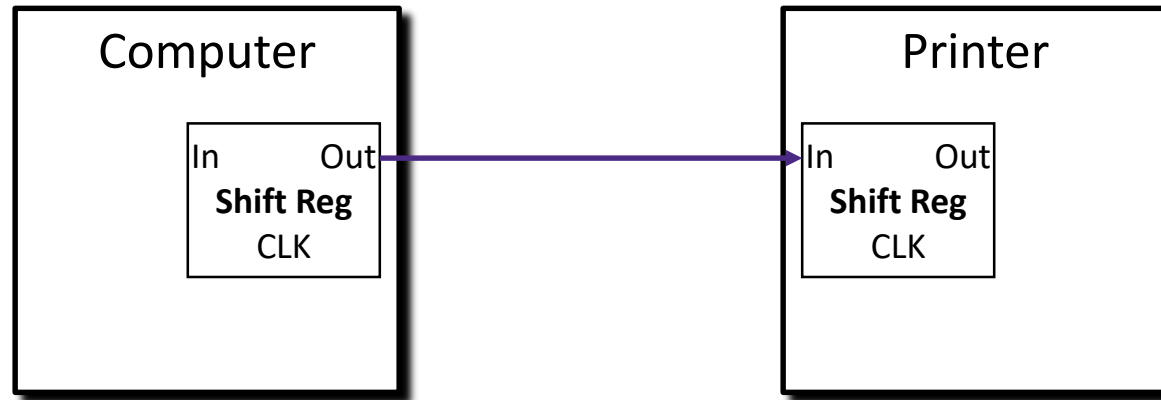
# Transfer of Data

- ❖ Two modes of communication
  - **Parallel:** all bits transferred at the same time
  - **Serial:** one bit transferred at a time
- ❖ Shift registers can be used for serial transfer:







- ❖ In general, shift registers can allow for either or both modes (S for serial, P for parallel) at input and output
  - Examples: SISO, SIPO, PISO

# Shift Register w/Parallel Load


Load	Shift	Action
0	0	Q = old Q
0	1	Shift (left)
1	X	Parallel load

 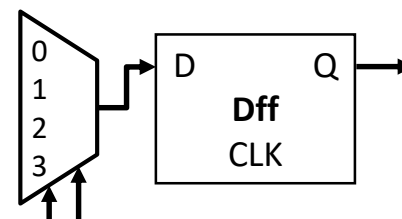  - ❖ **Note:** To avoid extra input, use  $D_0$  input as “shift in”





# Conversion between Parallel & Serial

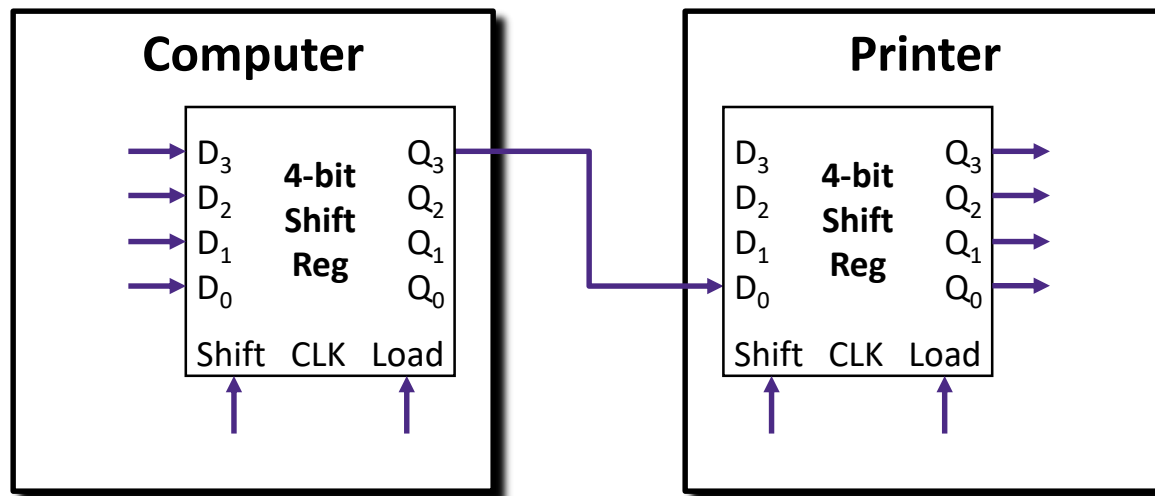

Cycle	Shift	Load	Q0	Q1	Q2	Q3
0			X	X	X	X
1						
2						
3						
4						
5						
6						

Shift	Load	Q0	Q1	Q2	Q3
		X	X	X	X

# Shifter in Verilog

```
module leftshifter #(parameter WIDTH=8)
  (s_out, p_out, shift, load, d_in, clk);


  output logic s_out;           // serial out
  output logic [WIDTH-1:0] p_out; // parallel out
  input logic [WIDTH-1:0] d_in; // data in (shift in d0)
  input logic shift, load, clk;

endmodule
```

# Outline

- ❖ Computer Components (Cont.)
  - Register File
  - Datapath teaser
  - Serial Communication
- ❖ **FPGAs**
- ❖ Course Wrap-up

# Field Programmable Gate Arrays (FPGAs)

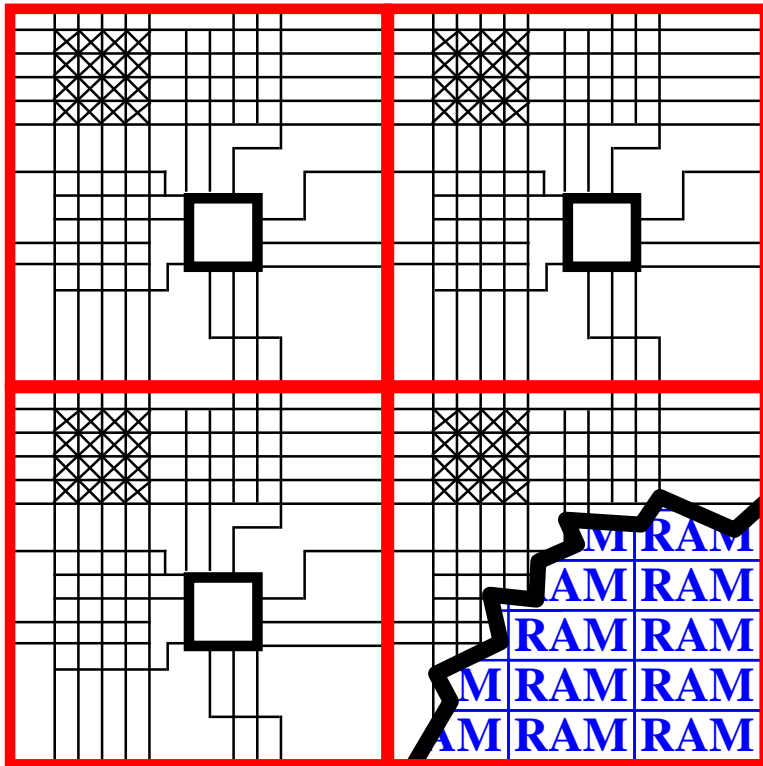

Logic cells imbedded in a general routing structure




Logic cells usually contain:

- 6-input Boolean function calculator
- Flip-flop (1-bit memory)

All features electronically (re)programmable

# Using an FPGA

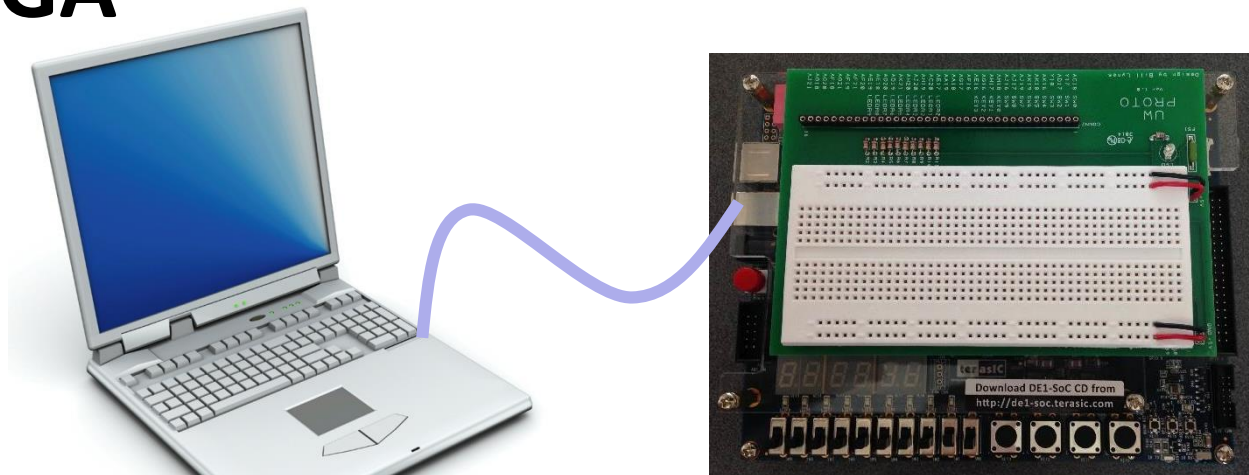

```
// Verilog code for 2-input
multiplexer
module AOI (F, A, B, C, D):
  output F;
  input A, B, C, D;
  assign F = ~((A & B) | (C &
D));
endmodule
module MUX2 (V, SEL, I, J); //
2:1 multiplexer
  output V;
  input SEL, I, J;
  wire SELB, VB;
  not G1 (SELB, SEL);
  AOI G2 (VB, I, SEL, SELB, J);
  not G3 (V, VB);
endmodule
```

Verilog




FPGA  
CAD  
Tools



```
00101010001010010
10010010010011000
10101000101011000
10101001010010101
00010110001001010
10101001111001001
01000010101001010
10010010000101010
10100101010010100
01010110101001010
01010010100101001
```


Bitstream

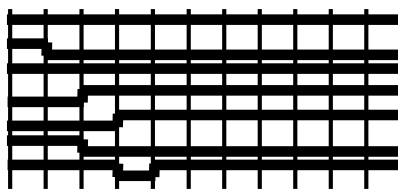

Simulation
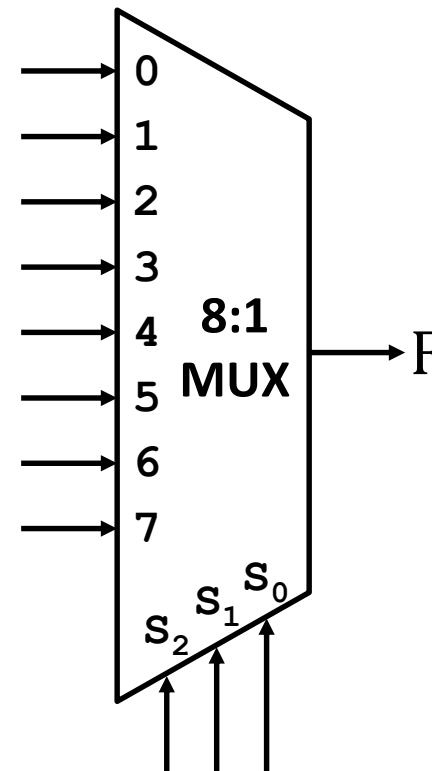
# FPGA Combinational Logic

- ❖ Create arbitrary combinational binary function  $F(A, B, C)$  using MUXes
  - Creates a **Lookup Table (LUT)**




# FPGA Programming

```

00101010001010010
10010010010011000
10101000101011000
10101001010010101
00010110001001010
10101001111001001
01000010101001010
10010010000101010
10100101010010100
01010110101001010
01010010100101001
    
```


Bitstream

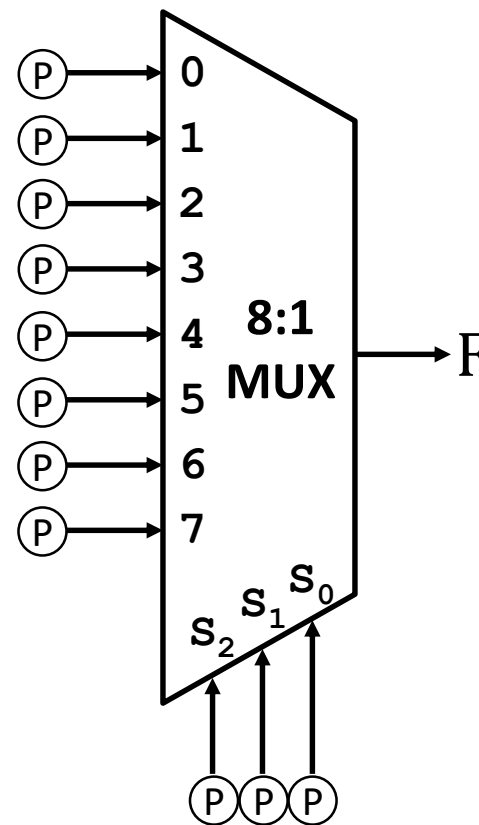

Ⓟ = 1 memory cell (stores 1 bit of info)
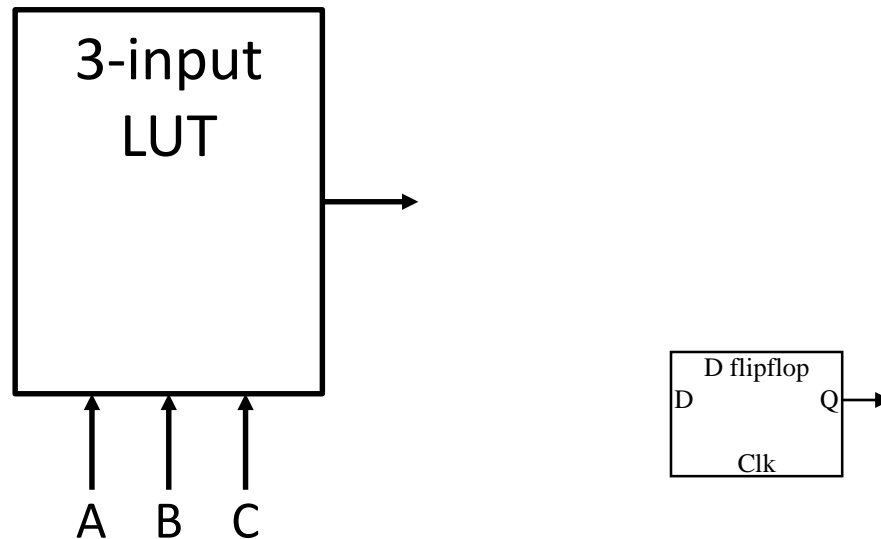
# FPGA Sequential Logic

- ❖ How do we put DFF's onto LUT outputs only when we need them?




- ❖ Creates an Logic Cell (or Logic Element)




# Cyclone V Adaptive Logic Modules

[https://www.altera.com/content/dam/altera-www/global/en\\_US/pdfs/literature/hb/cyclone-v/cv\\_5v2.pdf](https://www.altera.com/content/dam/altera-www/global/en_US/pdfs/literature/hb/cyclone-v/cv_5v2.pdf)

Figure 1-5: ALM High-Level Block Diagram for Cyclone V Devices

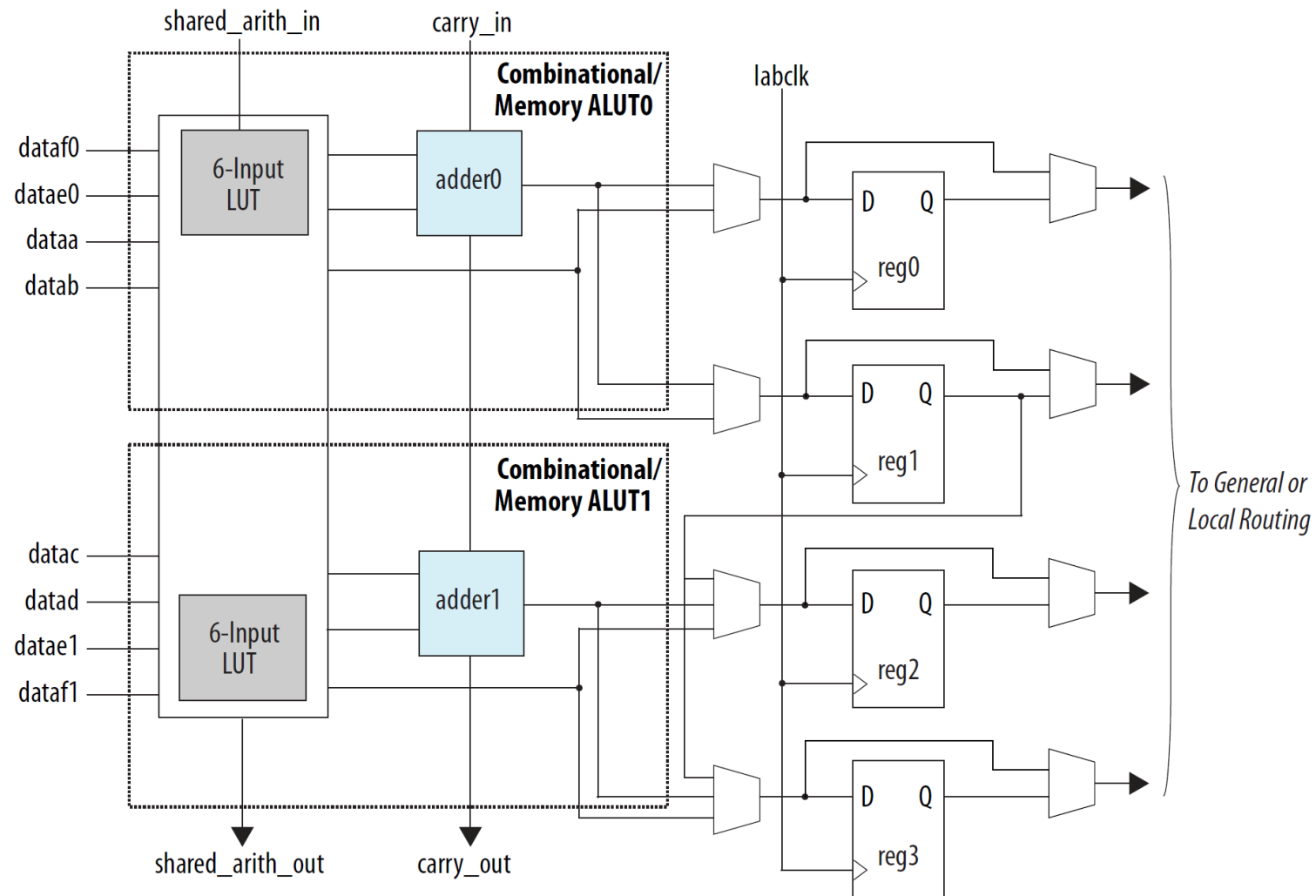


# Generic FPGA Logic Layout

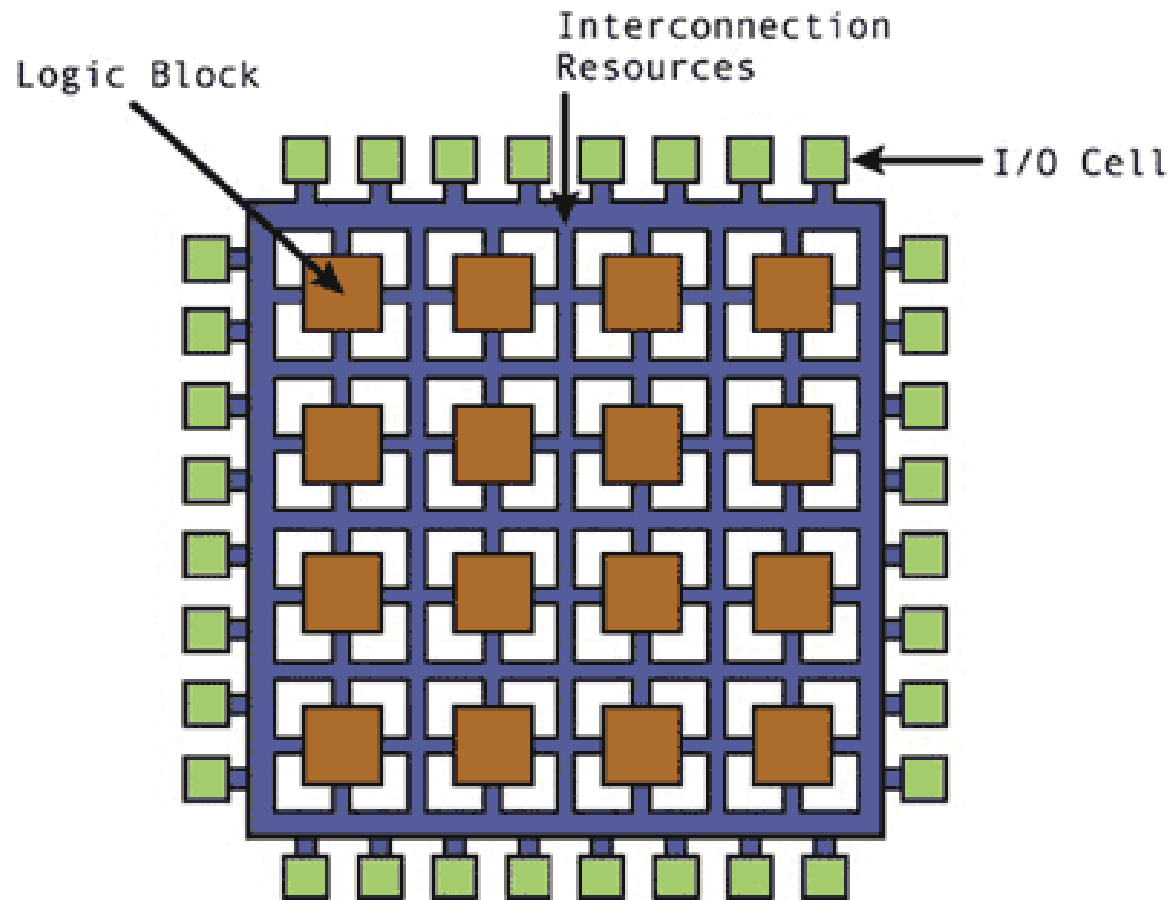

<http://www.chipdesignmag.com/print.php?articleId=434?issueld=16>

# Example Programmed Gate Array

⊗ Connected  
 × Not connected

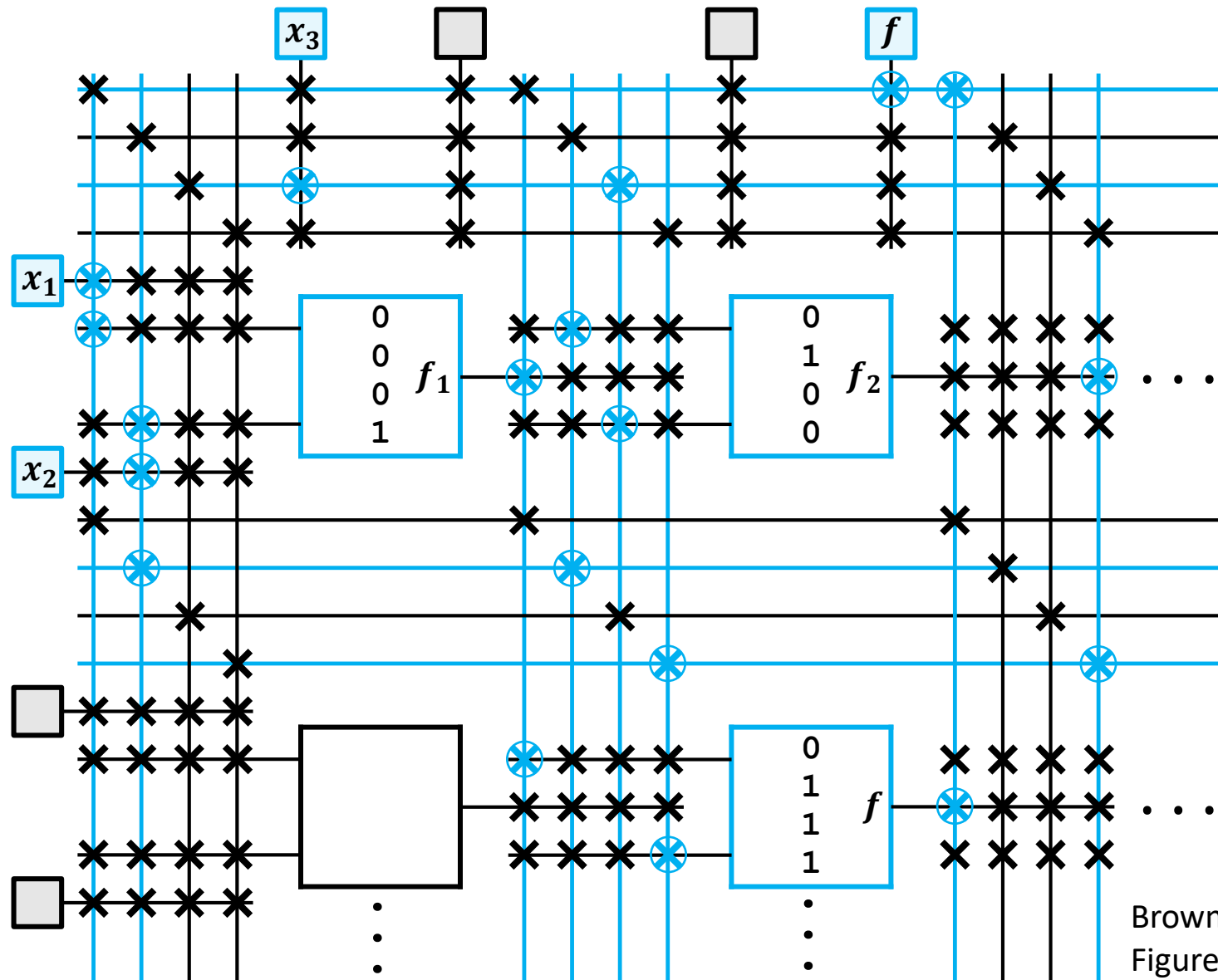

# FPGA CAD

❖ CAD = “Computer-Aided Design”

```
// Verilog code for 2-input
multiplexer
module AOI (F, A, B, C, D);
output F;
input A, B, C, D;
assign F = ~((A & B) | (C &
D));
endmodule
module MUX2 (V, SEL, I, J); //
2:1 multiplexer
output V;
input SEL, I, J;
wire SELB, VB;
not G1 (SELB, SEL);
AOI G2 (VB, I, SEL, SELB, J);
not G3 (V, VB);
endmodule
```

Verilog



FPGA  
CAD  
Tools




```
00101010001010010
10010010010011000
10101000101011000
10101001010010101
00010110001001010
10101001111001001
01000010101001010
10010010000101010
10100101010010100
01010110101001010
01010010100101001
```

Bitstream


- 1) **Tech Mapping:** Convert Verilog to LUTs
- 2) **Placement:** Assign LUTs to specific locations
- 3) **Routing:** Wire inputs to outputs
- 4) **Bitstream Generation:** Convert mapping to bits

# Gate Array vs. SoC

❖ SoC = “System on a Chip”

 


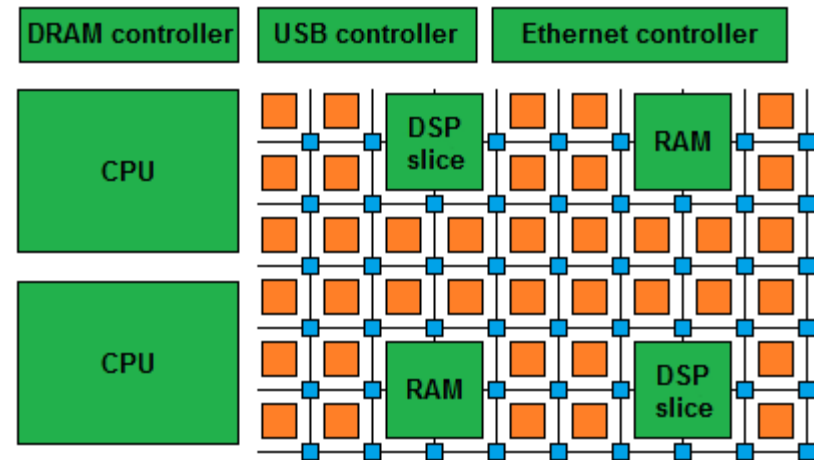"Clean slate" FPGA: programmable gates and routers




Modern FPGA: lots of hard, not-field-programmable gates

# DE1-SoC Board

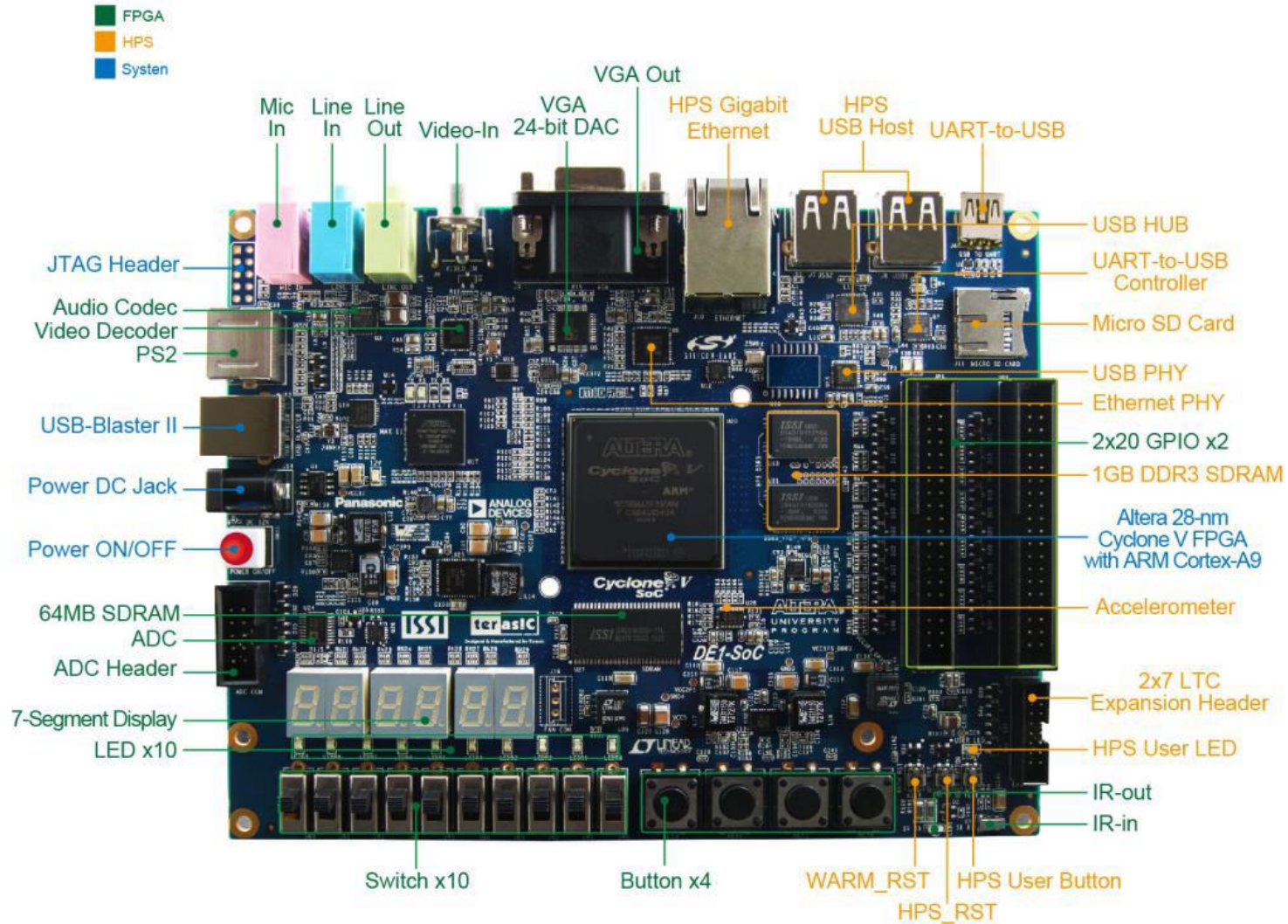

# DE1-SoC Board

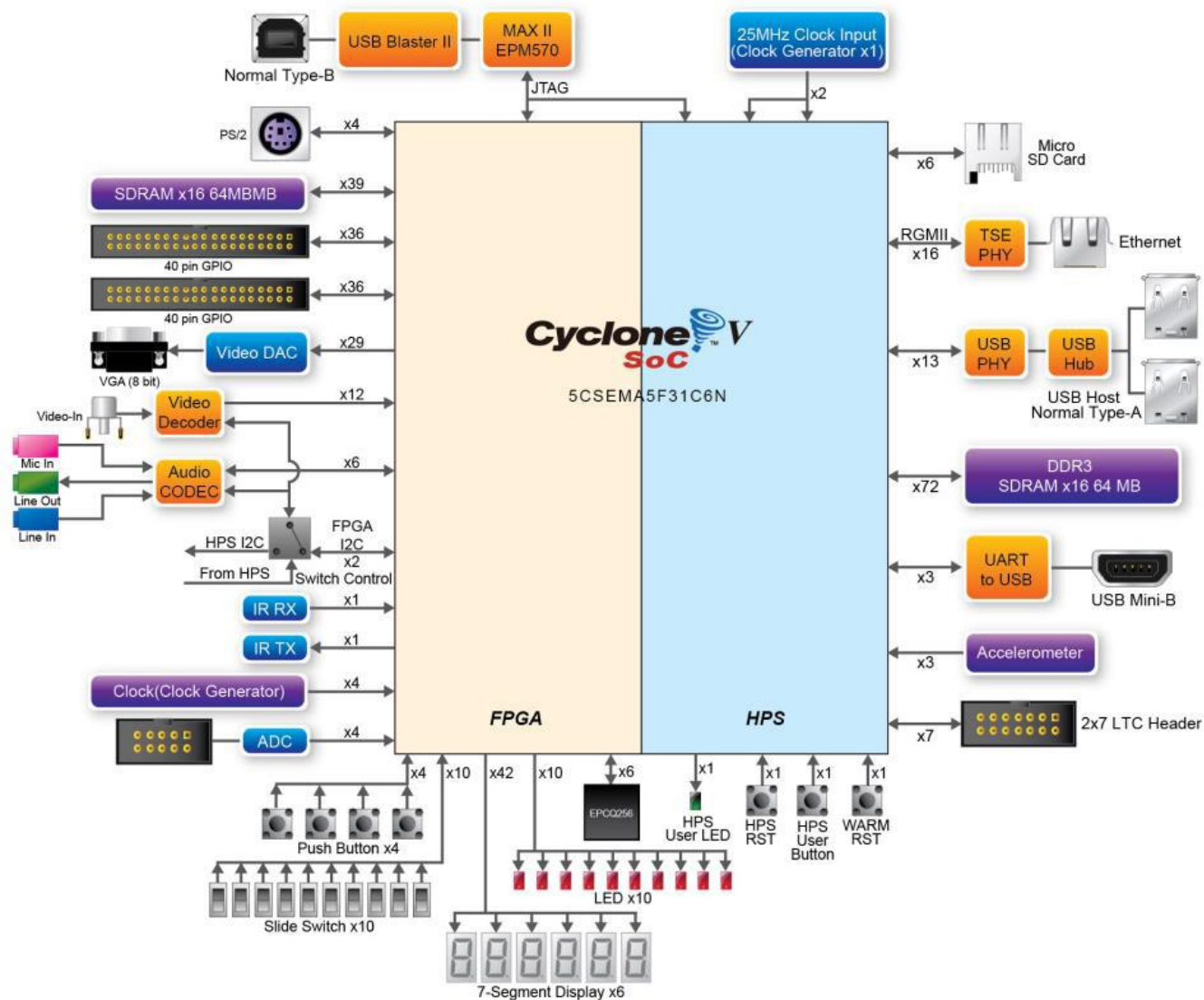

# FPGAs vs. CPUs

- ❖ Individual CPUs designed to handle sequential instruction execution
  - Design and layout determined by architecture
  - Computations “limited” to instruction set
  - Powerful, but also requires things like OS
- ❖ FPGAs
  - Programmable, so specially-designed logic for application
    - But can be difficult to specify certain applications
  - Good for parallelizing computations
    - Can perform separate computations if separated via routing



# Outline

- ❖ Computer Components (Cont.)
  - Register File
  - Datapath teaser
  - Serial Communication
- ❖ FPGAs
- ❖ **Course Wrap-up**

# Course Wrap-Up

- ❖ Combinational Logic
  - Karnaugh Maps
- ❖ Sequential Logic
  - Timing Considerations
- ❖ Finite State Machines
- ❖ Routing Elements
  - Multiplexor, Encoder, Decoder, Demultiplexor
- ❖ Computational Building Blocks
  - Adders, Registers, Shift Registers, Counters
- ❖ *SystemVerilog*

# Digital Workhorses

## ❖ Multiplexors

- Logic – can implement arbitrary logic as LUTs
- Routing – select between many simultaneous computations

## ❖ Flip-flops

- Store information → registers, shift registers, counters, FSMs, RAM cells
- Synchronization of system
  - Delay element – “holds up” information
- Deal with metastability

# Takeaways

- ❖ You can do a lot without actually digging into the hardware details!
  - Verilog is programmatic way to generate design hardware
  - High-level view is sufficient for system design in many cases
- ❖ ... but the hardware details are important
  - Timing especially – synchronization, metastability
  - Bits are always present – resets, unexpected situations
  - Design affects speed, power, size
- ❖ A CPU is not required for many applications

# Takeaways

- ❖ You now know how to design and implement fairly complex digital designs!
  - Could breadboard + wire packages
  - DE1-SoC (\$322): <http://www.terasic.com.tw/cgi-bin/page/archive.pl?Language=English&No=836>

# Final Words

- ❖ Please fill out course evaluation!
  - Will be released next week online
  - Let us know how to improve this class
  
- ❖ Future classes
  - EE 205/215 – details of electronics
  - EE/CSE 371 – digital design techniques and considerations (algorithms, communication, complexity)
  - EE/CSE 469 – computer architecture (CPU design)
  
- ❖ Hope you had fun this quarter!