

Intro to Digital Design

Finite State Machines

Instructor: Chris Thachuk

Teaching Assistants:

Jiuyang Lyu

Stephanie Osorio-Tristan

Nandini Talukdar

Wen Li


Relevant Course Information

- ❖ Quiz 1 grades will be out on Gradescope by Thursday
 - Both the quiz and solutions will be added to the question bank on the course website

- ❖ Lab 5 – Verilog implementation of FSMs
 - Step up in difficulty from Labs 1-4 (worth 100 points)
 - Bonus points for minimal logic *110 max possible*
 - Simplification through *design* (Verilog does the rest)

Review of Timing Terms

- ❖ **Clock:** steady square wave that synchronizes system
- ❖ **Flip-flop:** one bit of state that samples every rising edge of CLK (positive edge-triggered)
- ❖ **Register:** several bits of state that samples on rising edge of CLK (positive edge-triggered); often has a RESET
- ❖ **Setup Time:** when input must be stable *before* CLK trigger
- ❖ **Hold Time:** when input must be stable *after* CLK trigger
- ❖ **CLK-to-Q Delay:** how long it takes output to change from CLK trigger

 


SDS Timing Question (all times in ns)

$$t_{hold} \leq t_{input,i} \leq t_{period} - t_{setup}$$

❖ The circuit below has the following timing parameters

 - $t_{period} = 20, t_{setup} = 2$
- $t_{XOR} = t_{OR} = 5, t_{NOT} = 4$
- Input changes 1 ns after clock trigger



❖ What is the max t_{C2Q} ?

t_{setup} constraint
 $t_{input,n}$ - last time a register input changes

$$t_{C2Q} + t_{NOT} + t_{XOR} + t_{OR} \leq t_{period} - t_{setup}$$

$$4 + 5 + 5 \leq 20 - 2$$

$$t_{C2Q} \leq 4 \text{ ns}$$

❖ If $t_{C2Q} = 3$, what is the max t_{hold} ?

t_{hold} constraint
 $t_{input,1}$ - first time a register input changes

$$1 \text{ ns} + t_{XOR} \geq t_{hold}$$

$$1 + 5 \geq t_{hold}$$


$$t_{hold} \leq 6 \text{ ns}$$

Outline


- ❖ **Flip-Flop Realities**
- ❖ Finite State Machines
- ❖ FSMs in Verilog

Flip-Flop Realities: Gating the Clock

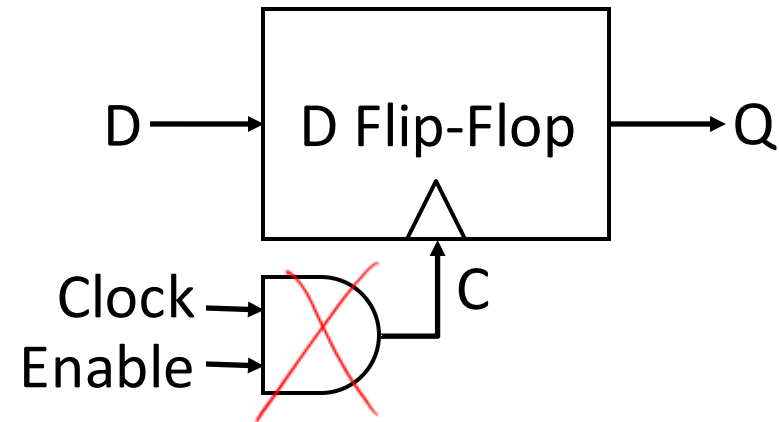- ❖ Delay can cause part of circuit to get out of sync with rest
 - More timing headaches!
 - Adds to *clock skew*




- ❖ Hard to track non-uniform triggers

 

- ❖ **NEVER GATE THE CLOCK!!!**


Flip-Flop Realities: External Inputs

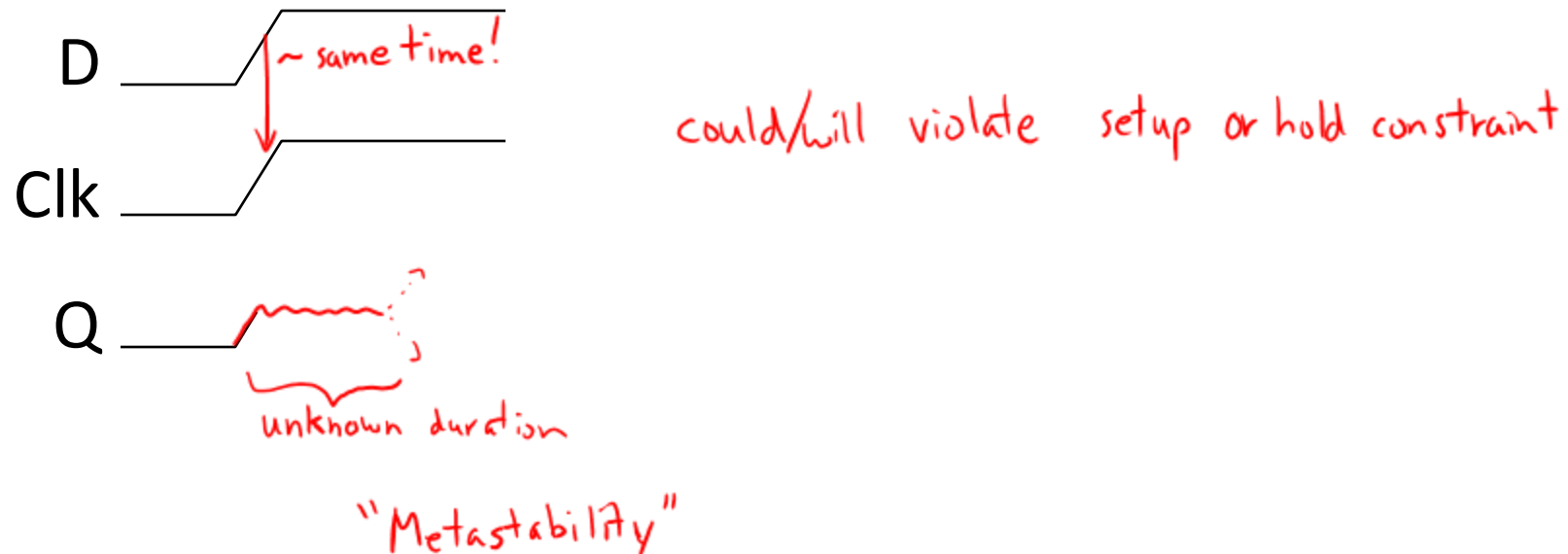- ❖ External inputs aren't synchronized to the clock
 - If not careful, can violate timing constraints
- ❖ What happens if input changes around clock trigger?



Flip-Flop Realities: Metastability

- ❖ **Metastability** is the ability of a digital system to persist for an unbounded time in an unstable equilibrium or metastable state
 - Circuit may be unable to settle into a stable '0' or '1' logic level within the time required for proper circuit operation
 - Unpredictable behavior or random value
 - https://en.wikipedia.org/wiki/Metastability_in_electronics
- ❖ State elements can help reject transients
 - Longer chains = more rejection, but longer signal delay

 


Outline

- ❖ Flip-Flop Realities
- ❖ **Finite State Machines**
- ❖ FSMs in Verilog

Finite State Machines (FSMs)

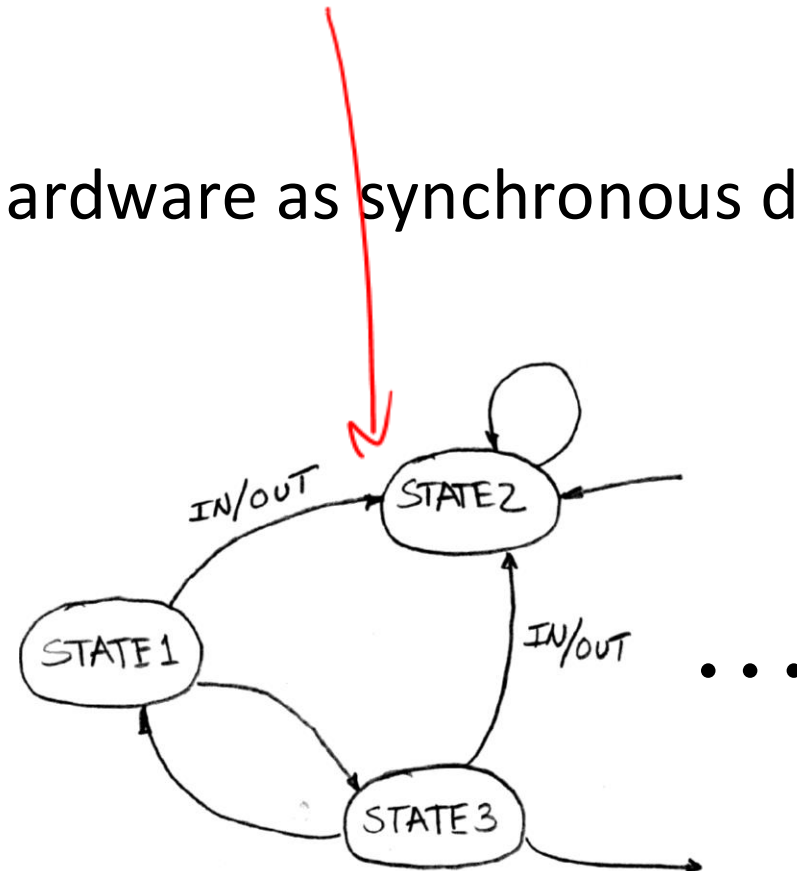- ❖ A convenient way to conceptualize computation over time
 - Function can be represented with a *state transition diagram*
 - You've seen these before in CSE311
- ❖ **New for CSE369:** Implement FSMs in hardware as synchronous digital systems
 - Flip-flops/registers hold “state”
 - Controller (state update, I/O) implemented in combinational logic




State Diagrams

- ❖ A state diagram (in this class) is defined by:
 - A set of *states* S (circles)
 - An *initial state* s_0 (only arrow not between states)
 - A *transition function* that maps from the current input and current state to the output and the next state (arrows between states)
 - **Note:** We cover Mealy machines here; Moore machines put outputs on states, not transitions
- ❖ State transitions are controlled by the clock:
 - On each clock cycle the machine checks the inputs and generates a new state (could be same) and new output

 
Example: Buggy 3 Ones FSM

- ❖ FSM to detect 3 consecutive 1's in the Input




Hardware Implementation of FSM

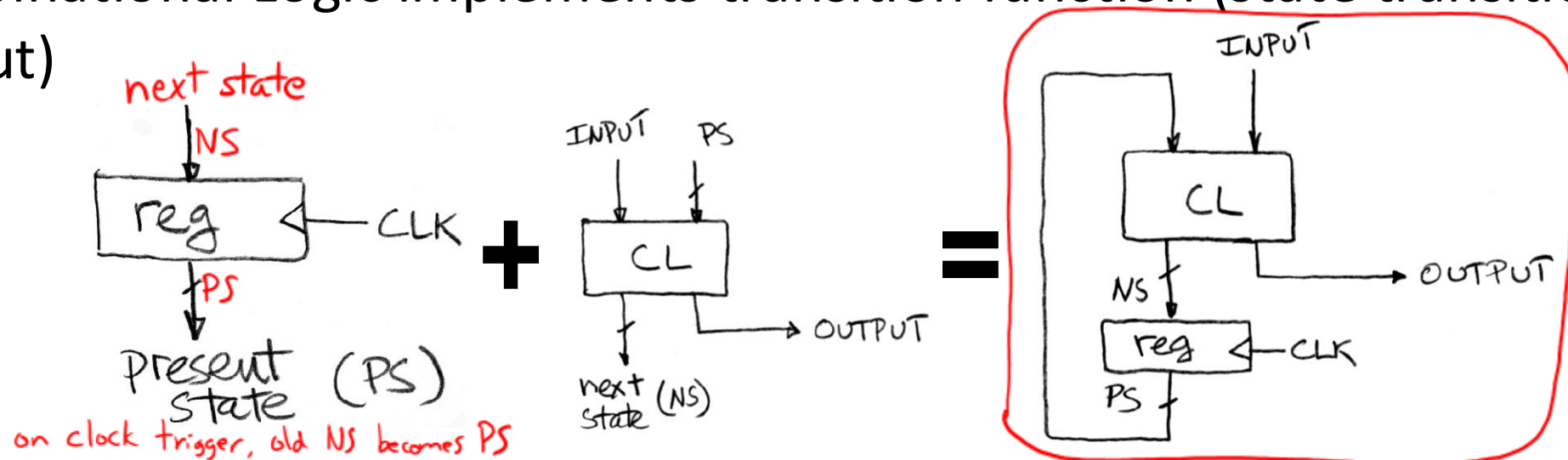- ❖ Register holds a representation of the FSM's state
 - Must assign a *unique* bit pattern for each state
 - Output is *present/current state* (PS/CS)
 - Input is *next state* (NS)
- ❖ Combinational Logic implements transition function (state transitions + output)



FSM: Combinational Logic

 - ❖ Read off transitions into Truth Table!
 - **Inputs:** Present State (PS) and Input (In)
 - **Outputs:** Next State (NS) and Output (Out)



PS	In	NS	Out
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

↑↑
↑

- ❖ Implement logic for *EACH* output (2 for NS, 1 for Out)

FSM: Logic Simplification

PS	In	NS	Out
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1
11	0	XX	X
11	1	XX	X

NS₁ ↓ *NS₀* ✓

NS₁

In \ PS	00	01	11	10
0	0	0	X	0
1	0	1	X	0

NS₀


In \ PS	00	01	11	10
0	0	0	X	0
1	1	0	X	0

Out

In \ PS	00	01	11	10
0	0	0	X	0
1	0	0	X	1

FSM: Implementation

 - ❖ $NS_1 = PS_0 \cdot In$
- ❖ $NS_0 = \overline{PS_1} \cdot \overline{PS_0} \cdot In$
- ❖ $Out = PS_1 \cdot In$



- ❖ How do we test the FSM?
 - “Take” every *transition* that we care about!


State Diagram Properties

- ❖ For S states, how many state bits do I use?

$$s = \lceil \log_2 S \rceil$$

- ❖ For I inputs, what is the *maximum* number of transition arrows on the state diagram?

$$S \times 2^I$$

 


- Can sometimes combine transition arrows:
 - Can sometimes omit transitions (don't cares)
- ❖ For s state bits and I inputs, how big is the truth table?

$$2^{I+s}$$


Vending Machine Example

❖ Vending machine description/behavior:

 - Single coin slot for dimes ^D and nickels ^N \Rightarrow 2 inputs \Rightarrow 4 transitions
 DN
 00
 01
 10
 11 \rightarrow X
- Releases gumball after ≥ 10 cents deposited
- Gives no change



❖ State Diagram:

 

Vending Machine State Table



PS	N	D	NS	Open
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	X	X
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	X	X

NS

D \ PS,N		PS,N			
		00	01	11	10
D	0	0	1	0	1
	1	0	X	X	0

$$NS = \bar{P}S \cdot N + P\bar{S} \cdot \bar{D}$$


Open

D \ PS,N		PS,N			
		00	01	11	10
D	0	0	0	1	0
	1	1	X	X	1

$$Open = D + P\bar{S} \cdot N$$

Vending Machine Implementation

 - ❖ $Open = D + PS \cdot N$
- ❖ $NS = \overline{PS} \cdot N + PS \cdot \overline{N} \cdot \overline{D}$




Outline

- ❖ Flip-Flop Realities
- ❖ Finite State Machines
- ❖ **FSMs in Verilog**

FSMs in Verilog: Overview

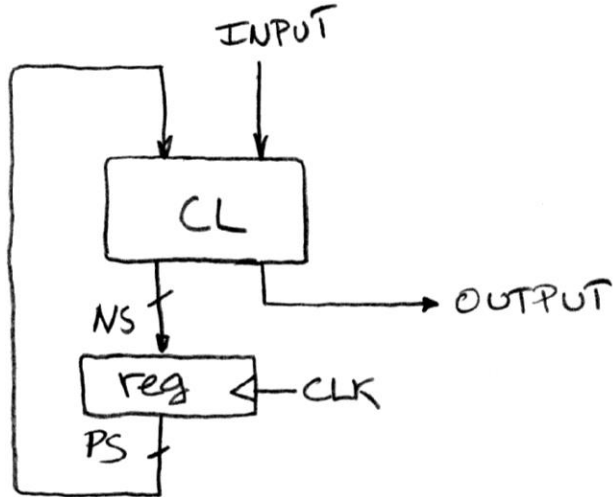- ❖ FSMs follow a very particular organizational structure:




- ❖ They can be implemented using the following design pattern:
 - 1) Define states and state variables
 - 2) Next state logic (ns)
 - 3) Output logic
 - 4) State update logic (ps)

FSMs in Verilog: Example

❖ Arbitrary 3-state FSM that outputs 1 when two consecutive 1's are seen on the input

- 2-bit state ps
- clk and reset inputs
- 1-bit input w
- 1-bit output out


*important to
"initialize"
hardware*

 

FSMs in Verilog: (0) Module Outline

```
module simpleFSM (clk, reset, w, out);  
  input  logic clk, reset, w;  
  output logic out;
```

```
endmodule // simpleFSM
```

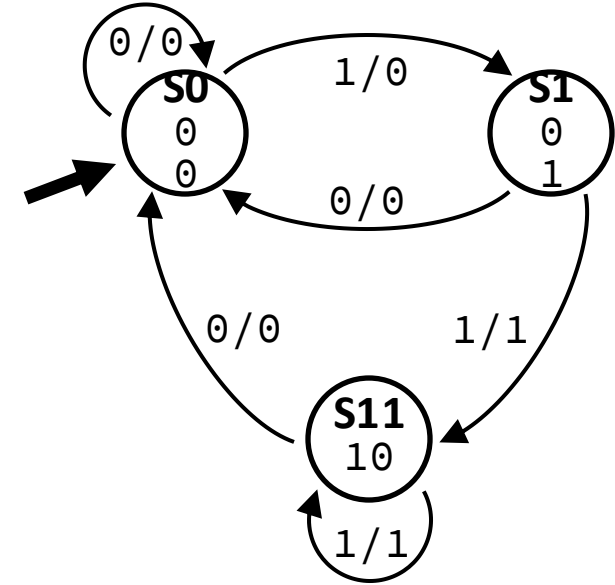

FSMs in Verilog: (1) State Declarations

```

module simpleFSM (clk, reset, w, out);
  input  logic clk, reset, w;
  output logic out;


  // State Encodings and variables
  // (ps = Present State, ns = Next State)
  enum logic [1:0] {S0=2'b00, S1=2'b01, S11=2'b10}
  ps, ns;

```

enumeration is restriction on existing type

defines new constants for these variables

 explicit definition of binary encoding is optional




```

endmodule // simpleFSM

```

FSMs in Verilog: (2) Next State Logic

```
module simpleFSM (clk, reset, w, out);  
    ... // (0) port declarations  
    ... // (1) state encodings and variables  
  
    // Next State Logic (ns)  
    always_comb  
        case (ps)  
            S0: if (w) ns = S1;  
                else ns = S0;  
            S1: if (w) ns = S11;  
                else ns = S0;  
            S11: if (w) ns = S11;  
                else ns = S0;  
        endcase  
  
endmodule // simpleFSM
```

 

FSMs in Verilog: (2) Output Logic

```


module simpleFSM (clk, reset, w, out);
... // (0) port declarations
... // (1) state encodings and variables
... // (2) Next State Logic (ns)

// Output Logic - could have been in "always" block
// or part of Next State Logic.
assign out = (ns == S11);

endmodule // simpleFSM

```

 output 1 from any transition
going into S11 (checking ns, not ps)



FSMs in Verilog: (2) Output Logic

```


module simpleFSM (clk, reset, w, out);
  ... // (0) port declarations
  ... // (1) state encodings and variables
  ... // (2) Next State Logic (ns)
  ... // (3) Output Logic

  // State Update Logic (ps)
  always_ff @(posedge clk)
    if (reset)
      ps <= S0; // "initial" state
    else
      ps <= ns;

endmodule // simpleFSM

```

update state
(or reset)
on clock trigger

 

Reminder: Blocking vs. Non-blocking

- ❖ NEVER mix in one `always` block!
- ❖ Each variable written in only one `always` block

Blocking (=) in CL:

```
// Output logic
assign out = (ns == S11);

// Next State Logic (ns)
always_comb
  case (ps)
    S0:  if (w) ns = S1;
         else ns = S0;
    S1:  if (w) ns = S11;
         else ns = S0;
    S11: if (w) ns = S11;
         else ns = S0;
  endcase
```

Non-blocking (<=) in SL:

```
// State Update Logic (ps)
always_ff @(posedge clk)
  if (reset)
    ps <= S0;
  else
    ps <= ns;
```

One or Two Blocks?

- ❖ We showed the state update in two separate blocks:
 - `always_comb` block that calculates the next state (ns)
 - `always_ff` block that defines the register (ps updates to last ns on clock trigger)
- ❖ Can this be done with a single block?
 - If so, which one: `always_comb` or `always_ff`

↑ means we need to use non-blocking statements

One or Two Blocks? *your choice!*

```
always_comb  
case (ps)  
  S0: if (w) ns = S1;  
      else ns = S0;  
  S1: if (w) ns = S11;  
      else ns = S0;  
  S11: if (w) ns = S11;  
       else ns = S0;  
endcase
```

```
always_ff @(posedge clk)  
  if (reset)  
    ps <= S0;  
  else  
    ps <= ns;
```

```
always_ff @(posedge clk)  
  if (reset)  
    ps <= S0;  
  else  
    case (ps)  
      S0: if (w) ps <= S1;  
          else ps <= S0;  
      S1: if (w) ps <= S11;  
          else ps <= S0;  
      S11: if (w) ps <= S11;  
           else ps <= S0;  
    endcase
```

FSMs Test Bench (1/2)


```
module simpleFSM_tb ();
  logic clk, reset, w, out;

  // instantiate device under test
  simpleFSM dut (.clk, .reset, .w, .out);

  // generate simulated clock
  parameter CLOCK_PERIOD=100;
  initial begin
    clk <= 0;
    forever #(CLOCK_PERIOD/2) clk <= ~clk;
  end

  ... // generate test vectors

endmodule // simpleFSM_tb
```

 


FSMs Test Bench (2/2)

```



// generate test vectors
initial begin
  reset <= 1; w <= 0; @(posedge clk); // reset
  reset <= 0;          @(posedge clk); // 4 cycles of 0 input
                          @(posedge clk);
                          @(posedge clk);
                          @(posedge clk);
  w <= 1; @(posedge clk);
  w <= 0; @(posedge clk);
  w <= 1; @(posedge clk); // 4 cycles of 1 input
                          @(posedge clk);
                          @(posedge clk);
                          @(posedge clk);
  w <= 0; @(posedge clk);
          @(posedge clk); // extra cycle

  $stop; // pause the simulation
end
endmodule // simpleFSM_tb

```

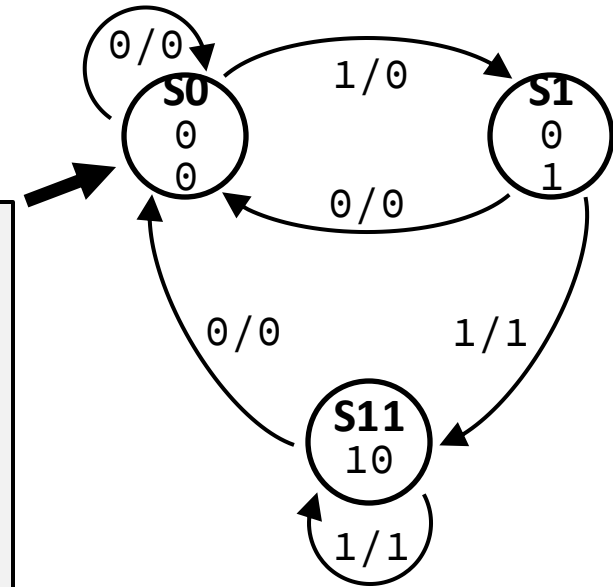

Testbench Waveforms

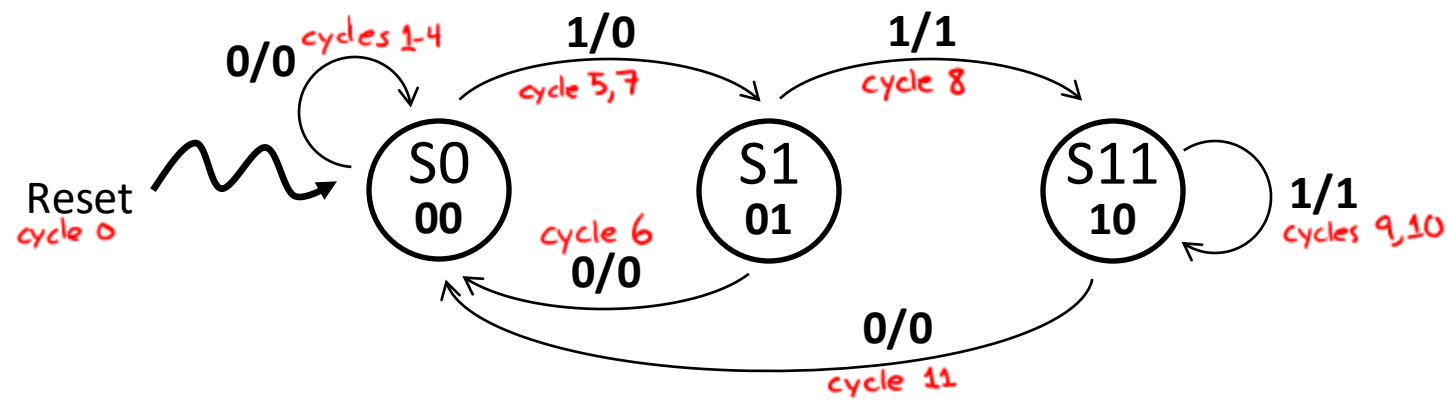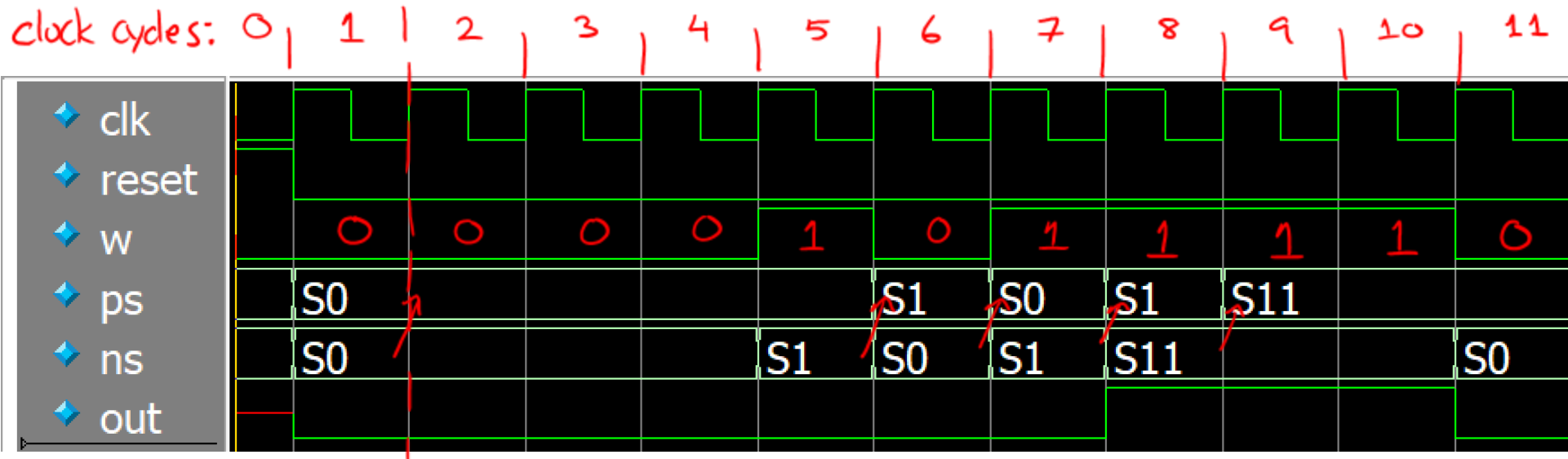

Summary

- ❖ Gating the clock and external inputs can cause timing issues and metastability
- ❖ FSMs visualize state-based computations
 - Implementations use registers for the state (PS) and combinational logic to compute the next state and output(s)
 - Mealy machines have outputs based on *state transitions*
- ❖ FSMs in Verilog usually have separate blocks for state updates and CL
 - Blocking assignments in CL, non-blocking assignments in SL
 - Testbenches need to be carefully designed to test all state transitions