

Intro to Digital Design

Project Tips, Memory

Instructor: Chris Thachuk

Teaching Assistants:

Jiuyang Lyu

Stephanie Osorio-Tristan

Nandini Talukdar

Wen Li

Relevant Course Information

❖ Lab 8 – Project

- 2 weeks to work on it – don't wait to start!
 - Reports due Friday, Mar 14 @ 11:59 pm
 - Lab 8 check-in due next week during demo slot, or by Friday O/H
 - Demos can be scheduled outside of the lab hours by making a *private* post on Ed Discussion
- 8 suggested projects
 - **Most use LED breakout board – included in your lab kit**
 - Not all are worth the same number of points (“full credit” is 150)
 - Think carefully about what you want to tackle
(*e.g.*, complex FSM, LED board, multiple “clock speeds”)
- Bonus points for adding cool features and early finish
 - Up to 20 points for extra features; up to 10 points for early finish

Practice




❖ Implement a **counter** that goes through the state sequence

000 → 001 → 011 → 010 → 110 → 111 → 101 → 100 → 000 → ...

- Include an Enable signal to count and a Reset signal (to 000)

P ₂	P ₁	P ₀	N ₂	N ₁	N ₀
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	1

   - $N_2 = P_2 \bar{P}_0 + P_1 \bar{P}_0$
- $N_1 = \bar{P}_2 P_0 + P_1 \bar{P}_0$
- $N_0 = \bar{P}_2 \bar{P}_1 + P_2 P_1$



Outline

- ❖ **Project Tips**
 - “Multiple clocks”
 - **Verilog generate**
 - **SystemVerilog Arrays**
- ❖ **Computer Components**
 - Memory/RAM

Comparator (Multibit)

- ❖ Equality ($A == B$)
 - XNOR corresponding bits of A and B, then AND together
 - NOR all bits of $A-B$

- ❖ Comparator ($A < B$, $A == B$, $A > B$)
 - $A < B$: MSB of $A-B$
 - $A == B$: NOR of all bits of $A-B$
 - $A > B$: NOT of MSB of $A-B$

“Multiple Clocks” Via Counters

- ❖ The `clock_divider` module is a 32-bit up counter
 - All output bits update at same time (t_{C2Q})
 - Output bits get us powers of 2 differences in speed
- ❖ Still want to use *single* clock for all state elements
 - We will instead control actions using the Enable signal
- ❖ Use comparator on a counter as Enable signal
 - May need to feedback into Reset signal on counter

Advanced Verilog: generate

- ❖ Condense your code using loops and conditionals
 - Often used with `assign` and module instantiation
- ❖ Details:
 - Loop variables must be declared as `genvar` outside of `generate` statement
 - Block statements (`for/if`) *must* have `begin` and `end` and be labeled

```
genvar <loop_var>;  
  
generate  
  for (<init>; <cond>; <update>) begin : <label>  
    // do something with loop_var  
  end  
endgenerate
```

Add/Sub in Verilog (parameterized)

❖ Variable-width add/sub (with overflow, carry)

```
module addN #(parameter N=32) (OF, CF, S, sub, A, B);
  output logic          OF, CF;
  output logic [N-1:0] S;
  input  logic          sub;
  input  logic [N-1:0] A, B;
  logic  [N-1:0] D;      // possibly flipped B
  logic          C2;    // second-to-last carry-out

  always_comb begin
    D = B ^ {N{sub}}; // replication operator
    {C2, S[N-2:0]} = A[N-2:0] + D[N-2:0] + sub;
    {CF, S[N-1]} = A[N-1] + D[N-1] + C2;
    OF = CF ^ C2;
  end
endmodule // addN
```


Add/Sub in Verilog (generate)

- ❖ Generate produces N fulladd modules

```
module addNgen #(parameter N=32) (OF, CF, S, sub, A, B);
  output logic OF, CF;           // overflow and carry flags
  output logic [N-1:0] S;       // sum output bus
  input  logic sub;             // subtract signal
  input  logic [N-1:0] A, B;    // input busses
  logic [N:0] C;                // carry signals between modules
```

- ❖ Reminder: `module fulladd (cout, s, cin, a, b);`

SystemVerilog Arrays


- ❖ A *bus* is known as a *vector* or **packed array**
 - e.g., `logic [31:0] divided_clocks;`
 - Can only be made of single bit datatypes
- ❖ “Regular” array syntax is known as an **unpacked array**
 - e.g., `logic an_unpacked_array[4:0];`
 - Can be made of any datatype
- ❖ **Multidimensional arrays** can be combinations of packed and unpacked dimensions
 - e.g., `logic [3:0] two_D_array[4:0];`
 - Accessed left to right, starting with unpacked dimensions

Outline

- ❖ Project Tips
 - “Multiple clocks”
 - Verilog generate
 - SystemVerilog Arrays
- ❖ **Computer Components**
 - **Memory/RAM**

Five Components of a Computer

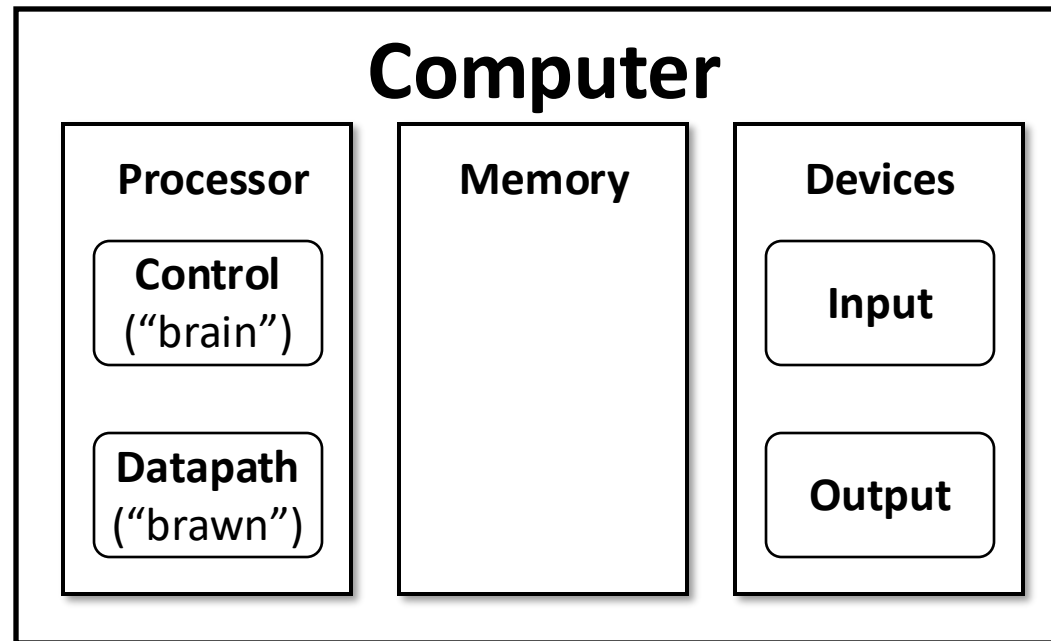- ❖ Components a computer needs to work:
 - Control
 - Datapath
 - Memory
 - Input
 - Output



Executing an Instruction

- ❖ Depends on ISA, but generally:
 - Instruction Fetch
 - Instruction Decode
 - Data Fetch
 - Computation
 - Store Result

 - ❖ Basic Datapath Components (idealized)
 - Register File
 - Memory Management Unit
 - Arithmetic Logic Unit (ALU)
 - Routing Elements
- } Next lecture
- } Today
- } Previous two lectures

Storage Element: Idealized Memory

❖ Memory (idealized)


- One input bus: **DataIn**
- One output bus: **DataOut**
- In reality, often combined

❖ Memory access:

- Read: Data at **Address** placed on **DataOut**
- Write: If **WriteEnable** = 1, **DataIn** written to **Address**



❖ For N addresses, need **Address** input to be $(\log_2 N)$ -bits wide

 ❖ Clock (**CLK**) is a factor ONLY during write operation




8x4 RAM

WriteEnable

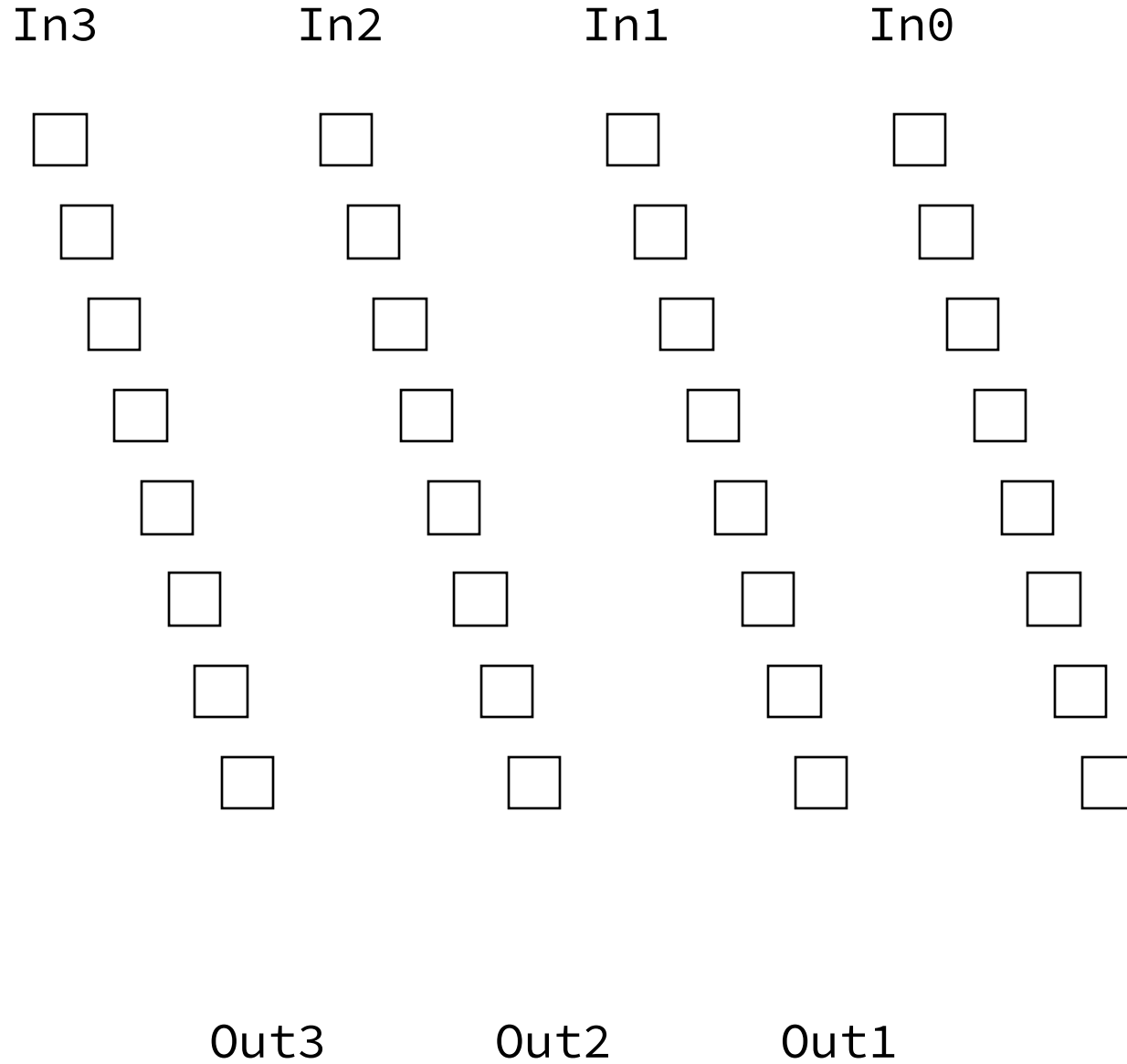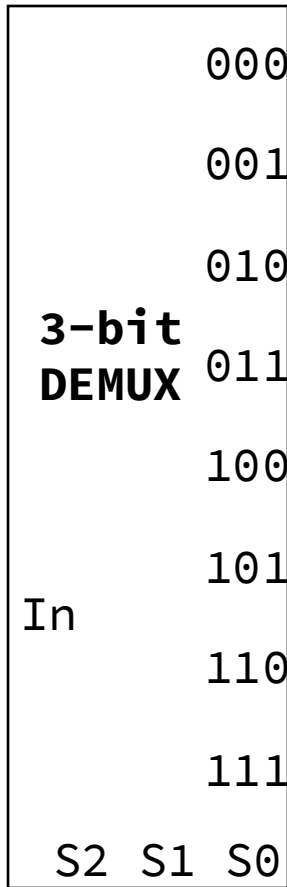

RAM Cell

 - ❖ Requirements:
 - Store one bit of data
 - Change data based on input when row is selected
- ❖ Just a controlled register!
 - No need to Reset
 - Use RowSelect as Enable



Verilog Memories

```
module memory16x8 (data_out, data_in, addr, write, clk);  
  
    output logic [7:0] data_out;  
    input  logic [7:0] data_in;  
    input  logic [3:0] addr;  
    input  logic      write, clk;  
  
    logic      [7:0] mem [15:0]; // array of vectors  
  
    assign data_out = mem[addr];  
  
    always @(posedge clk)  
        if (write)  
            mem[addr] <= data_in;  
  
endmodule // memory16x8
```