
Section 6

— User Input and Top-Level
Modules —

Administrivia

- **Lab 6:** Report due next Wednesday (02/19) @ 2:30 pm, demo by last OH on Friday (02/21), but expected during your assigned slot.
 - ⚠ This lab is a LOT harder than Lab 5 ⚠
- **Lab 7:** Report due 02/26, demo by last OH on 02/28.
 - Building on top of Lab 6 using building blocks; comparable in difficulty.



User Input

User Input Issues


- A major advantage of digital systems is the computational speed (*e.g.*, 50 MHz clock means a computation every 20 ns!)
- This can be difficult to reconcile with user inputs because humans can't move that quickly.
 - We can't control when in a clock cycle our input changes. How do we avoid metastability?
 - What if we only wanted to change an input for a clock cycle?

User Input Issues

- A major advantage of digital systems is the computational speed (*e.g.*, 50 MHz clock means a computation every 20 ns!)
- This can be difficult to reconcile with user inputs because humans can't move that quickly.
 - We can't control when in a clock cycle our input changes. How do we avoid metastability?
 - What if we only wanted to change an input for a clock cycle?
- Solutions:
 - Add a **synchronizer** (typically for all external inputs except reset).
 - Add an edge detector / **pulse generator** (typically for KEYS).

 
Exercise 1a (Synchronizer)

- We will use a **2 flip-flop synchronizer** to combat metastability:



- Implement this in a module called **synch**.

Exercise 1a (Solution)

 

- A **2 flip-flop synchronizer** to combat metastability:


```
module synch (input logic clk, reset, in, output logic out);  
    logic mid; // output of first FF, could be named anything  
  
    always_ff @(posedge clk)  
        if (reset)  
            {mid, out} <= 2'b00;  
        else  
            {mid, out} <= {in, mid};  
  
endmodule // synch
```

Exercise 1b (Pulse Generator)


- We will use a *finite state machine* to **generate pulses** for rising edges of an input signal (*i.e.*, outputs **1** for one clock cycle each time the input goes from low to high, no matter how long the input is held high).
 - Create an FSM state diagram.
 - Then create a SystemVerilog implementation in a module called **pulse**.

 Exercise 1b (Solution)

- **Generate pulses** for rising edges of an input signal:



Exercise 1b (Solution)

 

- **Generate pulses** for rising edges of an input signal:

```
module pulse (input logic clk, reset, in, output logic out);  
  
    enum logic {ZERO, ONE} ps, ns;  
  
    assign ns = in ? ONE : ZERO;  
  
    always_ff @(posedge clk)  
        ps <= reset ? ZERO : ns;  
  
    assign out = (ps == ZERO) & in;  
  
endmodule // pulse
```

Top-Level Module Block Diagrams

Block Diagrams (Review)

- **Block diagrams** are the basic design tool for digital logic.
 - The diagram itself is a module → **inputs and outputs shown and connected.**
 - Major components are represented by blocks (“black boxes”) with their internals abstracted away → **each block becomes its own module.**
 - All ports for each block should be shown and labeled and connected to the appropriate part(s) of the rest of the system → **sets your port connections.**
 - Wires and gates can be added/shown as needed.
- From [Wikipedia](#): The goal is to “[end] in block diagrams detailed enough that each individual block can be easily implemented.”
 - For designs that involve multiple modules, should always create your block diagram *before* coding anything!

HDL Organization

- A module is not a *function*, it is closest to a **class**.
 - Something that you **instantiate**, not something that you *call* – hardware cannot appear and disappear spontaneously.
- Treat modules as **resource managers** rather than temporary helpers.
 - Decompose problem into the major resources and computations and build separate modules around those.
- Hardware organization tends to be more **horizontal** (*i.e.*, modules computing things in parallel alongside each other) rather than **vertical** (*i.e.*, a call stack with functions waiting on each other).

Top-Level Modules

Top-Level Module Notes

- The top-level module interfaces with the actual device ports (*e.g.*, CLOCK_50, SW, KEY, LEDR, HEX).
 - We recommend putting as *little* logic (some gates and routing elements okay) in the top-level module to increase the portability of your code across different devices (*i.e.*, moving from DE1-SoC to DE0-Nano should only be reconnecting different I/O ports to modules).
 - For readability, can also “rename” signals using `assign` statements (*e.g.*, `assign clk = CLOCK_50;`, `assign reset = ~KEY[3];`) or use internal signal names in Wave pane in ModelSim.

Top-Level Module Implementation

- 1) Start with the normal module outline.
- 2) Generate/declare internal signals (*e.g.*, port connections for modules).
 - a) Use copy-and-paste from internal module definitions to avoid typos!
- 3) Instantiate internal modules and make port connections.
- 4) Can include some logic but generally want to keep this to a minimum.
 - a) Significant logic should be abstracted into internal modules.

Top-Level Module Test Bench


- Structurally like a normal test bench:
 - Module skeleton.
 - Create signals for module you're going to test.
 - Instantiate device under test
 - Generate clock (if needed)
 - Define test vectors in an `initial` block.

Top-Level Module Test Bench

- Structurally like a normal test bench:
 - Module skeleton.
 - Create signals for module you're going to test.
 - Instantiate device under test
 - Generate clock (if needed)
 - Define test vectors in an `initial` block.
- Test vectors should focus on testing module *interconnections*:
 - Test that the reset affects all of the internal modules that it should.
 - Don't thoroughly test internal modules again (rely on individual test benches).
 - Test connections between modules – data passing timing and reactions.

Exercise 2

- In Lecture 6, we drew out the block diagram for a **psychic tester**, where the user needs to correctly guess 8 consecutive 4-bit patterns to be declared a psychic. Here, we'll look at a slightly modified version of it:
 - The User Input module will use `synch` and `pulse`, making it sequential logic (SL).
 - To abstract away hardware, changed `KEY` and `SW` inputs to `guess_ext`, `submit_ext`.

 

Exercise 2a

- Implement **psychic_tester**:


- Provided modules:

```
module genPatt (clk, rst, pattern, next);
```

```
module userIn (clk, rst, guess, submit, guess_ext, submit_ext);
```


```
module checkGuess (pattern, guess, correct);
```
 
```
module countRight (clk, rst, correct, submit, next, psychic);
```



Exercise 2a (Solution)

- Module outline:

 


```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);  
    input logic      clk, rst, submit_ext;  
    input logic [3:0] guess_ext;  
    output logic     psychic;
```

```
endmodule // psychic_tester
```

Exercise 2a (Solution)


- Generate/declare internal signals:

 

```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);  
    input logic      clk, rst, submit_ext;  
    input logic [3:0] guess_ext;  
    output logic     psychic;  
  
    logic [3:0] pattern, guess;  
    logic correct, next, submit;  
  
endmodule // psychic_tester
```

Exercise 2a (Solution)

- Instantiate internal modules:

 


```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);
    input logic      clk, rst, submit_ext;
    input logic [3:0] guess_ext;
    output logic     psychic;

    logic [3:0] pattern, guess;
    logic correct, next, submit;

    genPatt    pat (.clk, .rst, .pattern, .next);
    userIn     inp (.clk, .rst,
                  .guess_ext, .submit_ext, .guess, .submit);
    checkGuess chk (.pattern, .guess, .correct);
    countRight cnt (.clk, .rst, .correct, .submit, .next, .psychic);
endmodule // psychic_tester
```

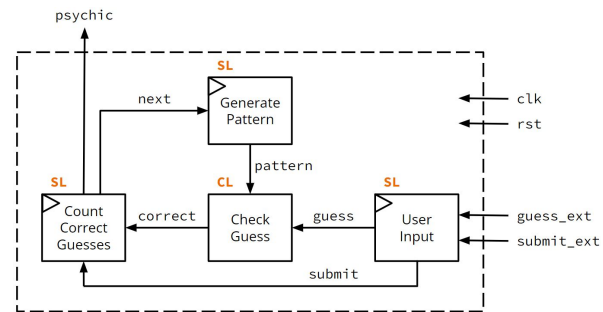Exercise 2a (Solution)

- There's no logic other than the port connections!



```
module psychic_tester (clk, rst, guess_ext, submit_ext, psychic);
    input logic      clk, rst, submit_ext;
    input logic [3:0] guess_ext;
    output logic     psychic;

    logic [3:0] pattern, guess;
    logic correct, next, submit;

    genPatt    pat (.clk, .rst, .pattern, .next);
    userIn     inp (.clk, .rst,
                  .guess_ext, .submit_ext, .guess, .submit);
    checkGuess chk (.pattern, .guess, .correct);
    countRight cnt (.clk, .rst, .correct, .submit, .next, .psychic);
endmodule // psychic_tester
```

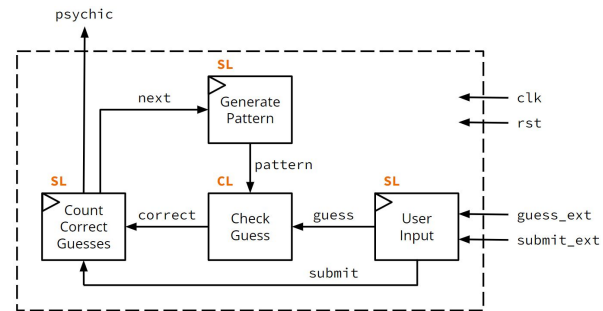

Exercise 2b

- Create a test bench for **psychic_tester**:

- The “randomly” generated patterns will be:

4'b0000 → 4'b0001 → 4'b0011 → 4'b0111 →
4'b1110 → 4'b1101 → 4'b1011 → 4'b0110.

- Remember that it will take 2 clock cycles for the *_ext signals to go through the `synch` modules in the User Input module to reach the rest of the system.
- **Group brainstorm:** What behaviors/situations do we want to test?




Exercise 2b

- Create a test bench for **psychic_tester**:

- **Group brainstorm:** What behaviors/situations do we want to test?

 - Reset behavior.
- submit should trigger a single update 2-3 clock cycles later, even when held.
- A correct guess should increment count and generate a new pattern.
- An incorrect guess should reset count and generate a new pattern.
- psychic going high after 8 guesses was likely tested in countRight's test bench but could test again.



Exercise 2b (Solution)

- Module outline, signal declarations, device under test instantiation:

```
module psychic_tester_tb ();  
    logic      clk, rst, submit_ext, psychic;  
    logic [3:0] guess_ext;  
  
    psychic_tester dut (.*);  
  
endmodule // psychic_tester_tb
```

Exercise 2b (Solution)

- Clock generation, skeleton for test vectors:

```
module psychic_tester_tb ();
  ... // signal declarations
  ... // dut instantiation

  parameter T = 20; // clock period
  initial
    clk = 0;
  always
    #(T/2) clk <= ~clk;

  initial begin
    $stop;
  end
endmodule // psychic_tester_tb
```

Exercise 2b (Solution)

- Test reset behavior.

```
module psychic_tester_tb ();  
    ... // signal declarations, dut instantiation, clock generation  
  
    initial begin  
        // test case 0: verify reset behavior  
        {rst, submit_ext, guess_ext} <= 6'b1_0_0000; @(posedge clk);  
        {rst, submit_ext, guess_ext} <= 6'b0_0_0000; @(posedge clk);  
        $stop;  
    end  
endmodule // psychic_tester_tb
```

Exercise 2b (Solution)

- Test submit signal unenabled.

```
module psychic_tester_tb ();
    ... // signal declarations, dut instantiation, clock generation

    initial begin
        ... // after reset
        // test case 1: user inputs guesses but did not trigger submit button
        // guess is not counted even if the guess matches the correct pattern
        {submit_ext, guess_ext} <= 5'b0_0000;    @(posedge clk);
        {submit_ext, guess_ext} <= 5'b0_0001;    @(posedge clk);
                                                @(posedge clk);

        $stop;
    end
endmodule // psychic_tester_tb
```

Exercise 2b (Solution)

- Test 8 correct guesses with a wrong guess in between

```
module psychic_tester_tb ();
... // signal declarations, dut instantiation, clock generation
initial begin
... // after reset
{submit_ext, guess_ext} <= 5'b0_0000;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // correct (1)
{submit_ext, guess_ext} <= 5'b0_0001;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // correct (2)
{submit_ext, guess_ext} <= 5'b0_0011;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // correct (3)
{submit_ext, guess_ext} <= 5'b0_0111;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // correct (4)
{submit_ext, guess_ext} <= 5'b0_1111;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // wrong guess
                                          @(posedge clk);

    $stop;
end
endmodule // psychic_tester_tb
```

Exercise 2b (Solution)

- Test psychic going high after 8 correct guesses

```
module psychic_tester_tb ();
... // signal declarations, dut instantiation, clock generation
initial begin
... // after reset
{submit_ext, guess_ext} <= 5'b0_0000;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // correct (1)
{submit_ext, guess_ext} <= 5'b0_0001;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // correct (2)
{submit_ext, guess_ext} <= 5'b0_0011;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // correct (3)
{submit_ext, guess_ext} <= 5'b0_0111;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // correct (4)
{submit_ext, guess_ext} <= 5'b0_1110;    @(posedge clk);
submit_ext <= 1'b1;                       @(posedge clk); // correct (5)
... // continue correct guess
$stop;
end
endmodule // psychic_tester_tb
```


Exercise 2b (Solution)

- Test psychic going high after 8 correct guesses


```
module psychic_tester_tb ();
    ... // signal declarations, dut instantiation, clock generation

    initial begin
        ... // user already guessed correctly 5 times
        {submit_ext, guess_ext} <= 5'b0_1101;    @(posedge clk);
        submit_ext <= 1'b1;                       @(posedge clk); // correct (6)
        {submit_ext, guess_ext} <= 5'b0_1011;    @(posedge clk);
        submit_ext <= 1'b1;                       @(posedge clk); // correct (7)
        {submit_ext, guess_ext} <= 5'b0_0110;    @(posedge clk);
        submit_ext <= 1'b1;                       @(posedge clk); // correct (8)
        submit_ext <= 1'b0;                       @(posedge clk);
                                                @(posedge clk);
                                                @(posedge clk);
                                                @(posedge clk); // psychic is HIGH

        $stop;
    end
endmodule // psychic_tester_tb
```


Exercise 2b (solution)

- Example of possible simulation

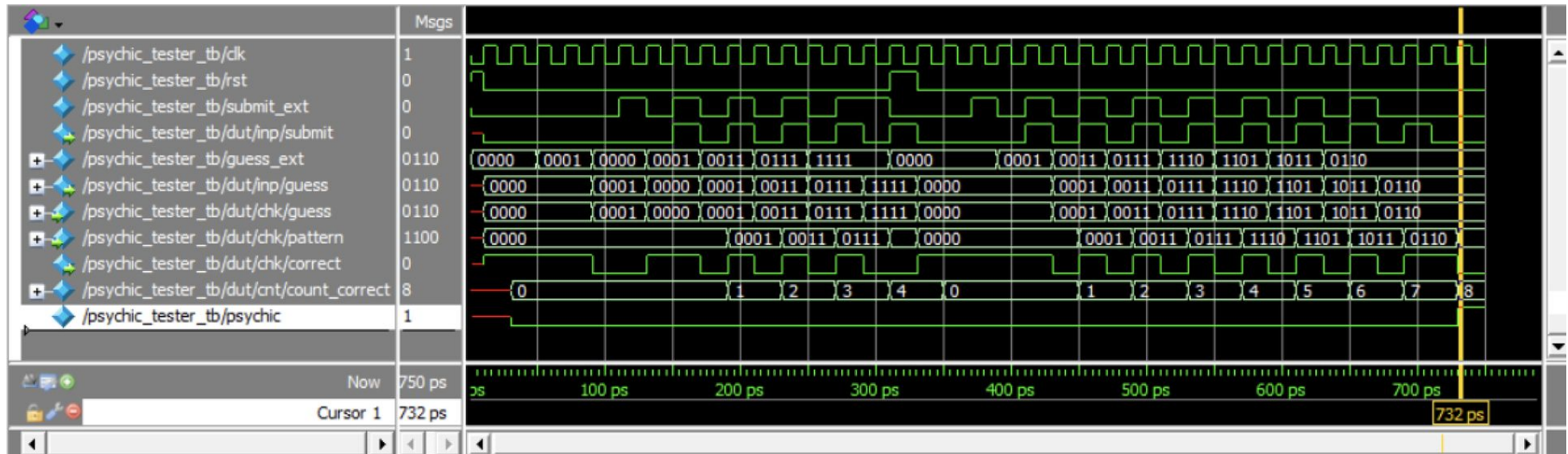


Exercise 2b (solution)

- Verify reset behavior

 

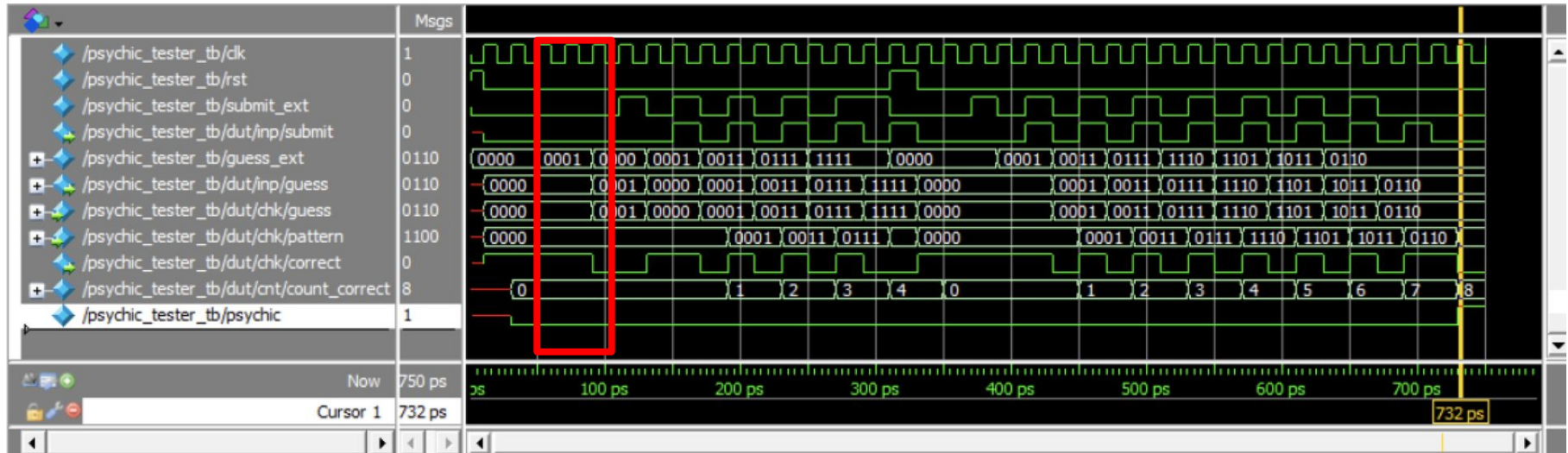
Exercise 2b (solution)

- User inputs guesses but did not trigger submit button
- guess doesn't submit even though the guess matches the correct pattern



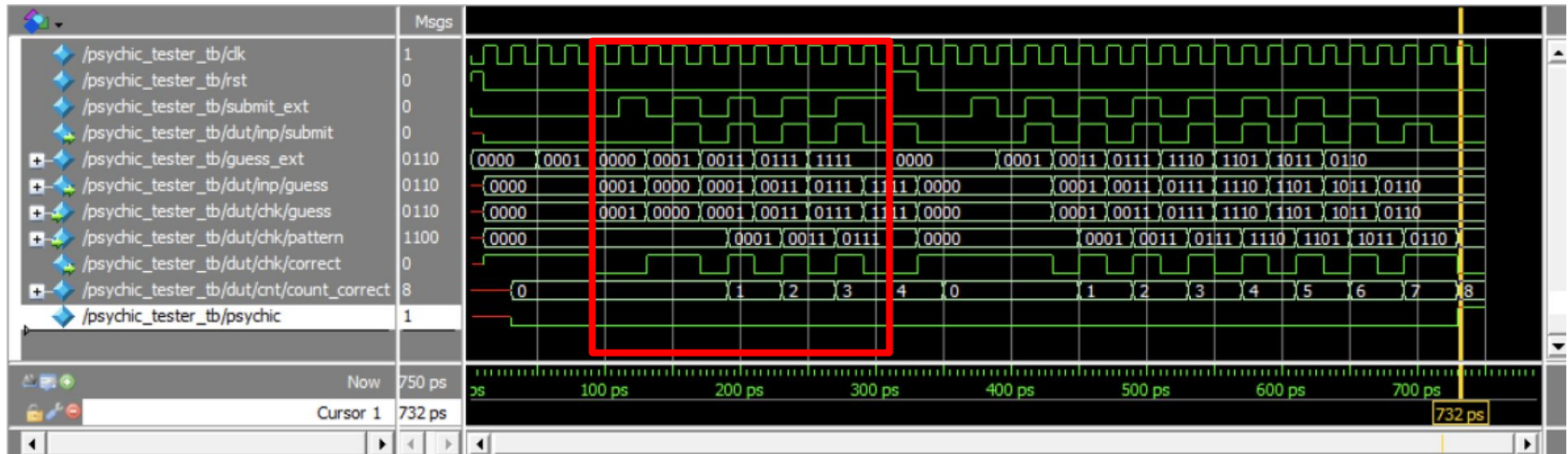
Exercise 2b (solution)

- User guesses wrong in their 5th try
- count_correct is cleared and psychic signal should be false




Exercise 2b (solution)

- Reset and user guesses correctly 8 times
- psychic signal is true after 8 guesses

 

 
Exercise 2c

- Implement **DE1_SoC** to connect to hardware:
 - Use $SW[3:0]$ as guess,
~KEY[3] as rst (reset),
~KEY[0] as submit, and
LEDR[0] as psychic.



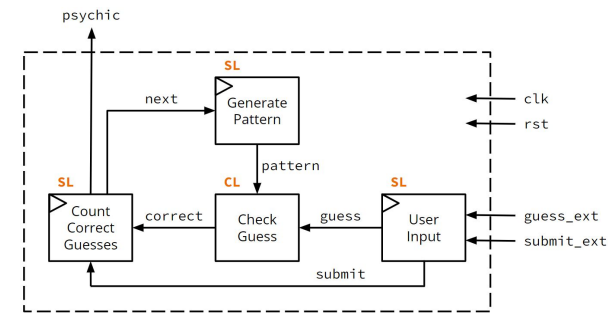Exercise 2c (Solution)

- Wrapper module for hardware (Version 1):



```
module DE1_SoC (CLOCK_50, SW, KEY, LEDR);
    input  logic      CLOCK_50;
    input  logic [9:0] SW;
    input  logic [3:0] KEY;
    output logic [9:0] LEDR;

    logic clk, rst, guess_ext, submit_ext, psychic;
    assign clk = CLOCK_50;
    assign rst = ~KEY[3];
    assign psychic = LEDR[0];
    assign guess_ext = SW[3:0];
    assign submit_ext = ~KEY[0];

    psychic_tester psych (. *);
endmodule // DE1_SoC
```