

Intro to Digital Design

L2: More CL, Verilog Basics

Instructor: Naomi Alterman

Teaching Assistants:

Derek de Leuw

Isabel Froelich

Kevin Hernandez

Aarjav Jain

Packard Stephenson

Administrivia

- ❖ Lab demo time slots have been assigned on Canvas
 - Check the comment on the “Demo Time Slot” assignment

- ❖ Lab 1 this week – Basic Logic
 - **Report + code due on Wednesday @ 2:30p**
 - Check the lab report requirements closely
 - Show up to your demo time with your design synthesized and your simulations ready to view 🙌

Today

- ❖ **Logic Minimization**
- ❖ Verilog Basics
- ❖ Debugging, Simulations and Waveform Diagrams

Translating between Truth Tables and Boolean Equations


"2-level equation"

- ❖ Terms of equation come from rows of table
 - For 1, write variable name
 - For 0, write complement of variable
- ❖ Sum of Products (SoP)
 - From CSE311, "DNF" (disjunctive normal form)
 - Take truth table rows that output 1:
 - AND the inputs together, OR the rows together
- ❖ Product of Sums (PoS)
 - From CSE311, "CNF" (conjunctive normal form)
 - Take truth table rows that output 0:
 - OR the complemented inputs together, AND the rows together

$$\rightarrow \text{SoP: } C = \bar{A}B + \bar{B}A$$

$$\text{PoS: } C = (A + B) \cdot (\bar{A} + \bar{B})$$

	a	b	c
row 0	0	0	0
row 1	0	1	1
" " 2	1	0	1
" " 3	1	1	0

 

Logic minimization

- ❖ Reduce complexity at gate level
 - Allows us to build smaller and faster hardware
 - Care about both # of gates, # of literals (gate inputs), # of gate levels, and types of logic gates

Logic minimization

- ❖ Reduce complexity at gate level
 - Allows us to build smaller and faster hardware
 - Care about both # of gates, # of literals (gate inputs), # of gate levels, and types of logic gates
- ❖ Faster hardware?
 - ➔ Fewer inputs implies faster gates in some technologies
 - ➔ Fan-ins (# of gate inputs) are limited in some technologies
 - Fewer levels of gates implies reduced signal propagation **delays**
 - # of gates (or gate packages) influences manufacturing costs
 - Simpler Boolean expressions → smaller transistor networks → smaller circuit delays → faster hardware


Are Logic Gates Created Equal? "Technology"

❖ No!

2-Input Gate Type	# of CMOS transistors
NOT	2
AND	6
OR	6
NAND	4
NOR	4
XOR	8
XNOR	8


❖ Can recreate all other gates using only NAND or only NOR gates

 - Called "universal" gates
- e.g., $A \text{ NAND } A = \bar{A}$, $B \text{ NOR } B = \bar{B}$
- DeMorgan's Law helps us here!



A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

DeMorgan's Law

 

NOR

- ❖ $\overline{X + Y} = \bar{X} \cdot \bar{Y}$
- ❖ $\overline{X \cdot Y} = \bar{X} + \bar{Y}$

NAND

X	Y	\bar{X}	\bar{Y}	NOR $\overline{X + Y}$	$\bar{X} \cdot \bar{Y}$	NAND $\overline{X \cdot Y}$	$\bar{X} + \bar{Y}$
0	0	1	1	1		1	
0	1	1	0	0		1	
1	0	0	1	0		1	
1	1	0	0	0		0	

❖ In Boolean Algebra, converts between AND-OR and OR-AND expressions

SOP


- $Z = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$

POS

- $\bar{Z} = (A + B + \bar{C}) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + \bar{C})$

❖ At gate level, can convert from AND/OR to NAND/NOR gates

 
▪ "Flip" all input/output bubbles and "switch" gate



DeMorgan's Law Practice Problem




Both Mean NOT

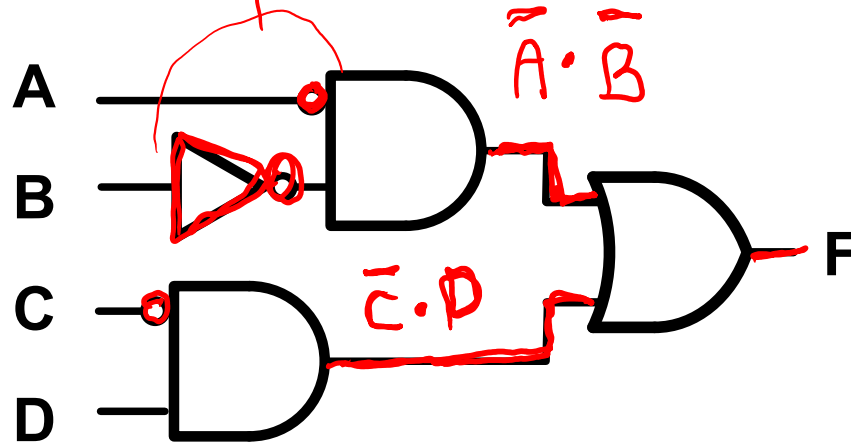❖ Implement this circuit with only NOR gates:



$$F = \bar{A} \cdot \bar{B} + \bar{C} \cdot D$$
   
$$= \overline{A + B} + \overline{C + \bar{D}}$$



Today

- ❖ Logic Minimization
- ❖ **Verilog Basics**
- ❖ Debugging, Simulations and Waveform Diagrams

Verilog

- ❖ A hardware description language (**HDL**)
 - Define circuit schematics using text editors
 - Simulate behavior before (wasting time) implementing
 - Find bugs early
- ❖ **Syntax** is like C/C++/Java, but **meaning** is *very* different
 - Borrows heavily from early concurrency-focused languages like *Modula*
 - VHDL (the other major HDL) borrows from Ada (per...the DoD??)
- ❖ Modern version is **SystemVerilog**
 - Superset of previous; cleaner and more efficient

Verilog: Hardware Descriptive Language

- ❖ Although it looks like code:

module definition ports

```
module myModule (F, A, B, C);
```

```
  output logic F;
```

```
  input logic A, B, C;
```

```
  logic AN, AB, AC;
```

```
  nand gate1(AB, AN, B);
```

```
  nand gate2(AC, A, C);
```

```
  nand gate3( F, AB, AC);
```

```
  not not1(AN, A);
```

```
endmodule
```


intermediate signals

no comp!

module instantiation

module nand (out, in1, in2)

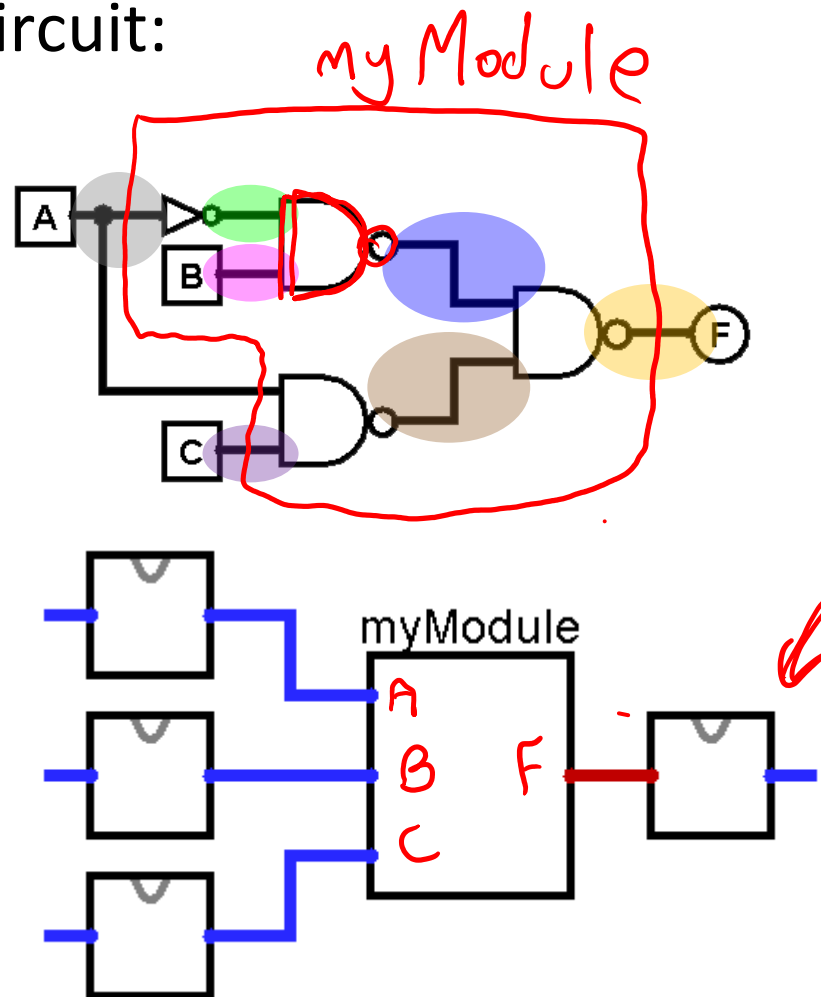- ❖ It directly represents a physical circuit:



Verilog Primitives

- ❖ **Nets:** carry bits from one gate to another
 - SystemVerilog type: “wire”
 - Think of it *like* an immutable reference to mutable data in C++
- ❖ **Variables:** like a net, but the circuit setting the voltage can change
 - SystemVerilog type: “reg” or “logic”
 - ➔ NB: nothing to do with “registers” from Assembly (☹) !
 - “Variable” refers to the source of the data, not the data itself (“driving the voltage”)
 - Think of it *like* a pointer whose location is determined by a switch case in C++
- ❖ ...In this class, we’ll just use “logic” for everything

Verilog Primitives

❖ Logic Values

- **0** = zero, low, FALSE
- **1** = one, high, TRUE
- **X** = unknown, uninitialized, contention (conflict)
- **Z** = floating (disconnected), high impedance

Verilog Primitives

❖ Gates:

Gate	Verilog Syntax
NOT a	$\sim a$
a AND b	$a \& b$
a OR b	$a b$
a NAND b	$\sim(a \& b)$
a NOR b	$\sim(a b)$
a XOR b	$a \wedge b$
a XNOR b	$\sim(a \wedge b)$

J


❖ Modules: “classes” in Verilog that define *blocks* of logic

- **Input:** Signals passed from outside to inside of block
- **Output:** Signals passed from inside to outside of block


Verilog Execution

- ❖ Physical wires transmit voltages (electrons) near-instantaneously
 - Wires by themselves have no notion of sequential execution
- ❖ Gates and modules are **constantly** performing computations
 - Can be hard to keep track of!
- ❖ In pure hardware, there is **no** notion of **initialization**
 - A wire that is not driven by a voltage will naturally pick up a voltage from the environment
- ❖ In pure hardware, there is **no** notion of **reassignment**
 - Verilog variables represent physical wires. The value carried by the wire can change, but the wire's endpoints do not

Structural Verilog

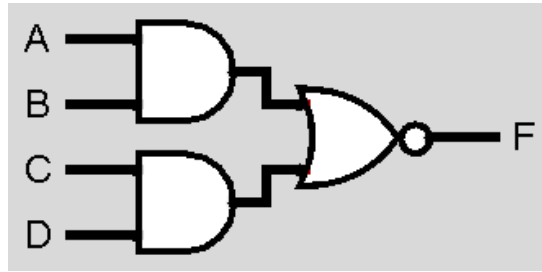

Block Diagram:

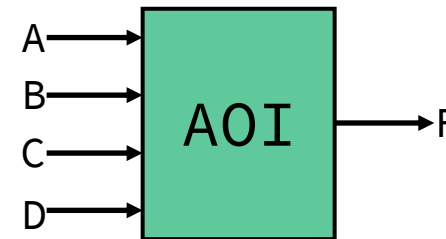


// Verilog code for AND-OR-INVERT gate

```
module AOI (F, A, B, C, D);  
    output logic F;  
    input  logic A, B, C, D;  
  
    assign F = ~((A & B) | (C & D));  
endmodule
```

// end of Verilog code

Verilog Wires

 


// Verilog code for AND-OR-INVERT gate

```

module AOI (F, A, B, C, D);
  ports { output logic F;
          input  logic A, B, C, D;
          logic  AB, CD, O; // now necessary } intermediates
  assign AB = A & B;
  assign CD = C & D;
  assign O  = AB | CD;
  assign F  = ~O;
endmodule

```

Verilog Gate Level

 

// Verilog code for AND-OR-INVERT gate

```
module AOI (F, A, B, C, D);  
  output logic F;  
  input  logic A, B, C, D;  
  logic  AB, CD, O; // now necessary  
  
  and a1(AB, A, B);  
  and a2(CD, C, D);  
  or  o1(O, AB, CD);  
  not n1(F, O);  
endmodule
```

} was:

```
assign AB = A & B;  
assign CD = C & D;  
assign O  = AB | CD;  
assign F  = ~O;
```

Verilog Hierarchy

// Verilog code for 2-input multiplexer

```

module AOI (F, A, B, C, D);
    output logic F;
    input  logic A, B, C, D;

    assign F = ~((A & B) | (C & D));
endmodule
    
```


// 2:1 multiplexer

```

module MUX2 (V, SEL, I, J);
    output logic V;
    input  logic SEL, I, J;
    logic  SELN, VN;

    not G1 (SELN, SEL);
    AOI G2 (.F(VN), .A(I), .B(SEL), .C(SELN), .D(J));
    not G3 (V, VN);
endmodule
    
```

Block
↓
Diagrams

 



Miso Moment



Today

- ❖ Logic Minimization
- ❖ Verilog Basics
- ❖ **Debugging, Simulations and Waveform Diagrams**

Using an FPGA

 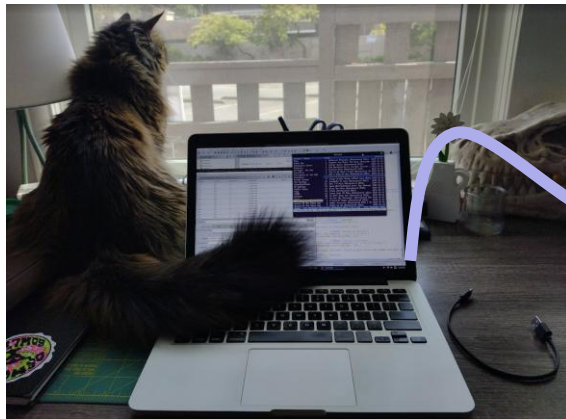

```

// Verilog code for 2-input
multiplexer
module AOI (F, A, B, C, D):
  output logic F;
  input logic A, B, C, D;
  assign F = ~((A & B) | (C &
D));
endmodule
module MUX2 (V, SEL, I, J); //
2:1 multiplexer
  output logic V;
  input logic SEL, I, J;
  logic SELB, VB;
  not G1 (SELB, SEL);
  AOI G2 (VB, I, SEL, SELB, J);
  not G3 (V, VB);
endmodule

```

Verilog


FPGA
CAD
Tools

```

00101010001010010
10010010010011000
10101000101011000
10101001010010101
00010110001001010
10101001111001001
01000010101001010
10010010000101010
10100101010010100
01010110101001010
01010010100101001

```

Bitstream

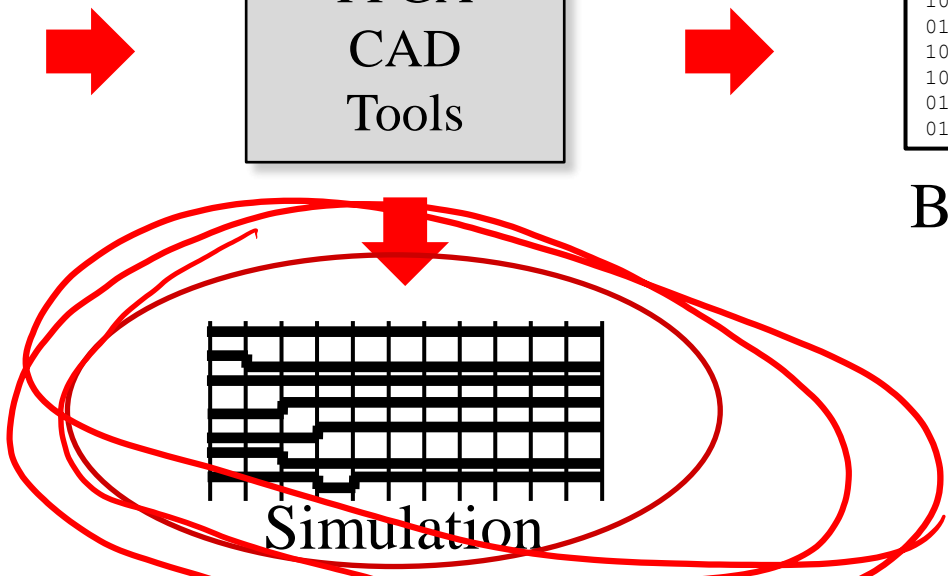

Simulation

Modelsim

Testbenches

- ❖ **ModelSim** is a digital logic simulator

- Runs entirely on your computer and simulates the operation of your FPGA
- Used for debugging the internals of buggy Verilog
 - No such thing as printf() in a physical circuit (at least not without microscopic tweezers)


➔ **Testbench** – a Verilog module that instantiates the circuit you're testing and provides a lil script to generate fake input signals

- We need to mockup fake signals for *every* input to our module, *and* the timing of how they change.

★ Doesn't/can't get synthesized

★ **You need a testbench for every single module you write. Period.**

Verilog Testbenches

 

```

module MUX2_tb ();
  logic SEL, I, J; // variables remember values
  logic V;        // acts as net for reading output
  
```

No ports
No ports

```

initial // build stimulus (test vectors)
begin // start of "block" of code
  SEL = 1; I = 0; J = 0; #10; // t=0: S=1, I=0, J=0 -> V=0
  I = 1; #10; // t=10: S=1, I=1, J=0 -> V=1
  SEL = 0; #10; // t=20: S=0, I=1, J=0 -> V=0
  J = 1; #10; // t=30: S=0, I=1, J=1 -> V=1
end // end of "block" of code
  
```

Advance simulated time

Script that runs top-to-bottom

```


MUX2 dut (.V, .SEL, .I, .J);
endmodule // MUX2_tb
  
```

"Device Under Test"

"Device Under Test"

List of module instances

see the data change over time

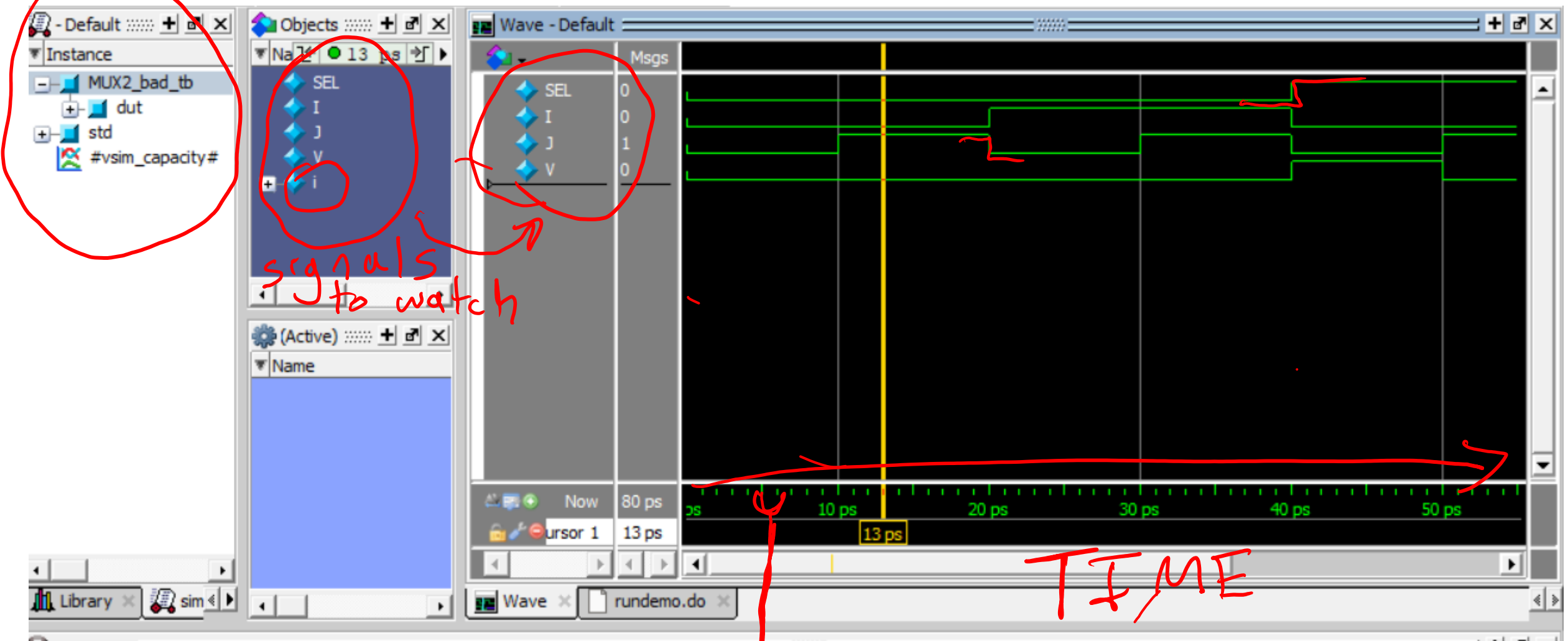


signals to watch

TIME

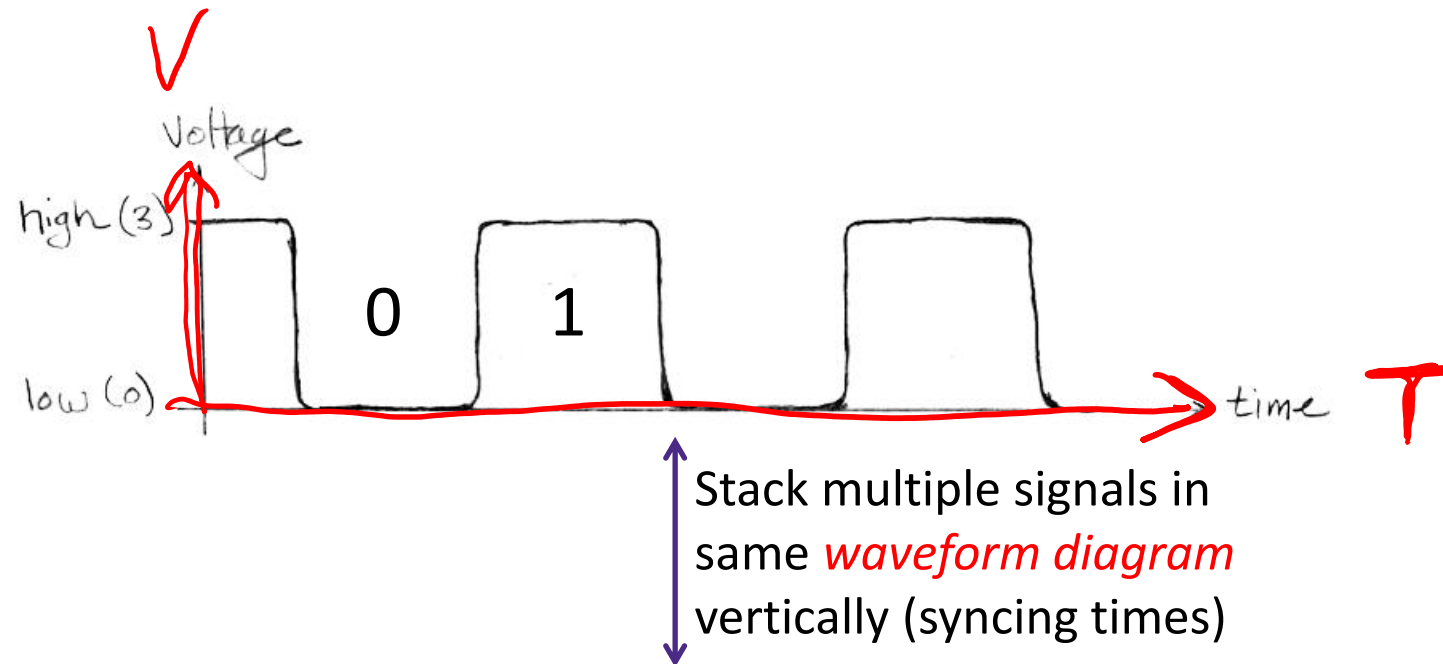
#1

Signals and Waveforms

- ❖ **Signals** transmitted over wires continuously
 - Transmission is effectively instantaneous
(a wire can only contain one value at any given time)
 - In digital system, a wire holds either a 0 (low voltage) or 1 (high voltage)





Signal Grouping

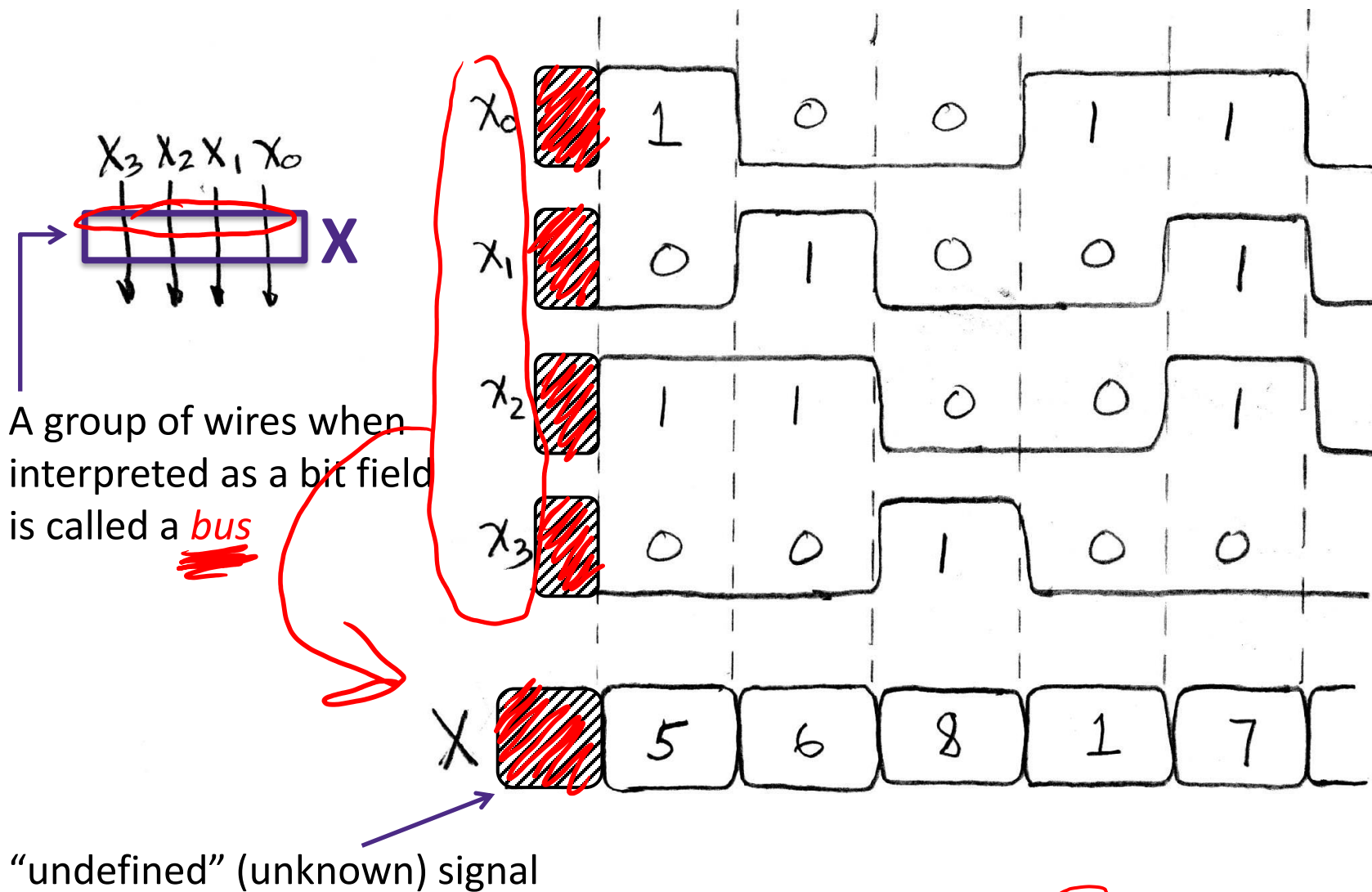

Circuit Timing Behavior

  - ❖ **Simple Model:** Gates “react” after fixed delay
- ❖ Example: Assume delay of all gates is 1 ns (= 3 ticks)




Timing Diagrams Matter



Who is in charge?



- Pilot?
- Copilot?
- ➔ Autopilot?

 

Circuit Timing: Hazards/Glitches

❖ Circuits can temporarily go to incorrect states!

  - Assume 1 ns (3 tick) delay for all gates



Summary

- ❖ Verilog is a hardware description language (HDL) used to program your FPGA
 - Programmatic syntax used to describe the connections between gates and registers
- ❖ Waveform diagrams used to track intermediate signals as information propagates through CL
- ❖ Hardware debugging is a critical skill
 - Similar to debugging software, but using different tools