



1. DeMorgan's Practice

Implement this circuit using *only* NOR gates:



