

# Intro to Digital Design

## L3: Karnaugh Maps

**Instructor:** Naomi Alterman

**Teaching Assistants:**

Derek de Leuw

Isabel Froelich

Kevin Hernandez

Aarjav Jain

Packard Stephenson

# Administrivia

- ❖ Lab 3 out – Logic simplification with K-maps and Verilog
  - Due a week from tomorrow (4/22 @ 2:30p)
  - Full credit for minimal logic

# Lecture Outline

- ❖ **Karnaugh Maps (K-maps)**
- ❖ Avoiding Hazards
- ❖ Design Examples
- ❖ More Verilog

# On and Off Sets

❖ *On Set* is the set of input patterns where the function is TRUE

- Here on set =  $\{\bar{A}\bar{B}C, \bar{A}BC, A\bar{B}\bar{C}, A\bar{B}C\}$

❖ *Off Set* is the set of input patterns where the function is FALSE

- Here off set =  $\{\bar{A}\bar{B}\bar{C}, \bar{A}B\bar{C}, A\bar{B}\bar{C}, ABC\}$

❖ **Recall:** Use the On Set for *Sum of Products* (SoP) and the Off Set for *Product of Sums* (PoS)

- Considered **two-level** Boolean expressions

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


# Two-Level Simplification

- ❖ Using Sum of Products, “neighboring” input combinations simplify
  - “Neighboring”: inputs that differ by a single signal
  - *The Uniting Theorem*:  $A(\bar{B} + B) = A$
  - *e.g.*,  $AB + \bar{A}B = B$ ,  $\bar{A}BC + \bar{A}B\bar{C} = \bar{A}B$
- ❖ **Goal**: Find neighboring subsets of the On Set to eliminate variables and simplify the expression
- ❖ **Technique**: A **Karnaugh map** (“K-map”) is a method of rearranging a truth table to *visualize* the terms that can be simplified with the uniting theorem


# Karnaugh Maps

- ❖ Rearrange table into a 2D grid with inputs on the edges and outputs in the grid cells
- ❖ If more than 2 inputs, “group” them along the edges and write out all combinations of bits arranged so that **neighboring combinations change only by 1 input (“Gray code”)**


**2 Inputs:**

 

**3 Inputs:**

 


**4 Inputs:**

 

# Karnaugh Maps

❖ Also see visualization with brackets for “asserted” simplifications:

**4 Inputs:**

 

# K-map Example: Majority Circuit

- ❖ Filling in a Karnaugh map:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		AB			
		00	01	11	10
C	0				
	1				

- ❖ Each row of truth table corresponds to ONE cell of Karnaugh map
- ❖ Note the jump when you go from input 011 to 100  
(*most mistakes made here*)

# K-map Example: Majority Circuit

- ❖ Filling in alternate Karnaugh map:


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		BC			
		00	01	11	10
A	0				
	1				

- ❖ Each row of truth table corresponds to ONE cell of Karnaugh map
- ❖ Note the jump when you go from input 001 to 010 and 101 to 110 (*most mistakes made here*)
 
# K-map Simplification

- ❖ Group neighboring 1's with circles
  - Each circle becomes an equation term
  - Make sure *all* 1's are circled
- ❖  $F = BC + AB + AC$
- ❖ Larger groups become smaller terms
  - The single 1 in top row  $\rightarrow ABC\bar{C}$
  - Vertical group of two 1's  $\rightarrow AB$
  - If entire lower row was 1's  $\rightarrow C$



# General K-map Rules


- ❖ Only group in powers of 2
  - Grouping should be of size  $2^i \times 2^j$
  - Applies for both directions
- ❖ Wraps around in all directions
  - “Corners” case is extreme example
- ❖ Always choose largest groupings possible
  - Avoid single cells whenever possible
- ❖  $F = BD + \overline{B}\overline{D} + ACD$

		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	0	1	1	0
	11	0	1	1	1
	10	1	0	0	1

- 1) NOT a valid group
- 2) IS a valid group
- 3) IS a valid group
- 4) “Corners” case
- 5) 1 of 2 good choices here

 
# K-Map Example

$$\diamond F = \overline{A}D + BD + \overline{B}C + A\overline{B}D$$



 
# Don't Cares

- ❖ Use symbol 'X' to mean it can be either a 0 or 1
  - Make choice to simplify final expression




Let all X = 0:

F =

 

Let all X = 1:

F =

 



Choose wisely:

F =
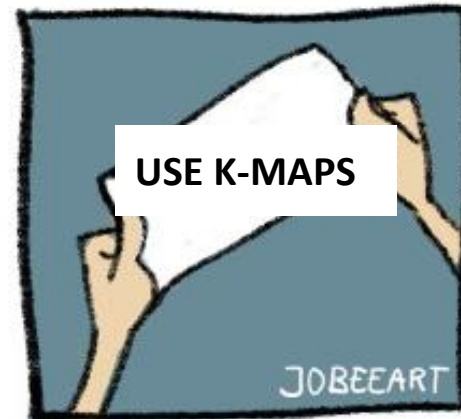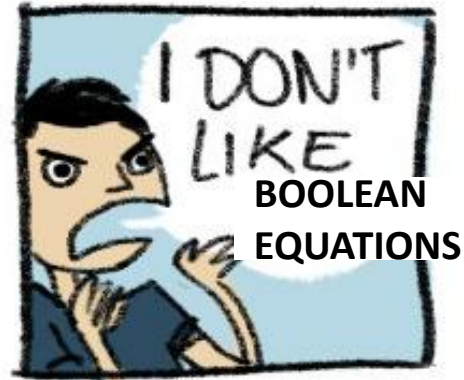
# Two-Level Simplification (at SCALE!)

- ❖ As an aside: K-Maps are for  $\leq 4$  dimensions
- ❖ For more, we use a computer implementation of the same technique called the “Quine-McCluskey algorithm”
  - This is part of what Quartus is doing when you hit the “synthesize” button





# Lecture Outline


- ❖ Karnaugh Maps (K-maps)
- ❖ **Avoiding Hazards**
- ❖ Design Examples
- ❖ More Verilog

# Timing Diagrams Matter





Who is in charge?

- Pilot?
- Copilot?
- Autopilot?

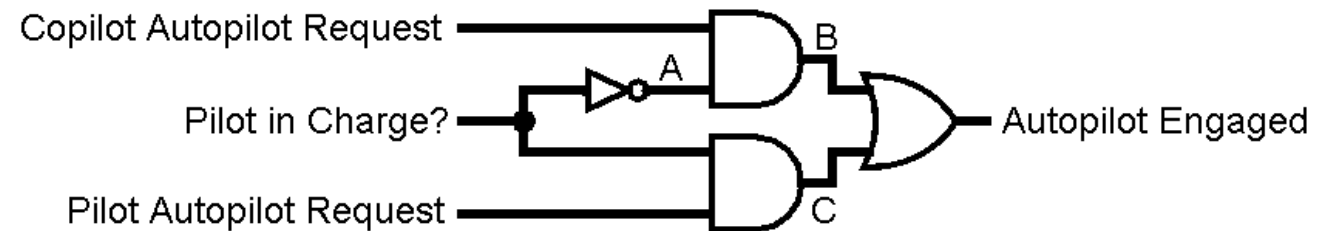

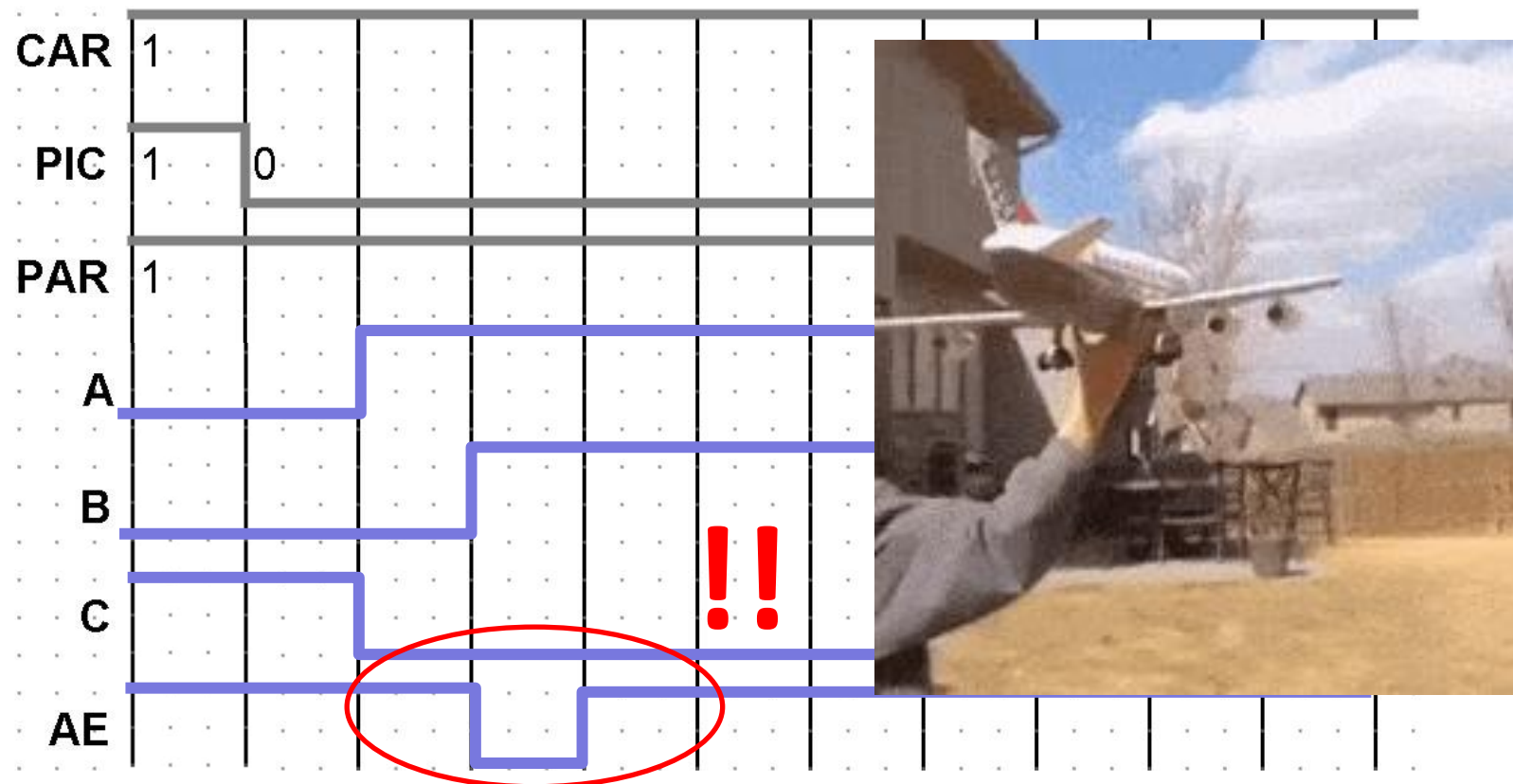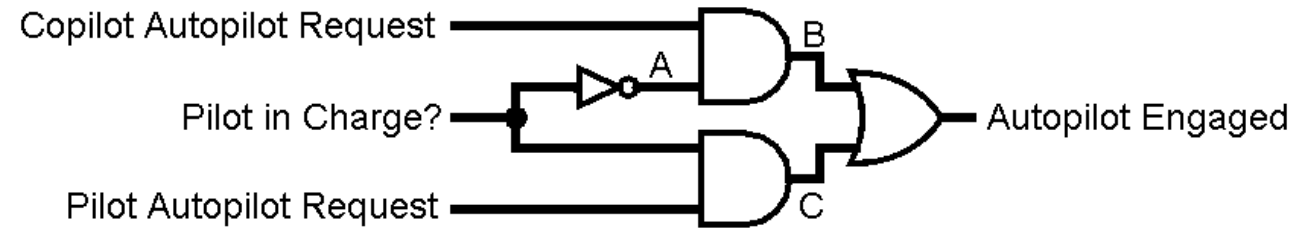
# Circuit Timing: Hazards/Glitches


- ❖ Circuits can temporarily go to incorrect states!
- Assuming gate delay of 1 ns / 3 ticks



# Circuit Hazards

- ❖ Momentary wiggles in output of combinational logic before it “settles” on the right answer
  - Mostly doesn’t matter (we’ll see why next week)
  - But when it does matter, it can make the plane crash 
  - Can be avoided with **redundant** gates (eg, not fully simplified equations)
- ❖ Classification:
  - “Static-0” (output spikes to 1 before settling to 0)
    - Only a problem for PoS equations
  - “Static-1” (output dips to 0 before settling to 1)
    - Only a problem for SoP equations
  - “Dynamic” (lots of wiggles)


# Static hazards visualized

 


	00	01	11	10
0				
1				

# Design Tradeoffs

**Minimal logic**

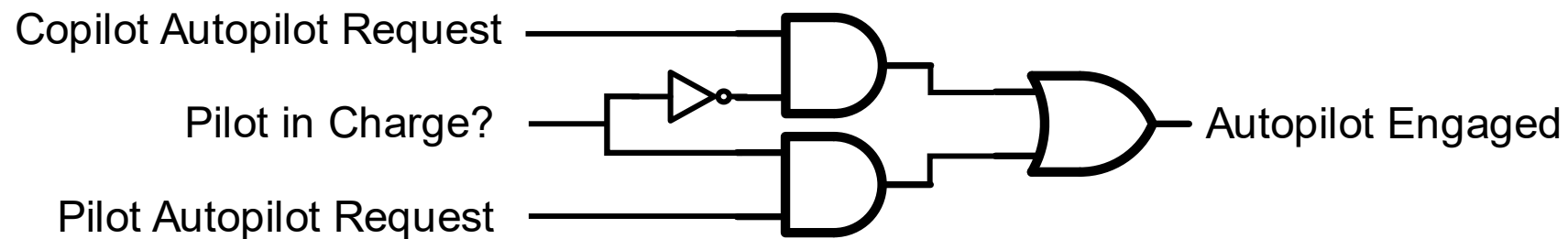

**No static hazards**

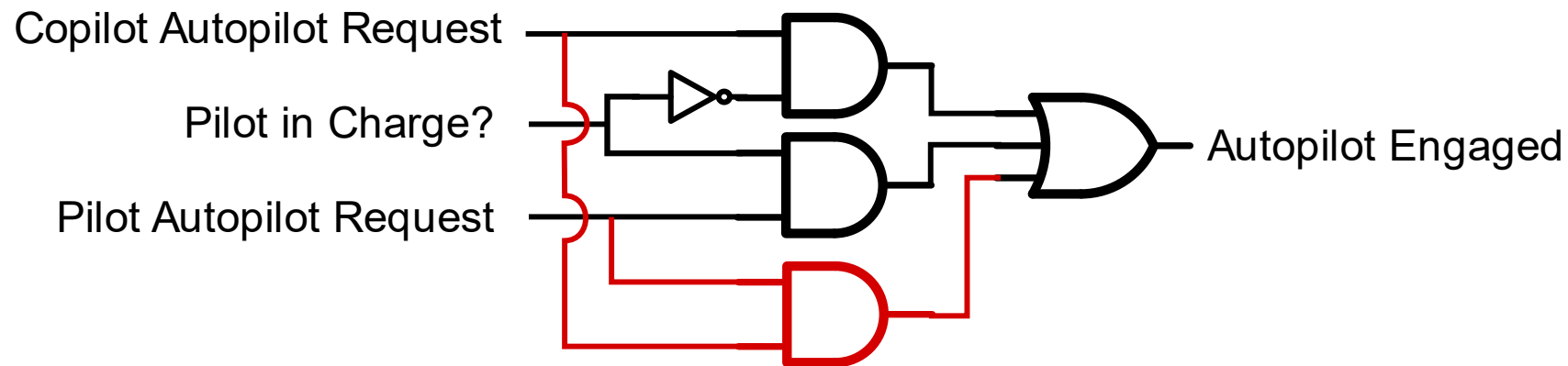

# Cool band names

- ❖ From the “See Also” section of the [Wikipedia article](#) for logic hazards:

## See also [\[edit\]](#)

---

- [Don't care](#)
- [Floating body effect](#), a probably cause for
- [Glitch](#)
- [Hazard \(computer architecture\)](#)
- [Logic redundancy](#)
- [Race condition](#)



# Miso Moment




# Lecture Outline

- ❖ Karnaugh Maps (K-maps)
- ❖ Avoiding Hazards
- ❖ **Design Examples**
- ❖ More Verilog

# Design Example: 2-bit Adder




❖ Block Diagram and Truth Table:

 

We'll need a new k-map for **each** output

A	B	C	D	X	Y	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

# Design Example: 2-bit Adder

  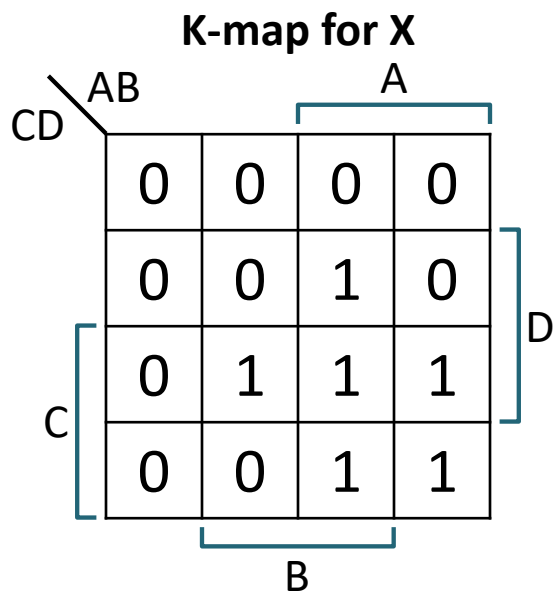


X =

Y =


Z =

# Case Study: Seven-Segment Display


- ❖ Chip to drive digital display

 

B3	B2	B1	B0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0

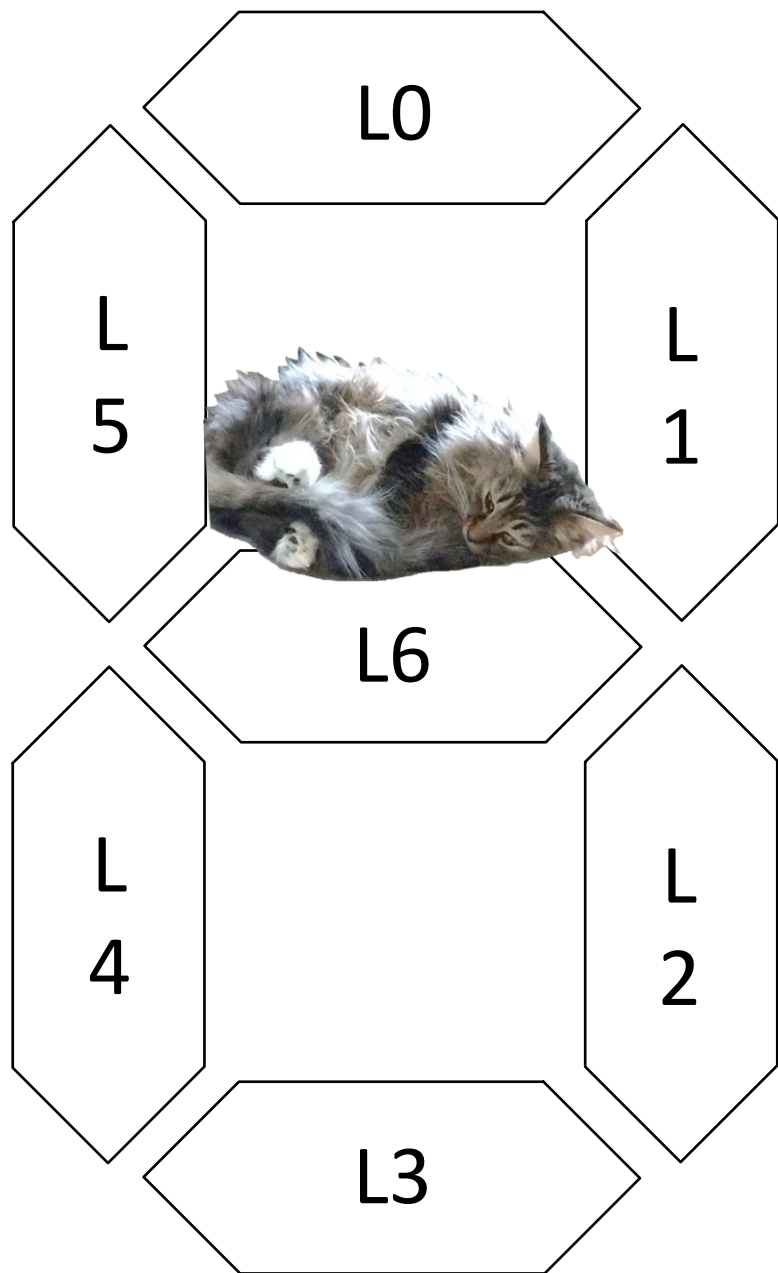



B3	B2	B1	B0	Val	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	0	1	1	0	0	0	0
0	0	1	0	2	1	1	0	1	1	0	1
0	0	1	1	3	1	1	1	1	0	0	1
0	1	0	0	4	0	1	1	0	0	1	1
0	1	0	1	5	1	0	1	1	0	1	1
0	1	1	0	6	1	0	1	1	1	1	1
0	1	1	1	7	1	1	1	0	0	0	0
1	0	0	0	8	1	1	1	1	1	1	1
1	0	0	1	9	1	1	1	1	0	1	1

 

# Case Study: Seven-Segment Display


❖ Implement **L5**:

B3	B2	B1	B0	L5
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1

  
 
# Practice Problem: Rock-Paper-Scissors

- ❖ Rock (00), Paper (01), Scissors (10) for two players P0 and P1
- ❖ **Output:** Win = Winner's ID (0/1)  
Tie = 1 if Tie, 0 else



P1		P0		Win	Tie
A	B	C	D		
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

# Lecture Outline

- ❖ Karnaugh Maps (K-maps)
- ❖ Avoiding Hazards
- ❖ Design Examples
- ❖ **More Verilog**

# 7-Seg Display in Verilog

```
module seg7 (bcd, leds);
  input  logic [3:0] bcd;
  output logic [6:0] leds;

  always_comb
    case (bcd)
      // 3210           6543210
      4'b0000: leds = 7'b0111111;
      4'b0001: leds = 7'b0000110;
      4'b0010: leds = 7'b1011011;
      4'b0011: leds = 7'b1001111;
      4'b0100: leds = 7'b1100110;
      4'b0101: leds = 7'b1101101;
      4'b0110: leds = 7'b1111101;
      4'b0111: leds = 7'b0000111;
      4'b1000: leds = 7'b1111111;
      4'b1001: leds = 7'b1101111;
      default: leds = 7'bX;
    endcase
endmodule
```

# Verilog “control flow”

- ❖ Verilog has synthesizable **if** and **case** statements
  - In hardware, each “clause” exists in parallel and is always computing its output whether the condition is true or not
  - A **multiplexer (“mux”)** is placed physically after these blocks to electrically connect one of them to the output signal
- ❖ Verilog requires us to wrap these statements in an **always\_comb** block
  - Block defines the full set of circuits that *may* drive the value on a **logic** variable
  - Idea: the last assignment in an always block to a given variable is the result that gets used
- ❖ There are several other kinds of “**always**” block.
  - We’ll learn about them next week!

# Verilog Signal Manipulation

- ❖ Bus definition: `[n-1:0]` is an n-bit bus
  - Good practice to follow bit numbering notation
  - Access individual bit/wire using “array” syntax (*e.g.*, `bus[1]`)
  - Can slice busses using similar notation (*e.g.*, `bus[4:2]`)
- ❖ Multi-bit constants: `n'r###...`
  - n is bit width, b is radix/base, #s are the actual digits
  - *e.g.*, `4'd12`, `4'b1100`, `4'hC`
- ❖ Concatenation: `{sig, ..., sig}`
  - Ordering matters; result will have combined widths of all signals
- ❖ Replication operator: `{n{m}}`
  - repeats value m, n times

# Let's check our understanding


```
logic [4:0] apple;  
logic [3:0] pear;  
logic [9:0] orange;  
assign apple = 5'd20;  
assign pear = {1'b0, apple[2:1], apple[4]};
```

- ❖ What's the value of pear?
- ❖ If we want orange to be the *sign-extended* version of apple, what is the appropriate Verilog statement?

```
assign orange =
```
 
# Practice Problem: Extend 7-Seg to Hex

- ❖ Show “A” on 0b1010 (ten) to “F” on 0b1111 (fifteen)



```
module seg7_hex (bcd, leds);
  input logic [3:0] bcd;
  output logic [6:0] leds;

  always_comb
  case (bcd)
    // 3210           6543210
    4'b0000: leds = 7'b0111111;
    4'b0001: leds = 7'b0000110;
    4'b0010: leds = 7'b1011011;
    4'b0011: leds = 7'b1001111;
    4'b0100: leds = 7'b1100110;
    4'b0101: leds = 7'b1101101;
    4'b0110: leds = 7'b1111101;
    4'b0111: leds = 7'b0000111;
    4'b1000: leds = 7'b1111111;
    4'b1001: leds = 7'b1101111;
    // TODO: What else??
    default: leds = 7'bX;
  endcase
endmodule
```